

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EE35

Third Semester B.E. Degree Examination, Aug./Sept.2020

## Digital System Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Convert the following equations into proper canonical form:
- $f(A, B, C) = A + ABC$  into standard SOP form. (10 Marks)
  - $f(A, B, C) = A.(A + B + C)$  into standard POS form. (10 Marks)
- b. Reduce the following function using K-Map technique:  
 $f(A, B, C, D, E) = \sum m(1, 4, 8, 10, 11, 20, 22, 24, 25, 26) + \sum d(0, 12, 16, 17)$  (10 Marks)

OR

- 2 a. Simply the following using Quine-McCluskey method:  
 $f(A, B, C, D) = \sum m(1, 2, 3, 5, 9, 12, 14, 15) + \sum d(4, 8, 11)$  (10 Marks)
- b. Design a logic circuit with inputs P, Q, R so that output Y is high whenever P is zero or whenever  $Q = R = 1$ . (10 Marks)

### Module-2

- 3 a. i) Implement  $f(A, B, C) = \sum m(1, 3, 5, 6)$  using 4:1 multiplexer. (10 Marks)
- ii) Implement  $f(P, Q, R, S) = \sum m(0, 1, 3, 4, 8, 9, 15)$  using 8:1 multiplexer. (10 Marks)
- b. Explain the concept of look ahead adder and hence realize 3 bit parallel adder using Look ahead carry generator. (10 Marks)

OR

- 4 a. Implement full subtractor using 3:8 decoder. (10 Marks)
- b. Design 2-bit magnitude comparator using gates. (10 Marks)

### Module-3

- 5 a. Explain the operation of gated S-R flipflop using NAND gates, with truth table. (10 Marks)
- b. Design synchronous MOD-6 counter using S-R flip flop. (10 Marks)

OR

- 6 a. With logic diagram, explain the working of master slave J-K flip flop along with waveforms. Explain about race around condition. (10 Marks)
- b. Design synchronous mod-3 counter using J-K flip flop. (10 Marks)

CMRIT LIBRARY  
BANGALORE - 560 037

**Module-4**

- 7 a. Construct the transition table, state table and state diagram for the given synchronous sequential circuit. (10 Marks)

 


Fig.Q.7(a)

- b. Obtain transition table and excitation table for the given state diagram. (10 Marks)

 


Fig.Q7(b)

**OR**

- 8 a. Construct the transition table, state table and state diagram for the Moore sequential circuit. (12 Marks)

 


Fig.Q.8(a)

- b. Compare Moore model and Mealy Model. (08 Marks)

**Module-5**

- 9 a. Write data flow description for full adder in both VHDL and verilog. (10 Marks)  
 b. Compare VHDL and verilog. (10 Marks)

**OR**

- 10 a. Describe different operators in VHDL and verilog. (10 Marks)  
 b. Briefly describe different styles of descriptions in VHDL. (10 Marks)

\*\*\*\*\*

CMRIT LIBRARY  
 BANGALORE - 560 037