 


CBCS SCHEME

15EC32



Module-1

- 1 a. Derive an expression for A_v , Z_i and Z_o for CE fixed bias using hybrid equivalent model. (08 Marks)
- b. With a neat circuit explain hybrid - π model for a transistor in CE configuration. (08 Marks)

OR

- 2 a. Derive an expression for Z_i , Z_o and A_v for emitter - Follower configuration using r_e model. (08 Marks)
- b. For the network shown in Fig Q2(b). Determine :
 i) r_e ii) Z_i iii) Z_o ($r_o = \alpha\Omega$) iv) A_v ($r_o = \alpha\Omega$) v) A_i ($r_o = \alpha\Omega$).

 


Fig Q2(b) (08 Marks)

Module-2

- 3 a. Derive an expression for Z_i , Z_o and A_v of FET self bias configuration with bypassed R_s . (08 Marks)
- b. Explain the construction and working principle of n-channel depletion type MOSFET and draw the characteristic curves. (08 Marks)

OR

- 4 a. The fixed bias configuration of Fig Q4(a) has an operating point defined by $V_{GSQ} = -2V$ and $I_{DQ} = 5.625mA$ with $I_{DSS} = 10mA$ and $V_p = -8V$. Determine :
 i) g_m ii) r_d iii) Z_i iv) Z_o v) A_v .

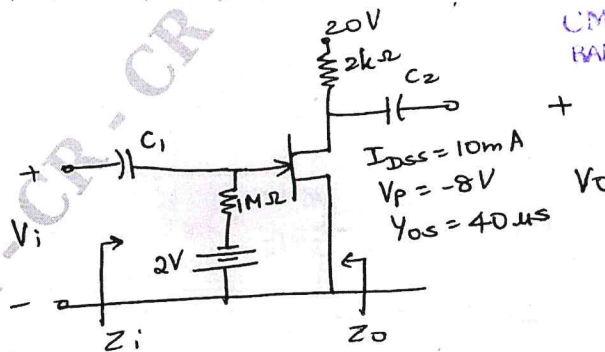


Fig Q4(a) (08 Marks)

CMRIT LIBRARY
BANGALORE - 560 037

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- b. Draw the JFET common drain configuration circuit. Derive Z_i , Z_o and A_v using small signal model. (08 Marks)

Module-3

- 5 a. The i/p power to a device is 10,000w at a voltage of 1000V. The output power is 500W and the output impedance is 20Ω .
 i) Find power gain in db
 ii) Find voltage gain in db
 iii) Find input impedance. (06 Marks)
- b. Describe Miller's effect and derive an equation for Miller input and output capacitance. (10 Marks)

OR

- 6 a. Explain high frequency response of FET amplifier. (06 Marks)
- b. Determine A_v , Z_i , A_{v_s} , F_{L_S} for the low frequency response of the BJT amplifier circuit shown in Fig Q6(b). Assume $r_o = \infty$.

 


Fig Q6(b)

(10 Marks)

Module-4

- 7 a. Explain with neat circuit diagram the operation of transistor Colpitt's oscillator. (08 Marks)
- b. What are the effects of negative feedback in an amplifier? Show how bandwidth of an amplifier increases with negative feedback. (08 Marks)

OR

- 8 a. Mention the types of Feedback connections. Draw their block diagrams indicating i/p and o/p signal. (08 Marks)
- b. With a neat circuit and waveforms, explain the working operation of UJT relaxation oscillator. (08 Marks)

Module-5

- 9 a. Explain the operation of class B push pull amplifier and show that maximum conversion η is 78.5% (10 Marks)
- b. The Following distortion readings are available for a power amplifier $D_2 = 0.1$, $D_3 = 0.02$, $D_4 = 0.01$ with $I_1 = 4A$, $R_c = 8\Omega$.
 i) Calculate the THD
 ii) Determine the fundamental power component
 iii) Calculate the total power. (06 Marks)

OR

- 10 a. Explain series voltage regulator using transistor. (08 Marks)
- b. Explain series Fed class A power amplifier. Show that its maximum conversion η is 25%. (08 Marks)
