

IAT1 - DSD (18EE35) - A Section

Max Marks: 50M

Total No. of Questions: 27

Instructions:

1. You must login through official email id
2. Attempt all questions.
3. Symbols and abbreviations carry their intended meaning
4. A' is read as NOT(A) or A bar
5. Read 2^n as 2 to the power of n
6. Read m(1,2,3) as MINTERMS and M(1,2,3) as MAXTERMS
7. Q1 to Q10 carries ONE mark each (Total 10M)
8. Q11 to Q25 carries TWO marks each (Total 30M)
9. Q26 to Q27 carries 5 marks each (Total 10M)

Your email address (kashif.a@cmrit.ac.in) will be recorded when you submit this form. Not you? [Switch account](#)

* Required

Name *

Enter your FULL NAME in CAPITAL LETTERS

Your answer

USN *

Enter your Complete USN in CAPITAL LETTERS (Ex: 1CR19EE001)

Your answer



[CO1,L1] Q1. $A \cdot A' = *$

1 point

- 0
- 1
- Undefined
- $A + A'$

[CO1,L1] Q2. $A + A'B = *$

1 point

- $A'B$
- A
- $A + B$
- $A' + B$

[CO1,L1] Q3. A 4-variable K-map has *

1 point

- 2 Cells
- 4 Cells
- 8 Cells
- 16 Cells

[CO1,L1] Q4. Binary number 11110 is represented in decimal as *

1 point

- 30
- 29
- 65
- 44



[CO1,L1] Q5. The function $f(X,Y,Z) = X'YZ + XZ + XYZ' + X'Y'Z$ is in *

1 point

- standard sum of product form
- sum of product form
- product of sum form
- standard product of sum form

[CO1,L1] Q6. For converting the function $f(A,B,C) = A + ABC$ into its standard form the first term in the expression has to be *

1 point

- anded with $(B + B')(C + C')$
- anded with $(B \cdot B')(C \cdot C')$
- ored with $(B + B')(C + C')$
- ored with $(B \cdot B')(C \cdot C')$

[CO1,L1] Q7. In Quine McClusky method of minimization the two minterms compared from the consecutive groups will be grouped only when they have *

1 point

- 2 bit change
- 3 bit change
- 4 bit change
- 1 bit change



[CO1,L1] Q8. An m bit decoder has how many possible outputs? *

1 point

$2^{(m+1)}$

2^n

$2^{(n-1)}$

2^m

[CO1,L1] Q9. IC 74139 is a *

1 point

Dual 2:4 decoder

3:8 decoder

5:32 decoder

4:16 decoder

[CO1,L1] Q10. A decoder with active low outputs must be connected to which gate to get a SOP expression? *

1 point

ABD gate

NAND gate

OR gate

NOR gate



[CO1,L1] Q11. Minimum number of _____ are required to implement a 2-input XNOR gate * 2 points

4 NAND gates

4 NOR gates

6 NAND gates

6 NOR gates

[CO1,L2] Q12. From the given boolean expression choose the equivalent boolean expression written using maxterms $f(A,B,C) = m(1,2,5)+d(0,3)$ * 2 points

$f(A,B,C) = M(4,6,7)+d(0,3)$


$f(A,B,C) = M(4,5,7)+d(0,3)$

$f(A,B,C) = M(4,6,7)+d(0,4)$

$f(A,B,C) = M(3,6,7)+d(0,3)$



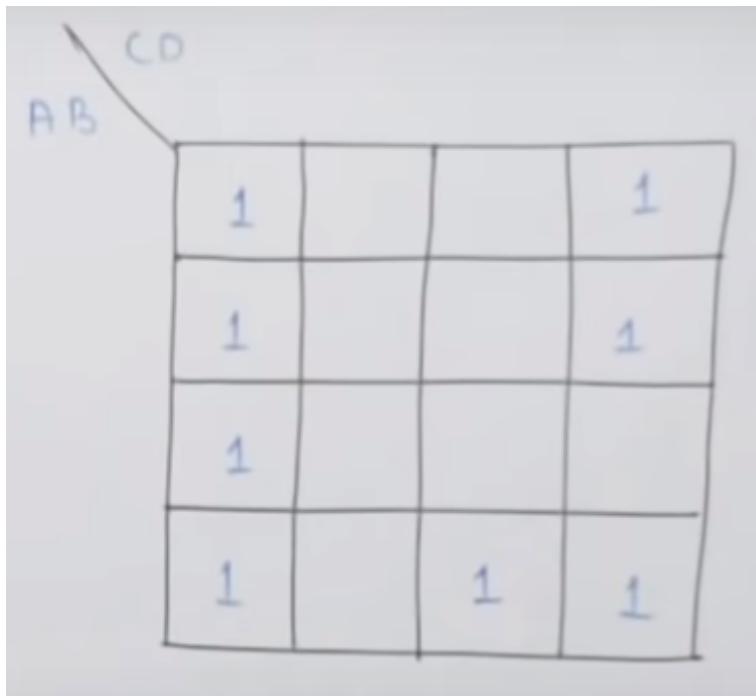[CO1,L2] Q13. In the k map shown how many essential prime implicants are 2 points available? *



- 4
- 3
- 2
- 1

[CO1,L2] Q14. Convert the following SOP to its standard SOP. $f(A,B,C) =$ 2 points
 $AC + AB + BC$ *

- $ABC + A'BC + AB'C$
- $ABC + A'BC + ABC'$
- $ABC + A'B'C' + AB'C' + A'BC'$
- $ABC + A'BC + AB'C + ABC'$



[CO1,L2] Q15. Convert the following POS to its proper canonical form.

2 points

$$f(A,B,C) = (A+B')(B'+C)$$

- (A+B'+C)(A+B'+C')(A'+B'+C)
- (A+B'+C)(A+B'+C')
- (A+B'+C)(A+B+C')(A'+B'+C')
- (A+B'+C)(A'+B'+C')(A'+B'+C)

[CO1,L2] Q16. Minimize the following function in POS minimal form using

2 points

$$K\text{-Maps: } f(A,B,C,D) = M(6,7,8,9) + d(10,11,12,13,14,15)$$

- Y = A'(B'+C') + (A'+B')
- Y = A'(B'+C)
- Y = A'(B'+C') + (A+B'+C)
- Y = A'(B'+C')

[CO1,L2] Q17. Minimize the following function in SOP minimal form using

2 points

$$K\text{-Maps: } f(A,B,C,D) = m(1,5,6,12,13,14) + d(2,4)$$

- Y = BC'+BD'+A'C'D'
- Y = BC'+B'D'+A'C'D
- Y = BC'+BD'+A'C'D
- Y = B'C'+ABD'+A'C'D




[CO1,L2] Q18. In the prime implicant selection chart shown which terms are considered as essential prime implicants? * 2 points

		0	1	2	5	6	7	8	9	10	14
(0, 1, 8, 9)	$b'c'$	X	X					X	X		
(0, 2, 8, 10)	$b'd'$	X		X				X		X	
(2, 6, 10, 14)	cd'			X	X	X				X	X
(1, 5)	$a'c'd$			X	X						
(5, 7)	$a'bd$					X	X				
(6, 7)	$a'bc$							X	X		

- b'c' and a'bc
- b'c', b'd', cd', a'c'd, a'bd, a'bc
- b'c' and cd'
- a'c'dd , a'bd and cd'

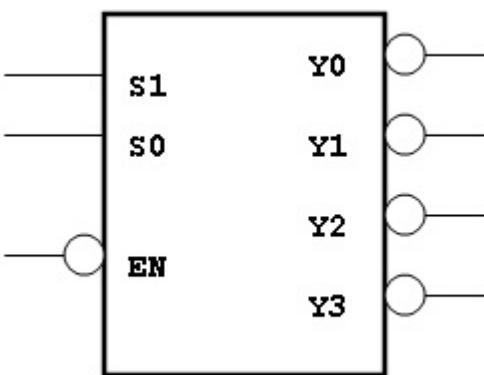[CO1,L2] Q19. For the 2 to 4 decoder shown if the input S0 and S1 are 1 and 0 respectively and the enable input E is 1 then which output pin is activated? * 2 points



- Y0
- Y2
- none will get activated
- Y1


[CO1,L2] Q20. If two 2-bit numbers (assume AB and CD as the two 2-bit numbers) are multiplied then the SOP expression for the MSB of the output will be * 2 points

- ABCD
- AB'C + ABD'
- BD
- A'BC+BCD'+AC'D+AB'D



[CO1,L2] Q21. The decoder shown in the figure is a *

2 points

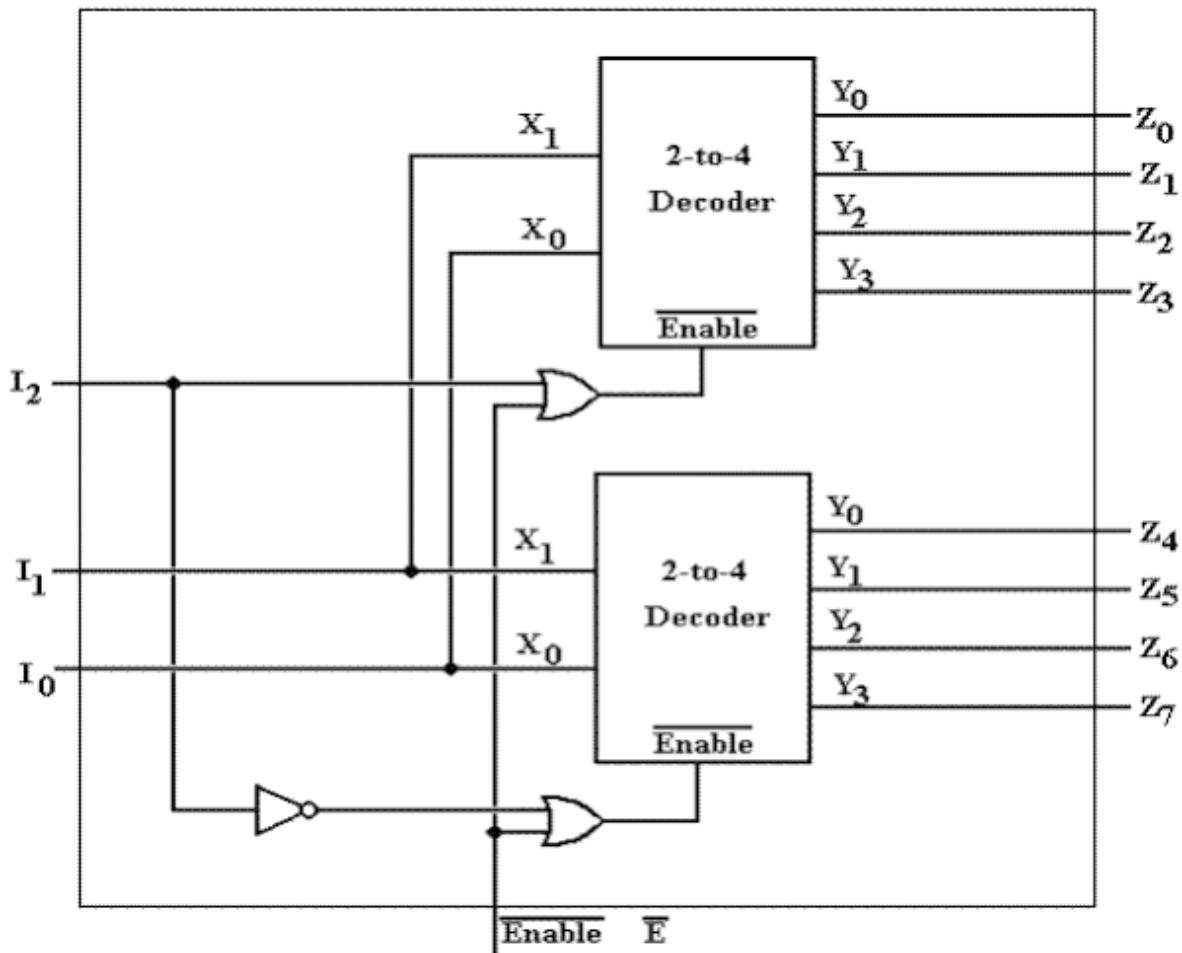


- 4:8 decoder
- 3:8 decoder
- 2:4 decoder
- 4:16 decoder



[CO1,L2] Q22. The output F is *

2 points

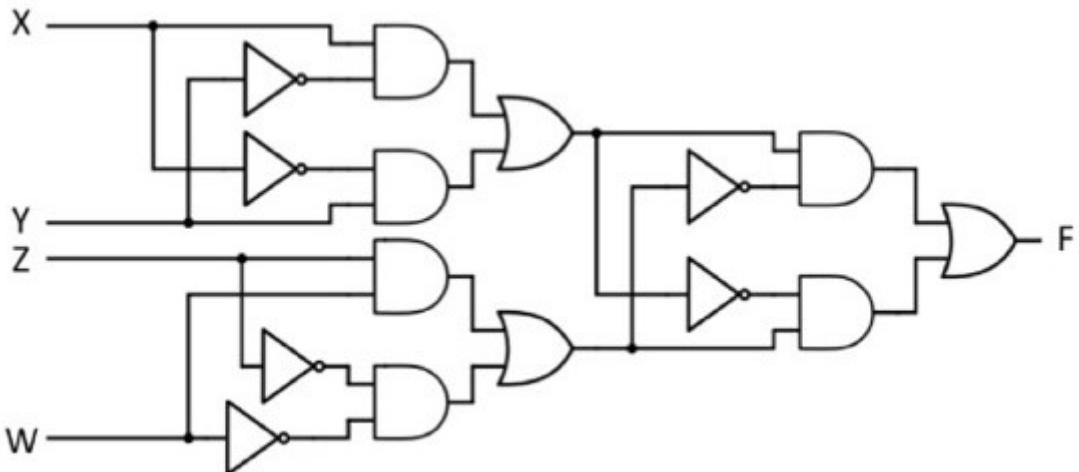

- (X xor Y) xor (Z xnor W)
- (X xor Y) xnor (Z xnor W)
- (X xnor Y) xnor (Z xor W)
- (X xnor Y) xor (Z xor W)

[CO1,L2] Q23. Minimize the function using k-map $f(A,B,C,D,E) = m(0,1,4,5,8,9,12,13,16,17,20,21,24,25,28,29)$ *


2 points

- $Y = A'D'$
- $Y = D'$
- $Y = A'D' + AD'E + ABCD'E' + A'B'C'E$
- $Y = AD' + A'D + ABC'D + B'C'E$



[CO1,L2] Q24. Output Q in the figure shown is equal to *


2 points

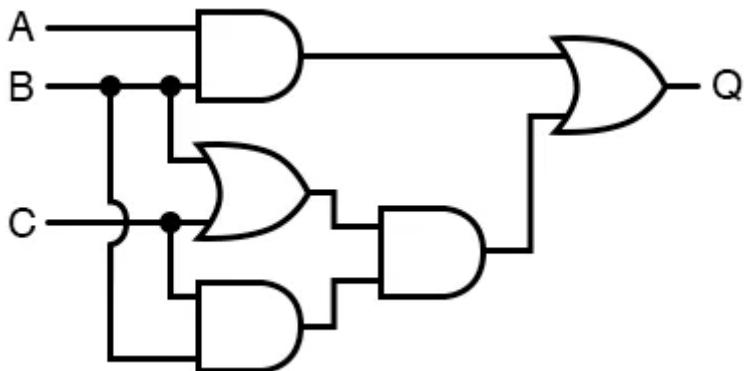

- AB + BC + (B+C)
- AB + BC
- A(B+C)
- B(A+C)

[CO1,L2] Q25. Minterms for output Q in the figure shown are *

2 points

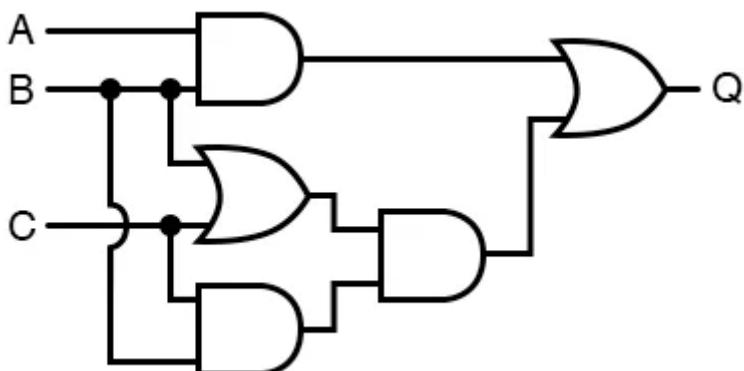

- m(3,7)
- m(1,2,3,5,6,7)
- m(3,6,7)
- m(6,7)




[CO1,L3] Q26. Solve the function $f(W,X,Y,Z) = m(2,6,8,9,10,11,14,15)$ using Quine McClusky method and select the final expression containing all the essential prime implicants. *

5 points


- $YZ' + WX' + WY'$
- $YZ' + WX' + WY$
- $XYZ' + W'X + WY'$
- $Y'Z' + WXZ' + W'XY'$

[CO1,L3] Q27. Which of the logic circuit represents the implementation of a full adder using a decoder? *


5 points

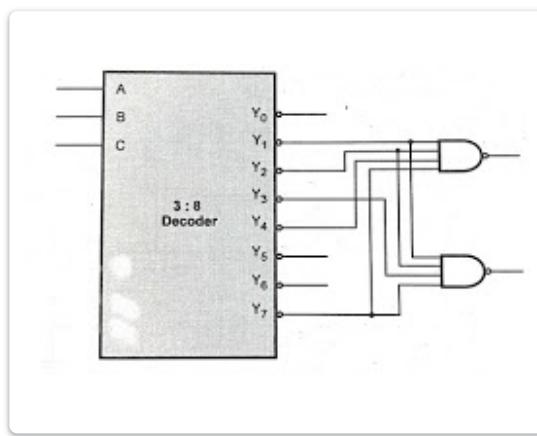


Option 1

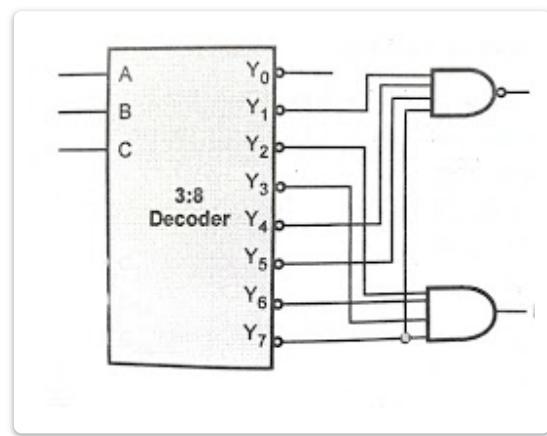

Option 2

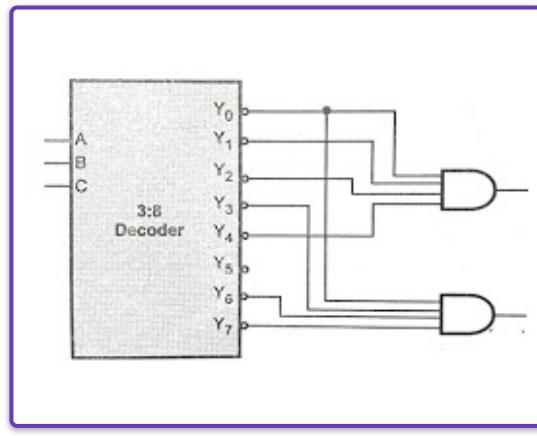

Option 3

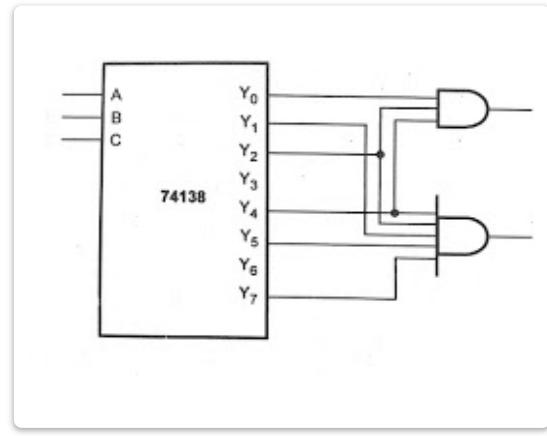

Option 4

Submit



Never submit passwords through Google Forms.

This form was created inside of CMR Institute of Technology. [Report Abuse](#)

Google Forms

