

Sixth Semester B.E. Degree Examination, Jan./Feb. 2021
Power System Analysis and Stability

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO full questions from each part.

PART – A

- 1 a. What are single line diagrams? Explain the procedure for finding per-unit reactance diagrams by stating all the assumptions involved. (08 Marks)
- b. The three parts of a single phase power system are designated as A, B and C and are connected to each other through transformers T_1 and T_2 as shown below in Fig.Q.1(b). The transformers are rated as,
 T_1 : 10,000KVA, 13.8-138KV, leakage reactance = 10%
 T_2 : 10,000KVA, 69-138KV, leakage reactance = 8%
 If the base in circuit-B is chosen as 10000KVA, 138KV, find the per – unit impedance of 300Ω resistive load in circuit – C. (04 Marks)

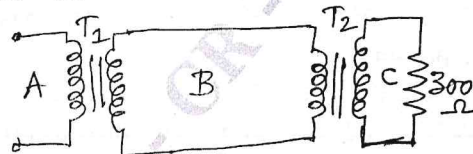


Fig.Q.1(b)

- c. The single line diagram of a power system is shown below in Fig.Q.1(c). Draw the per unit impedance diagram.

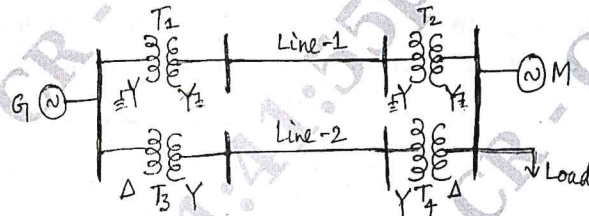



Fig.Q.1(c)

- G: 90MVA, 11KV, $X'' = 18\%$ Line 1: $Z = j80\Omega$
 T_1 : 70MVA, 11/110KV, $X = 15\%$ Line 2: $Z = j120\Omega$
 T_2 : 60MVA, 110/11KV, $X = 10\%$ M: 85MVA, 11KV, $X'' = 13\%$
 T_3 : Three 1ϕ units each rated 10MVA, 11/127KV, $X = 9\%$
 T_4 : Three 1ϕ units each rated 16.6667MVA, 127/11KV, $X = 12\%$
 The load absorbs 74MVA, 0.8pf lagging at 6.5KV. Select a common base of 100MVA, 11KV on the generator side. (08 Marks)

- 2 a. Explain with a neat circuit model, short circuit transients on a transmission line with the assumptions involved. Also explain the doubling effect on line under 3ϕ short-circuit, with the neat waveforms. (10 Marks)
- b. A transformer is rated at 50MVA and having a short circuit reactance of 5% is connected to the bus-bar which is supplied through two 66KV feeder cables (lines) each having an impedance of $(1.5 + j2.5)\Omega$. One of the feeders is connected to a generating station rated at 80MVA and having a short-circuit reactance of 10% and the other feeder is connected to another generating station rated at 100MVA with short circuit reactance of 15%. Determine the MVA at the fault when a 3ϕ short circuit occurring between the secondary terminals of the transformer. Choose base MVA as 400 and base KV as 66 on the generator side. (10 Marks)


- 3 a. Determine the symmetrical components of the asymmetrical phasors given below. $V_R = 100 \angle 250^\circ$ volts, $V_Y = 50 \angle -110^\circ$ volts and $V_B = 40 \angle 100^\circ$ volts (06 Marks)
- b. Show that the symmetrical component transformation is power invariant. (04 Marks)
- c. A delta connected balanced resistive load is connected across an unbalanced three phase supply as shown below in Fig.Q.3(c). Find the symmetrical components of line currents and phase currents. (10 Marks)

Fig.Q.3(c)

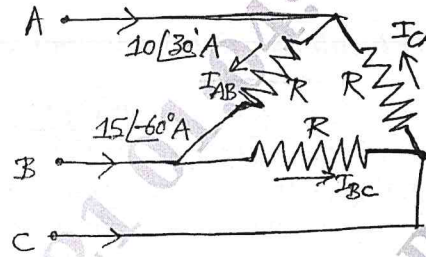

- 4 a. The symmetrical components of phase A in a 3 ϕ - Y connected system of phase voltages are $V_{a_1} = 200 \angle 30^\circ$ V, $V_{a_2} = 60 \angle 60^\circ$ V and $V_{a_0} = 20 \angle -30^\circ$ V. The symmetrical components of line currents of phase A are $I_{a_1} = 20 \angle 10^\circ$ A, $I_{a_2} = 5 \angle 20^\circ$ A and $I_{a_0} = 3 \angle -10^\circ$ A. Determine the 3 ϕ power in KVA and also in pu if the base power is 1KVA. Compute, also the active and reactive powers. (06 Marks)
- b. Draw all the sequence networks for the power system shown in Fig.Q.4(b) below. Choose a base of 50MVA, 220KV in $j50\Omega$ transmission lines and mark all reactances in pu. The ratings are, G_1 : 25MVA, 11KV, $X_d'' = 20\%$, G_2 : 25MVA, 11KV, $X_d'' = 20\%$
 T_1 to T_4 : Three single phase units each 6.6667MVA, 6.35KV/127KV, $X = 15\%$.
 The negative sequence reactance of each machine is its subtransient reactance. The zero sequence reactance of each machine is 8%. Assume that the zero sequence reactances of lines are 250% of their positive sequence reactances. (14 Marks)


Fig.Q.4(b)

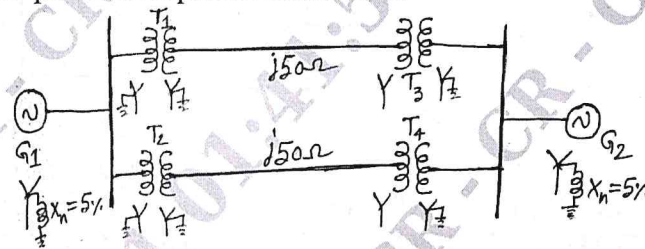

PART - B

- 5 a. Obtain an expression for the fault current, when a LG fault occurs at the terminals of an unloaded generator through a fault impedance Z_f . (08 Marks)
- b. A synchronous motor is receiving 10MW of power at 0.8pf lag at 6KV as shown in Fig.Q.5(b) below. A L-L fault occurs at the middle point of transmission line. Find the fault current. The ratings of the components are,
 G : 20MVA, 11KV, $X_1 = 0.2$ pu, $X_2 = 0.1$ pu and $X_0 = 0.1$ pu
 M : 15MVA, 6.9KV, $X_1 = 0.2$ pu, $X_2 = X_0 = 0.1$ pu
 T_1 : 18MVA, 11.5-34.5KV, $X = 0.1$ pu
 T_2 : 15MVA, 6.9-34.5KV, $X = 0.1$ pu
 T.L: $X_1 = X_2 = 5\Omega$ and $X_0 = 10\Omega$

Fig.Q.5(b)

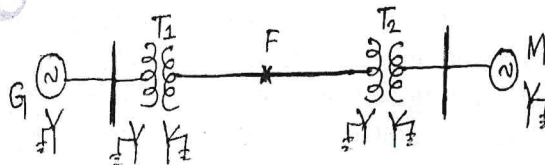

Choose the base values as 20MVA, 11KV on generator side.

(12 Marks)

