 


CBCS SCHEME

15CS32



Third Semester B.E. Degree Examination, Jan./Feb. 2021 Analog and Digital Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain the construction and working of JEFT. (10 Marks)
b. Explain the opamp window comparator circuit. (06 Marks)

OR

- 2 a. Explain the working of opamp Schmitt trigger. (08 Marks)
b. Explain 555 timer based Astable Multivibrator. (08 Marks)

Module-2

- 3 a. Define hazard. Explain static 1 and static 0 hazard. (06 Marks)
b. Simplify the Boolean function using Quine-McClusky method:
 $Y = F(A, B, C, D) = \sum m(2, 3, 7, 9, 11, 13) + d(1, 10, 15)$ (10 Marks)

OR

- 4 a. Write the verilog code for the logic circuit given in Fig.Q4(a) using structural and behavioral models.

 


Fig.Q4(a)

- b. For the expression given below, use entered variable map technique and simplify the expression. Also draw the logic circuit using basic gates
 $f(A, B, C, D) = Y = \sum m(1, 5, 10, 11, 12, 13)$ (08 Marks)

Module-3

- 5 a. Define a multiplexer. Analyze a 32:1 multiplexer using 4:1 multiplexers. Give detailed design and connections for the logic circuit. Use one 2:1 MUX. (10 Marks)
b. Explain the odd parity checker and generator circuit. (06 Marks)

OR

- 6 a. Implement 7-segment decoder using PLA. (06 Marks)
b. Explain n-bit Magnitude Comparator. (06 Marks)
c. Write verilog code to implement a 4:1 Multiplexer. (04 Marks)

Module-4

- 7 a. Explain with timing diagram, working of JK Master Slave flip flop. Also give the state transition diagram. (06 Marks)
- b. Draw the logic diagram for a 4 bit serial-in-serial-out shift register using edge triggered J-K flip flop and explain the circuit with waveform and the truth table. (10 Marks)

OR

- 8 a. Mention two differences between asynchronous and synchronous counter. With a neat block diagram, timing diagram and truth table, explain a 3 bit binary ripple down counter using negative-edge triggered JK flip flop. (10 Marks)
- b. Explain how a modulus 10 counter can be converted to modulus 8 counter using 7490 IC. (06 Marks)

Module-5

- 9 a. Write the verilog code to implement mod-8 up down counter. (06 Marks)
- b. Explain the dual slope ADC circuit. (10 Marks)

OR

- 10 a. Explain binary ladder network type DAC. (08 Marks)
- b. Explain the block diagram of digital clock constructed using counter cascading. (08 Marks)
