

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

15TE73



Seventh Semester B.E. Degree Examination, Jan./Feb.2021

CMOS VLSI Design

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain the DC transfer characteristics of CMOS inverter and mark all the regions of operation with necessary expressions for V_{out} in each region. (08 Marks)
- b. Explain with a neat diagram, enhancement mode transistor action of nMOS transistor. (08 Marks)

OR

- 2 a. Using neat diagram, describe fabrication steps for n-MOS transistor. (08 Marks)
- b. Elaborate the concept of n-well fabrication with neat sketches. (08 Marks)

Module-2

- 3 a. List the colour, stick encoding, mask layout encoding for n-diffusion, P-diffusion polysilicon, metal 1. (08 Marks)
- b. With the truth table, draw the schematic, stick diagram and physical layout for 2 : 1 mux. (08 Marks)

OR

- 4 a. Describe the delay unit τ in terms of sheet resistance and area capacitance for the CMOS inverter pair shown in Fig. Q4 (a). Calculate the total delay. (08 Marks)

 


Fig. Q4 (a)

- b. Calculate the area of capacitance of a multilayer structure shown in Fig. Q4 (b), if feature size = $5 \mu\text{m}$ and relative value of metal to substrate = 0.075, polysilicon = 0.1, diffusion = 0.25. (08 Marks)

 
 


Fig. Q4 (b)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

**Module-3**

- 5 a. What are the scaling factors for the following device parameters:
 (i) Gate capacitance C_g (ii) Max-operating frequency f_0
 (iii) Current density (iv) Power dissipation per gate P_g .
- b. Discuss general considerations in the design of subsystem design process.

(08 Marks)

(08 Marks)

OR

- 6 a. How to implement arithmetic and logic operation with a standard adder? Explain with the help of logic expression. (08 Marks)
- b. Explain FPGA architecture using block diagram. (08 Marks)

Module-4

- 7 a. Give the basic concept of parity generator and draw its stick diagram, using n-MOS technology. (10 Marks)
- b. Obtain the logic implementation of 4-way multiplexer (selector) using nMOS switches with necessary diagrams. (06 Marks)

OR

- 8 a. Discuss the architectural issues to be followed in the design of a VLSI subsystem. (08 Marks)
- b. Discuss carry look ahead adder with suitable equations and structure design. (08 Marks)

Module-5

- 9 a. Discuss the various system timing considerations. (04 Marks)
- b. Explain 3 transistor dynamic RAM cell. (06 Marks)
- c. Draw the schematic of 6 transistor SRAM cell. Discuss read/write operations with appropriate schematic diagrams. (06 Marks)

OR

- 10 a. Mention the types of I/O pads and discuss their functionalities. (08 Marks)
- b. What are the ground rules for successful design? (08 Marks)
