

## Third Semester B.E. Degree Examination, Jan./Feb. 2021 Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Define Passive and Active Elements with example. (06 Marks)  
 b. Determine  $R_{AB}$  using star - Delta transformation in the network show Fig Q1(b).

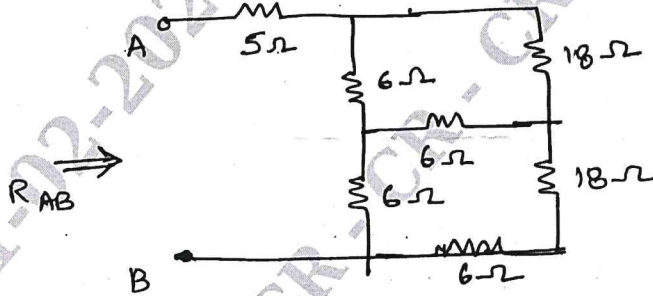


Fig Q1(b)

(10 Marks)

OR

- 2 a. A series RLC circuit consists of a resistance is  $1k\Omega$  and an inductance of  $100mA$  in series with capacitance is  $10pF$ . If  $100V$  is applied as input across the combination determine :  
 i) Resonant Frequency    ii) Maximum current in the circuit    iii) Q factor of the circuit  
 iv) Half power frequencies. (08 Marks)  
 b. Use nodal analysis to obtain current  $I$  in the Network shown Fig Q2(b).

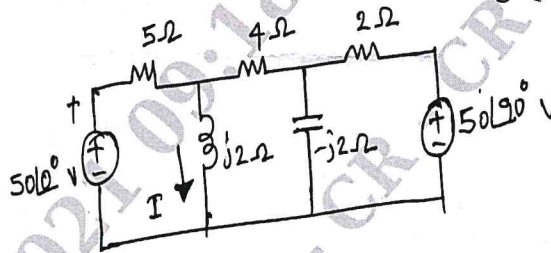


Fig Q2(b)

(08 Marks)

### Module-2

- 3 a. Using Millmans theorem calculate the current through the load (Ref. Fig Q3(a))

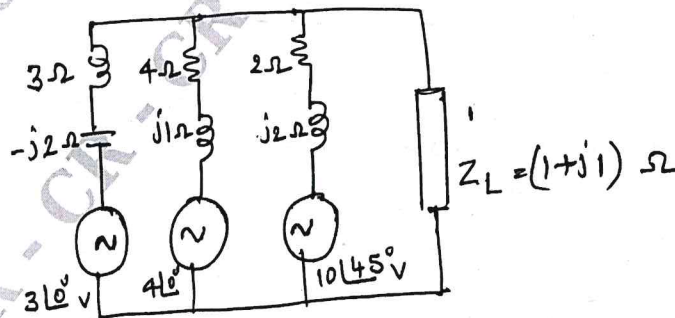


Fig Q 3(a)

(08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- b. Using superposition Theorem find the current  $I$  for the network shown Fig Q3(b).

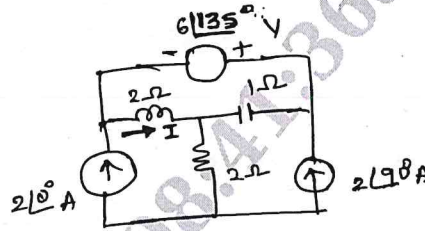


Fig Q3(b)

(08 Marks)

OR

- 4 a. In the circuit shown below Q4(a), find the current through  $R_L = 7.5\Omega$ , using superposition theorem.


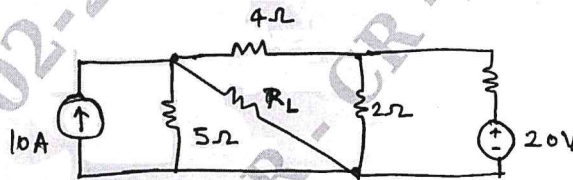


Fig Q4(a)

(08 Marks)

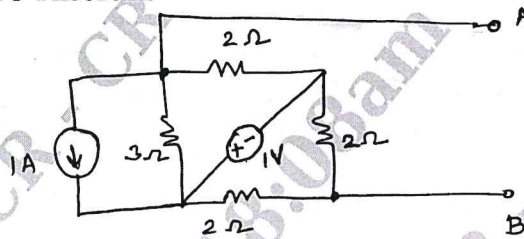- b. Determine the current through  $1\Omega$  resistor connected across AB in the network shown Fig Q4(b). Using Norton's Theorem.



Q4(b)

(08 Marks)

**Module-3**

- 5 a. In the circuit shown in Fig Q5(a), switch 'K' is kept at position A for long time. At  $t = 0$ , switch is moved to position B. Find the expression for current for  $t > 0$ . Find the value of the current at  $t = 13.334$  msec.

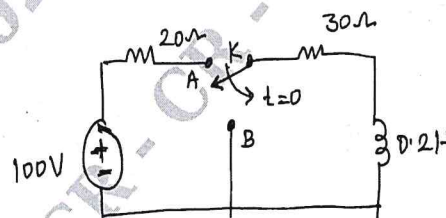


Fig Q5(a)

(08 Marks)

- b. Obtain the expression for current  $i(t)$  for  $t \geq 0$ , using time domain approach for the circuit shown in Fig Q5(b).


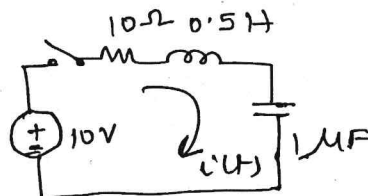


Fig Q5(b)

(08 Marks)

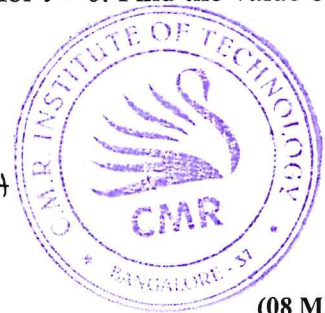

OR

- 6 a. The Network shown Fig Q6(a), is under steady state condition with switch K is at position 1 find expression for  $i(t)$ , if switch K is moved to position 2.

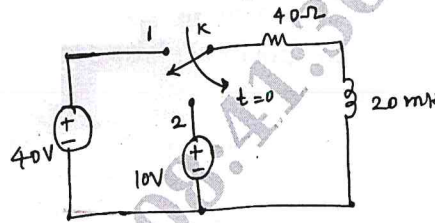


Fig Q6 (a)

(08 Marks)

- b. Find the expression for current in a series RLC circuit fed by a d.c voltage of 20V with  $R = 4\Omega$ ,  $L = 1H$ ,  $C = \frac{1}{4}F$ . Assume initial conditions to be zero.

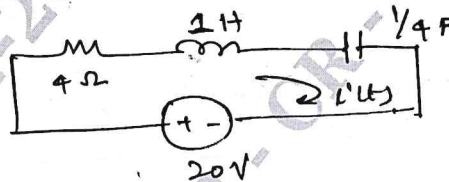


Fig Q6(b)

(08 Marks)

**Module-4**

- 7 a. Express the wave from shown Fig Q7(a), is using of step function

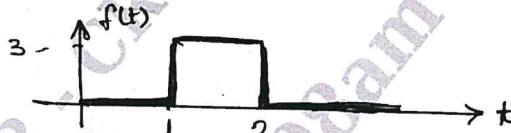


Fig Q7(a)

(06 Marks)

- b. In the series R-C circuit shown Fig Q7 (b), the switch is closed at  $t = 0$ . Obtain the expression for current.

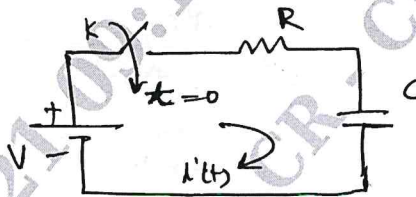


Fig Q7(b)

(10 Marks)

OR

- 8 a. Express the waveform shown in Fig Q8(a) in term of standard functions

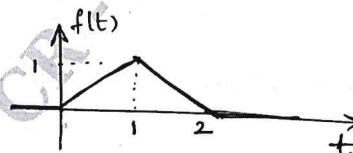


Fig Q8(a)

(08 Marks)

- b. In the circuit shown Fig Q8(b) the switch is closed at  $t = 0$ , derive the expression of the resulting current using Laplace Transform

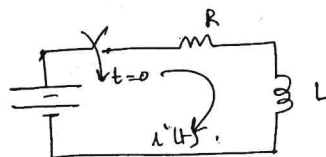


Fig Q8(b)

(08 Marks)

**Module-5**

- 9 a. The balanced load shown in Fig Q9(a), is fed by a balanced three phase system having  $V_{ab} = 230 \angle 0^\circ \text{ V}_{\text{rms}}$ , and position phase sequence, find the reading in each wattmeter and total power drawn by the load.

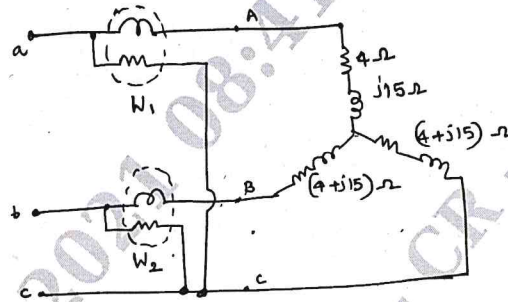


Fig Q9(a)

(08 Marks)

- b. Find the z- parameters for the network shown Fig Q9(b).

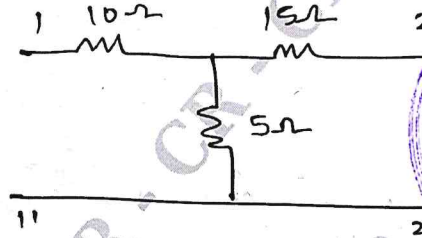


Fig Q9(b)

(08 Marks)

**OR**

- 10 a. For the circuit shown in Fig Q10(a), the loads are  $Z_A = 25 \angle 60^\circ \Omega$ ,  $Z_B = 50 \angle -60^\circ \Omega$ ,  $Z_C = 50 \angle 60^\circ \Omega$ ,  $V_{AB} = 600 \angle 0^\circ \text{ V}_{\text{rms}}$ , and locate point 'x' at C, find  $P_A, P_B, P_C$

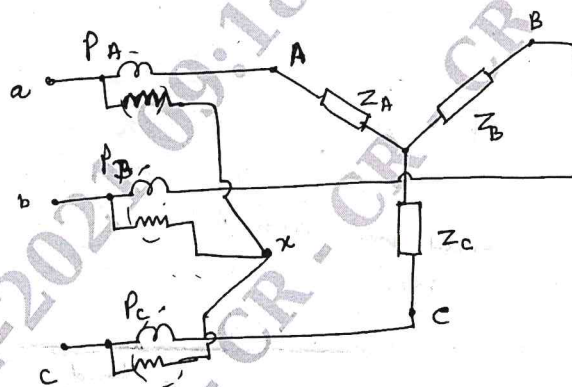


Fig Q10(a)

(08 Marks)

- b. Find Y parameter of the two port Network shown in Fig.Q10(b).

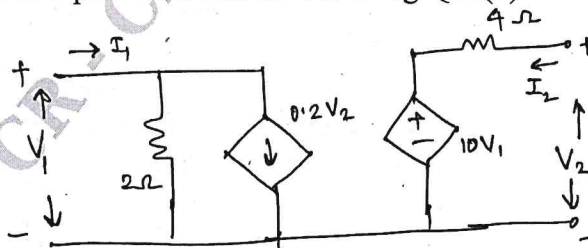


Fig Q10(b)

(08 Marks)

\*\*\*\*\*