



CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EE72

Seventh Semester B.E. Degree Examination, Jan./Feb.2021 Power System Protection

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. With a neat diagram, explain zones of protection in a power system. (06 Marks)
- b. Derive an expression for torque produced by an induction relay. (08 Marks)
- c. List the merits and demerits of static relays. (06 Marks)

OR

- 2 a. Draw a neat sketch of an induction disc relay and discuss its operating principle. (07 Marks)
- b. What are the various types of over current relays? Discuss their area of applications. (06 Marks)
- c. Describe the realization of a overcurrent relay using numerical technique. Show its flowchart with neat diagram. (07 Marks)

Module-2

- 3 a. With a neat schematic diagram, explain the construction and working of static reactance relay using an amplitude comparator. (08 Marks)
- b. With a neat sketch, explain the construction and working principle of induction disc type reverse power relay. (08 Marks)
- c. With neat diagram, explain induction cup type impedance relay. (04 Marks)

OR

- 4 a. Draw and explain the circuit connections of three MHO units used at a particular location for three zones of protection. (07 Marks)
- b. With neat connection diagrams, explain the working of directional earth fault relay. (07 Marks)
- c. With neat diagram, explain static impedance relay using amplitude comparator. (06 Marks)

Module-3

- 5 a. With neat diagram, explain percentage differential protection of star-delta connected transformer. (08 Marks)
- b. With neat diagram, explain the working of Buchholz relay. (05 Marks)
- c. An 11 kV, 150 MVA alternator is provided with differential protection. The percentage of winding to be protected against phase to ground fault is 80%. The relay is set to operate when there is 20% out of balance current. Determine the value of the resistance to be placed in the neutral to ground protection. (07 Marks)

OR

- 6 a. Define the term 'pilot' with reference to power line protection. List the different types of wire pilot protection schemes and explain any one of the schemes. (08 Marks)
- b. With neat diagram, explain harmonic restraint relay used to protect against magnetizing inrush current of transformer. (08 Marks)
- c. With a neat circuit diagram, explain rotor earth fault protection of alternator. (04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

Module-4

- 7 a. In a 132 kV system, reactance and capacitance upto the location of the circuit breaker is 4Ω and $0.02 \mu\text{F}$ respectively. A resistance of 500Ω is connected across the break of the C.B. Determine the (a) natural frequency of oscillation (b) damped frequency of oscillation (c) critical value of resistance. (08 Marks)
- b. Explain working of SF_6 circuit breaker with the help of diagrams. Write two of its advantages. (08 Marks)
- c. Explain recovery rate theory to explain the zero current interruption of the arc. (04 Marks)

OR

- 8 a. Derive expressions for restriking voltage and RRRV in terms of system voltage, inductance and capacitance during fault on feeder. (08 Marks)
- b. With neat circuit diagram, explain the synthetic testing of circuit breaker. (06 Marks)
- c. With neat diagram, explain Air-break circuit breaker. Write any two of its applications. (06 Marks)

Module-5

- 9 a. Describe the construction and operation of the HRC cartridge fuse with indicator. Write any four of advantages of HRC fuses. (08 Marks)
- b. Describe the phenomenon of lightning and explain the terms pilot streamer, stepped leader, return streamer, dart leader, cold lightning stroke and hot lightning stroke. (08 Marks)
- c. Write short note on Arcing horn with diagram. (04 Marks)

OR

- 10 a. Describe the construction and principle of operation of valve type lightning arrester with detailed diagram. (08 Marks)
- b. Write note on klydonograph and magnetic link. (06 Marks)
- c. Describe the protection of stations and sub-stations against direct lightning strokes. (06 Marks)

