

**Third Semester B.E. Degree Examination, Jan./Feb. 2021**  
**Analog Electronic Circuit**

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting atleast TWO questions from each part.**

**PART – A**

- 1 a. Explain the different diode equivalent circuits with necessary approximations if any. (06 Marks)
- b. For the circuit shown in Fig.Q1(b) write transfer characteristic equations and draw the transfer characteristic. The input  $V_{in} = 40\sin\omega t$ . Assume ideal diodes.

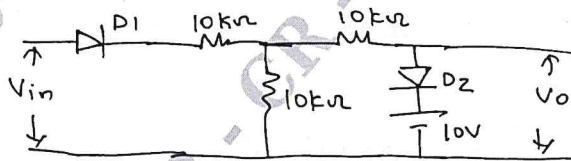


Fig.Q1(b)

(08 Marks)

- c. With a neat circuit explain the working of a biased positive peak clamper. (06 Marks)
- 2 a. Discuss the causes of bias instability in a transistor. (06 Marks)
  - b. With a neat diagram, explain the various time components of practical transistor switching. (06 Marks)
  - c. A voltage divider biased circuit has  $R_1 = 33k\Omega$ ,  $R_2 = 8.2k\Omega$ ,  $R_C = 3.9k\Omega$ ,  $R_E = 1k\Omega$ ,  $V_{CC} = 20V$ . The silicon transistor used has  $\beta$  of 100. Find Q – point and stability factor  $S_{ICO}$ . (08 Marks)
- 3 a. What is modelling of transistor? Draw the different transistor models used with neat labeling of parameters. (06 Marks)
  - b. Derive expression for  $A_V$ ,  $Z_0$ ,  $Z_{in}$  for a voltage divider biased amplifier using re-model. (06 Marks)
  - c. A transistor in CE-mode has  $h_{ie} = 1100\Omega$ ,  $h_{re} = 2 * 10^{-4}$ ,  $h_{fe} = 100$ ,  $h_{oe} = 25\mu S$ . Find  $A_V$ ,  $Z_0$ ,  $Z_{in}$ ,  $A_I$ . Take  $R_L = 1.0k\Omega$  and  $R_S = 500\Omega$ . Also find overall voltage and current gain. (08 Marks)
- 4 a. Draw the high frequency ac equivalent circuit of a voltage divider biased amplifier. Explain with relevant expression the effect of parasitic and wiring capacitance on the high frequency response of amplifier. (10 Marks)
  - b. Derive an expression for miller input and output capacitance. (10 Marks)

**PART – B**

- 5 a. With neat diagram explain the advantage of using :  
 i) Cascade connection    ii) Darlington pair. (06 Marks)
- b. What are the different types of feedback connections? Derive the expression for gain, input impedance and output impedance for a voltage–series feedback circuit. (10 Marks)
- c. List the advantages of negative feedback circuit. (04 Marks)

- 6 a. What are the classification of power amplifiers based on location of operating point. Also mention the operating cycle in each case. (06 Marks)
- b. Explain the working of a class-A transformer coupled power amplifier and devise expression for maximum efficiency. (08 Marks)
- c. Define harmonic distortion. A power amplifier has harmonic distortions  $D_2 = 0.1$ ,  $D_3 = 0.02$ ,  $D_4 = 0.01$ . The fundamental current  $I_1 = 5A$  and  $R_L = 10\Omega$ . Calculate total harmonic distortion, fundamental power and total power. (06 Marks)
- 7 a. Draw the equivalent circuit of a crystal with a neat diagram, explain working of series-resonant crystal oscillator circuit. (08 Marks)
- b. With a circuit diagram, explain working of Hartley oscillator. Give expression for frequency generator. (06 Marks)
- c. Calculate the frequency generated by a BJT RC-phase shift oscillator given  $R = 10k\Omega$ ,  $C = 1200pt$ ,  $R_C = 20k\Omega$ . Determine minimum current gain of the transistor required for sustained oscillations. (06 Marks)
- 8 a. List the differences between BJT and FET. (06 Marks)
- b. With necessary equivalent circuit obtain the expression for  $A_v$ ,  $Z_{in}$ ,  $Z_0$  of a fixed biased common source JFET amplifier. (10 Marks)
- c. A JFET has  $g_m = 6m\Omega$  at  $V_{as} = -1V$ . Find  $I_{DSS}$  if pinch off voltage  $V_p = -2.5V$ . (04 Marks)

\*\*\*\*\*

