

--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, Jan./Feb. 2021 Digital Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Write the following equation in proper canonical form:
 - i) $P = f(a, b, c) = a\bar{b} + \bar{a}b + bc$
 - ii) $T = f(a, b, c) = (a + \bar{b})(\bar{b} + c)$ (06 Marks)
- b. Find all the prime-implicant and essential prime implicant for the given function.
 - i) $D = f(a, b, c, d) = \sum_m(6, 7, 9, 10, 13) + \sum_d(1, 4, 5, 11, 15)$ using K-map and draw the logic diagram.
 - ii) $P = \pi_m(0, 1, 2, 3, 7, 8, 10, 11, 15). \pi_d(9, 14)$ using K-map and draw the logic diagram. (10 Marks)

OR

- 2 a. Simplify the following three-variable equation using K-map. List all the prime-implicant and essential prime implicants. $J = F(x, y, z) = \sum(0, 2, 3, 4, 5, 7)$ (04 Marks)
- b. Find all the prime implicant and essential prime implicant of the function $S = f(a, b, c, d) = \sum(1, 3, 13, 15) + \sum_d(8, 9, 10, 11)$ using Quine-McClusky's algorithm. Draw the logic diagram. (12 Marks)

Module-2

- 3 a. Implement the following multiple output function using 74LS138 3:8 decoder and external gates

$$F_1(A, B, C) = \sum_m(1, 4, 5, 7)$$

$$F_2(A, B, C) = \pi_m(2, 3, 6, 7)$$
 (06 Marks)
- b. What do you mean by priority encoder? Explain 8 to 3 encoder, with highest number having the highest priority with the help of a truth table. (No need of logic circuit). (06 Marks)
- c. Design a 1-bit comparator using logic gates. (04 Marks)

OR

- 4 a. Implement full-Adder using 4:1 Multiplexer. (06 Marks)
- b. Design a 4-bit ripple parallel adder using full adder-blocks. (05 Marks)
- c. Design a full-subtractor using logic gates. (05 Marks)

Module-3

- 5 a. Explain the working of switch debouncer using SR latch. (06 Marks)
- b. Obtain the characteristic equation of i) SR flip-flops ii) JK flip-flops. (04 Marks)
- c. Explain clocked SR flip-flop using NAND gates. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 6 a. Explain the working of Master-Slave JK flip-flop with functional table and timing diagram. Show how race around condition is overcome. (12 Marks)
- b. What is meant by triggering of flip-flops? Name the different triggering methods. (04 Marks)

Module-4

- 7 a. Explain the different types of shift register SISO, PISO, SIPO, PIPO with relevant circuit diagram. (10 Marks)
- b. Design 4-bit asynchronous down counter and explain, using negative edge triggered JK flip flops. (06 Marks)

OR

- 8 a. Design synchronous MOD-8 counter using clocked JK flip-flops. (08 Marks)
- b. Design synchronous MOD-6 counter using clocked T-flip-flops. (08 Marks)

Module-5

- 9 a. Explain the Mealy model and Moore model of a clocked synchronous sequential network. (08 Marks)
- b. Design a clocked sequential circuit that operates according to the state diagram shown in Fig.9(b). Implement the circuit using D-flip-flop. (08 Marks)

 


Fig.9(b)

OR

- 10 a. Give recommended steps for the design of a clocked synchronous sequential networks. (06 Marks)
- b. Design a synchronous counter using JK flip-flops to count the sequence 0, 1, 2, 4, 5, 6, 0, 1, 2. Use state diagram and state table. (10 Marks)
