

Third Semester B.E. Degree Examination, Jan./Feb.2021

Network Analysis

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define the terms with an example,
- (i) Linear and non linear elements.
 - (ii) Lumped and distributed elements.
 - (iii) Unilateral and Bilateral elements.
 - (iv) Active and Passive elements.
- b. Find the current in 28Ω resistor using mesh analysis in Fig. Q1 (b). (08 Marks)

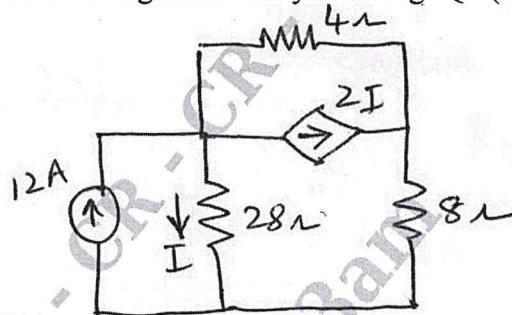


Fig. Q1 (b)

OR

- 2 a. Reduce the network in Fig. Q2 (a) to a single voltage source in series with a resistance using source shift and source transformation.

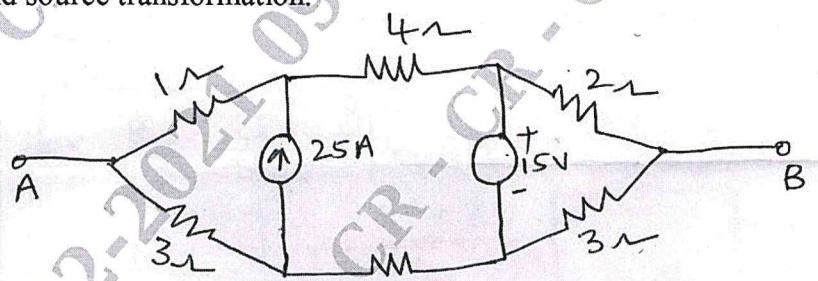


Fig. Q2 (a)

(08 Marks)

- b. The node voltage equations of a network are,

$$\left[\frac{1}{5} + \frac{1}{j2} + \frac{1}{4} \right] V_1 - \frac{1}{4} V_2 = \frac{50 \angle 0^\circ}{5}$$

and

$$-\frac{1}{4} V_1 + \left[\frac{1}{4} + \frac{1}{-2j} + \frac{1}{2} \right] V_2 = \frac{50 \angle 90^\circ}{2}$$

Derive the network.

(08 Marks)

Module-2

- 3 a. State and prove superposition theorem. (08 Marks)
 b. For the circuit shown in fig. Q3 (b), find the current through R_L using Thevenins theorem. (08 Marks)

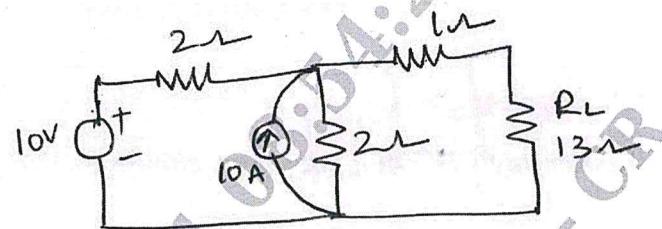


Fig. Q3 (b)

OR

- 4 a. State and prove Millers theorem. (08 Marks)
 b. Find the value of Z_L for which power transferred to the load is maximum and also determine the maximum power for the circuit shown in Fig. Q4 (b). (08 Marks)

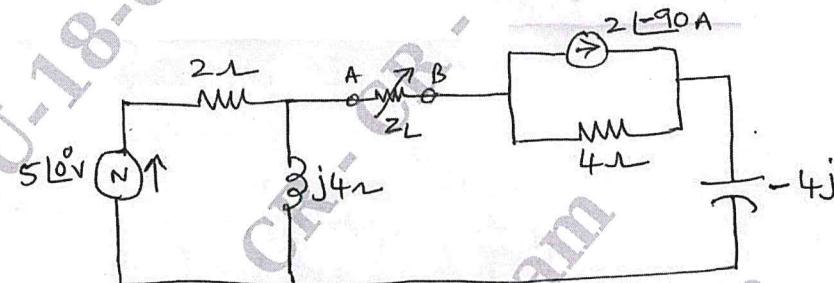


Fig. Q4 (b)

Module-3

- 5 a. In the circuit of Fig. Q5 (a). Switch K is opened at $t = 0$. Find the value of V , $\frac{dV}{dt}$ and $\frac{d^2V}{dt^2}$ at $t = 0^+$. (08 Marks)

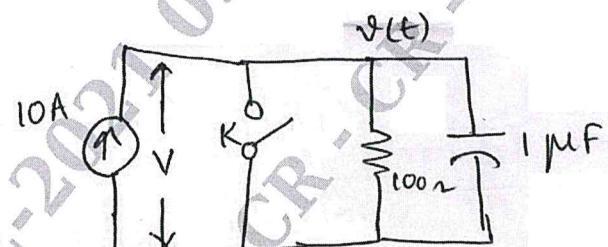


Fig. Q5 (a)

- b. Obtain the Laplace transform of the square wave shown in Fig. Q5 (b). (08 Marks)

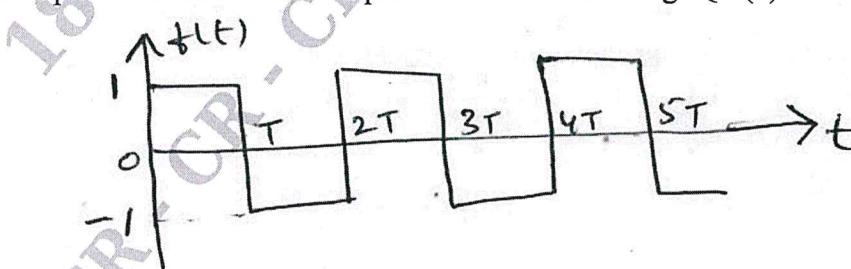


Fig. Q5 (b)

OR

- 6 a. State and prove initial value and final value theorem. (08 Marks)
- b. For the network shown in Fig. Q6 (b) the switch is moved from position 1 to position 2 at $t = 0$ the steady state has been reached before switching. Calculate i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$. (08 Marks)

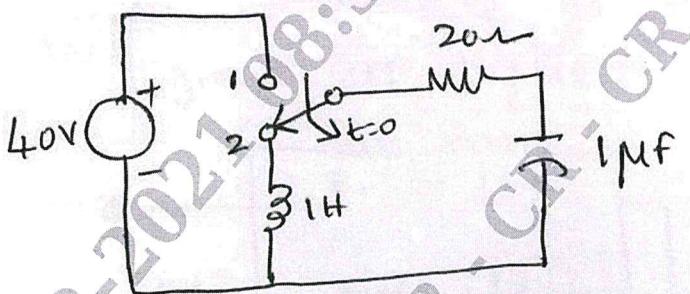


Fig. Q6 (b)

Module-4

- 7 a. Define the following terms :
 (i) Resonance
 (ii) Q-factor
 (iii) Bandwidth
 (iv) Selectivity. (04 Marks)
- b. Derive an expression for frequency of resonance of a parallel resonant circuit containing resistance in both the branches. (06 Marks)
- c. It is required that a series RLC circuit should resonate at 500 kHz. Determine the values of R, L and C if the bandwidth of the circuit is 10 kHz and its impedance is 100 Ω at resonance. Also find the voltages across L and C at resonance, if the applied voltage is 75 volts. (06 Marks)

OR

- 8 a. Show that a two branch parallel resonant circuit is resonant at all the frequencies if $R_L = R_C = \sqrt{\frac{L}{C}}$ where R_L = Resistance in the inductor branch, R_C = Resistance in the capacitor branch. (06 Marks)
- b. Give the comparison between series and parallel resonance. (04 Marks)
- c. Find the value of R_1 such that the circuit given in Fig. Q8 (c) is resonant. (06 Marks)

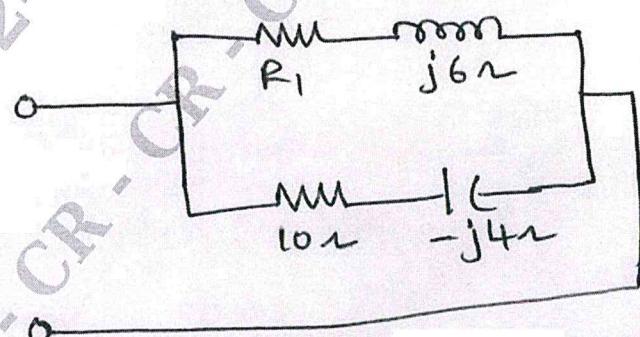


Fig. Q8 (c)

Module-5

- 9 a. Express Y parameters in terms of Z and T parameters.
 b. Find the transmission parameters for the network shown in Fig. Q9 (b).

(08 Marks)

(08 Marks)

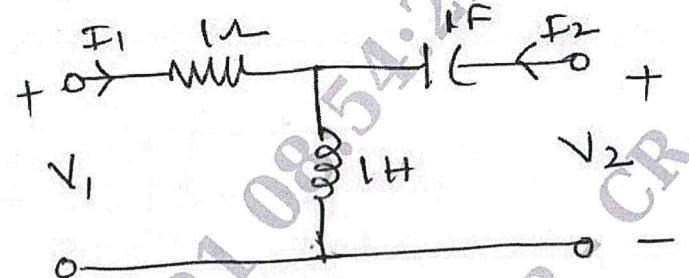


Fig. Q9 (b)

OR

- 10 a. Express ABCD parameters in terms of Y and h parameters.
 b. Find the h parameters of the network shown in Fig. Q10 (b).

(08 Marks)

(08 Marks)

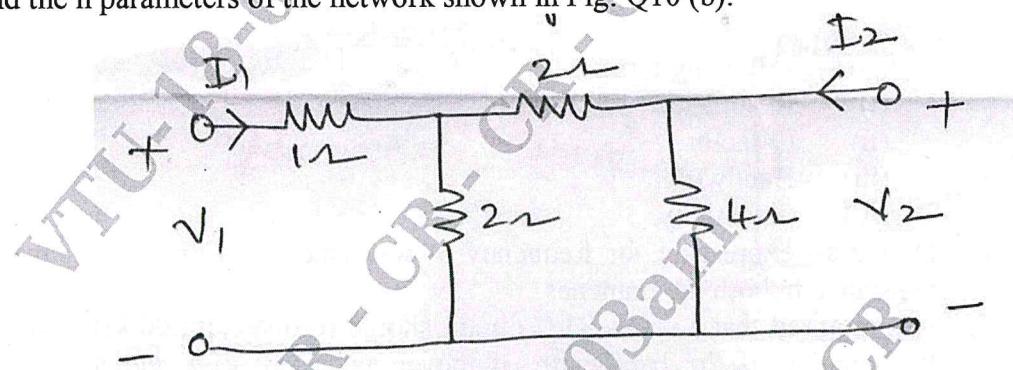


Fig. Q10 (b)
