

CBCS SCHEME

17EE32

Third Semester B.E. Degree Examination, Jan./Feb. 2021 Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define and distinguish the following network elements :
 - i) Active and passive elements
 - ii) Linear and nonlinear circuits
 - iii) Unilateral and Bilateral circuits
 - iv) Lumped and distributed elements. (08 Marks)
- b. Reduce the network shown in Fig.Q1(b) to a single voltage source in series with a resistance using source transformations.

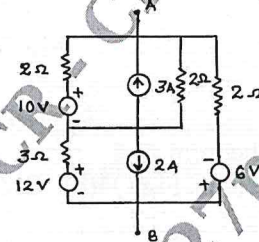


Fig.Q1(b)

(06 Marks)

- c. Derive an expression for Δ to Y transformations. (06 Marks)

OR

- 2 a. The network contains two voltage sources v_1 and v_2 as shown in Fig.Q2(a) with $v_1 = 30\angle 0^\circ$ volts. Determine v_2 , such that current in $2 + j3\Omega$ impedance is zero. Use Mesh analysis.

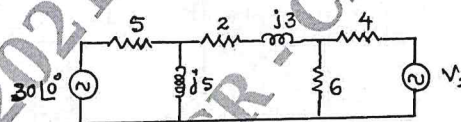


Fig.Q2(a)

(06 Marks)

- b. Determine v_1 and v_2 for the circuit shown in Fig.Q2(b) by using node analysis.

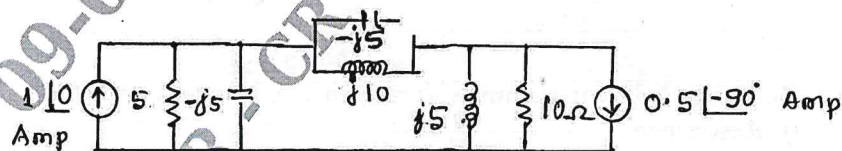


Fig.Q2(b)

(08 Marks)

- c. For the network shown in Fig.Q2(c), draw its dual network.

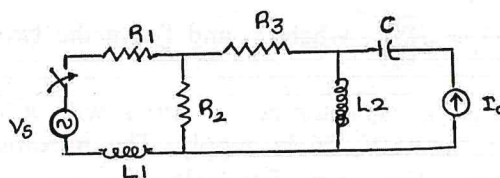


Fig.Q2(c)

(06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-2

- 3 a. State the super position theorem. (06 Marks)
 b. In the circuit of Fig.Q3(b), use super position principle to determine the value of i_x .

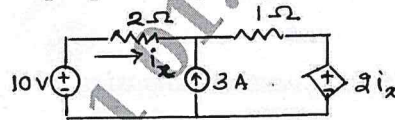


Fig.Q3(b)

(06 Marks)

- c. Find the current i_x and hence verify reciprocity theorem for the network in Fig.Q3(c).

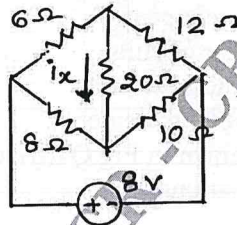


Fig.Q3(c)



(08 Marks)

OR

- 4 a. State the Thevenin's theorem. (06 Marks)
 b. For the network shown in Fig.Q4(b). Obtain the Thevenin's equivalent as seen from the terminals p and q.

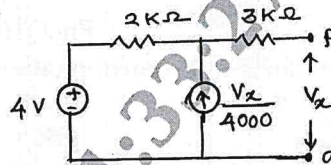


Fig.Q4(b)

(08 Marks)

- c. Find the Norton's equivalent for the circuit shown in Fig.Q4(c).

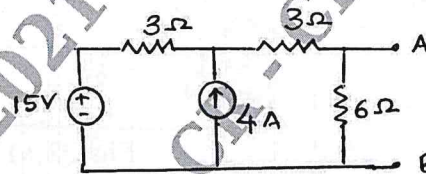


Fig.Q4(c)

(06 Marks)

Module-3

- 5 a. Define the following terms with reference to resonant circuit. (08 Marks)
 i) Resonance
 ii) Q – factor
 iii) Selectivity
 iv) Bandwidth.
 b. Prove that $f_r = \sqrt{f_1 f_2}$, where f_1 and f_2 are the two half power frequencies of a resonant circuit. (06 Marks)
 c. A resistor and a capacitor are in series with a variable inductor. When the circuit is connected to a 200V, 50Hz supply. The maximum current obtainable by varying the inductance is 0.314 Amp. The voltage across the capacitor is 300V. Find the circuit constants. (06 Marks)

OR

- 6 a. In the network of Fig.Q6(a), K is changed from position a to b at $t = 0$. Solve for i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0+$, if $R = 1000\Omega$, $L = 1H$, $c = 0.1\mu F$ and $v = 100$ volts.

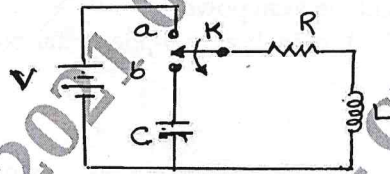


Fig.Q6(a)

(10 Marks)

- b. In the network shown in Fig.Q6(b), the switch K is opened at $t = 0$. At $t = 0+$, solve for the value of v , $\frac{dv}{dt}$ and $\frac{d^2v}{dt^2}$, if $I = 10$ Amp, $R = 1000\Omega$ and $c = 1\mu F$.

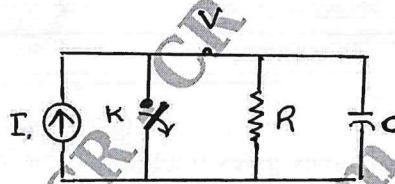


Fig.Q6(b)

(10 Marks)

Module-4

- 7 a. Find the Laplace transform of the periodic wave form as shown in Fig.Q7(a).

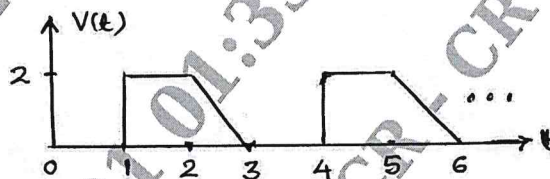


Fig.Q7(a)

- b. Find the Laplace transform of the periodic wave form as shown in Fig.Q7(b).

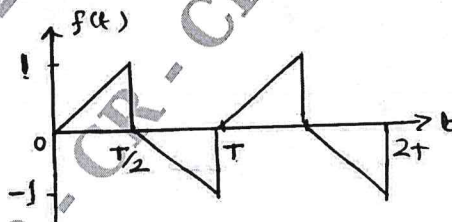


Fig.Q7(b)

(10 Marks)

OR

- 8 a. State and prove :
 i) Initial value theorem
 ii) Final value theorem. (10 Marks)

- b. Calculate $i(0+)$ using initial value theorem, given that the transform function of the current

$$I(s) = \frac{2s+5}{(s+1)(s+2)}. \text{ Determine } i(t) \text{ and obtain its value at } t = 2\text{sec.} \quad (10 \text{ Marks})$$



Module-5

- 9 a. A three – phase, four wire, 208 volts ABC system supplies a star connected load in which $Z_A = 10\angle 0^\circ$ ohms $Z_B = 15\angle 30^\circ$ ohms and $Z_C = 10\angle -30^\circ$ ohms. Find the line currents, the neutral current and the total power. (12 Marks)
- b. Explain the method of analyzing 3-phase star connected load by using Milliman's theorem. (08 Marks)

OR

- 10 a. Obtain Z and Y parameters for the circuit shown in Fig.Q10(a).

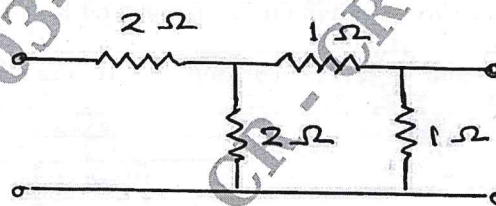


Fig.Q10(a)

(10 Marks)

- b. The following equations gives the relationship between the voltage and currents of a two-port network $I_1 = 0.25v_1 - 0.2v_2$, $I_2 = -0.2v_1 - 0.1v_2$. Obtain T-parameters. (10 Marks)
