

CBCS SCHEME

17EE35



Third Semester B.E. Degree Examination, Jan./Feb. 2021 Digital System Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define the following terms with example :
i) Literal ii) Maxterm iii) Sumterm iii) Product of sum v) Canonical sum of products. (05 Marks)
- b. Reduce the following function using K-map technique and implement using NAND gates only
i) $f_1(P, Q, R, S) = \sum m(0, 1, 4, 7, 8, 9, 10) + d(2, 11)$
ii) $f_2(A, B, C, D) = \pi(0, 2, 4, 10, 11, 14, 15)$ (10 Marks)
- c. Reduce the following function using K-map and implement using NOR gate only
 $f_3(A, B, C, D) = \sum m(0, 5, 7, 8, 10, 13) + d(2, 4, 14, 15)$ (05 Marks)

OR

- 2 Reduce the following function using Quine - McClusky method and shall all the tables including Reduced prime implicant table
 $Q_1 = f(a, b, c, d, e) = \sum(1, 3, 4, 5, 6, 7, 10, 11, 12, 13, 14, 15, 18, 19, 20, 21, 22, 23, 26, 27)$ (20 Marks)

Module-2

- 3 a. Implement the following multiple output function using single 74LS138 (3 to 8 decoder) and external gates.
 $F_1(A, B, C) = \overline{AB} + ABC + AC$
 $F_2(A, B, C) = \pi M(2, 3, 6, 7)$ (04 Marks)
- b. Implement the following function
i) $f_1(A, B, C, D) = \sum m(0, 2, 6, 10, 11, 12, 13) + d(3, 8, 14)$ using 74LS151 (8:1 MUX) considering Lower order inputs as select inputs.
ii) $f_2(A, B, C, D) = \sum m(0, 2, 3, 4, 6, 7, 9, 11, 13, 15)$ using 74LS153 (4:1 MUX) considering higher order inputs as select inputs. (08 Marks)
- c. Develop the following combinational logic
i) Construct full subtracter using 74LS153
ii) Construct 4 to 16 decoder using 2 to 4 decoders only. (08 Marks)

OR

- 4 a. Draw the full Adder ckt from truth table. Construct a four bit adder and explain it. (06 Marks)
- b. Draw a 1 bit comparator and explain. (04 Marks)
- c. Develop a look ahead carry adder from full adder. Draw the compute structure including look ahead carry generator and final Adder. (10 Marks)

Module-3

- 5 a. Analyze the application of SRFF as switch debouncer with waveforms. (04 Marks)
- b. Explain the working principles of gated SR latch with truth table next state table, excitation table and characteristic equation. (08 Marks)
- c. Draw the Master - Slave JK flip-flop and explain its working. Draw the truth table, what is race around condition? How it can overcome? (08 Marks)

OR

- 6 a. Draw and explain universal shift Registers. (12 Marks)
- b. Design and draw Mod 6 Asynchronous counter. (08 Marks)

Module-4

- 7 a. Construct the sequential logic circuit of following state diagram using JKFF. Clearly show the state table, transition table, excitation table, expression and sequential logic diagrams.

 


Fig Q7(a)



(10 Marks)

- b. Analyze the sequential circuit below :
 - i) Derive the state table
 - ii) Sketch the transition state diagram
 - iii) Describe in words the functionality of the circuit


 


Fig Q7(b)

(10 Marks)

OR

 - 8 a. Design Mod 4 synchronous up down counter using JKFF. (10 Marks)
- b. Design a synchronous counter that counts the following sequence



(10 Marks)

Module-5

- 9 a. What are the different VHDL Descriptions? (05 Marks)
- b. Write the VHDL program for Half Adder in
 - i) Behavioral Descriptions
 - ii) Structural Descriptions
 - iii) Dataflow Descriptions. (15 Marks)

OR

- 10 a. Explain the structure of Data-flow Descriptions. (07 Marks)
- b. What are the different operators and data types in VHDL? (08 Marks)
- c. Compare VHDL and Verilog. (05 Marks)
