

# IAT -3 (ADE)

The respondent's email address (**srri19cs@cmrit.ac.in**) was recorded on submission of this form.

NAME \*

Sreena Rizal

SECTION \*

C

USN \*

1CR19CS216

In an SR latch made by cross-coupling two NAND gates, if both S and R inputs are set to 0, then it will result in \* 1 point

- MEMORY State
- RESET State
- SET State
- FORBIDDEN State
- Other: .....

How is a J-K flip-flop made to toggle? \*

1 point

- J = 1, K = 0
- J = 0, K = 0
- J = 1, K = 1
- J = 0, K = 1

Which statement BEST describes the operation of a negative-edge-triggered D flip-flop? \*

2 points

- The logic level at the D input is transferred to Q on NGT of CLK.
- The Q output is ALWAYS identical to the CLK input if the D input is HIGH.
- The Q output is ALWAYS identical to the D input when CLK = PGT.
- The Q output is ALWAYS identical to the D input.

How many flip-flops are required to produce a divide-by-128 device? \*

1 point

- 128
- 64
- 7
- None of These

On a master-slave flip-flop, when is the master enabled? \*

1 point

- When clock is HIGH
- When clock is LOW
- Both of the above
- Neither of the above

Which of the following is correct for a gated D flip-flop? \*

1 point

- The output toggles if one of the inputs is held HIGH.
- Only one of the inputs can be HIGH at a time.
- The output complement follows the input when enabled.
- Q output follows the input D when the enable is HIGH.


A J-K flip-flop is in a "no change" condition when \*

1 point

- $J = 1, K = 1$
- $J = 1, K = 0$
- $J = 0, K = 1$
- $J = 0, K = 0$

The figure shows mod-K counter, where k value is \*

2 points

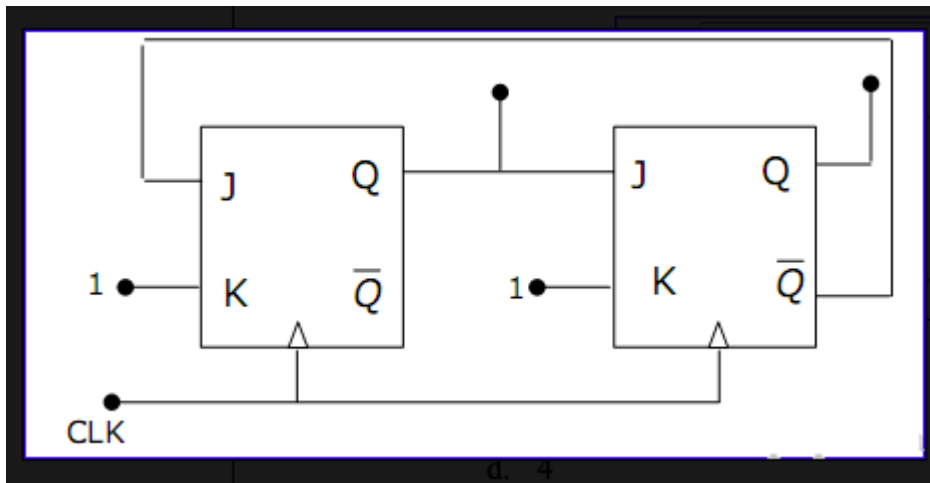

- 1
- 2
- 3
- 4

What is the maximum possible range of bit-count specifically in n-bit binary counter consisting of 'n' number of flip-flops? \*

2 points

- 0 to  $2^n$
- 0 to  $2^n + 1$
- 0 to  $2^n - 1$
- 0 to  $2^{(n+1/2)}$

A counter circuit is usually constructed of \*

1 point

- A number of NOR gates connected in cascade form
- A number of latches connected in cascade form
- A number of NAND gates connected in cascade form
- A number of flip-flops connected in cascade

Three decade counter would have \*

1 point

- 2 BCD counters
- 3 BCD counters
- 4 BCD counters
- 5 BCD counters

The parallel outputs of a counter circuit represent the \*

1 point

- Parallel data word
- Clock frequency
- Counter modulus
- Clock count

How many flip-flops are required to construct a decade counter? \*

1 point

- 4
- 5
- 8
- 10

The terminal count of a typical modulus-10 binary counter is \_\_\_\_\_ \*

2 points

- 0000
- 1010
- 1001
- 1111

A 5-bit asynchronous binary counter is made up of five flip-flops, each with a 12 ns propagation delay. The total propagation delay ( $t_{p(\text{total})}$ ) is \*

2 points

- 12 ms
- 24 ns
- 48 ns
- 60 ns

Three cascaded decade counters will divide the input frequency by \*

1 point

- 0
- 20
- 100
- 1000

A 4-bit counter has a maximum modulus of

1 point

- 3
- 6
- 8
- 16

In a 3-bit asynchronous down counter, at the first negative transition of the clock, the counter content becomes \*

2 points

- 000
- 111
- 101
- 010

Modulus refers to \_\_\_\_\_ \*

1 point

- A method used to fabricate decade counter units
- The modulus of elasticity, or the ability of a circuit to be stretched from one mode to another
- An input on a counter that is used to set the counter state, such as UP/DOWN
- The maximum number of states in a counter sequence

The minimum number of flip-flops that can be used to construct a modulus-5 counter is 1 point

- 3
- 8
- 5
- 10

What is state diagram? \*

1 point

- It provides the graphical representation of states
- It provides exactly the same information as the state table
- It is same as the truth table
- It is similar to the characteristic equation



In mealy machine, the O/P depends upon? \*

2 points

- Present States of FlipFlops
- Previous State of FlipFlops
- Present States of FlipFlops and Input Sequence
- Only Input Sequence


The major difference between Mealy and Moore machine is about: \*

1 point

- Output Variations
- Input Variations
- Both
- None of the mentioned

Two D flipflops are to be connected as a synchronous counter as shown below, that goes through the following  $Q_1Q_0$  sequence  $00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00 \rightarrow \dots$ . The inputs  $D_0$  and  $D_1$  should be connected as \*

4 points

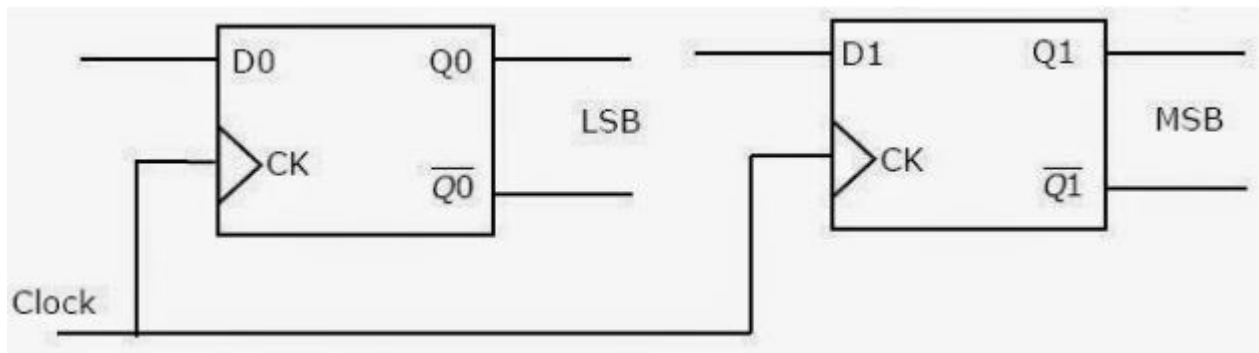

- $Q_1' \& Q_0$
- $Q_1'Q_0 \& Q_1Q_0'$
- $Q_1'Q_0' \& Q_1Q_0$
- $Q_0' \& Q_0 \oplus Q_1$


Consider a 4 bit Johnson counter with an initial value of 0000. The counting sequence of this counter is: \*

2 points

- 0, 1, 3, 7, 15, 14, 12, 8, 0
- 0, 1, 3, 5, 7, 9, 11, 13, 15, 0
- 0, 2, 4, 6, 8, 10, 12, 14, 0
- 0, 8, 12, 14, 15, 7, 3, 1, 0

For the circuit shown, the counter state (Q<sub>0</sub>Q<sub>1</sub>) follows the sequence \*


3 points

 

- 00,01,10,11,00
- 00,01,10,00,01
- 00,01,11,00,01
- 00,10,11,00,10

The circuit shown choose the correct timing diagram for the o/p Y from the given waveforms. \*

2 points

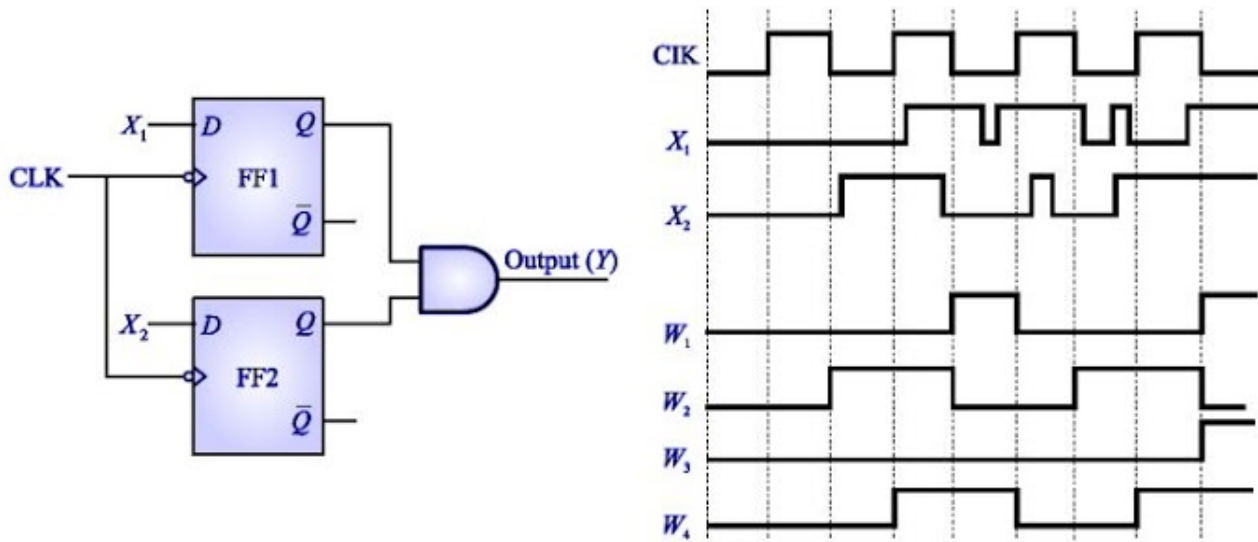

- W1  
 W2  
 W3  
 W4


The number of flipflops required to construct a 8 bit shift register is \*

1 point

- 4  
 8  
 16  
 32

In the below drawn schematic, what does an arrow between the circles indicate? \*

1 point

 

- Present state
- Next state
- State transition
- Don't care condition

On the second falling edge of clock in ring counter, if the generated output of second clock pulse is '0100', what will be the output after the fourth clock pulse? \*

1 point

- 1000
- 0001
- 0010
- 0000


For a ring counter, the number of output states are always equal to \_\_\_\_\_ \*

1 point

- Number of input states
- Number of clock pulses
- Number of registers
- Number of flip flops

Referring to the diagram, if all inputs are loaded simultaneously and output is loaded bit by bit, then what will be the mode of operation for a shift register? \*

1 point

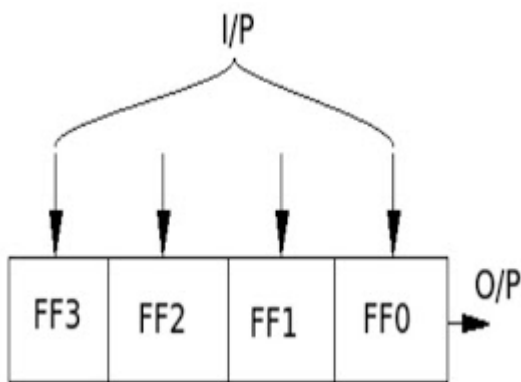

- Serial Input Serial Output (SISO)
- Serial Input Parallel Output (SIPO)
- Parallel Input Serial Output (PISO)
- Parallel Input Parallel Output (PIPO)

A counter is fundamentally a \_\_\_\_\_ sequential circuit that proceeds through the predetermined sequence of states only when input pulses are applied to it. \*

1 point

- register
- memory unit
- flipflop
- arithmetic logic unit

Match the following sequential Circuits with associated functions \*

3 points

	Storage of Program & data in a digital computer	Generation of timing variables to sequence the digital system operations	Design of Sequential Circuits
Counter	<input type="radio"/>	<input checked="" type="radio"/>	<input type="radio"/>
Register	<input type="radio"/>	<input type="radio"/>	<input checked="" type="radio"/>
Memory	<input checked="" type="radio"/>	<input type="radio"/>	<input type="radio"/>

This form was created inside of CMR Institute of Technology.

Google Forms