

# Internal Assessment Test 1 -18EE32 - ECA-3rd Sem

Your email address ([agalya@cmrit.ac.in](mailto:agalya@cmrit.ac.in)) will be recorded when you submit this form. Not you? [Switch account](#)

\* Required

Name \*

Your answer

US NUMBER \*

Your answer

Email ID \*

Your answer

Section \*

Your answer



what is the formula to check the number of loops,nodes and branches CO1 1 point [L2]

- $l = b+n+1$
- $l = b-n+1$
- $l = b+n-1$
- $i = b-n-1$

Clear selection

Potential difference in electrical terminology is known as? CO1 [L2] 1 point

- Voltage
- Current
- Resistance
- Conductance

Clear selection

The circuit in which current has a complete path to flow is called \_\_\_\_\_ 1 point circuit CO1 [L2]

- short
- open
- closed
- open loop

Clear selection



Kirchhoff's current law is applied at CO1 [L2]

1 point

- loops
- none of the mentioned
- nodes
- both loop and node

Clear selection

For a voltage source to be neglected, the terminals across the source should be CO1 [L2]

1 point

- replaced by inductor
- short circuited
- none of the mentioned
- replaced by some resistance

Clear selection

In case of ideal current sources, they have CO1 [L2]

1 point

- zero internal resistance
- low value of voltage
- large value of current
- infinite internal resistance

Clear selection



A practical current source can also be represented as CO1 [L2]

1 point

- a resistance in parallel with an ideal voltage source
- a resistance in parallel with an ideal current source
- a resistance in series with an ideal current source
- none of the mentioned

Clear selection

A dependent source CO1 [L2]

1 point

- may be a current source or a voltage source
- is always a voltage source
- is always a current source
- none of the mentioned

Clear selection

In a circuit with more number of loops, which law can be best suited for the analysis? CO1 [L2]

1 point

- KCL
- Ohm's law
- KVL
- none of the mentioned

Clear selection



In nodal analysis how many nodes are taken as reference nodes? CO1 [L2] 1 point

- 1
- 2
- 3
- 4

Clear selection

Constant voltage source is CO1 [L2] 1 point

- active and bilateral
- passive and bilateral
- active and unilateral
- passive and unilateral

Clear selection

If the voltage-current characteristics are a straight line through the origin, then the element is said to be? CO1 [L2] 1 point

- Linear element
- Non-linear element
- Unilateral element
- Bilateral element

Clear selection



The current law represents a mathematical statement of fact that CO1 [L2] 1 point

- voltage cannot accumulate at node
- charge cannot accumulate at node
- charge at the node is infinite
- none of the mentioned

Clear selection

An electric current of 10 A is the same as CO1 [L2]

1 point

- 10 J/C
- 10 V/C
- 10C/sec
- 10 W/sec

Clear selection

In which of the following cases is Ohm's law not applicable? CO1 [L2]

1 point

- Electrolytes
- Arc lamps
- Insulators
- Vacuum ratio values

Clear selection



In a network consisting of linear resistors and ideal voltage source, if the value of resistors are doubled, then voltage across each resistor CO1 [L2] 1 point

- increases four times
- remains unchanged
- doubled
- halved

Clear selection

If a current source is to be neglected, the terminals across the source are CO1 [L2] 1 point


- replaced by a source resistance
- open circuited
- replaced by a capacitor
- short circuited

Clear selection



Determine the current  $I_1$  in the given circuit CO1 [L2]

4 points

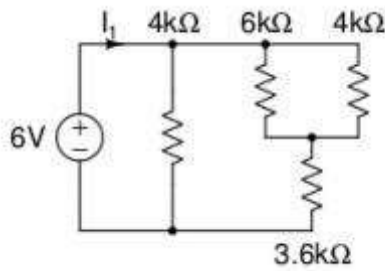


- 2mA
- 2.5mA
- 1mA
- 2.25mA

Clear selection

Using nodal analysis, determine the node 1 voltage in the network shown in the figure CO1 [L3]

4 points

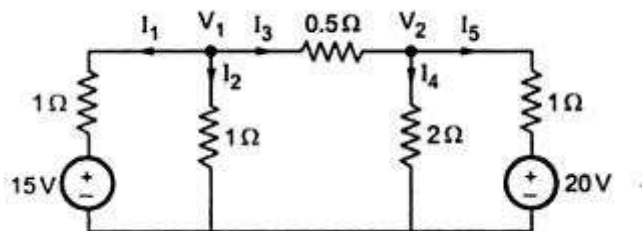

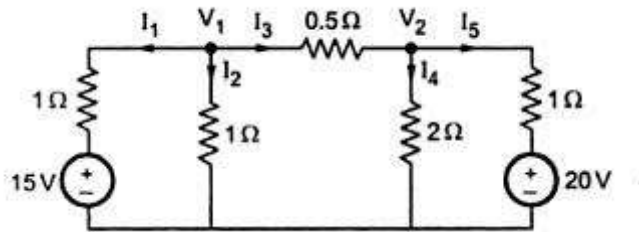
- 9.21V
- 9.42V
- 9.45V
- 9.25V

Clear selection






Using nodal analysis, determine the node 2 voltage in the network shown in the figure CO1 [L3] 3 points



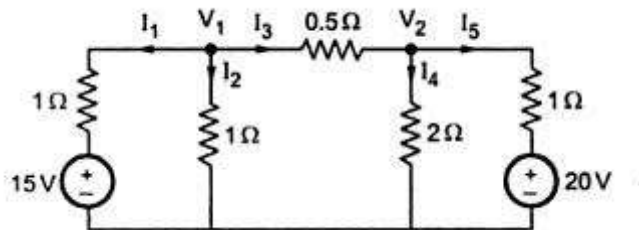- 11.3V
- 11.25V
- 11V
- 11.37V

Clear selection

Using nodal analysis, determine the current through 1Ω resistor in the network shown in the figure CO1 [L3] 4 points




- 9A
- 9.5A
- 9 A
- 9.5A

Clear selection



Write the mesh equation 1 for the given problem CO1 [L3]

3 points

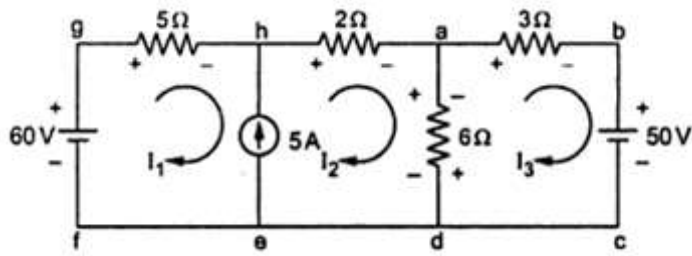

$$5I_1 + 8I_2 - 6I_3 = 60$$

 Option 1

$$5I_1 - 8I_2 - 6I_3 = 60$$

 Option 2

$$-5I_1 - 8I_2 - 6I_3 = 60$$

 Option 3

$$-5I_1 - 8I_2 + 6I_3 = 60$$


 Option 4

Clear selection



Write the mesh equation 2 for the given problem CO1 [L3]

3 points

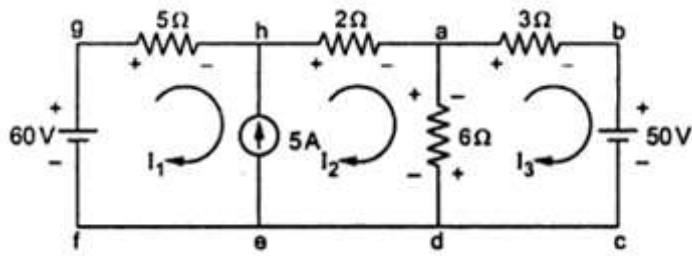

$$-6I_2 - 9I_3 = -50$$

Option 1

$$-6I_2 + 9I_3 = -50$$

Option 2

$$6I_2 - 9I_3 = -50$$

Option 3

$$6I_2 + 9I_3 = -50$$


Option 4

Clear selection



Find the current through a-b using mesh analysis CO1 [L3]

3 points

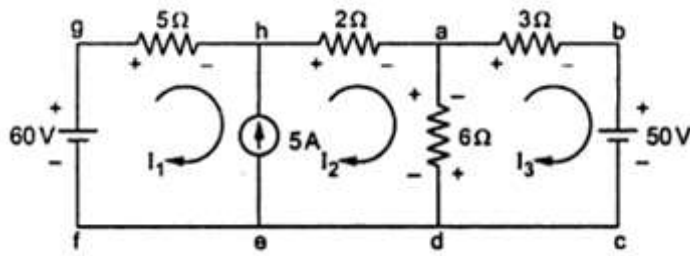


- 1.72A
- 1.73A
- 1.78A
- 1.7A

Clear selection

Using nodal analysis, determine the node 1 voltage in the network shown in the figure CO1 [L3]

3 points

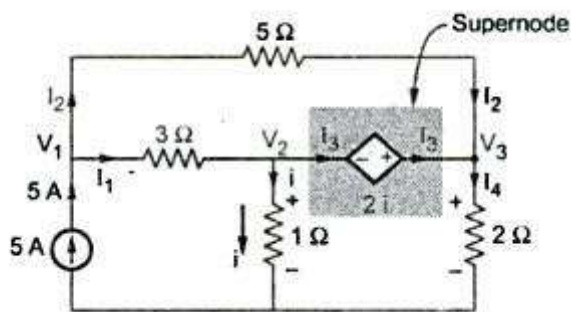


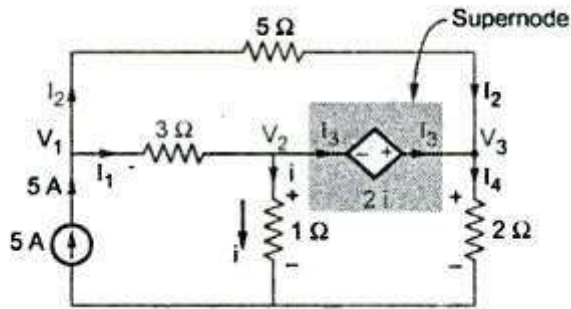- 8.1V
- 8.1V
- 8.12V
- 8.13V

Clear selection




Using nodal analysis, determine the node 2 voltage in the network shown in the figure CO1 [L3] 3 points



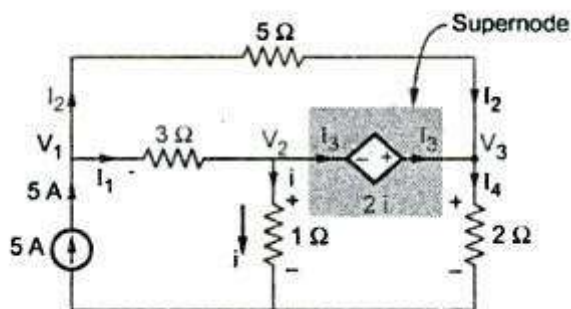- 10.5V
- 10.15V
- 10V
- 10.25V

Clear selection

Using nodal analysis, determine the current through 5Ω resistor in the network shown in the figure CO1 [L3] 3 points



- 4.372A
- 4.373A
- 4.375A
- 4.378A

Clear selection



Send me a copy of my responses.

Submit

Never submit passwords through Google Forms.

This form was created inside of CMR Institute of Technology. [Report Abuse](#)

Google Forms

