

# IAT-1 EEM 2020

For A and B sections

The respondent's email address (**udch19ee@cmrit.ac.in**) was recorded on submission of this form.

To increase the Q factor of a coil, the wire should be \*

1 point

- long
- thin
- thick
- long and thin

USN \*

1CR19EE086

Name(IN CAPITAL LETTERS)

UDAY KIRAN CHINTALA

Assertion (A): De sauty's bridge is suitable only for a pure capacitor. Reason (R): Capacitors are mostly perfect. \*

1 point

- Both A and R are true and R is correct explanation of A
- Both A and R are true but R is not correct explanation of A
- A is true R is false
- A is false R is true

In the simplest form, an AC bridge consists of \_\_\_\_\_ \*

1 point

- a) arms, source and a detector
- b) arms and source
- c) source and detector
- d) arms and detector

At high frequency, source consists of \_\_\_\_\_ \*

1 point

- a) amplifiers
- b) regulators
- c) oscillators
- d) op amps

Commonly used balance detectors for AC bridges are headphones, tuned amplifiers, and vibration galvanometers. \* 1 point

- a) True
- b) False

AC bridge is an outcome of \_\_\_\_\_ \* 1 point

- a) Kelvin bridge
- b) Megger
- c) De Sauty bridge
- d) Wheatstone bridge

When the bridge is balanced, what is the current flowing through the galvanometer? \* 1 point

- a) 0
- b) depends on the ratio arms R1 and R2
- c) varies by a factor of 2
- d) depends on the type of null detector used

Amount of deflection of the galvanometer depends on \_\_\_\_\_ \*

1 point

- a) resistance of the ratio arms
- b) sensitivity
- c) current flowing through the bridge
- d) emf across the circuit

Sensitivity is defined as \_\_\_\_\_ \*

1 point

- a) amount of voltage per unit current
- b) amount of power per unit voltage
- c) amount of resistance per unit voltage
- d) amount of deflection per unit current

Sensitivity is expressed in \_\_\_\_\_ \*

1 point

- a) cm/A
- b) m/mA
- c) mm/ $\mu$ A
- d) inch/nA

What is the relation between the sensitivity and deflection for a galvanometer? \*

1 point

- a) directly proportional
- b) inversely proportional
- c) independant of each other
- d) depends on the type of galvanometer used

The voltage sensitivity of a galvanometer is given by \_\_\_\_\_ \*

1 point

- a)  $S_v = e/\theta$
- b)  $S_v = \theta/e$
- c)  $S_v = 1/e$
- d)  $S_v = 1/\theta$

Unit of voltage sensitivity is \_\_\_\_\_ \*

1 point

- a) volts per degrees
- b) amps per ohms
- c) degrees per volts
- d) watts per amps

Bridge sensitivity is defined as \_\_\_\_\_ \*

1 point

- a)  $SB = \theta/R$
- b)  $SB = \theta/\Delta R$
- c)  $SB = 1/(\Delta R/R)$
- d)  $SB = \theta/(\Delta R/R)$

High resistances are of the order of \_\_\_\_\_ \*

1 point

- a)  $0.1 \text{ M}\Omega$
- b)  $10 \text{ m}\Omega$
- c)  $1 \text{ k}\Omega$
- d)  $10 \text{ G}\Omega$

Megger is a \_\_\_\_\_ \*

1 point

- a) source of e.m.f
- b) source to measure high resistance
- c) type of a null detector
- d) current carrier

Megger is also used for \_\_\_\_\_ \*

1 point

- a) providing additional e.m.f
- b) bridge balance
- c) testing insulation resistance
- d) controlling the temperature

Megger works on the principle of \_\_\_\_\_ \*

1 point

- a) kirchhoff's current laws
- b) ohm's law
- c) gauss's law
- d) electromagnetic induction

Kelvin's bridge consists of \_\_\_\_\_ \*

1 point

- a) double bridge
- b) single bridge
- c) half bridge
- d) three fourth bridge

What is the balance equation of the Kelvin bridge? \*

1 point

- a)  $R_x = R_2 R_3 / R_1$
- b)  $R_x = R_1 R_2 / R_3$
- c)  $R_x = R_1 / R_2$
- d)  $R_x = R_1 R_3 / R_2$

What is the effect of load and contact resistance in the Kelvin bridge? \*

1 point

- a) independent
- b) fully dependent
- c) partially dependent
- d) depends on the resistance value

The relation between the ratio of resistance arms and the ratio of resistance arms of the second bridge is \_\_\_\_\_ \*

1 point

- a) unequal
- b) equal
- c) twice
- d) one forth



Why Kelvin bridge is used for measurement of low resistance? \*

1 point

- a) due to e.m.f source used
- b) due to a large current flow
- c) due to contact and lead resistance
- d) due to power dissipation across the circuit

Why can't a Kelvin bridge be used for the measurement of low-Quality factor value? \* 1 point

- a) due to thermoelectric effect
- b) due to balance problem
- c) due to the dull detector used
- d) due to temperature

How is the condition of an earth electrode measured? \*

1 point

- a) by measuring the voltage
- b) by measuring the current
- c) by measuring the power
- d) by measuring resistance

After earthing, the different parts of an electrical machinery are at \_\_\_\_\_ \* 1 point

- a) infinite potential
- b) intermediate potential
- c) zero potential
- d) undefined potential

Connection of the various parts of a circuit to earth has a \_\_\_\_\_ \* 1 point

- a) medium resistance
- b) high resistance
- c) very high resistance
- d) very low resistance

What is an earth electrode? \* 1 point

- a) electrode that is connected to earth
- b) material used for earthing
- c) electrode connected to the circuit
- d) electrode which is connected to the mains

At very low frequencies in a AC bridge, the source is \_\_\_\_\_ \*

1 point

- a) power line
- b) e.m.f
- c) galvanometer
- d) tuned circuit

At high frequencies in an AC bridge, the source is \_\_\_\_\_ \*

1 point

- a) tuned amplifiers
- b) oscillators
- c) vibration galvanometer
- d) high voltage source

How many coils are required in the megger? \*

1 point

- a) One
- b) four
- c) Two
- d) Five

What will be the reading of megger if the measuring terminals are open-circuited? \* 1 point

- a) Infinity
- b) 500 ohms
- c) Zero
- d) 10,000 ohms

The bridge by which inductance is measured in terms of capacitance and resistance is called \* 1 point

- a) Maxwell-Wein bridge
- b) Wein bridge
- c) Anderson bridge
- d) Schering bridge

Which of the following instrument can be used in ac bridges for lesser frequencies up to 200 Hz only? \* 1 point

- Headphone
- Tunable amplifier detector
- Vibration galvanometer
- All of the above

Maxwell bridge is used to measure \*

1 point

- Resistance
- Inductance
- Capacitance
- Frequency

..... bridge is used for measuring an unknown inductance in terms of a known capacitance and resistance. \*

1 point

- (a) Maxwell's L/C
- (b) Hay's
- (c) Owen
- (d) Anderson

Hay's bridge is particularly useful for measuring \*

1 point

- (a) inductive impedance with large phase angle
- (b) mutual inductance
- (c) self inductance
- (d) capacitance and dielectric loss

The most useful ac bridge for comparing capacitances of two air capacitors is ..... bridge. \* 1 point

- (a) Schering
- (b) De Sauty
- (c) Wien series
- (d) Wien parallel

Wheatstone bridge is used to find unknown \* 1 point

- (a) resistance
- (b) reactance
- (c) inductance
- (d) capacitance

In an ac bridge, the null detector is usually \* 1 point

- (a) a galvanometer
- (b) an ammeter
- (c) a head phone
- (d) a voltmeter

The capacitive reactance of a capacitor ( $X_C$ ) is given by the following equation \*

1 point

- (a)  $X_C = 1/fC$
- (b)  $X_C = 1/(2\pi fC)$
- (c)  $X_C = 2\pi/fC$
- (d)  $X_C = 2\pi f/C$

Hay bridge is suitable for the coils having a Quality factor \*

1 point

- (a)  $Q > 10$
- (b)  $Q < 10$
- (c)  $Q = 10$
- (d)  $Q < 1$

Kelvin double bridge uses Standard resistance = 100 milliohms, Inner ratio arms = 15 Ohm and 30 Ohm, Outer ratio arms = 40 W and 60 W .If the resistance of the connecting leads from standard to unknown resistance is 800 mOhms. Calculate the unknown resistance under this condition. \*

2 points

- 100.6 milli-ohms
- 151.28 milli-ohms
- 100.6 micro-ohms
- 151.28 micro-ohms

The four impedances of an ac bridge are  $Z_1 = 500 \angle 40^\circ \text{ ohm}$ ,  $Z_2 = 100 \angle -90^\circ \text{ ohm}$ ,  $Z_3 = 45 \angle 20^\circ \text{ ohm}$ ,  $Z_4 = 30 \angle 30^\circ \text{ ohm}$ . Find out the bridge is balance condition. \* 2 points

- Phase condition satisfied,magnitude condition satisfied and Bridge balance
- Phase condition unsatisfied,magnitude condition satisfied and Bridge balance
- Phase condition satisfied,magnitude condition unsatisfied and Bridge unbalance
- Phase condition satisfied,magnitude condition satisfied and Bridge unbalance

The arms of a four-arm bridge a, b, c, and d supplied with sinusoidal voltage have the following values. arm ab: A resistance of 800 ohms in parallel with a capacitance of 2 micro-Farad, bc: 400 ohms resistance, arm cd: 1 kilo-ohm resistance, arm da: A resistance R2 in series with 2 micro-Farad capacitance. Determine the value of R2 and frequency at which the bridge will balance. \* 2 points

- R2=1.6Kohms and Frequency= 86.6 Hz
- R2=1.2Kohms and Frequency= 72.6 Hz
- R2=1.2ohms and Frequency= 50 Hz
- R2=1.2 ohms and Frequency= 72.6 Hz

In Maxwell's capacitance bridge for calculating unknown inductance, the various values at balance are,  $R_1 = 300 \Omega$ ,  $R_2 = 700 \Omega$ ,  $R_3 = 1500 \Omega$ ,  $C_4 = 0.8 \mu\text{F}$ . Calculate R1, L1, and Q factor, if the frequency is 1100 Hz. \* 2 points

- a) 240  $\Omega$ , 0.12 H, 3.14
- b) 140  $\Omega$ , 0.168 H, 8.29
- c) 140  $\Omega$ , 0.12 H, 5.92
- d) 240  $\Omega$ , 0.36 H, 8.29



This form was created inside of CMR Institute of Technology.

