

USN										
-----	--	--	--	--	--	--	--	--	--	--



CMR INSTITUTE OF TECHNOLOGY

Internal Assessment Test - II

Sub:	Electric Circuit Analysis						Code:	18EE32	
Date:	02/11/2020	Duration:	90 mins	Max Marks:	50	Sem:	3 rd	Branch:	EEE
Answer Any FIVE FULL Questions									

Marks/CO/RBT
(5)(CO2)(L2)

1. (a) Derive expression for Delta-Star Transformation.


When a circuit cannot be simplified in normal series parallel reduction technique, the star delta transformation technique is used.

Equations for star-delta transformation:

$$R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$
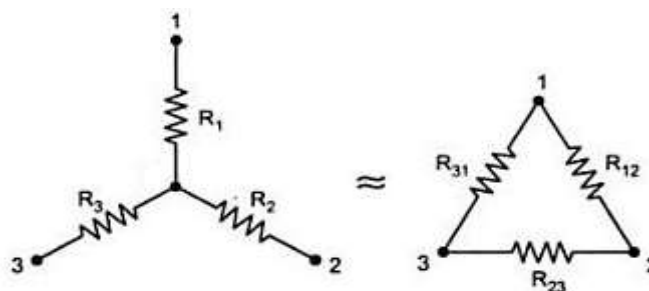
$$R_{31} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$




Equations for delta-star transformation:

$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$


$$R_2 = \frac{R_{23} R_{12}}{R_{12} + R_{23} + R_{31}}$$
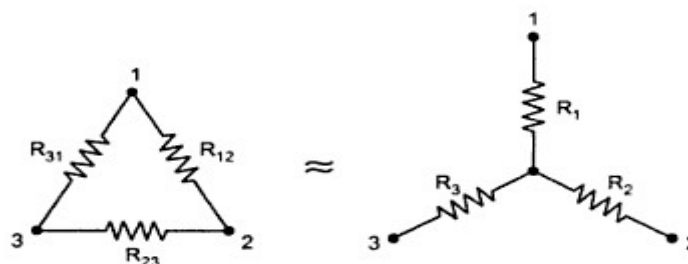
$$R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}}$$



(b) Find the equivalent resistance R_{AB} using Delta-Star Transformation.

(5)(CO2)(L3)

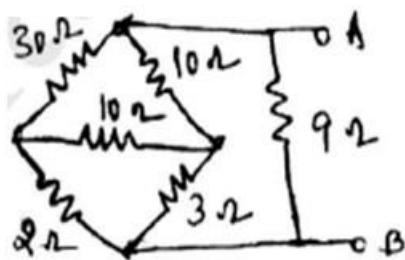

Converting delta into star

$R_1 = \frac{30(10)}{30+10+10} = 6\Omega$
 $R_2 = \frac{10(10)}{30+10+10} = 2\Omega$
 $R_3 = \frac{10(30)}{30+10+10} = 6\Omega$


$R_{xy} = (2+2) \parallel (6+3)$ } parallel
 $= \frac{4(9)}{4+9} = 2.76\Omega$
 $R_{xy} = 2.76\Omega$

$R_{MY} = 6 + 2.76 = 8.76\Omega$
 $R_{AB} = 9 \parallel 8.76$
 $= \frac{9(8.76)}{9+8.76} = 4.42\Omega$

$\therefore R_{AB} = 4.42\Omega$ ✓


2. (a) Draw the dual of the following circuit.


(4)(CO2) (L3)

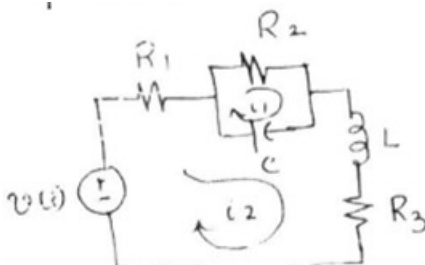

(b) Convert the given circuit into a single voltage source in series with a single resistance using source transformation & shifting.



(6)(CO2) (L3)

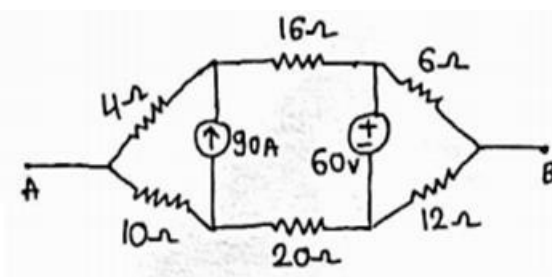

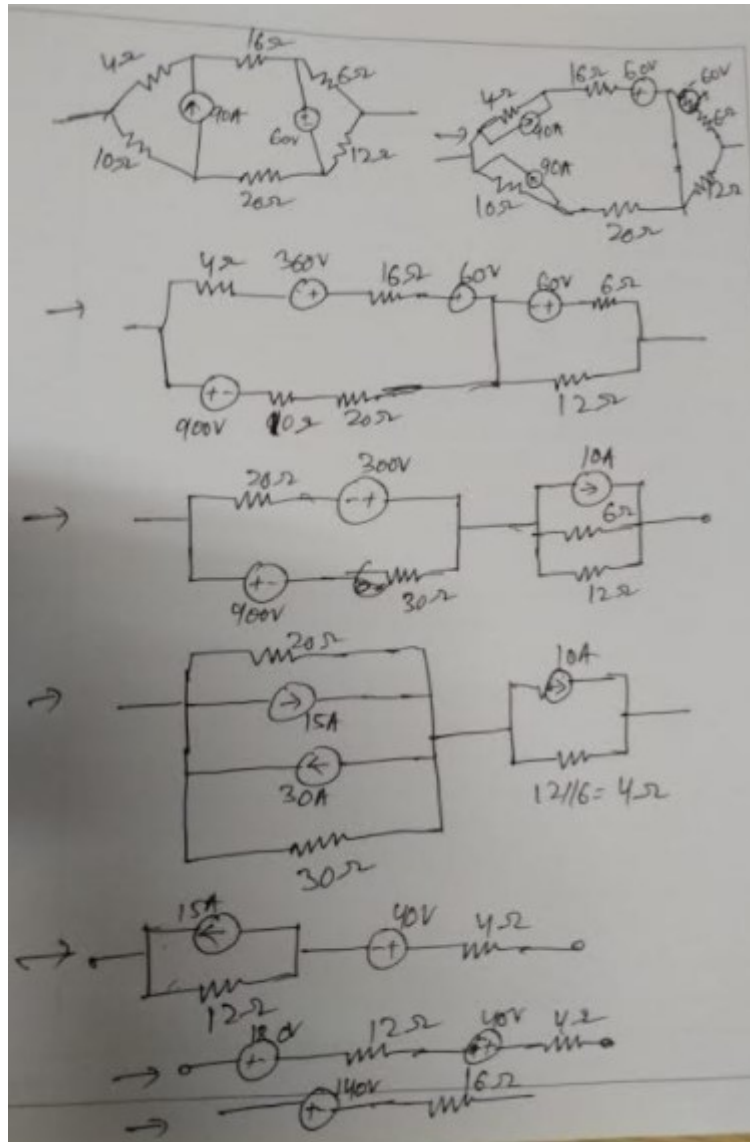


3. (a) Find power delivered by 50V source using source transformation.

(5)(CO2) (L3)

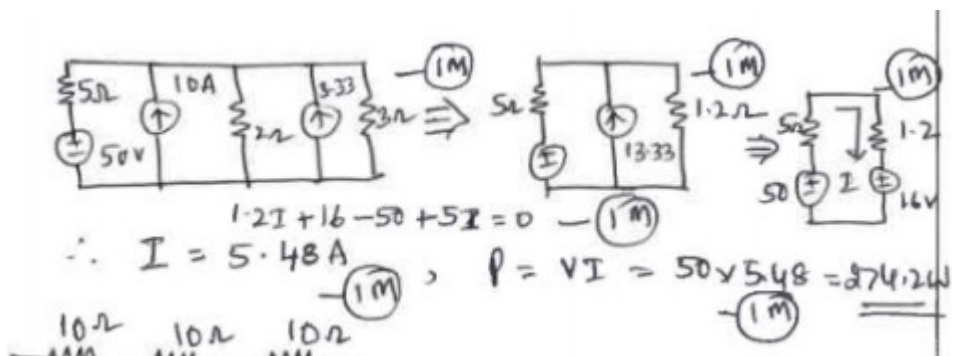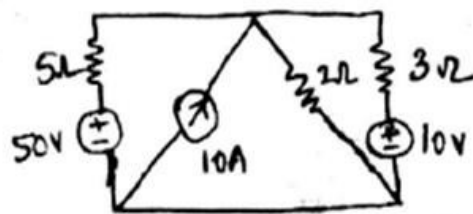

(b) Find R_{ab} using Delta-Star Transformation. All resistances are of same value 10Ω .

(5)(CO2) (L3)

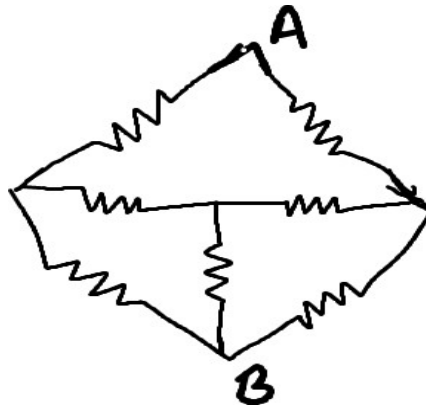

Converting star - delta

$$R_1 = \frac{10(10)}{10+10+10} = \frac{100}{30} = 3.33\Omega$$

$$R_2 = \frac{10(10)}{10+10+10} = 3.33\Omega$$

$$R_3 = \frac{10(10)}{10+10+10} = 3.33\Omega$$

$\therefore R_1 = R_2 = R_3 = 3.33\Omega$

Now, circuit will be —

Similarly, $R_4 = \frac{10}{3} = 3.33\Omega$, $R_5 = R_6 = 3.33\Omega$

$R_{xy} = (R_4 + R_5) \parallel (R_6 + R_3)$ — parallel

$$= (3.33 + 3.33) \parallel (3.33 + 3.33)$$

$$= \frac{6.66 \times 6.66}{6.66 + 6.66}$$

$$R_{xy} = 3.33\Omega$$

$R_{AV} = 10 + R_4 = 10 + 3.33 = 13.33\Omega$

$R_{MB} = (R_4 + R_5) \parallel (R_6 + R_3)$

$$= (3.33 + 3.33) \parallel (3.33 + 3.33)$$


$$R_{MB} = 3.33\Omega$$

R_{AV}, R_{BY}, R_{XY} — parallel connection


$R_{AB} = 13.33 + 3.33 + \frac{13.33(3.33)}{6.66} = 25.33\Omega$

$R_{XB} = \frac{6.66 + 3.33}{3.33} + \frac{6.66(3.33)}{13.33} = 11.66\Omega$

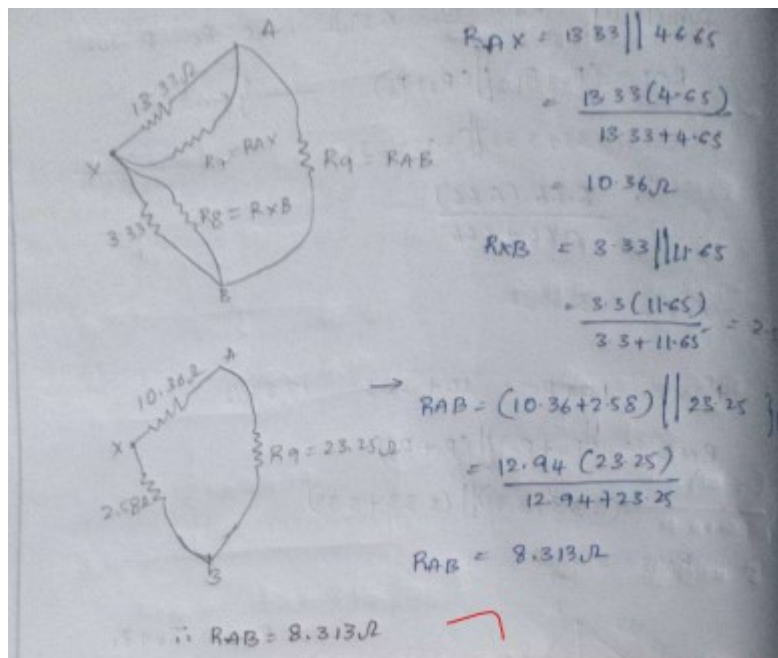
$R_{AY} = \frac{6.66 + 3.33}{3.33} + \frac{6.66(3.33)}{13.33} = 11.66\Omega$



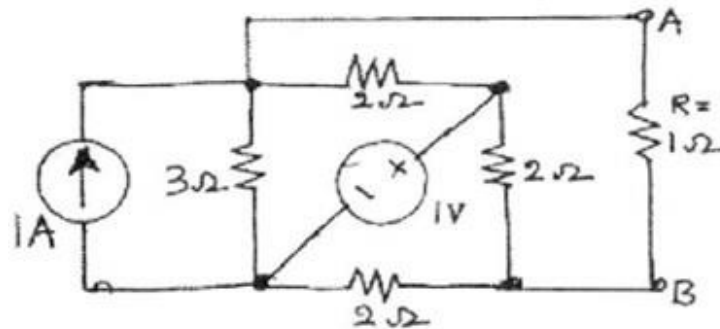
4. Find current in 1Ω resistor using Thevenin's & Superposition Theorem simultaneously. (10)(CO3)(L3)



\therefore shorting terminals A & B

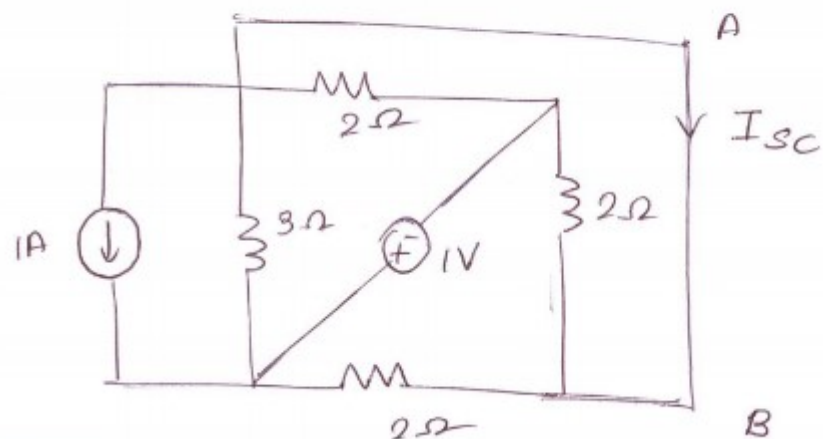

Using source transformation.

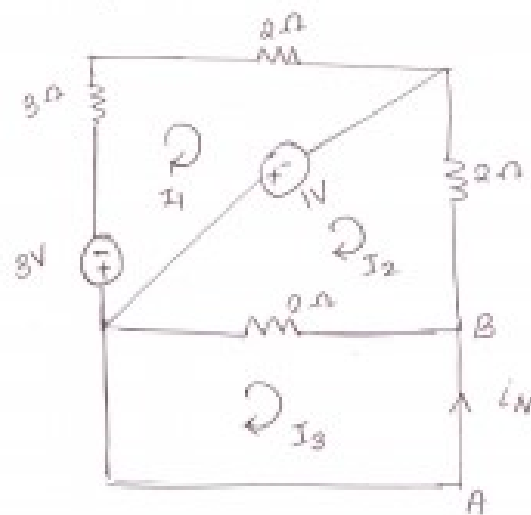

Applying mesh analysis in loop 1

$$-3 - 3I_1 - 2I_1 + 1 = 0$$

$$-5I_1 - 2 = 0$$

$$I_1 = -2/5 \text{ A}$$

Applying mesh analysis in loop 2

$$-1 - 2I_2 - 2(I_2 - I_3) = 0$$

$$-1 - 4I_2 + 2I_3 = 0 \rightarrow \textcircled{2}$$

Applying mesh analysis in loop 3.

$$-2(I_3 - I_2) = 0$$

$$-2I_3 + 2I_2 = 0$$

$$I_3 = I_2$$

$$\text{Substituting in } -I - 4I_2 + 3I_2 = 0$$

$$-I - 4I_2 + 3I_2 = 0$$

$$-I - 2I_2 = 0$$

$$-I = 2I_2$$

$$I_2 = \frac{-I}{2} = -0.5A$$

$$\text{We know } I_N = -I_2 =$$



$$I_N = \underline{0.5A}$$

Req

$$R_N = (3 \parallel 2) + (2 \parallel 2)$$

$$\frac{3 \times 2}{3+2} + \frac{2 \times 2}{2+2}$$
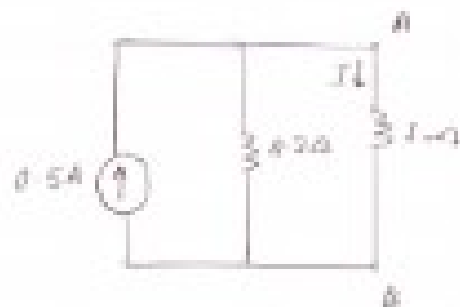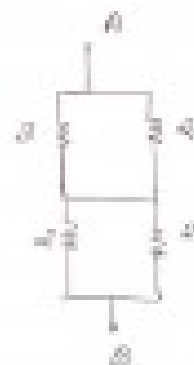
$$\frac{6}{5} + 1 = \frac{11}{5} = 2.2 \Omega$$





By current division rule

$$I = 0.5 \times \left(\frac{2.2}{2.2+1} \right)$$

$$I = \underline{0.34375A}$$

5. (a) Find the value of R_L for which maximum power is delivered to it.

(6)(CO3) (L3)

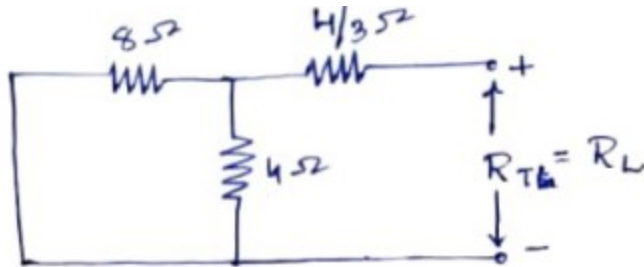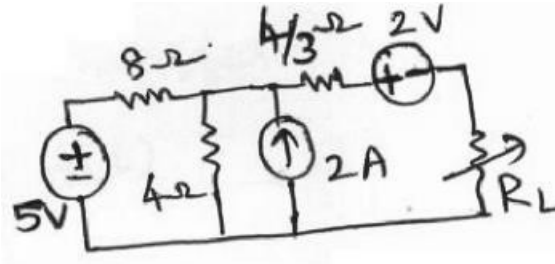

$$R_T = R_L = 4 \frac{8(4)}{8+4} + \frac{4}{3} = \frac{32}{12} + \frac{4}{3}$$


$$= \frac{32 + 16}{12}$$

$$= \frac{48}{12}$$

$$R_T = R_L = 4 \Omega$$


(b) Find current through I using Millman's Theorem.

(4)(CO3) (L3)

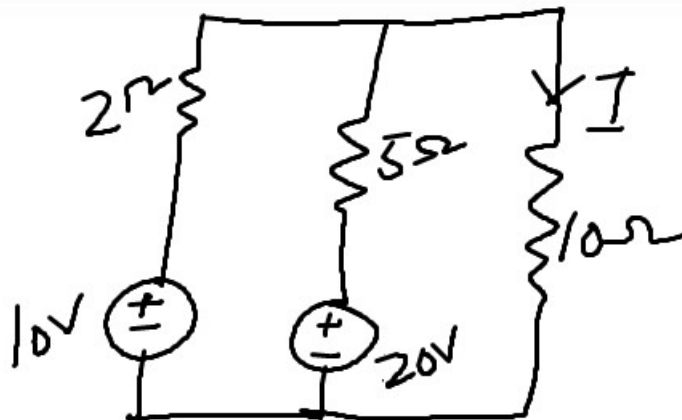

6. Find Thevenin's & Norton's equivalent circuit for the given network.

(10)(CO3) (L3)

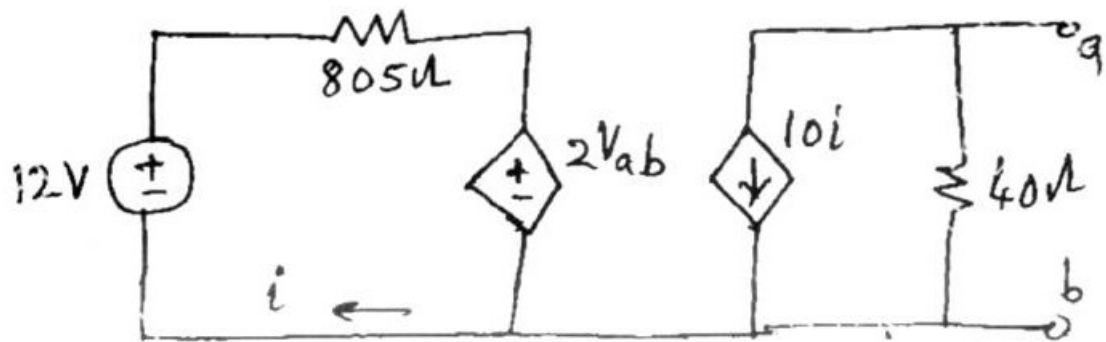

Apply KVL to loop 1

$$12 - 805i - 2V_{ab} = 0$$

$$805i + 2V_{ab} = 12 \quad \text{--- (1)}$$

Apply KVL to loop 2

$$V_{ab} = 40(-10i)$$

$$i = \frac{-V_{ab}}{400} \quad \text{--- (2)}$$

Sub (2) in (1)

$$805 \left(\frac{-V_{ab}}{400} \right) + 2V_{ab} = 12$$

$$-2.0125 \frac{V_{ab}}{1} + 2V_{ab} = 12$$

$$-0.0125 V_{ab} = 12$$

$$V_{oc} = V_{ab} = -960V$$



$$\therefore i = \frac{-V_{ab}}{400}$$

$$= \frac{-(-960)}{400} = 2.4A$$

$$i_{40} = 10i = 10 \times 2.4 = 24A \text{ (A to b)}$$

7. (a) Find current through 16Ω resistor using Norton's Theorem.

(5)(CO3) (L3)

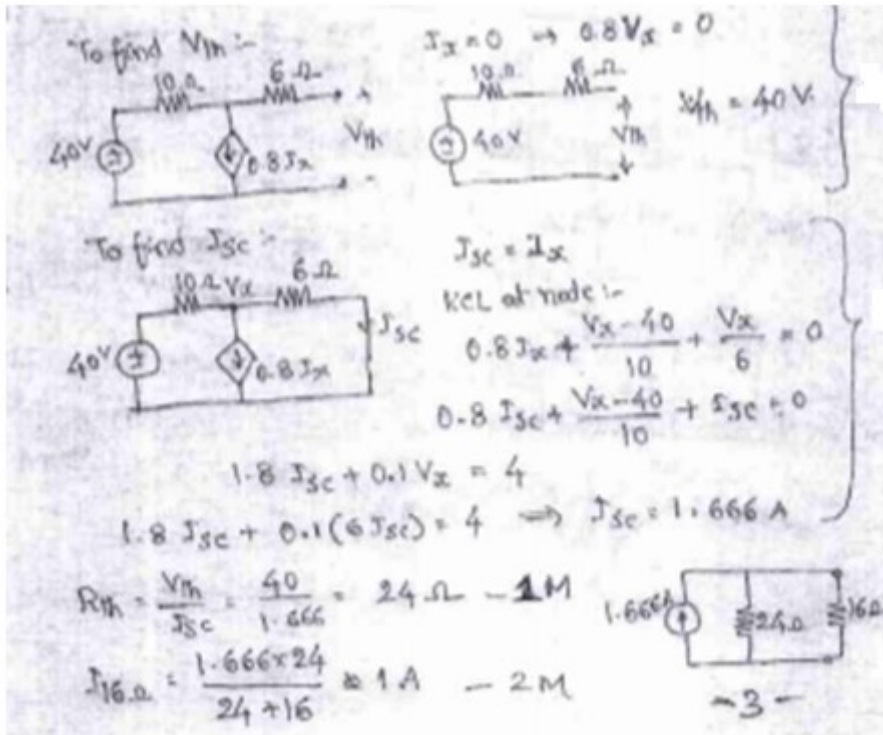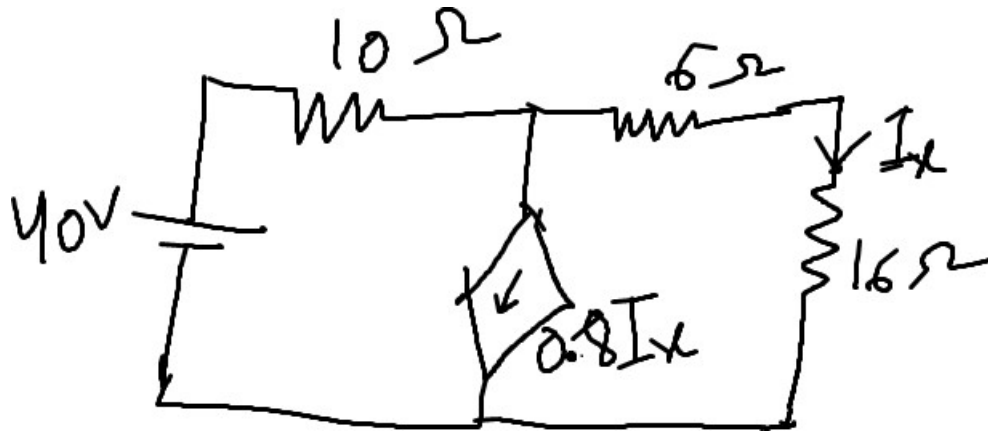

(b) Find current through R_L using Thevenin's Theorem

(5)(CO3) (L3)

