

IAT 3 Solution

5.

$$\text{i) } Z_i = R_G = 1 \text{ M}\Omega$$

$$\text{ii) } Z_o = r_d \parallel R_D = 50 \text{ K} \parallel 5.1 \text{ K} = 4628 \Omega$$

iii) Voltage Gain A_v : We have

$$A_v = -g_m (r_d \parallel R_D)$$

$$= -2 \text{ mS} (50 \text{ K} \parallel 5.1 \text{ K})$$

$$= -2 \text{ mS} (4628)$$

$$= -9.256$$

6.

$$q) \quad A_{V1} = \frac{Z_{12}}{Z_{O1} + Z_{12}} \quad A_{VN1} = \frac{1 \text{ k}\Omega}{3.8 \text{ k}\Omega + 1 \text{ k}\Omega} \times -430 \\ = -95.56$$

$$A_{V2} = \frac{R_L}{Z_0 + R_L} = \frac{2.7}{2.7 + 3.5} \times -430 \\ = -187$$

$$A_{II} = -Av_1 \frac{Z_i}{Z_{i2}} = 95.56 \times \frac{1}{1} = 95.56.$$

$$A_{I2} = -Av_2 \frac{Z_{i2}}{R_L} = 187 \frac{1}{2.7} = 69.26$$

b) $A_{VT} = Av_1 \cdot Av_2 = 17.869 \times 10^3, \text{ (or)}$
 17869.72

$$A_{IT} = A_{II} \cdot A_{I2} = 6618.4856 \text{ (or)} \\ 6.618 \times 10^3.$$

7.

i) g_m : We have,

$$g_m = \frac{2 I_{DSS}}{|V_p|} = \frac{2 (8 \times 10^{-3})}{8 V} = 2 \text{ mS}$$

Also we have,

$$g_m = g_m \left(1 - \frac{V_{GSQ}}{V_p} \right) = 2 \text{ mS} \left(1 - \frac{(-2 \text{ V})}{(-8 \text{ V})} \right) = 1.5 \text{ mS}$$

ii) r_d :

$$r_d = \frac{1}{Y_{os}} = \frac{1}{20 \mu S} = 50 \text{ k}\Omega$$

iii) Z_i : We have,

$$Z_i = R_G = 1 \text{ M}\Omega$$

iv) Z_o : We have,

$$Z_o = r_d \parallel R_D = 50 \text{ K} \parallel 5.1 \text{ K} = 4628 \Omega$$

v) A_v : We have,

$$A_v = \frac{V_o}{V_i} = -g_m (r_d \parallel R_D) = -1.5 \text{ mS} (50 \text{ K} \parallel 5.1 \text{ K}) = -1.5 \text{ mS} (4628)$$
$$= -6.942$$