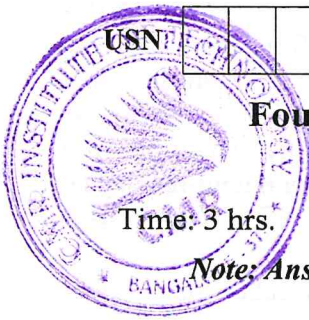


CBCS SCHEME

18EC42



USN:

--	--	--	--	--	--	--	--	--	--

Fourth Semester B.E. Degree Examination, Jan./Feb. 2021 Analog Circuits

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

1.
 - a. What is meant by biasing? Explain the need for biasing and the stability of Q-point with respect to BJT. (04 Marks)
 - b. Design a voltage divider bias network to operate a BJT at $V_{CE} = 6\text{ V}$ and $I_C = 4\text{ mA}$. Use $V_{CC} = 12\text{ V}$, $V_E = V_{CC}/4$ and the current through the voltage-divider resistors as $I_E/10$. Assume $\beta = 100$ and $V_{BE} = 0.7\text{ V}$. (08 Marks)
 - c. For a BJT amplifier circuit, obtain the expressions for small-signal collector current, transconductance and voltage gain. (08 Marks)

OR

2.
 - a. A MOSFET having $V_t = 1.5\text{ V}$, $W = 10\text{ }\mu\text{m}$, $L = 1\text{ }\mu\text{m}$, $K'_n = 200\text{ }\mu\text{A/V}^2$ and $\lambda = 0$ has to be biased at $I_D = 5\text{ mA}$. Design a drain-to-gate feedback bias network using $V_{DD} = 10\text{ V}$. (08 Marks)
 - b. For the circuit shown in Fig.Q2(b), determine the small-signal voltage gain, input resistance and output resistance. Assume $V_t = 1.5\text{ V}$, $K'_n W/L = 0.25\text{ mA/V}^2$ and $V_A = 50\text{ V}$.

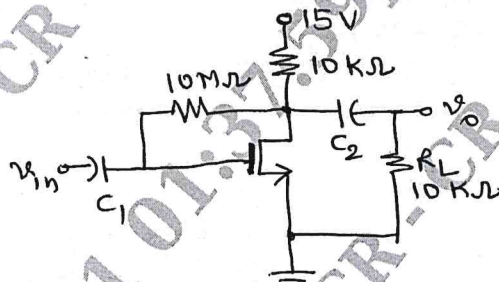


Fig.Q2(b)

(12 Marks)

Module-2

3.
 - a. Define the terms input resistance, output resistance, voltage gain and overall voltage gain of an amplifier. (04 Marks)
 - b. Analyze the circuit of common-drain amplifier, and derive the expressions for no-load voltage gain, overall voltage gain, input resistance and output resistance. (10 Marks)
 - c. An n-channel MOSFET has $t_{ox} = 10\text{ nm}$, $w = 10\text{ }\mu\text{m}$, $L = 1\text{ }\mu\text{m}$ and $L_{ov} = 0.05\text{ }\mu\text{m}$. calculate the values of C_{ox} , C_{gs} and C_{gd} when the transistor is operating in its saturation region. Assume $\epsilon_{ox} = 34.53\text{ pF/m}$. (06 Marks)

OR

4.
 - a. Draw the high-frequency model of MOSFET used in computer analysis, and the simplified model used in manual analysis. (04 Marks)
 - b. A common-source amplifier has signal resistance $R_{sig} = 10\text{ K}\Omega$, gate resistance $R_G = 10\text{ M}\Omega$, drain resistance $R_D = 15\text{ K}\Omega$, load $R_L = 15\text{ K}\Omega$, $r_0 = 150\text{ K}\Omega$, $g_m = 10\text{ mA/V}$, $C_{gs} = 1\text{ pF}$, $C_{gd} = 0.4\text{ pF}$, coupling capacitor $C_1 = C_2 = 1\text{ }\mu\text{F}$ and bypass capacitor $C_s = 1\text{ }\mu\text{F}$. Determine the maximum gain in dB and bandwidth of the amplifier. (08 Marks)
 - c. Draw the circuit of MOSFET based RC phase-shift oscillator and explain its operation. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-3

- 5 a. List the advantages of negative feedback in amplifiers. (04 Marks)
 b. An amplifier has open-loop gain $A = 10,000$. Find the feedback factor β required to get the closed-loop gain $A_F = 10$, Now if A decreases by 20%, determine the corresponding decrease in A_F . (06 Marks)
 c. Draw the diagram of series-series feedback amplifier (trans-conductance amplifier) and derive the expressions for closed-loop voltage gain, input resistance and output resistance. (10 Marks)

OR

- 6 a. Define a power amplifier. Classify power amplifiers based on the location of Q-point, conduction angle, efficiency and applications. (08 Marks)
 b. What is cross-over distortion? How can it be eliminated? (04 Marks)
 c. A complementary symmetry push-pull amplifier is operated using $V_{CC} = 10$ V to deliver power to a load $R_L = 5 \Omega$. Calculate the maximum power output and the power ratings of the transistors. (08 Marks)

Module-4

- 7 a. Draw the circuit of non-inverting amplifier and derive the expressions for exact gain, ideal gain, input resistance and output resistance. (10 Marks)
 b. What is meant by virtual ground? Explain. (04 Marks)
 c. An inverting amplifier with feedback resistor $R_f = 4.7$ K Ω and the input resistor $R_1 = 1$ K Ω is fed with 5V peak-to-peak sinusoidal of frequency 1 kHz. Draw the input and output waveforms. (06 Marks)

OR

- 8 a. Design an op-amp circuit with three input voltage V_1 , V_2 and V_3 such that to get an output of $V_0 = -(0.5V_1 + V_2 + 2V_3)$. (08 Marks)
 b. What is meant by offset-nulling? How is it done in 741C op-amp? (04 Marks)
 c. Determine the bandwidth of the amplifier shown in Fig.Q8(c) if the unity-gain bandwidth of the op-amp is 1 MHz.


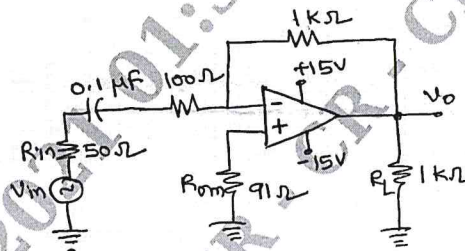


Fig.Q8(c)

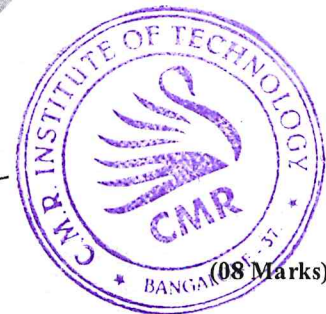

(08 Marks)

Module-5

- 9 a. With circuit diagram and waveform, explain the working of binary-weighted resistors 4-bit digital-to-analog converter. (08 Marks)
 b. In a R-2R Digital-to-Analog converter, $R_f = 12$ K Ω , $R = 5$ K Ω , calculate the output voltage when only the LSB is ON, and the output voltage when all the four bits are ON. Assume reference voltage is +5V. (04 Marks)
 c. Explain the working of positive half-wave precision rectifier using op-amp and a single diode. (08 Marks)

OR

- 10 a. A second-order low-pass filter is to be designed to have cutoff frequency 1.6 kHz and passband gain 1.586. Design and draw the circuit. (07 Marks)
 b. Draw the circuit of first order wide band-pass filter and explain operation. (08 Marks)
 c. Design a circuit using 555 timer to get a mono-shot pulse of width 10 ms. Choose $C = 1 \mu\text{F}$. (05 Marks)