

CBCS SCHEME

17CS32



Third Semester B.E. Degree Examination, Jan./Feb. 2021

Analog and Digital Electronics

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain with the constructional details and characteristics curves, the working of n-channel JFET. (08 Marks)
- b. Define the following op-amp parameters: (i) CMRR (ii) Slew Rate (04 Marks)
- c. With circuit diagram, explain the operation of Astable Multivibrator using IC 555. (08 Marks)

OR

- 2 a. Design a voltage divider bias network using DE-MOSFET with supply voltage $V_{DD} = 16\text{ V}$, $I_{DSS} = 10\text{ mA}$, $V_p = -5\text{ V}$ to have Quiescent drain current of 5 mA and gate voltage of 4V (assume the drain resistance R_D to be 4 times the source resistor R_S) (08 Marks)
- b. List the Ideal characteristics of op-amp. (04 Marks)
- c. With circuit diagram and waveforms, explain the working of Relaxation Oscillator. (08 Marks)

Module-2

- 3 a. Explain positive logic and negative logic. (07 Marks)
- b. Use K-map to simplify the following functions:
 - (i) $f(A, B, C, D) = \sum m(0, 2, 6, 10, 11, 12, 13) + d(3, 4, 5, 14, 15)$
 - (ii) $f(A, B, C, D) = \pi M(1, 2, 4, 5, 6, 7, 8, 10, 11, 13, 14)$ (06 Marks)
- c. Explain Static-1 Hazard and Hazard cover with an example. (07 Marks)

OR

- 4 a. Write HDL code for the Boolean expression $Y = AB + CD$. (08 Marks)
- b. Get the simplified expression of, $Y(A, B, C, D) = \sum m(0, 1, 3, 7, 8, 9, 11, 15)$. Using Quine Mc Clustery method. (12 Marks)

Module-3

- 5 a. Show how two 1:16 deMUX can be connected to get 1:32 deMUX. (10 Marks)
- b. With IEEE symbol, logic symbol, explain NAND gate SR latch. Justify the Truth Table. (10 Marks)

OR

- 6 a. Explain the positive edge triggered JK flipflop. (10 Marks)
- b. List the differences between PAL and PLA. Explain 7-segment decoder using PLA. (10 Marks)

Module-4

- 7 a. What are the various ways of representing flip flop? Explain the various representation of JK, SR, D, T flip flop. (10 Marks)
- b. Define Register. Explain SISO using four D- flip flops. Assume initial values of 4 flip flop QRST as 1010, write truth table and plot waveforms. (10 Marks)

OR

- 8 a. Design mod-3 counter using JK flip flop. Also draw state diagram and write the truth table. (10 Marks)
b. Explain Linear Feedback Shift Register [LFSR] for the polynomial $x^4 + x^3 + 1$. (10 Marks)

Module-5

- 9 a. Explain Digital Clock with block diagram. (10 Marks)
b. What is Binary ladder? Explain Binary ladder with digital input of 1000. (10 Marks)

OR

- 10 a. Explain Successive Approximation A/D converter. (10 Marks)
b. Write short note on A/D Accuracy and Resolution. (04 Marks)
c. Design mod-5 counter using JK flip flops. Write the truth table and draw the waveforms. (06 Marks)

