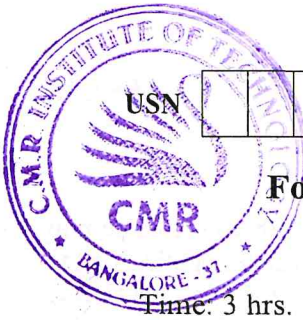


CBCS SCHEME



USN									
-----	--	--	--	--	--	--	--	--	--

15EE46

Fourth Semester B.E. Degree Examination, Jan./Feb. 2021 Operational Amplifiers and Linear IC's

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Analyze the given circuit in [Fig Q1(a)] and derive expressions for closed loop voltage gain (A_f), Inpt Resistance (R_{if}) and Output Resistance (R_{of}) of the circuit, with required diagrams.

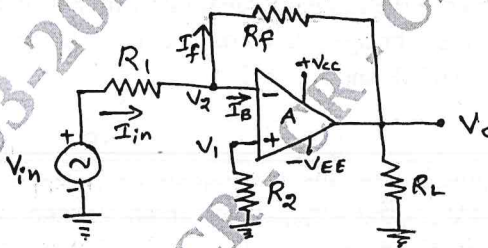


Fig Q1(a)

(10 Marks)

- b. Define the terms slew rate, common-mode rejection ratio and supply voltage rejection rate. (06 Marks)

OR

- 2 a. Explain how a transducer bridge can be connected to an instrumentation amplifier. With required diagram, derive an expression for output voltage of the circuit. What are the applications of instrumentation amplifier? (08 Marks)
- b. Derive an expression for output voltage (V_o) in the given summing amplifier circuit (Fig Q2(b)).

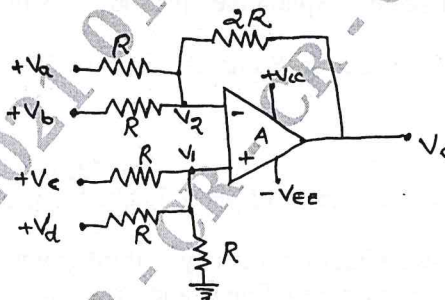


Fig Q2(b)

(08 Marks)

Module-2

- 3 a. Derive equations for gain magnitude and phase angle of a First Order Low Pass Filter with required diagrams. Also show how the gain magnitude varies for different input frequencies. (10 Marks)
- b. Design a wide Band Pass Filter with $f_L = 200\text{Hz}$, $f_H = 1\text{KHz}$ and a passband gain = 4. Given that capacitance for High pass section = $0.05\mu\text{F}$ and that of Low Pass section = $0.01\mu\text{F}$. Also find quality factor (Q). (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 4 a. Design a precision Voltage Regulator circuit to provide a 12V output with 50mA maximum load current. Find the value of supply voltage (V_s) required and power dissipation of the circuit. [Use op-amp 741, $I_{B(max)} = 500nA$ and Zener diode 1N757, $V_z = 9.1V$] (10 Marks)
- b. With a neat circuit diagram, explain the positive voltage regulator circuit using LM317 IC. Show the output voltage (V_o) equation of the circuit. (06 Marks)

Module-3

- 5 a. Explain the working of a Triangular wave generator circuit with Duty Cycle and Frequency controls. Write the required equations with a neat circuit diagram. (10 Marks)
- b. Design a Wein bridge oscillator circuit using op-amp to produce a 1KHz and $\pm 9V$ output. [Use $C_1 = 0.01\mu F$ and $A_{CL} = 3$]. (06 Marks)

OR

- 6 a. With required diagrams and equations, explain how an op-amp circuit output switches between $+V_{osat}$ and $-V_{osat}$ when input voltage, V_{in} arrives at UTP and LTP, when non-inverting configuration is used. (08 Marks)
- b. Write short notes on Inverting Zero Crossing Detector, Non-inverting zero crossing Detector and current amplifier. (08 Marks)

Module-4

- 7 a. Sketch an op-amp precision clamping circuit, draw the input and output waveforms and explain the circuit operation. (08 Marks)
- b. Draw the diagram of op-amp sample and Hold circuit. Sketch the waveforms and explain the circuit operation. (08 Marks)

OR

- 8 a. With a neat sketch, explain the operation of 8-bit Digital to Analog converter using IC 1408. (08 Marks)
- b. Briefly explain Linear Ramp Analog to Digital converter with the circuit diagram and waveforms. (08 Marks)

Module-5

- 9 a. Draw the block diagrams of phase Locked loop and explain its components briefly. (08 Marks)
- b. Discuss the working of frequency multiplier with a block diagram. (04 Marks)
- c. Define the terms Capture Range and Tracking Range. (04 Marks)

OR

- 10 a. Draw the internal block diagram of IC 555 and explain its operation. (08 Marks)
- b. With required diagrams, waveforms and equations, explain the Astable operation of IC 555 timer. (08 Marks)

