

*Modified*

# CBCS SCHEME

USN

--	--	--	--	--	--	--

18EC32

## Third Semester B.E. Degree Examination, Jan./Feb. 2021 Network Theory

Time: 3 hrs.

Max. Marks: 100

**Note:** Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Using source transformation and source shifting techniques, find voltage across  $2\Omega$  resistor as shown in Fig.Q.1(a). (07 Marks)

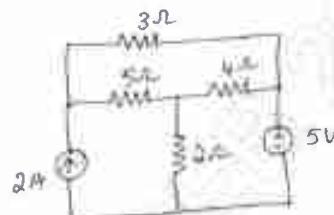


Fig.Q.1(a)

- b. For the network shown in Fig.Q.1(b), find the equivalent resistance between A and B using Star-Delta transformation. (05 Marks)

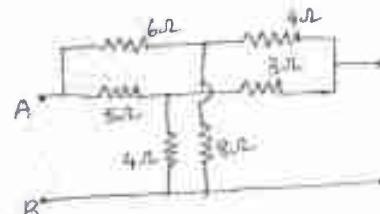


Fig.Q.1(b)

- c. Determine the node voltages  $V_1$  and  $V_2$  by nodal analysis for the network in Fig.Q.1(c). (08 Marks)

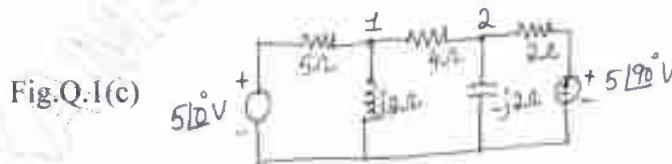


Fig.Q.1(c)

**OR**

- 2 a. Find the potential difference between M and N using source transformation, for the network shown in Fig.Q.2(a). (05 Marks)



Fig.Q.2(a)

- b. Find  $V_x$  using nodal analysis for the network shown in Fig.Q.2(b). (08 Marks)

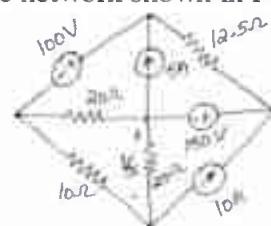
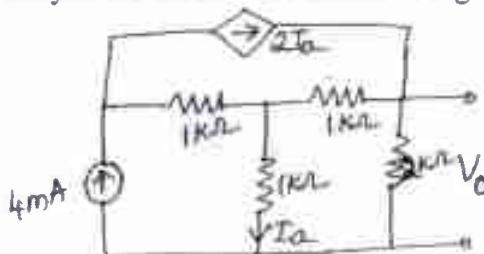


Fig.Q.2(b)

- c. Determine  $V_0$  using mesh analysis for the network shown in Fig.Q.2(c).


(07 Marks)

Fig.Q.2(c)

**Module-2**


- 3 a. State and prove Millman's theorem. (06 Marks)  
 b. Find the current through  $Z_3$  using superposition theorem for the network shown in Fig.Q.3(b). (10 Marks)

Fig.Q.3(b)

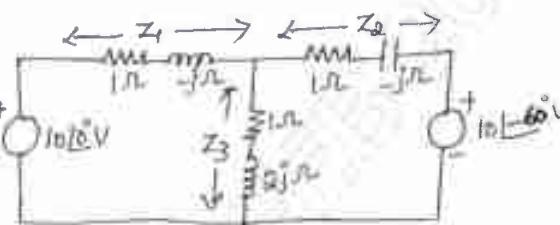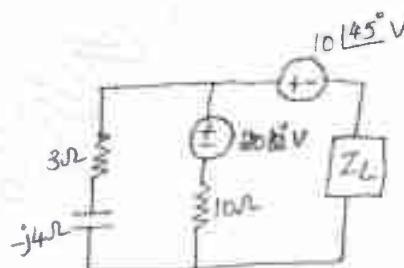


- c. Find the value of  $Z_L$  for which maximum power transfer occurs in the network shown in Fig.Q.3(c). (04 Marks)

Fig.Q.3(c)

**OR**


- 4 a. Obtain Thevenin's and Norton's equivalent circuit at terminals AB for the network shown in Fig.Q.4(a). Hence, find the current through 10Ω resistor across AB. (12 Marks)

Fig.Q.4(a)

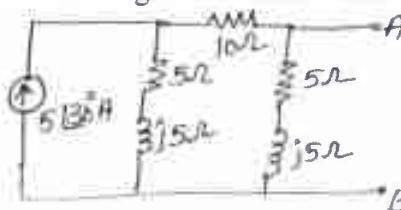


- b. Find the value of  $R_L$  for which maximum power is delivered. Also find the maximum power that is delivered to the load  $R_L$ . Refer Fig.Q.4(b). (08 Marks)

Fig.Q.4(b)

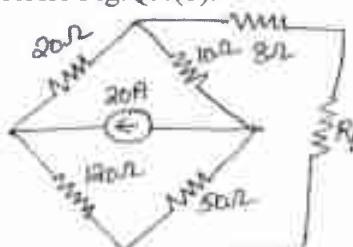


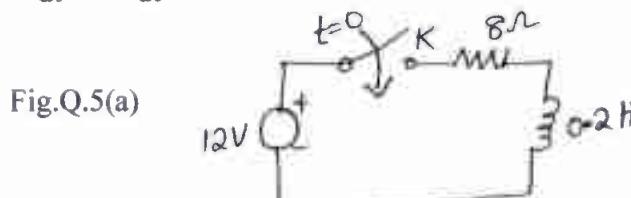**Module-3**


- 5 a. In the given network Fig.Q.5(a), K is closed at  $t = 0$ , with zero current in the inductor. Find the values of  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ . (05 Marks)



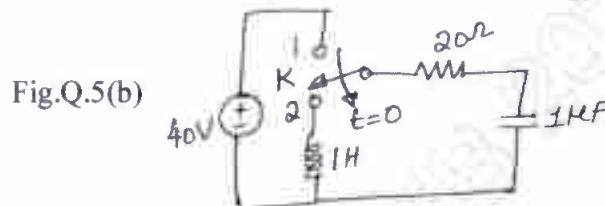- b. In the network Fig.Q.5(b), the switch is moved from position 1 to position 2 at  $t = 0$ . The steady-state has been reached before switching. Calculate  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ . (07 Marks)




- c. In the network Fig.Q.5(c), the switch K is opened at  $t = 0$ . At  $t = 0^+$ , solve for  $v$ ,  $\frac{dv}{dt}$  and  $\frac{d^2v}{dt^2}$ . (08 Marks)

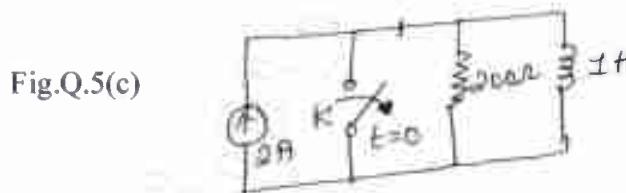**OR**

- 6 a. For the circuit shown in Fig.Q.6(a), steady state is reached with switch K open. The switch is closed at  $t = 0$ . Find  $i_1$ ,  $i_2$ ,  $\frac{di_1}{dt}$  and  $\frac{di_2}{dt}$  at  $t = 0^+$ . (10 Marks)

Fig.Q.6(a)

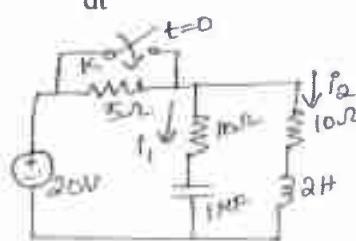


- b. For the circuit in Fig.Q.6(b). Find:

- $v(0^+)$  and  $i(0^+)$
- $\frac{dv(0^+)}{dt}$  and  $\frac{di(0^+)}{dt}$
- $v(\infty)$  and  $i(\infty)$ .

(10 Marks)

Fig.Q.6(b)

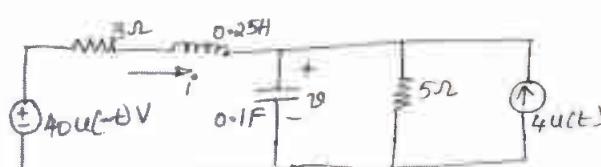


**Module-4**

- 7 a. Determine the current  $i_L(t)$  for  $t \geq 0$  for the circuit in Fig.Q.7(a).

(10 Marks)


Fig.Q.7(a)

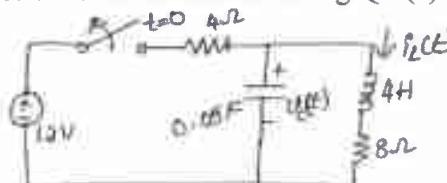

- b. Find the Laplace transform of the function  $f(t)$  shown in Fig.Q.7(b).

(10 Marks)


Fig.Q.7(b)

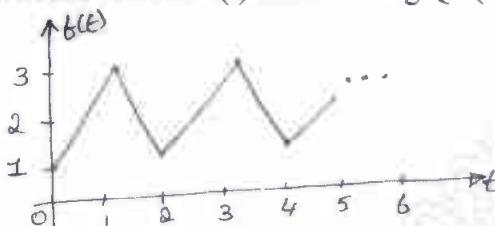**OR**

- 8 a. Determine the voltage  $v_c(t)$  and the current  $i_c(t)$  for  $t \geq 0$  for the circuit shown in Fig.Q.8(a).

(10 Marks)


Fig.Q.8(a)

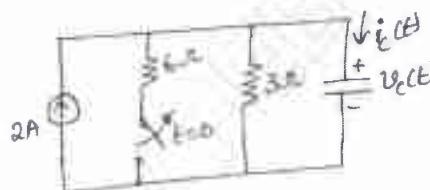

- b. Find the Laplace transform of  $f(t)$  shown in Fig.Q.8(b).

(10 Marks)

Fig.Q.8(b)

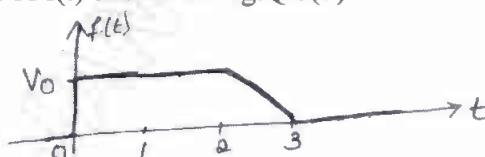**Module-5**


- 9 a. Express Y parameters in terms of h-parameters.

(06 Marks)

- b. Find Z-parameters for the network shown in Fig.Q.9(b).

(06 Marks)

Fig.Q.9(b)

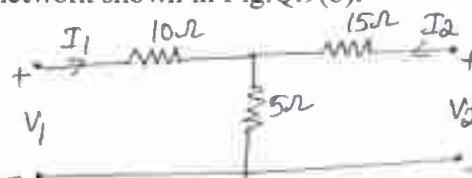

- c. The Z-parameters of a two port network are  $z_{11} = 20\Omega$ ,  $z_{22} = 30\Omega$ ,  $z_{12} = z_{21} = 10\Omega$ . Find Y and ABCD parameters of the network.

(08 Marks)

**OR**

- 10 a. Prove that the resonant frequency is the geometric mean of the two half power frequencies.

(06 Marks)


- b. A series RLC circuit has  $R = 10\Omega$ ,  $L = 0.01H$  and  $C = 0.01\mu F$  and it is connected across 10mv supply. Calculate: i)  $f_0$  ii)  $Q_0$  iii) bandwidth iv)  $f_1$  and  $f_2$  v)  $I_0$ .

(06 Marks)

- c. Find the value of  $R_1$  such that the circuit shown in Fig.Q.10(c) is resonant.

(08 Marks)

Fig.Q.10(c)

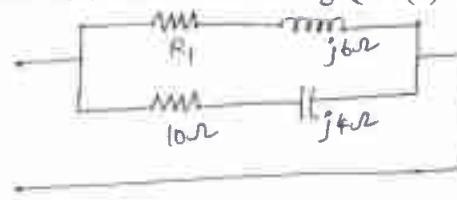

\*\*\*\*\*

**Re: Sir, regarding Modification of scheme and solutions (18EC32)**

"Mrityunjaya Vithal Latte" <mvlatte@rediffmail.com>

April 22, 2021 3:28 PM

To: boe@vtu.ac.in, "mvlatteBOEVTU" <mvlatte.boe.vtu@gmail.com>

Dear sir,

The scheme of 18EC32 is verified and it is inline with the question paper .  
Regards

PROF. MRITYUNJAYA V. LATTE

Principal,

JSS Academy of Technical Education,  
Uttarahalli-Kengeri Main Road,Bangalore  
Karnataka 560 060

From: <boe@vtu.ac.in>

Sent: Thu, 08 Apr 2021 17:12:35

To: mvlatte@rediffmail.com, mvlatte25@gmail.com

Subject: Sir, regarding Modification of scheme and solutions (18EC32)

**"APPROVED"**  
*Ranjeet S*  
Registrar (Evaluation)  
Sri Sathya Sai Baba Polytechnic University  
Belagavi - 590018



201218EC3228336



Visvesvaraya Technological University  
Belagavi, Karnataka - 590 018.

*Signature of Scrutinizer*

Scheme & Solutions

Subject Title : Network Theory



Subject Code : 18EC32

Question Number	Solution	Marks Allocated
1(a)	<p><math>I_{AB} = 1.493A</math></p> <p><math>V_{2\Omega} = 2 I_{AB} = 2.986V</math></p>	(3M) (2M) (1M)
1(b)	<p><math>R_{AB} = 5.44\Omega</math></p>	(2M) (2M) (5M)
1(c)	<p>Node1: <math>(0.45 - j0.5)V_1 - 0.25V_2 = 1 \rightarrow ①</math></p> <p>Node2: <math>-0.25V_1 + (0.75 + j0.5)V_2 = 2.5 \angle 90^\circ \rightarrow ②</math></p> <p><math>V_1 = 2.48 \angle 72.1^\circ V</math></p> <p><math>V_2 = 3.44 \angle 26.47^\circ V</math></p>	2M (8M) 4M
2(a)	<p><math>V_{MN} = -1.2V</math></p>	(3M) (2M) (5M)

Question Number	Solution	Marks Allocated
2(b)	<p><u>KCL at 1-3</u></p> $\frac{V_1}{10} + \frac{V_1 - V_2}{20} + \frac{V_3 - V_4}{12.5} = 5 \quad (1M)$ <p><u>KCL at 2-4</u></p> $\frac{V_2 - V_1}{20} + \frac{V_2}{25} + \frac{V_4 - V_3}{12.5} + 5 = 10 \quad (1M)$ $\therefore V_1 = 74.77V \quad (4M)$ $V_2 = V_3 = 63.06V \quad (4M)$	(8M)
2(c)	<p><math>I_2 = 4mA</math></p> <p><math>I_1 = 2I_2 = 2(I_2 - I_3) \quad (2M)</math></p> <p>KVL to Maths</p> $10^3(I_3 - I_2) + 10^3(I_3 - I_1) \quad (2M)$ $+ 2 \times 10^3 I_3 = 0 \quad (7M)$ $I_3 = 2mA \quad (1M)$ $V_0 = 2 \times 10^3 I_3 = 4V \quad (2M)$	(4M)
3(a)	<p>Millman's Theorem: If 'n' voltage sources <math>V_1, V_2, \dots, V_n</math> having internal impedances <math>Z_1, Z_2, \dots, Z_n</math> are in parallel, then these sources may be replaced by a single voltage source of voltage <math>V_M</math> having a series impedance <math>Z_M</math> given by</p> $V_M = \frac{\sum_{k=1}^n V_k Y_k}{\sum_{k=1}^n Y_k} \quad (2M)$ $Z_M = \frac{1}{\sum_{k=1}^n Y_k} \quad (6M)$ <p>- proof required (4M)</p>	
3(b)	<p>Considering only <math>10L^0V</math>, current through <math>Z_3</math> <math>-j2.5A</math> <math>-(4M)</math></p> <p>Considering only <math>10L^{60^\circ}V</math>, current through <math>Z_3</math> <math>1.247 - j2.17A</math> <math>-(4M)</math></p> <p><math>\therefore</math> Total current through <math>Z_3 = \boxed{4.834 \angle -75^\circ A} \quad (2M)</math></p>	(10M)

Question Number	Solution	Marks Allocated
3(c)	$Z_0 = 7.97 - j2.16\Omega \quad (1M)$ $Z_L = Z_0 = 7.97 + j2.16\Omega \quad (1M) \quad (4M)$	
4(a)	<p>Thevenin's Eqn Ckt</p> $E_{TH} = 11.18 \angle 93.43^\circ V \quad (5M)$ $Z_{TH} = 4 + j3\Omega \quad (5M)$	(12M)
	<p>Norton's Eqn Ckt</p> $I_N = 2.24 \angle 56.56^\circ A \quad (5M)$ $Z_N = 4 + j3\Omega \quad (5M)$ $I_{10\Omega} = 0.78 \angle 81.33^\circ A \quad (2M)$	
4(b)	$V_{TH} = 20V, R_L = 41.96\Omega \quad \} \rightarrow (6M)$ $P_{max} = \frac{V_{TH}^2}{4R_L} = 2.383W \rightarrow (2M)$	(8M)
5(a)	$i(0^+) = 0, R_i + L \frac{di}{dt} = 12, \frac{di(0^+)}{dt} = 60A/\mu sec \quad (3M)$ $8 \frac{di}{dt} + 0.2 \frac{d^2i}{dt^2} = 0 \quad \frac{d^2i(0^+)}{dt^2} = -2400A/\mu sec^2 \quad (2M)$	(5M)
5(b)	$i(0^+) = 0, R_i + L \frac{di}{dt} + v_c(t) = 0, \frac{di(0^+)}{dt} = -40A/\mu sec \quad (3M)$ $v_c(0^+) = 40V \quad (2M)$ $\frac{R di}{dt} + \frac{L d^2i}{dt^2} + \frac{1}{C} = 0, \frac{d^2i(0^+)}{dt^2} = 800A/\mu sec^2 \quad (2M)$	(7M)
5(c)	$v(0^+) = IR = 400V, I = \frac{v(t)}{R} + \frac{1}{L} \int_{0^+}^t v(\tau) d\tau \quad (2M)$ $\frac{dv(0^+)}{dt} = -8 \times 10^4 V/\mu sec \quad (4M)$	

$$\frac{dv(0^+)}{dt} = -8 \times 10^4 V/\mu sec$$

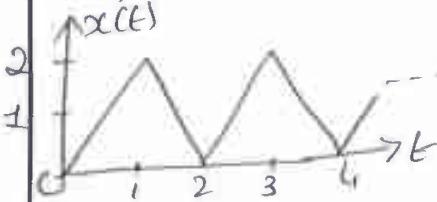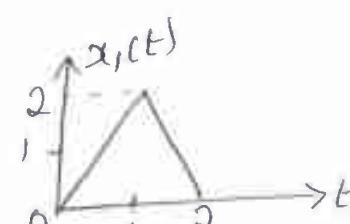Question Number	Solution	Marks Allocated
6(a)	$\frac{1}{R} \frac{d^2 v(t)}{dt^2} + \frac{1}{L} \frac{dv(t)}{dt} = 0$ , $\frac{d^2 v(0^+)}{dt^2} = 16 \times 10^6 V/sec^2$ (8M) $i_2(0^+) = 1.33A$ $i_1(0^+) = 0.67A$ $v_c(0^+) = 13.3V$ (2M) $10i_1 + \frac{1}{C} \int_{0^+}^t i_1(\tau) d\tau = 20$ (4M) $\frac{di_1(0^+)}{dt} = -0.67 \times 10^5 A/sec$ (4M) $10i_2 + 2 \frac{di_2}{dt} = 20$ , $\frac{di_2(0^+)}{dt} = 3.35 A/sec$	(2M)
6(b)	$i(0^+) = 5A$ , $v(0^+) = 25V$ (2M) $4 + i = C \frac{dv}{dt} + \frac{v}{5}$ , $\frac{dv(0^+)}{dt} = 40V/sec$ (3M) (10M) $3i + 0.25 \frac{di}{dt} + v = 0$ , $\frac{di(0^+)}{dt} = -160 A/sec$ (3M) $i(\infty) = -2.5A$ , $v(\infty) = 7.5V$ (2M)	
7(a)	$i_L(0^+) = 1A$ , $v_c(0^+) = 8V$ (2M) $-\frac{8}{S} + \frac{20}{S} I_L(s) + 4sI_L(s) - 4 + 8I_L(s) = 0$ (3M) (10M) $I_L(s) = \frac{s+1}{(s+1)^2 + 2^2} + \frac{1}{2} \left[ \frac{2}{(s+1)^2 + 2^2} \right]$ (3M) $i_L(t) = [e^{-t} \cos 2t + \frac{1}{2} e^{-t} \sin 2t] u(t) A.$ (2M)	
7(b)	$f(t) = x(t) + u(t)$  	(2M)

10(a) Proof for  $\omega_0 = \sqrt{\omega_1\omega_2}$  is required (6M)

10(b)  $f_0 = 15,915.5\text{Hz}$ ,  $Q_0 = 100$

B.W =  $159.155\text{Hz}$ ,  $f_1 = 15,835.92\text{Hz}$  [ $1 \times 6 = (6\text{M})$ ]

$f_2 = 15,995.1\text{Hz}$ ,  $I_0 = \pm 1\text{mA}$

10(c)  $\gamma_1 = \frac{1}{R_1 + j6}$        $\gamma_2 = \frac{1}{10 - j4}$  (2M)

$\gamma = \gamma_1 + \gamma_2$ , For the circuit to be resonant,  
the imaginary part of  $\gamma$  must  
be zero. (4M)

$$\frac{4}{116} = \frac{6}{R_1^2 + 36} \quad \therefore [R_1 = 11.75\Omega] \quad 2M \quad (8M)$$

Question Number	Solution	Marks Allocated
7(b) contd.,	$x_i(t) = \begin{cases} 2t, & 0 < t < 1 \\ 4-2t, & 1 < t < 2 \end{cases}$ $X_i(s) = \frac{2}{s^2} (1-e^{-s})^2$ (2M) $X(s) = \frac{x_i(s)}{1-e^{-3s}} = \frac{2(1-e^{-s})^2}{s^2(1-e^{-2s})}$ $F(s) = X(s) + U(s)$ (2M) $F(s) = \frac{2(1-e^{-s})^2}{s^2(1-e^{-2s})} + \frac{1}{s}$ - (2M)	(10M)
8(a)	$i_i(0^-) = \frac{4}{3} A, v_c(0^+) = 4V$ - (2M) $\frac{v_c(s)}{3} + \frac{s}{2} v_c(s) = 2 + \frac{2}{s} \therefore v_c(s) = \frac{6}{s} - \frac{2}{s+2}$ (4M) $v_c(t) = [6 - 2e^{-\frac{2}{3}t}] u(t) V$ - (2M) $I_c(s) = \frac{v_c(s)}{\frac{2}{s}} - 2 = \frac{\frac{2}{3}}{s+2}$ (2M) $i_c(t) = \frac{2}{3} e^{-\frac{2}{3}t} u(t) A$	(10M)
8(b)	$f(t) = \begin{cases} V_0 & 0 < t < 2 \\ -V_0 t + 3V_0 & 2 < t < 3 \\ 0 & \text{ow} \end{cases}$ (3M) $f(t) = V_0 [u(t) - u(t-2)] + [-V_0 t + 3V_0] [u(t-2) - u(t-3)]$ (8M) $F(s) = \frac{V_0}{s} - \frac{V_0}{s^2} e^{-2s} + \frac{V_0}{s^2} e^{-3s}$ - (4M)	(10M)
9(a)	$y_{11} = \frac{1}{h_{11}}, y_{12} = -\frac{h_{12}}{h_{11}}, y_{21} = \frac{h_{21}}{h_{11}}, y_{22} = \frac{\Delta h}{h_{11}}$ (6M)	
9(b)	$Z_{11} = 15\Omega, Z_{21} = 5\Omega, Z_{12} = 5\Omega, Z_{22} = 20\Omega$ (6M)	
9(c)	$y_{11} = 0.0625$ $y_{12} = -0.0125$ (4M) $y_{21} = -0.0125$ $y_{22} = 0.0425$	$A = 2$ $B = -5\Omega$ (4M) $C = 0.125$ $D = 3$ (8M)