

GBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EC36

Third Semester B.E. Degree Examination, Jan./Feb. 2021 Power Electronics and Instrumentation

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Discuss various power converter circuits with necessary sketches and applications of each. (07 Marks)
- b. With necessary sketches, explain the static V-I characteristics of SCR and its operation. (08 Marks)
- c. List different turn-on methods, explain all in brief. (05 Marks)

OR

- 2 a. Explain turn-ON/turn-OFF dynamic characteristics of SCR with neat diagram. (07 Marks)
- b. With suitable diagram and waveform, explain the working of RC full wave firing circuit. (08 Marks)
- c. Describe the operation of UJT with neat sketches. (05 Marks)

Module-2

- 3 a. Explain the working of 1ϕ full wave center tapped controlled rectifier for resistive load with necessary sketches and also develop mathematical model to evaluate performance parameter of same (V_{dc} , V_{rms} , Efficiency). (10 Marks)
- b. Evaluate performance parameter of 1ϕ half controlled rectifier with resistive load, has a transformer secondary voltage of 230V, 50Hz with $R = 10\Omega$ and firing angle $\alpha = 60^\circ$. Determine:
 - i) Average voltage and current
 - ii) Rms value of voltage and current
 - iii) Efficiency
 - iv) Ripple factor
 - v) Form factor. (10 Marks)

OR

- 4 a. Input to the step-up chopper is 200V the output required is 600V, if the conduction time of thyristor is $200\mu\text{sec}$. Compute:
 - i) Chopping frequency
 - ii) If the pulse width is halved for constant frequency operation, find the new output voltage. (07 Marks)
- b. Explain the operation step-up chopper with neat diagram and derive an expression for output voltage. (08 Marks)
- c. Elaborate on the control techniques used in choppers and also give detailed classification of choppers. (05 Marks)

Modified

Module-3

- 5 a. With neat circuit diagram and waveforms. Explain the operation of 1ϕ full bridge inverter for RL load. (07 Marks)
- b. Design a multi range ammeter with range 0-1A, 0-5A and 0-10A employing individual shunt in each a D'Arsonval movement with an internal resistance of 500Ω and full scale deflection of 10mA is available. (08 Marks)
- c. What are the errors encountered in measurement process? Explain all with suitable example. (05 Marks)

OR

- 6 a. Design modified multirange voltmeter with basic D'Arsonval movement with an internal resistance of 50Ω and full scale deflection of 2mA, with voltage ranges of 0-10V, 0-50V, 0-100V and 0-250V. Draw the schematic diagram and show all values after design. (07 Marks)
- b. Explain the various static characteristics of measuring instruments. (08 Marks)
- c. With neat diagram, explain the operation of isolated flyback converter. (05 Marks)

Module-4

- 7 a. With neat block diagram, explain the operation of Ramp type Digital voltmeter. (07 Marks)
- b. Explain the operation of Time measurement with neat block diagram. (08 Marks)
- c. Draw the schematic diagram of Wheatstone's bridge and derive an expression for calculating unknown resistance and explain. (05 Marks)

OR

- 8 a. Explain the operation inductance comparison bridge with necessary equations. (07 Marks)
- b. Discuss the operation of successive approximation type DVM with necessary diagram. (08 Marks)
- c. An unbalanced Wheatstone bridge shown in Fig.Q.8(c), calculate the current through the galvanometer. (05 Marks)

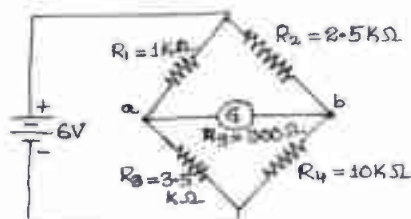


Fig.Q.8(c)

Module-5

- 9 a. Draw the schematic diagram to measure displacement using resistive transducer and explain. (07 Marks)
- b. Explain the operation of PLC with neat block diagram. (05 Marks)
- c. Explain the operation of Instrumentation amplifier using transducer bridge and derive equation for output voltage. (08 Marks)

OR

- 10 a. Explain the construction and working principle of LVDT with characteristic curve. (07 Marks)
- b. What are factors to be considered for selecting the transducer? (08 Marks)
- c. Illustrate working of analog weight scale. (05 Marks)

Re: Sir, regarding Modification of scheme and solutions (18EC36)

"Mrityunjaya Vithal Latte" <mvlatte@rediffmail.com>

April 8, 2021 9:05 AM

To: "boe" <boe@vtu.ac.in>, "mvlatteBOEVTU" <mvlatte.boe.vtu@gmail.com>

Dear sir,

The scheme of 18EC36 is verified and it is inline with the question paper .
Regards

PROF. MRITYUNJAYA V. LATTE
Principal,
JSS Academy of Technical Education,
Uttarahalli-Kengeri Main Road, Bangalore
Karnataka 560 060

From: boe@vtu.ac.in
Sent: Wed, 31 Mar 2021 10:48:47
To: mvlatte@rediffmail.com, mvlatte25@gmail.com
Subject: Sir, regarding Modification of scheme and solutions (18EC36)





*** APPROVED ***
Rang SE
Registrar (Evaluation)
Visvesvaraya Technological University
BELAGAVI - 590018



[Signature]
Signature of Scrutinizer

Scheme & Solution

Subject Title : Power Electronics & Instrumentation, Subject Code : 18EC36.

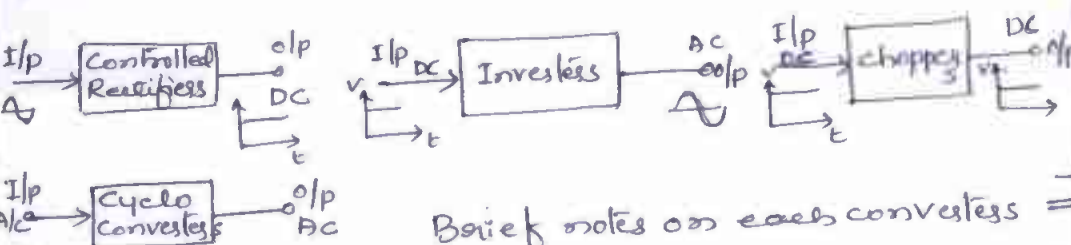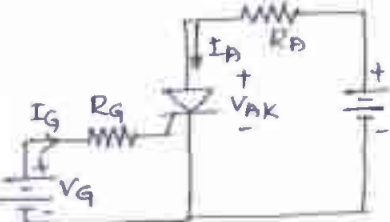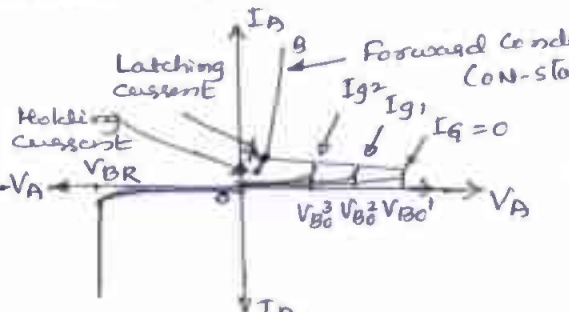
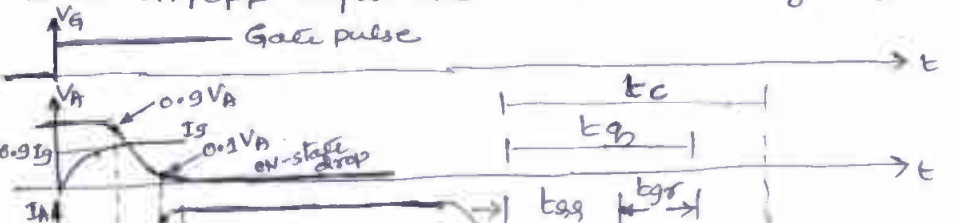
Question Number	Solution	Marks Allocated
1 @	<p>Power Converter Circuits: Inverters</p> <p>i) AC to DC ii) DC to AC (choppers) iii) DC to DC (choppers)</p> <p>iv) AC to AC v) regulators</p>  <p>Brief notes on each converter ⇒ 2M Applications; ⇒ 2M</p> <p>i) SMPS ii) Energy storage system iii) Electrical m/c control iv) Lighting drives v) power generations & distributions vi) Renewable energy conversion vii) Traction control etc</p>	03M 2M 2M
(b)	<p>Circuit diagram:</p>   <p>Explanation with reference;</p> <p>i) when $I_g = 0$ and V_A is positive.</p> <p>ii) when $I_g = +ve$ finite value & V_A is positive</p> <p>iii) when $I_g = 0$ and V_A is negative</p>	(02+02) 04M 04 03M
(c)	<p>Turn-ON methods;</p> <p>i) Forward voltage trigger</p> <p>ii) Gate triggering</p> <p>iii) Light triggering</p> <p>iv) Temperature triggering</p> <p>v) dv/dt triggering</p> <p>+ Brief note on each</p>	(02+03) 05M
2 @	<p>Turn-ON/OFF dynamic characteristics of SCR</p> 	03M

Question Number	Solution	Marks Allocated
-----------------	----------	-----------------

2. (b)

Explanation with intervals (time) + Necessary definitions and note on each $\Rightarrow 04M$

RC Full wave trigger circuit:

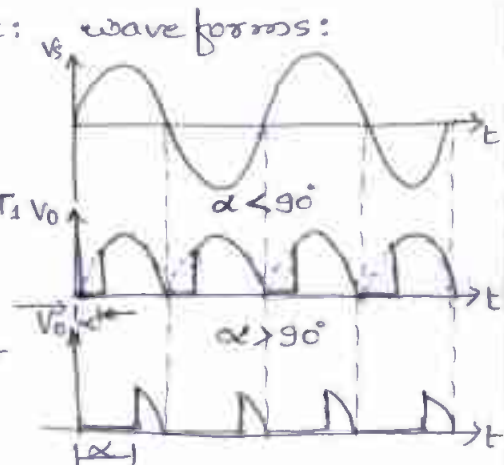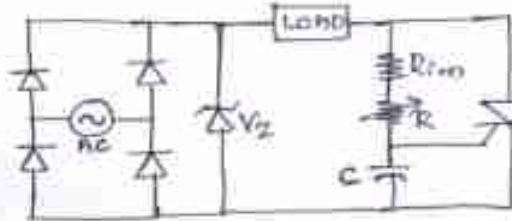


ckt = 2M
w/f = 2M
Expl = 4M


Detailed explanation for $\alpha < 90^\circ$ & $\alpha > 90^\circ$

(c)

UJT Circuit:

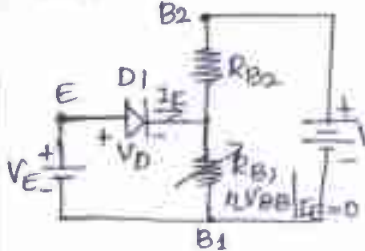

Characteristic curve

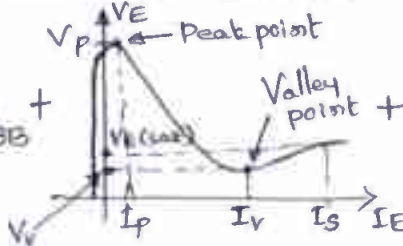

Brief note on operation


1.5M +
1.5M +
2M (Expl)

05M


Module - 2

3 (a)

Circuit diagram:

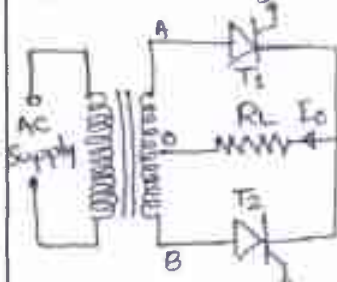

Wave forms:

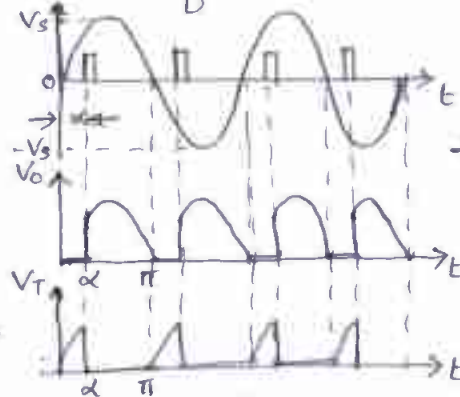

+ Explanation

2M +
2M +
2M } 06M

Explanation for both ~~cycle~~ cycle

$$V_{de} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d(\omega t) = \frac{2V_m}{\pi} (1 + \cos \alpha)$$

$$I_{de} = V_{de} / R_L = V_m / \pi R_L (1 + \cos \alpha)$$

$$V_{o,rms} = \left[\frac{1}{\pi} \int_{\alpha}^{\pi} V_o^2 d(\omega t) \right]^{1/2} =$$

$$\text{Efficiency} = \frac{V_{de}^2}{V_{o,rms}^2} =$$

(b)

Given: $V_s = 230V$; $\alpha = 60^\circ$; $f = 50Hz$; $R_L = 10\Omega$

$$V_{de} = \frac{V_m}{2\pi} \int_{\alpha}^{\pi} (1 + \cos \alpha) = \frac{325.26}{2\pi} \int_{60^\circ}^{\pi} (1 + \cos \alpha) = 51.76V$$

$$V_{o,rms} = V_m \left[\frac{\pi - \alpha}{4\pi} + \frac{\sin 2\alpha}{8\pi} \right]^{1/2} = 115.99V$$

$$\eta = \text{efficiency} = \frac{V_{de}^2}{V_{o,rms}^2} = \frac{51.76^2}{115.99^2} = 19.91\%$$

$$\text{Form factor} = V_{o,rms} / V_{de} = 115.99 / 51.76 = 2.24$$



$$\text{Ripple factor} = (FF^2 - 1)^{1/2} = 2.00$$


2M }
2M }
2M } 10M

Derivation

04M

10M

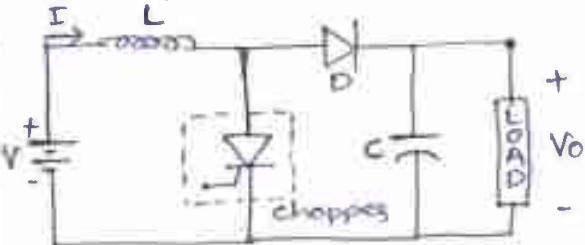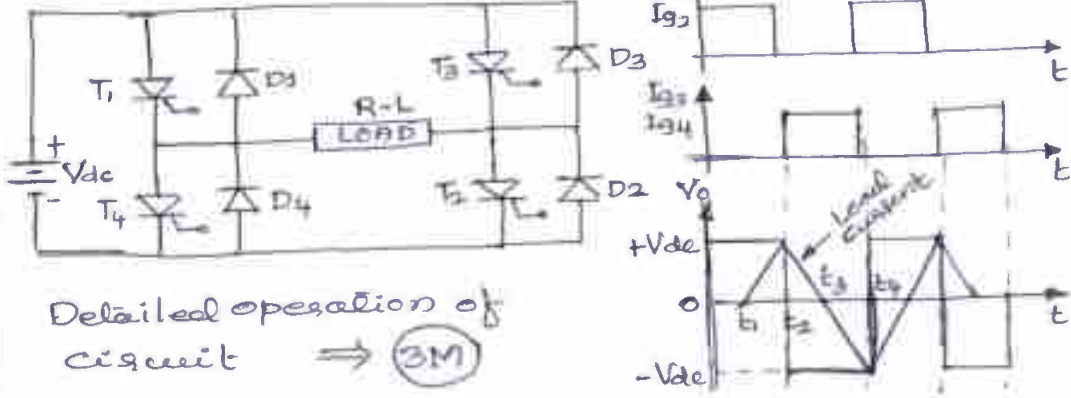
Question Number	Solution	Marks Allocated
4 a)	<p>Given: $V = 200 \text{ Volts}$ $t_{ON} = 200 \mu\text{s}$ $V_{ode} = 600 \text{ Volts}$</p> <p>$\therefore V_{ode} = V \times \left(\frac{T}{T - t_{on}} \right)$ $600 = 200 \left(\frac{T}{T - 200 \mu\text{s}} \right)$ $\therefore T = 300 \mu\text{s} \Rightarrow 2M$</p> <p>$\therefore$ chopping frequency $= f = 1/T = 1/300 \mu\text{s} = 3.33 \text{ KHz} \Rightarrow 2M$</p> <p>If pulse width is halved $\therefore t_{ON} = \frac{200 \mu\text{s}}{2} = 100 \mu\text{s} \Rightarrow 1M$</p> <p>$\therefore$ New o/p Voltage $= V'_{ode} = V \left(\frac{T}{T - t_{on}} \right) = 200 \left(\frac{300 \mu\text{s}}{300 \mu\text{s} - 100 \mu\text{s}} \right)$</p> <p>$V'_{ode} = 300 \text{ Volts} \Rightarrow 2M$</p>	
b)	<p>step-up chopper circuit:</p>  <p>+ Detailed explanation $\Rightarrow 2M$</p> <p>+ Derivation $\Rightarrow 3M$</p> <p>when chopper is ON; Voltage a/c inductor $L = V$ \therefore energy a/c $L = VI t_{ON}$</p> <p>when chopper is OFF Voltage a/c Inductor $L = V_o - V$ \therefore Energy a/c $L = (V_o - V) I t_{OFF}$</p> <p>$\therefore VI t_{ON} = (V_o - V) I t_{OFF}$</p> <p>$\therefore V_o = V \left(\frac{T}{T - t_{ON}} \right)$ where $T = t_{ON} + t_{OFF}$</p> <p>$\therefore V_o = V \left(\frac{1}{1 - \delta} \right)$</p>	<p>5M</p> <p>3M</p>
c)	<p>Techniques used in choppers</p> <p>i) Pulse width modulation control + brief notes with diagrams $\Rightarrow 3M$</p> <p>ii) Variable frequency control + diagrams $\Rightarrow 2M$</p> <p>Detailed chopper classification $\Rightarrow 2M$</p> <p style="text-align: center;"><u>Module - 3</u></p>	
5 a)	<p>1ϕ Full bridge Inverter ckt: waveforms:</p>  <p>Detailed operation of circuit $\Rightarrow 3M$</p>	<p>ckt = 2M</p> <p>w/f = 2M</p> <p>Expⁿ = 3M</p> <p>07M</p>

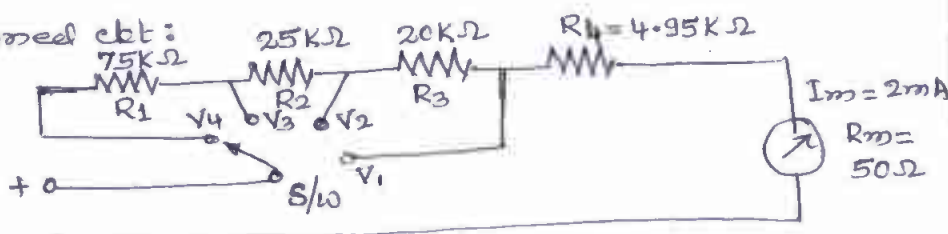Question Number	Solution	Marks Allocated
5 (b)	<p>Given: $I_m = 10\text{mA}$; $R_m = 500\Omega$</p> <p>We know that: $R_{sh} = \frac{I_m R_m}{I - I_m}$</p> <p>$\therefore$ Case 1: 0-1A</p> <p>i.e $R_{sh1} = \frac{10\text{mA} \times 500}{1\text{A} - 10\text{mA}} = 5.05\Omega$</p> <p>$\therefore$ Case 2: 0-5A</p> <p>$R_{sh2} = \frac{10\text{mA} \times 500\Omega}{5\text{A} - 10\text{mA}} = 1.002\Omega$</p> <p>$\therefore$ Case 3: 0-10A</p> <p>$R_{sh3} = \frac{10\text{mA} \times 500\Omega}{10\text{A} - 10\text{mA}} = 0.050\Omega$</p>	<p>Design: 0.6M</p> <p>Circuit: 2M</p> <p>0.8M</p>
5 (c)	<p>Errors Encountered in Measurements are;</p> <p>1) Gross Error 2) Systematic Error 3) Random errors</p> <p>+ Brief note on each with Example</p>	<p>0.1M + 0.4M</p> <p>0.5M</p>
6 (a)	<p>Given: $R_m = 50\Omega$ $I_m = 2\text{mA}$</p> <p>Case 1: For 10V range $R_t = \frac{V}{I_{fsd}} = \frac{10\text{V}}{2\text{mA}} = 5\text{K}\Omega$</p> <p>$\therefore R_4 = R_t - R_m = 5\text{K} - 50 = 4.95\text{K}\Omega$</p> <p>Case 2: For 50V Range $R_t = \frac{V}{I_m} = \frac{50\text{V}}{2\text{mA}} = 25\text{K}\Omega$</p> <p>$\therefore R_3 = R_t - (R_4 + R_m) = 25\text{K} - (4.95\text{K} + 50) = 20\text{K}\Omega$</p> <p>Case 3: For 100V Range; $R_t = \frac{100}{2\text{mA}} = 50\text{K}\Omega$</p> <p>$\therefore R_2 = R_t - (R_3 + R_4 + R_m) = (50\text{K} - (20\text{K} + 4.95\text{K} + 50)) = 25\text{K}\Omega$</p> <p>Case 4: For 250V $R_t = \frac{250}{2\text{mA}} = 125\text{K}\Omega$</p> <p>$\therefore R_1 = R_t - (R_2 + R_3 + R_4 + R_m) = 75\text{K}\Omega$</p> <p>Designed ckt:</p> 	<p>0.5M</p> <p>2M</p>
(b)	<p>Static characteristics of Instruments:</p> <p>i) Accuracy ii) Precision iii) Resolution iv) Sensitivity</p> <p>v) Repeatability vi) Expected Value</p> <p>+ Brief note on each characteristics</p>	<p>2M</p> <p>6M</p>
(c)	<p>Circuit diagram of Hydraulic converter</p> <p>Explanation</p>	<p>2M</p> <p>3M</p>



Question Number	Solution Module - IV	Marks Allocated
7 a		03M + Explanation ⇒ 04M
b		⇒ 04M + Explanation ⇒ 04M
c	<p>Wheatstone Circuit To have bridge balance equation</p> <p> $I_1 R_1 = I_2 R_2$ $\therefore I_1 = I_3 = E / (R_1 + R_3)$ $\therefore I_2 = I_x = E / (R_2 + R_x)$ $\therefore \frac{E R_1}{R_1 + R_3} = \frac{E R_2}{R_2 + R_x} \therefore R_x = \frac{R_2 R_3}{R_1}$ </p>	ckt = 1M Proof = 2M Expl ⁿ = 2M } 05 M
8 a	<p>Inductance comparison bridge</p> <p> Balance condition $Z_1 Z_x = Z_2 Z_3 \therefore L_x = \frac{R_2}{R_1} L_3$ $R_x = \frac{R_2 R_3}{R_1}$ </p> <p>+ Brief explanation</p>	ckt = 2M eq ⁿ s = 2M Expl ⁿ = 3M } 07 M
b		ckt = 03M + Explanation of each block ⇒ 05M "APPROVED" Registrar (Evaluation) VIT-TECHNICAL UNIVERSITY VIT-AGAM - 590015

Q.8.c $E_{th} = E_a - E_b = E \left(\frac{R_4}{R_2 + R_4} - \frac{R_3}{R_1 + R_3} \right) = 0.132 \text{ Volts} \Rightarrow 0.2 \text{ M}$
 $= E_b - E_a \Rightarrow 0.2 \text{ M}$
 $R_{th} = \frac{R_1 R_3}{R_1 + R_3} + \frac{R_2 R_4}{R_2 + R_4} = 2.778 \text{ K}\Omega$
 $\therefore I_g = R_{th} / (R_{th} + R_g) = 0.132 / (2.77 \text{ K} + 0.3 \text{ K}) = 42.88 \mu\text{A} \Rightarrow 0.1 \text{ M}$

Module-5

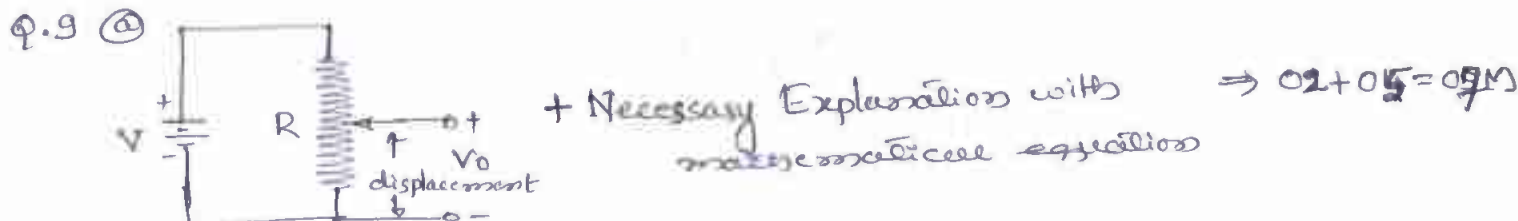

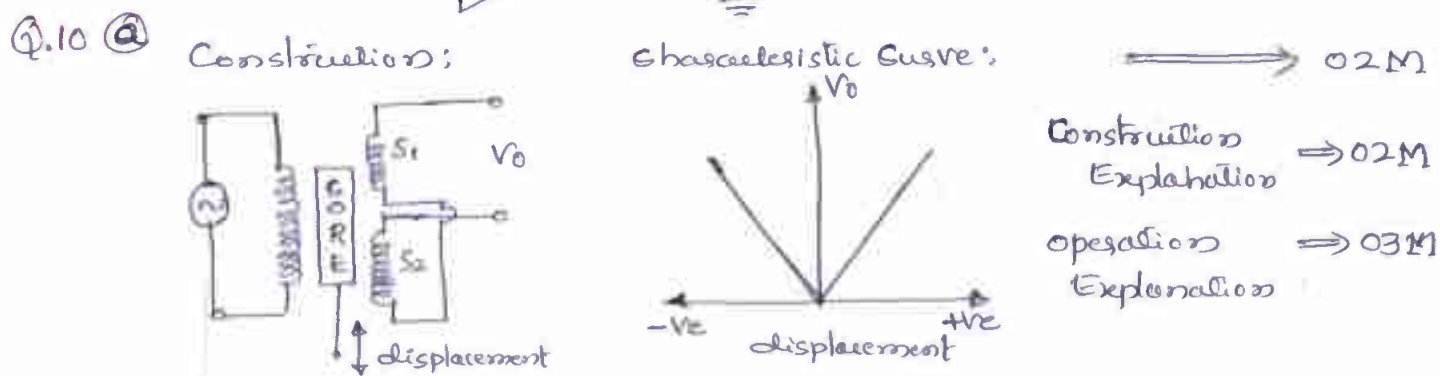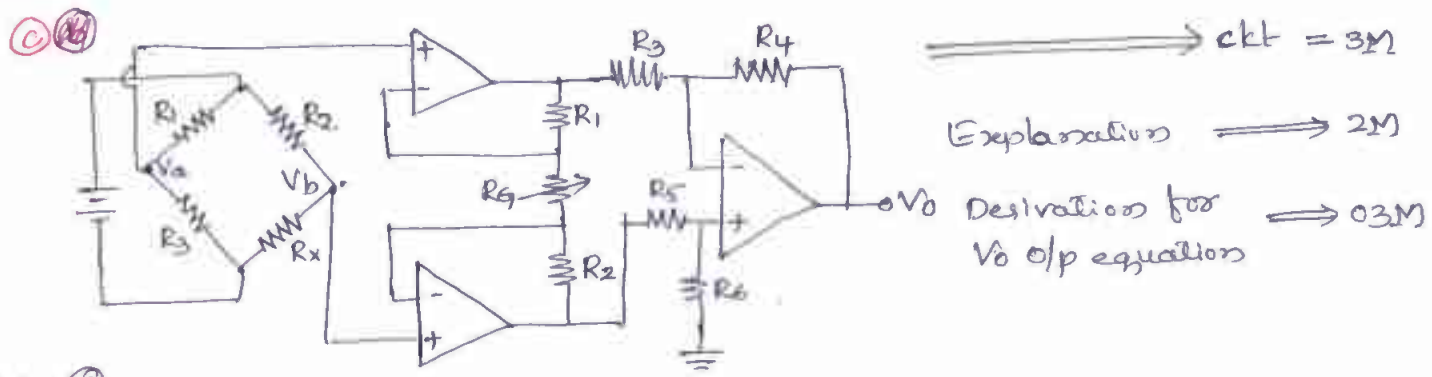b) Block diagram of PLC + Explanation $\Rightarrow 0.2 + 0.3 = 0.5 \text{ M}$



- b) Factors for selecting transducers
 i) operating range ii) Accuracy iii) Sensitivity
 iv) Ruggedness vs stability v) static characteristics
 vi) Loading effect + short notes on each $\Rightarrow 0.8 \text{ M}$

c) Analog Weight Block Diagram with PLC $\Rightarrow 2 \text{ M}$
 Explanation $\Rightarrow 0.3 \text{ M}$