

CMR Institute of Technology, Bangalore
DEPARTMENT OF PHYSICS
I - INTERNAL ASSESSMENT

Semester: 2-CBCS 2018

Subject: BASIC ELECTRICAL ENGINEERING (18ELE23)

Faculty: Ms Nithara P V

Date: 24 Jun 2021



Time: 02:15 PM - 03:45 PM

Max Marks: 50


Instructions to Students :

Answer Any FIVE FULL Questions

Answer any 5 question(s)

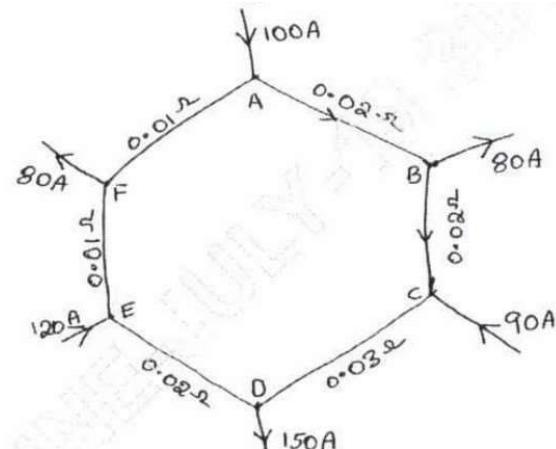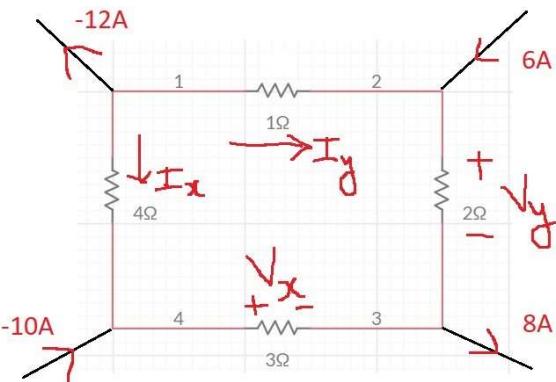Q.No		Marks	CO	BT/CL
1 a	State and explain ohm's law with an illustration. List its limitations.	4	CO1	
b	A DC circuit comprised two resistors R1 of value 30Ω and R2 of unknown value. The R1 and R2 are connected in parallel, together with the third resistor R3 of the value 6Ω connected in series with the parallel group. The P.D across R3 is 84V. If the total power in the circuit is 4312W, Calculate i) The value of R2 ii) The applied voltage to the ends of the whole circuit, and iii) The current in each resistor.	6	CO1	
2 a	For the sinusoidal signal, Define a) Cycle b) Time period c) Phase difference, and d) Form factor e) Peak factor.	5	CO1	
b	The instantaneous values of two alternating voltages are represented respectively by $v_1(t) = 2\sin(5t + 30^\circ)$ Volts and $v_2(t) = \sin(5t + 60^\circ)$ Volts. Derive an expression for the instantaneous value of (i) the sum (ii) the difference of these voltages.	5	CO1	
3 a	Determine the currents in various branches of the given network.	5	CO1	
				
b	Determine V_x , V_y , I_x , I_y .	5	CO1	
				
4 a	Define RMS Value of Alternating current, show that Its value is proportional to the maximum value.	5	CO1	
b	The equation for an AC voltage as $V = 0.04\sin(2000t + 60^\circ)$ Volts. Determine the frequency, angular frequency, instantaneous voltage when $t = 160\mu s$. What is the time represented by a 60° phase angle?	5	CO1	
5 a	Two 12V batteries with internal resistance 0.2Ω and 0.25Ω respectively are joined in parallel and a resistance of 1Ω is placed across the terminals. Find the current supplied by each battery.	5	CO1	
b	State and Explain Kirchoff's laws as applied to an electric circuit.	5	CO1	

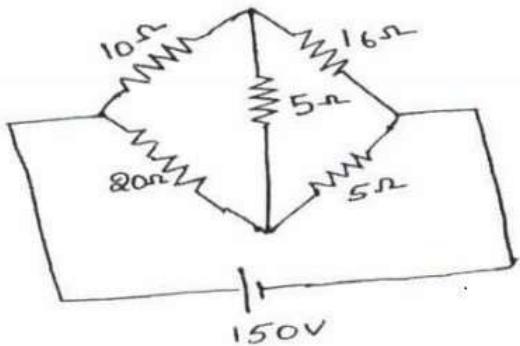For the bridge circuit shown in Fig. Calculate current in all the branches and power supplied by the source.




6 a

5 CO1

b Explain the generation of single-phase AC induced emf with a suitable diagram.

5 CO1

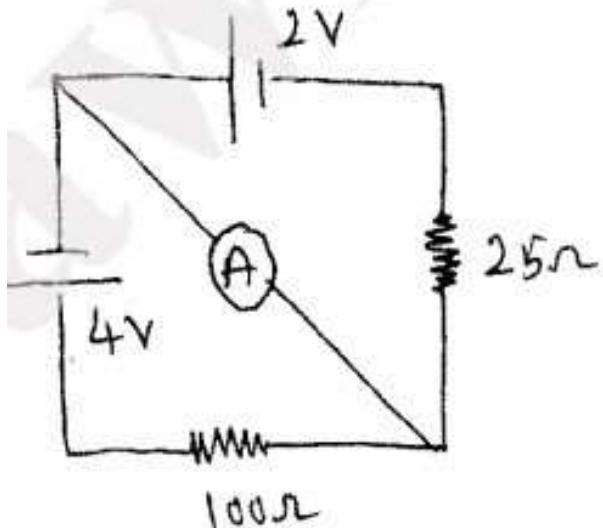
For the network shown in Fig. determine current flow in the Ammeter "A" having a resistance of 10Ω .



7 a

5 CO1

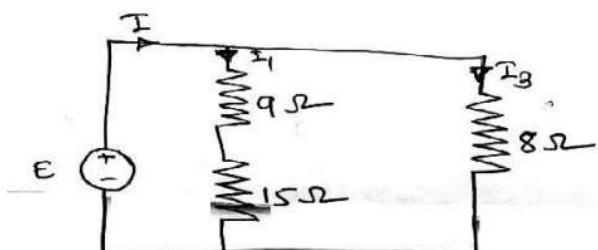For the network shown in Fig. determine I_1 , I_3 , E , and I . If the voltage across 9Ω resistor is 27V.



b

5 CO1

State and Explain Ohm's law, and its limitations.

Ohm's law: States that the current passing through a conductor in a circuit is directly proportional to the potential difference applied across the ends of the conductor and inversely proportional to the resistance of the conductor at constant temperature → (2M)


Equation, $V = IR$ → (1 M)

- Limitations
- ① not applicable when temperature is not constant
 - ② not applicable to non-linear circuits & devices
 - ③ not applicable to non-metallic conductors

Given $P = 4312 \text{ W}$

$$\frac{I}{R} = \frac{V}{R}$$

$$= \frac{84}{6} = 14 \text{ A}$$

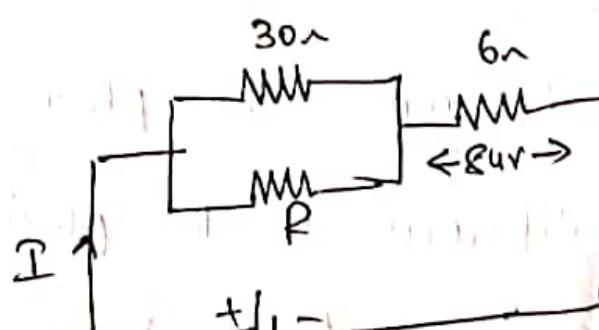

(1M)

(1 M)

$$P = I^2 R \Rightarrow 4312 = (14)^2 R_T, R_T = \frac{4312}{196} = 22 \Omega \quad (1 \text{ M})$$

$$\frac{30 \times R_2}{30 + R_2} + 6 = 22 \Rightarrow R_2 = 34.28\Omega \quad \text{(1M)}$$

$$I_{30\Omega} = 7.46A$$

$$I_{34\Omega} = 6.53A \quad \text{(3M)}$$

$$I_{6\Omega} = 14A$$

Definitions: ① cycle: A cycle is a series of events that are repeated in the same order. (8) (1M)

when a wave-form reaches a complete set of positive & negative values in called a cycle.

② Time period: The time taken by in seconds by an alternating quantity to complete one cycle is known as time period

③ phase difference: The phase difference can be defined as the difference in the phase when two alternating quantities are started at the same instant.

$$④ \text{form factor} = \frac{\text{RMS value}}{\text{Avg Value}} = 1.11$$

⑤ Peak factor:

$$P.f = \frac{\text{Max. Value}}{\text{RMS Value}} = 1.412$$

(b) $V_1(t) = 2 \sin(5t + 30^\circ)$, $V_2(t) = \sin(5t + 60^\circ)$

Polar form of V_1, V_2 in $V_1 = 2(30^\circ)$, $V_2 = 1(60^\circ)$

$$\text{Sum} = V = V_1 + V_2 = 2(30^\circ + 160^\circ) \quad (1M)$$

Polar to cartesian variables = $2 \cos 30^\circ + j 2 \sin 30^\circ + \cos 60^\circ + j \sin 60^\circ$

$$= 1.732 + j + 0.5 + j 0.866$$

$$= 2.232 + j 1.866$$

$$V = 2.91 \angle 39.9^\circ \quad (2M)$$

$$\therefore V(t) = 2.91 \sin(5t + 39.9^\circ) \rightarrow (2M)$$

3a Apply KCL & KVL to the loop

$$-0.02I - 0.02(I-20) - 0.03(I+10) - 0.02(I-140) -$$

$$0.01(I-20) - 0.01(I-100) = 0$$

$$I = 48.18A$$

- 2M

$$AB = 48.14A$$

$$EF = 28.18A$$

$$BC = -31.8A$$

$$FA = -51.82A$$


$$CD = 58.15A$$

$$DE = -91.82A$$

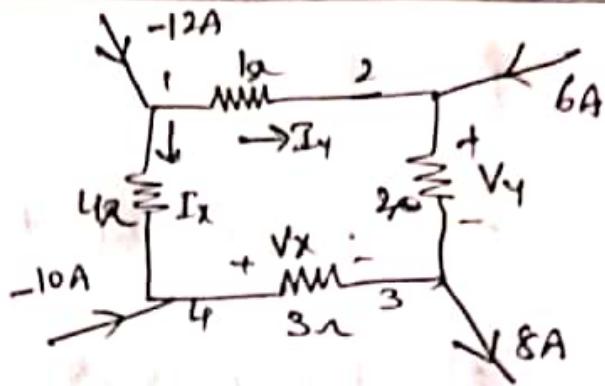3.6

Apply KVL

$$\begin{aligned} & \{I_y x_1 + 2(I_y + 6) + 3(I_y - 2) \\ & + 4(I_y - 12) = 0 \end{aligned}$$



$$10I_y + 12 - 6 - 48 = 0$$

$$10I_y = 42 \Rightarrow I_y = 4.2 \text{ A}$$

$$V_y = 2 \times (I_y + 6) = 2(4.2 + 6)$$

$$V_y = 20.4 \text{ V}$$

$$V_x = 3 \times (I_y - 2) = 3 \times (4.2 - 2) = 6.6 \text{ V}$$

$$V_x = 6.6 \text{ V}$$

$$I_x = -(I_y - 12) = -(4.2 - 12) = I_x = 7.8 \text{ A}$$

4.9

RMS: An AC current is the current which when passed through a given resistance for a given time, produces same heat as produced by flow of one ampere of DC current through the same resistance for the same time.


(2 M)

derivation:

$$i = I_m \sin \theta \rightarrow ①$$

Area of first half cycle of the

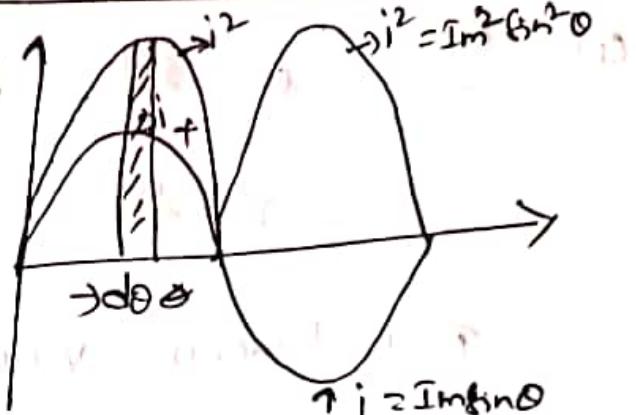Squared value = $\int_0^{\pi} i^2 d\theta \rightarrow ②$



$$\text{Area} = \int_0^{\pi} (I_m \sin \theta)^2 d\theta$$

$$= \int_0^{\pi} I_m^2 \sin^2 \theta d\theta \quad \left| \frac{I_m^2}{2} \left[(\pi - 0) - \left(\frac{\sin 2\pi - \sin 0}{2} \right) \right] \right.$$

$$= I_m^2 \int_0^{\pi} \sin^2 \theta d\theta \quad \left| = \frac{I_m^2}{2} (\pi - (0 - 0)) \right.$$

$$= I_m^2 \int_0^{\pi} \left[\frac{1 - \cos 2\theta}{2} \right] d\theta \quad \left| = \frac{I_m^2 \pi}{2} \right.$$

$$= \frac{I_m^2}{2} \int_0^{\pi} 1 - \cos 2\theta d\theta$$

$$= \frac{I_m^2}{2} \left[\theta - \frac{\sin 2\theta}{2} \right]_0^{\pi}$$

$$\therefore \text{RMS of } I = \sqrt{\frac{\text{Area of first half cycle squared}}{\text{Base}}} \quad \left| \text{Area of first half cycle squared} \right.$$

$$= \sqrt{\frac{I_m^2 \cdot \pi}{2\pi}} = \sqrt{\frac{I_m^2}{2}} = \frac{I_m}{\sqrt{2}}$$

$$I_{\text{rms}} = 0.707 I_m$$

4b

Given $\omega = 2\pi f = 2000 \text{ rad/sec}$

$$f = \frac{\omega}{2\pi} = \frac{2000}{2\pi} = \underline{318.3 \text{ Hz}} \quad (\text{1M})$$

Instantaneous value @ $t = 160 \mu\text{s}$ is

$$V = 0.04 \sin(2000 \times 160 \times 10^{-6} + 60) \text{ V}$$

$$= 0.04 \sin(0.32 \text{ rad} + 60) \text{ V}$$

$$= 0.04 \sin\left(0.32 \times \frac{180}{\pi} + 60\right) \text{ V}$$

$$= 0.04 \sin(18.3^\circ + 60^\circ) \text{ V}$$

$$= 0.0392 \text{ V}$$


$$\boxed{V = 39.2 \text{ mV}}$$

(2M)

② Time period, $T = 1/f = \frac{1}{318.3} = \underline{3.14 \text{ ms}} \quad (\text{1M})$

@ 60° , $t = \frac{60}{360} \times 3.14 \text{ ms} = \underline{0.52 \text{ ms}} \quad (\text{1M})$

59

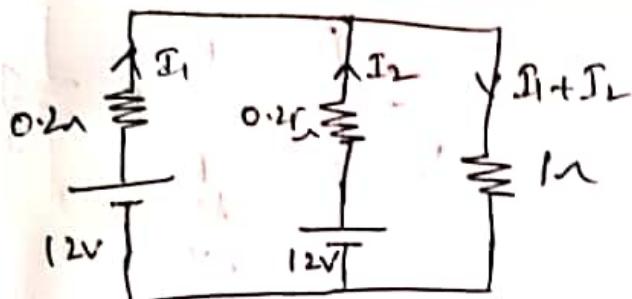

(1M)

(2M)

Apply KVL & form the loops

Solving the two loop equations

$$I_1 = 6 \text{ A}$$

(1M)

(1M)

$$I_2 = 4.8 \text{ A}$$


Kirchoff's Law: ① Kirchoff's Current Law

② Kirchoff's Voltage Law

⇒ The sum of currents entering the circuit at a node is equal to the sum of the currents leaving the node

$$-I_1 + I_2 - I_3 - I_4 = 0$$

$$I_1 + I_3 + I_4 = I_2$$

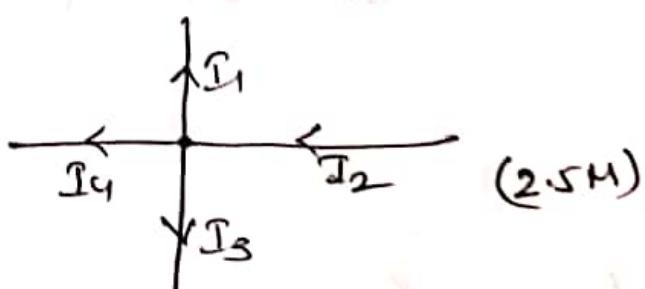


(2.5M)

⇒ In a closed circuit the sum of the P.D's across the resistors plus Emf's is equal to zero.

$$V = I_1 R_1 + I_2 R_2 + I_3 R_3$$

$$\boxed{V = V_1 + V_2 + V_3}$$

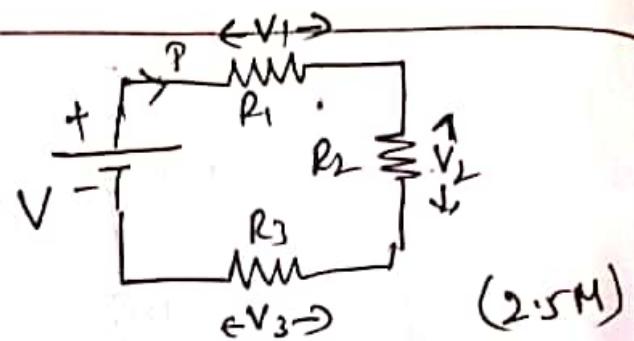

6G

Apply KVL to the loops

~~$-I_1 + 10 - 8(I_1 - I_2) - 20I_1 = 0$~~

$38I_1 - 8I_2 - 20I_3 = 0 \rightarrow \textcircled{1}$

Loop 2:

$-I_2 \times 15 = 5(I_1 - I_3) - 8(I_2 - I_1) = 0$

$-15I_2 - 5I_2 + 5I_3 - 8I_2 + 8I_1 = 0$

(2M)

$-8I_1 + 28I_2 - 5I_3 = 0 \rightarrow \textcircled{2}$

Loop 3:

$-20I_1 - 5I_2 + 25I_3 = 150 \rightarrow \textcircled{3}$

Solving $\textcircled{1}, \textcircled{2}, \textcircled{3}$

$I_1 = 8A$

$I_2 = 4.67 A$

$I_3 = 13.3 A$

(1M)

(1M)

(1M)

6L

Generation of sinusoidal voltage:-

Explanation of Faraday's law of electromagnetic induction with diagram.

(5M)

Q1 Apply KVL to the loops


$$-110I_1 - 10I_2 - 4 = 0 \rightarrow \textcircled{1}$$

$$-10I_1 + 35I_2 - 2 = 0$$

Solving \textcircled{1} & \textcircled{2} $I_1 = -0.04 A$

$$I_2 = -0.06 A$$
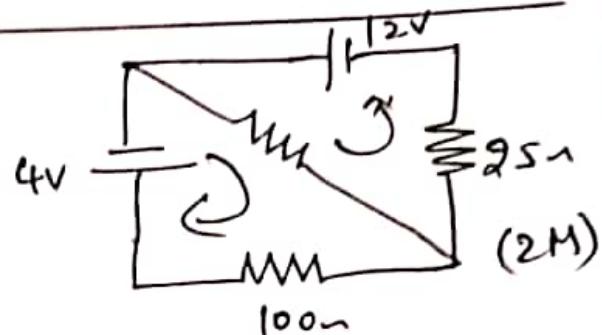
$$I_1 - I_2 = -0.04 + 0.06 = \underline{\underline{0.02 A}}$$



(1M)


(1M)

(1M)

$$I_1 = \frac{V}{R}$$

$$I_1 = \frac{27}{9} = \underline{\underline{3A}}$$
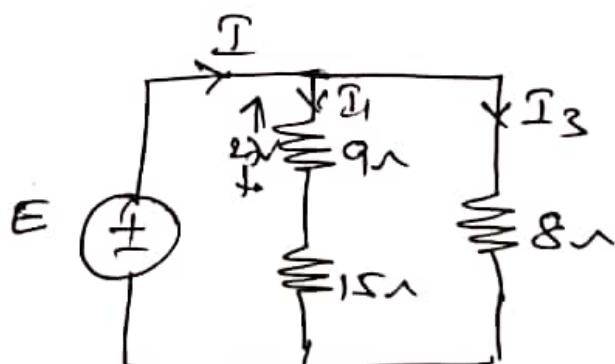
$$\boxed{I_1 = I_2 = \underline{\underline{3A}}}$$



(2M)

$$V_{15\Omega} = IR \Rightarrow V_{15\Omega} = 45V$$

$$V_{8\Omega} = 27 + 45 = \underline{\underline{72V}} \quad \therefore \boxed{E = 72V}$$

$$I_3 = 72/8 = 9A \quad \boxed{I_3 = 9A}$$

(1M)

$$\boxed{I = 18A}$$

(1M)