

USN : 

CMR Institute of Technology, Bangalore  
DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING  
I - INTERNAL ASSESSMENT


Semester: 6-CBCS 2018  
Subject: POWER SYSTEM ANALYSIS – 1 (18EE62)  
Faculty: Ms Keka Mukhopadhyaya

Date: 19 May 2021  
Time: 09:00 AM - 10:30 AM  
Max Marks: 50

**Instructions to Students :**

Answer any FIVE full Questions.  
Assume data wherever necessary.

Answer any 5 question(s)
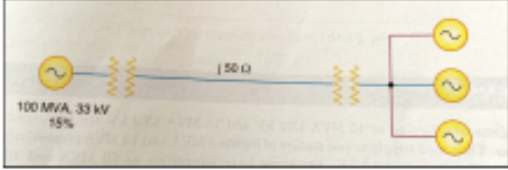
| Q.No |   | Marks | CO  | PO  | BT/CL |
|------|---|-------|-----|-----|-------|
| 1    | Derive the expression of maximum momentary current when a three phase short circuit occurs on a transmission line initially on no load condition. Draw the necessary diagram to model the transmission line and the waveforms of current.   | 10    | CO2 | PO1 | L2    |
| 2    | <p>A 100 MVA, 33 kV, 3<math>\phi</math> generator has a subtransient reactance of 15%. The generator is connected to the motors through a transmission line and transformers as shown in figure. The motors have rated inputs of 30 MVA, 20 MVA, and 50 MVA at 30 kV with 25% subtransient reactance. The three phase transformers are rated at 110MVA, 32kV <math>\Delta</math>/110kV Y with leakage reactance 8%. The line has a reactance of 50<math>\Omega</math>. Selecting the generator rating as the base quantities in the generator circuit, determine the base quantities in other parts of the system and evaluate the corresponding p.u values. Draw the reactance diagram.</p>        | 10    | CO1 | PO1 | L3    |
| 3    | a Define per unit system. Outline the advantages of working with per unit quantities.   | 5     | CO1 | PO1 | L2    |
|      | b Two generators are connected in parallel to a 6.6 kV bus. One of the generators has a rating of 20 MVA and a reactance of 15% while the second generator is rated at 15 MVA and has a reactance of 12%. Calculate the pu reactance on a 50 MVA and 6.6 kV base.   | 5     | CO1 | PO1 | L2    |
| 4    | A three-phase 20 MVA, 11 kV generator has a reactance of 10% and is connected via a bank of three single-phase transformers to a transmission line whose series reactance is 100 $\Omega$ . The transmission line is supplying a load of 10 MVA at 10 kV and 0.8 power factor lagging. The transformer bank at the generator end is connected in delta on the generator side and in star on the transmission line side and the transformer on the load side is star-star connected. Each of the single phase transformers in the bank of transformers is rated at 10 MVA, 11/110 kV with a reactance of 8%. Draw the one line diagram and hence draw the pu circuit diagram for a system base of 10 MVA, 15 kV in the load circuit. Calculate the voltage at the generator terminals. | 10    | CO1 | PO1 | L3    |
| 5    | a Show that the per unit impedance of a transformer is independent of its primary or secondary side.  | 5     | CO1 | PO1 | L2    |
|      | b The primary and secondary sides of a single phase 2 MVA, 4kV/2kV transformer have leakage reactance of 2 $\Omega$ and 4 $\Omega$ respectively. Find the p.u reactance of the transformer referred to primary and secondary side.  | 5     | CO1 | PO1 | L3    |
| 6    | With respect to synchronous machine explain the concept of subtransient, transient and synchronous reactance and explain how to model synchronous machine for a three phase symmetrical fault. Draw the necessary diagram along with current wave form.   | 10    | CO2 | PO1 | L2    |

A 3-bus system is given in figure. The ratings of the various components are listed below:

Generator 1: 50 MVA, 13.8 kV,  $X''=0.15$  pu

Generator 2: 40 MVA, 13.2 kV,  $X''=0.20$  pu

Generator 3: 30 MVA, 11 kV,  $X''=0.25$  pu


Transformer 1: 45 MVA, 11kV  $\Delta$ / 110kV Y,  $x=0.1$  pu

Transformer 2: 25 MVA, 12.5V  $\Delta$ / 115kV Y,  $x=0.15$  pu

Transformer 3: 40 MVA, 12.5kV  $\Delta$ / 110kV Y,  $x=0.1$  pu

The line impedances are shown in figure. Determine the reactance diagram based on 50 MVA and 13.8kV as base quantities in Generator 1.

7

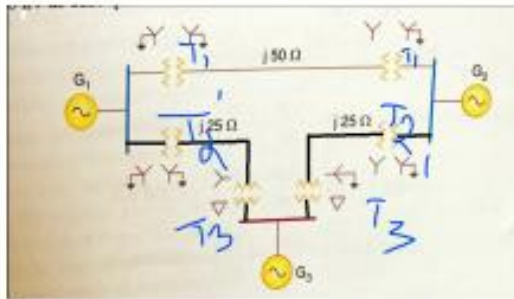

10

CO1

PO1

L4

Page view | Read aloud | Draw | Highlight

### Transient On A Transmission Line :-


Let us consider short circuit transient on a T.L

#### Assumption :

- (i) The line is fed from a constant voltage source (the case when the line is fed from a realistic synchronous machine will be treated)
- (ii) Short circuit takes place when the line is unloaded.
- (iii) Line capacitance is negligible and the line can be represented by a lumped RL series circuit.

Scanned with CamScanner

1.

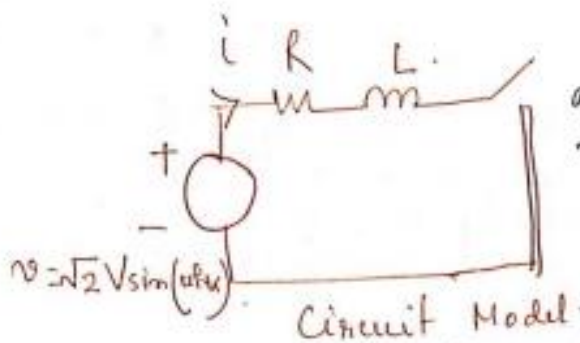

The short circuit is assumed to take place at  $t = 0$ .

The parameter  $\alpha$  controls the instant on the

voltage wave when short circuit occurs.

Current after short circuit composed of two parts!

$$i = i_s + i_t \quad \text{where } i_s = \text{steady state current}$$

$$i_s = \frac{\sqrt{2} V}{|Z|} \sin(\omega t + \alpha - \theta)$$

$$Z = (R^2 + \omega^2 L^2)^{1/2} \quad \angle \theta = \tan^{-1} \frac{\omega L}{R}$$

$$i_t = \text{transient current [it is such that } i(0) = i_s(0) + i_t(0) = 0]$$

being an inductive circuit;

it decays corresponding to time constant  $\frac{L}{R}$

$$= -i_s(0) e^{-(R/L)t} = \frac{\sqrt{2} V}{|Z|} \sin(\theta - \alpha) e^{-Rt/L}$$

$\therefore$  short circuit current is

$$i = \frac{\sqrt{2} V}{|Z|} \sin(\omega t + \alpha - \theta) + \frac{\sqrt{2} V}{|Z|} \sin(\theta - \alpha) e^{-Rt/L}$$

symmetrical short circuit current
DC-offset current



- \* In power system terminology
- sinusoidal steady state current is called symmetrical short circuit current.
  - unidirectional transient component is called DC off-set current  $\Rightarrow$  causes total short circuit current to be unsymmetrical till the transient decays.

Maximum momentary short circuit current  $I_{mm}$  corresponds to first peak.

If the decay of transient current in this time <sup>short</sup> is neglected.

$$I_{mm} = \frac{\sqrt{2}V}{|Z|} \cos \alpha + \frac{\sqrt{2}V}{|Z|}$$

Since T.L. resistance is small,  $\theta \approx 90^\circ$

$$\therefore I_{mm} = \frac{\sqrt{2}V}{|Z|} \cos \alpha + \frac{\sqrt{2}V}{|Z|}$$

This has maximum possible value when  $\alpha = 0$  i.e. short circuit occurring when the voltage wave is going through zero.

$$\therefore I_{mm} \big|_{\text{max possible}} = \frac{2\sqrt{2}V}{|Z|}$$

= twice the maximum of symmetrical short circuit current (doubling effect)

- \* In power system terminology current is called
- sinusoidal steady state current is called symmetrical short circuit current.
  - unidirectional transient component is called DC off-set current  $\rightarrow$  causes total short circuit current to be unsymmetrical till the transient decays.

Maximum momentary short circuit current  $I_{mm}$  corresponds to first peak.

If the decay of transient current in this time <sup>short</sup> is neglected.

$$I_{mm} = \frac{\sqrt{2}V}{|Z|} \cos \alpha + \frac{\sqrt{2}V}{|Z|}$$

Since T.L resistance is small,  $\theta \approx 90^\circ$



$$\therefore I_{mm} = \frac{\sqrt{2}V}{|Z|} \cos \alpha + \frac{\sqrt{2}V}{|Z|}$$

This has maximum possible value when  $\alpha = 0$  i.e. short circuit occurring when the voltage wave is going through zero.

$$\therefore I_{mm} |_{\text{max possible}} = \frac{2\sqrt{2}V}{|Z|}$$

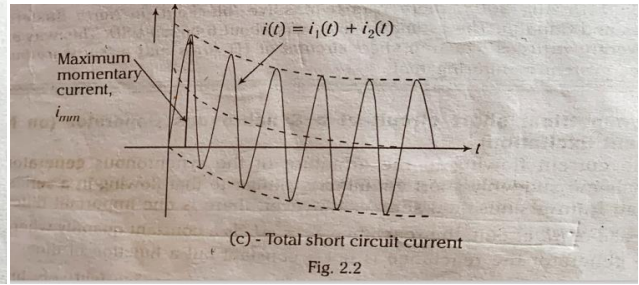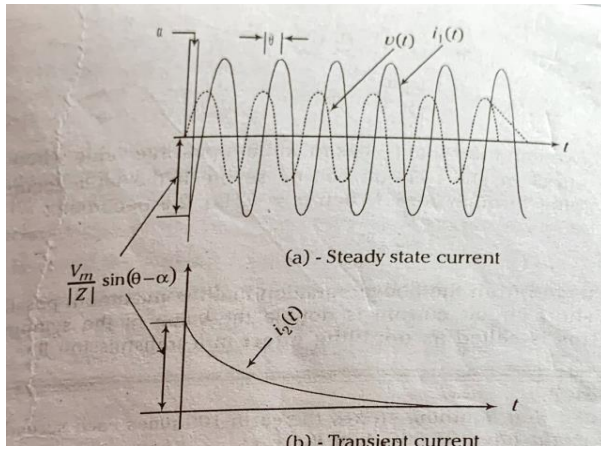= twice the maximum of symmetrical short circuit current (doubling effect)





2.

Base power 100 MVA  
 Base voltage at generator = 33 kV.  
 $\therefore$  Base voltage of transmission line =  $33 \times \frac{110}{32}$   
 $= 113.44 \text{ kV}$

Base voltage of Motors =  $113.44 \times \frac{32}{110} = 33 \text{ kV}$ .

$$X_{G1, \text{new}} = X_{G1, \text{old}} \times \frac{(MVA)_{\text{old}}}{(MVA)_{\text{new}}} \times \frac{(KV_{\text{B}})_{\text{old}}^2}{(KV_{\text{B}})_{\text{new}}^2}$$


$$= j0.15 \times \frac{100}{100} \times \frac{33^2}{33^2} = j0.15 \text{ p.u.}$$

$$X_{T1, \text{new}} = j0.08 \times \frac{100}{110} \times \frac{32^2}{33^2} = j0.068 \text{ p.u.}$$

$$X_{TL} = X(\Omega) \times \frac{(MVA)_{\text{B}}}{(KV_{\text{B}})^2} = \frac{j50 \times 100}{113.44^2} = j0.388 \text{ pu}$$

$$X_{T2, \text{new}} = j0.08 \times \frac{100}{110} \times \frac{32^2}{33^2} = j0.068$$
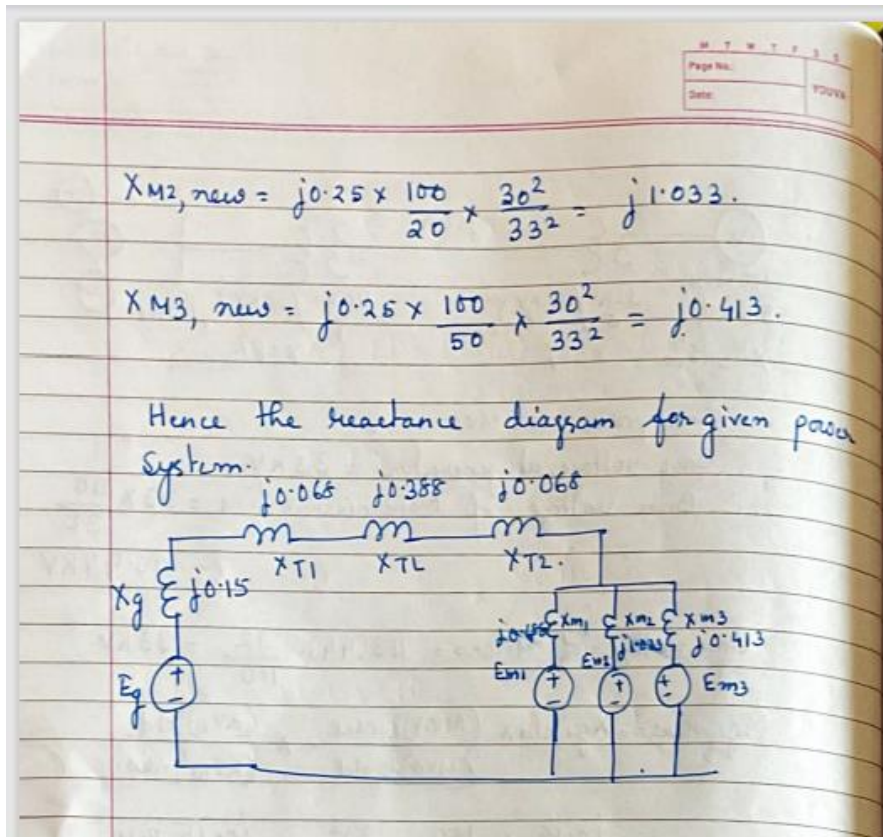
$$X_{M1, \text{new}} = j0.25 \times \frac{100}{20} \times \frac{30^2}{33^2} = j0.688 \text{ p.u.}$$



3a. Per unit value of any quantity is defined as the ratio as the actual value of the quantity in any unit to the base or reference value in the same unit. It is dimensionless.



### Advantages of p.u. Computations:

- 1) The greatest advantage of using p.u. values is that it considerably simplified the calculations thus making the analysis of the system easier. Other advantages are:
  - (1) Per unit impedance of transformers is the same ref. to either side of it.
  - (2) The method of connection of transformers ( $\Delta$ - $\Delta$ ,  $\Delta$ - $\Delta$  etc) do not effect the p.u. impedance of the transformer.
  - (3) Manufacture usually specify the impedance of an apparatus in p.u. or percent value on the name plate based on the power rating and voltage rating of the apparatus. Rated impedance can be used directly in any analysis if the base chosen are the same as the name plate ratings of the apparatus.
  - (4) In case of machines absolute values (ohmic) values of impedances may differ widely based on the constructing materials and the ratings of the machine.  
p.u. impedance will lie within a narrow range.  
Therefore where actual values are not known, good approx values can be used.



- (5) The tools of circuit analysis (ex Kirchoff's Law, Thevenin's theorem) may be directly applied to circuits with components in p.u. values.
- (6) For simulating the steady state and transient models in computer, the p.u. method is very handy.




3b.


2b). Base power  $(MVA)_B = 50 \text{ MVA}$ .  
 Base voltage  $(KV)_B = 6.6 \text{ KV}$ .  
 for gen1 and gen2

$$X_{p.u. \text{ new}} = X_{p.u. \text{ old}} \times \frac{(MVA)_{B, \text{ new}}}{(MVA)_{B, \text{ old}}} \times \frac{(KV)_{B, \text{ old}}^2}{(KV)_{B, \text{ new}}^2}$$


$$X_{g1, \text{ new}} = j0.15 \times \frac{50}{20} \times \frac{6.6^2}{6.6^2} = j0.375 \text{ p.u.}$$
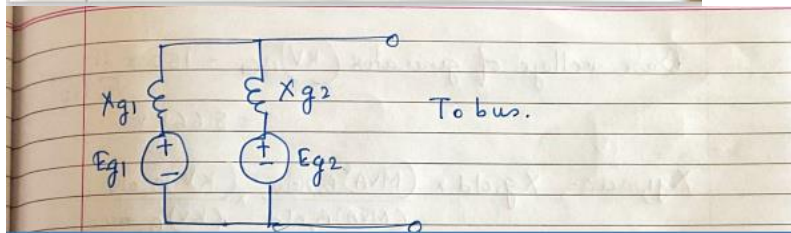
$$X_{g2, \text{ new}} = j0.12 \times \frac{50}{15} \times \frac{6.6^2}{6.6^2} = j0.4 \text{ p.u.}$$


4.

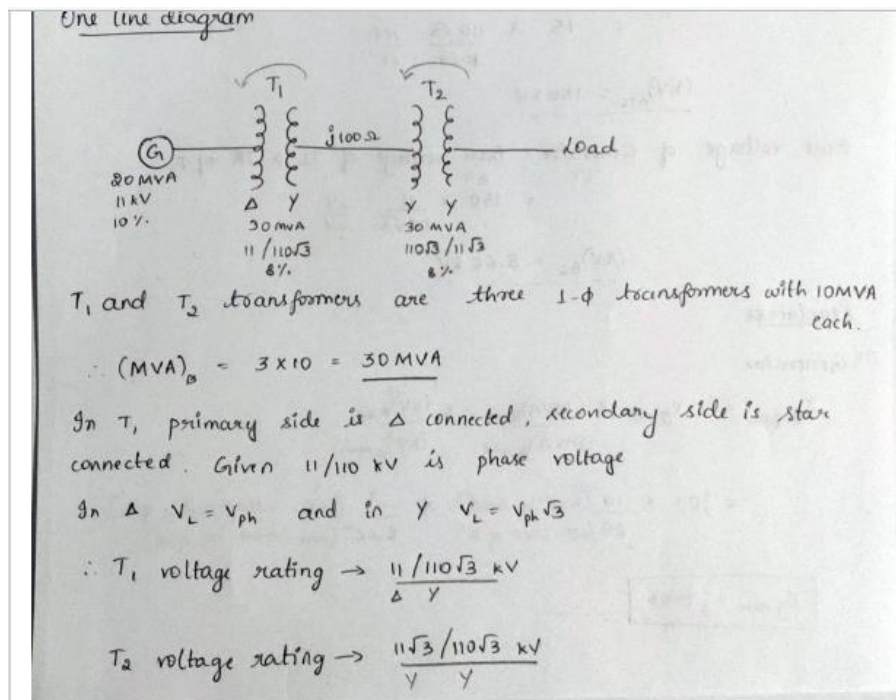

## Reactance diagram:

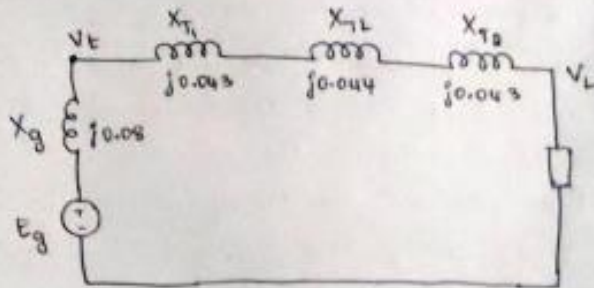

$$\text{Base power (MVA)}_B = 10 \text{ MVA}$$

$$\text{Base voltage (KV)}_B = 15 \text{ KV at load.}$$

$$\begin{aligned} \text{Base voltage of TL} &= \text{Base voltage of load} \times \text{TR of } T_2 \\ \text{HT} &= 15 \times \frac{110\sqrt{3}}{11} \frac{\text{KV}}{\text{KV}} \end{aligned}$$

$$\underline{\underline{(\text{KV})_{BTL} = 150 \text{ KV}}}$$

$$\begin{aligned} \text{Base voltage of Generator} &= \text{Base voltage of TL} \times \text{TR of } T_1 \\ \text{LT} &= 150 \times \frac{11}{110\sqrt{3}} \frac{\text{KV}}{\text{KV}} \end{aligned}$$

$$\underline{\underline{(\text{KV})_{BG} = 8.66 \text{ KV}}}$$

### Reactances:

(i) Generator

$$X_{g, \text{new}} = X_{g, \text{old}} \times \frac{(\text{MVA})_{B, \text{new}}}{(\text{MVA})_{B, \text{old}}} \times \frac{(\text{KV})_{B, \text{old}}^2}{(\text{KV})_{B, \text{new}}^2}$$

$$= j0.1 \times \frac{10 \text{ (Base of load)}}{20 \text{ (old-MVA of G)}} \times \frac{11^2 \text{ (old-voltage rating of G)}}{8.66^2 \text{ (new-base vlg of G)}}$$

$$\boxed{X_{g, \text{new}} = j0.08}$$

(ii) Transformer  $T_1$  and  $T_2$

$$X_{T_1} = X_{T_2} = X_{T,old} \times \frac{(MVA)_{B,new}}{(MVA)_{B,old}} \times \frac{(KV)_{B,old}^2}{(KV)_{B,new}^2}$$

$$= j0.05 \times \frac{10 \text{ [new base of load]}}{30 \text{ [old MVA of } X^*]} \times \frac{11^2 \text{ [old - LT side vlg wrt } T_1]}{8.66^2 \text{ [new - LT side base vlg wrt } T_1]}}$$

$$X_{T_1} = X_{T_2} = j0.043$$

(or)  $\frac{(110\sqrt{3})^2 \text{ [old - AT side vlg]}}{150^2 \text{ [new - AT side base vlg]}}$   
 (or)  $\frac{(11\sqrt{3})^2 \text{ [old - LT side vlg wrt } T_2]}{15^2 \text{ [new - LT side base vlg wrt } T_2]}}$

(iii) Transmission Line

$$X_{j100\Omega} = X(\Omega) \times \frac{(MVA)_B}{(KV)_{BTL}^2}$$

$$= j100 \times \frac{10}{150^2}$$

$$X_{j100\Omega} = 0.044j$$

Load  $\rightarrow$  10 MVA, 10 KV, 0.8 pf lag

$$pf = -\cos^{-1} 0.8$$

$$= -36.87^\circ$$

$$Power = 10 \angle -36.87^\circ$$

$$pu \text{ power of load} = \frac{\text{Actual load MVA}}{\text{Base load MVA}}$$

$$= \frac{10 \angle -36.87^\circ}{10}$$

$$pu \text{ power of load} = 1 \angle -36.87^\circ \text{ pu}$$

$$pu \text{ voltage of load} = \frac{\text{Actual load voltage}}{\text{Base load voltage}} = \frac{10}{15}$$



$$\text{pu value of load voltage} = \underline{0.66 \angle 0^\circ} \text{ pu}$$

Let  $I$  be pu value of current

$$I = \frac{\text{pu value of power}}{\text{pu value of voltage}} = \frac{1 \angle -36.87^\circ}{0.66 \angle 0^\circ}$$

$$\underline{I = 1.51 \angle -36.87^\circ \text{ pu}}$$

Terminal voltage of generator in pu value

$$\begin{aligned} V_t &= V_L + I_L [X_{T1} + X_{T2} + X_{TL}] \\ &= 0.66 + 1.51 \angle -36.87^\circ [j0.043 + j0.043 + j0.044] \end{aligned}$$

$$\underline{V_{t, \text{pu}} = 0.79 \angle 11.42^\circ}$$

$$\begin{aligned} \text{Actual terminal voltage } V_t &= \text{Base voltage of generator} \times \text{pu value of } V_t \\ &= 8.66 \times 0.79 \angle 11.42^\circ \end{aligned}$$

$$\boxed{V_t = 6.84 \angle 11.42^\circ \text{ kV}}$$

5.a

Soln Base Values  $(\text{MVA})_B = \text{rated MVA of the transformer}$   
 $(\text{KV}_1)_B = \text{Base voltage in the primary side.}$   
 $(\text{KV}_2)_B = \text{Base voltage in secondary side.}$

Also, let  $Z_{eq1}$  be the impedance of the transformer ref. to primary side and  $Z_{eq2}$  ref. to secondary side.

$$(Z_{eq1})_{\text{p.u.}} = Z_{eq1}(\Omega) \times \frac{(\text{MVA})_B}{(\text{KV}_1)_B^2} \quad \text{--- (1)}$$

$$(Z_{eq2})_{\text{p.u.}} = Z_{eq2}(\Omega) \times \frac{(\text{MVA})_B}{(\text{KV}_2)_B^2} \quad \text{--- (2)}$$

$$Z_{eq2}(\Omega) = Z_{eq1}(\Omega) \times \frac{(\text{KV}_2)_B}{(\text{KV}_1)_B} \quad \text{--- (3)}$$

Substituting (3) in (2),

$$(Z_{eq2})_{\text{p.u.}} = Z_{eq1}(\Omega) \times \frac{(\text{KV}_2)_B}{(\text{KV}_1)_B} \times \frac{(\text{MVA})_B}{(\text{KV}_2)_B^2}$$

$$(Z_{eq2})_{\text{p.u.}} = (Z_{eq1})_{\text{p.u.}}$$

5b

Page No.:  
Date: YDUVA

5. b)  $(MVA)_B = 2 \text{ MVA}$ .

primary side base voltage = 4 kV  
secondary side base voltage = 2 kV.

$X_1 = 2 \Omega$ ,  $X_2 = 4 \Omega$ .

Reactance w.r.t primary side.

$$X_{eq1} = X_1 + X_2' = 2 + 4 \times \left(\frac{4}{2}\right)^2 = 18 \Omega.$$
$$X_{pu} = X_{eq1} \times \frac{(MVA)_B}{(kV)_B^2} = 18 \times \frac{2}{4^2} = j2.25 \text{ pu}$$

Reactance w.r.t secondary side.

$$X_{eq2} = X_1' + X_2 = 2 \times \left(\frac{2}{4}\right)^2 + 4 = 4.5 \Omega.$$
$$X_{pu} = \frac{4.5 \times 2}{2^2} = 2.25 \text{ pu}.$$

6.

## Short Circuit of a Synchronous Machine (On No load)


Under steady state short circuit conditions, the armature reaction of a synchronous generator produces a demagnetizing flux.

In terms of a circuit this effect is modelled as a reactance  $X_a$  in series with the induced emf.

This reactance when combined with leakage reactance  $X_l$  of the machine is called synchronous reactance  $X_d$  (direct axis syn. reactance for salient pole machine).

Armature resistance being small can be neglected.

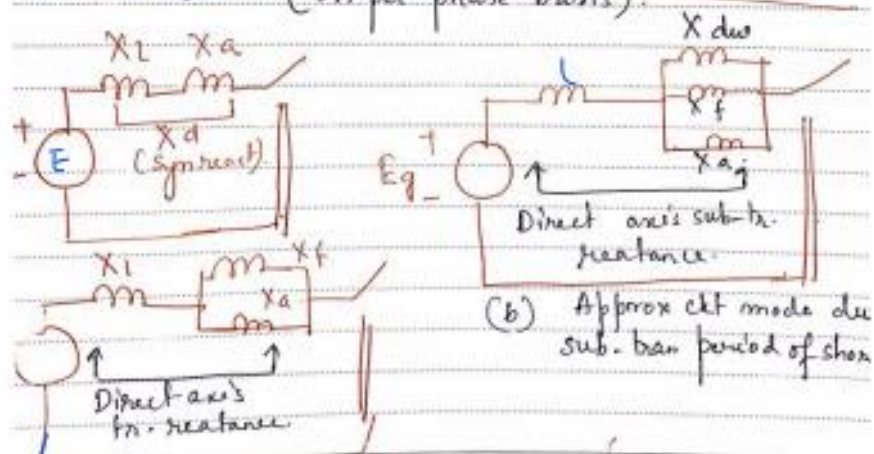The steady state short circuit model of Syn M/C  
(on per phase basis).



Approx ckt model during  $t_n$  period of short ckt.



Let us consider, sudden short circuit (three phase) of a synchronous generator, initially operating on open circuit conditions.

M/C undergoes a transient in all three phases finally ending up in steady state condition.

CB must interrupt the current much before steady conditions are reached.

Immediately, upon short circuit, the off-set currents appear in all the three phases with a different magnitude since the point on the voltage wave at which short circuit occurs is different for each phase. These D.C. offset currents are accounted for separately on an empirical basis and  $\Rightarrow$  therefore concentrate on Symmetrical (sinusoidal) short circuit currents.

Immediately in the event of a short circuit the symmetrical short circuit current is limited by the leakage reactance of the machine.

Since the air gap flux can not change instantaneously (theorem of constant flux linkages) to counter the demagnetization of the armature short circuit current, currents appear in the field winding as well as in the damper winding in a direct

to help the main flux. These currents decay in accordance with the winding time constants. The time constant of the damper winding which has low leakage inductance is much less than that of the field winding which has high leakage inductance. Thus during the initial part of the short circuit, the damper and field windings have transformer currents induced in them so that in the circuit model, their reactances —  $X_f$  for field winding,  $X_{dw}$  — damper winding.  $\rightarrow$  appear in parallel with  $X_a$ .

As the  $d_w$  currents are first to die out,  $X_{dw}$  effectively becomes open circuited, at a later  $X_f \Rightarrow$  becomes open circuited

The machine reactance thus changes from the parallel combination of  $X_a$ ,  $X_f$  and  $X_{dw}$  during the initial period of the short circuit to  $X_a$  and  $X_f$  in the middle period of short circuit and finally  $X_a$  in steady state.

The reactance presented by the machine in the initial period of the short circuit

$$X_2 + \frac{1}{\left(\frac{1}{X_a} + \frac{1}{X_f} + \frac{1}{X_{dw}}\right)} = X_{d''}$$


$X_{d''}$  = sub transient reactance of the machine.

After the damper winding currents have died,  
 $X'd = X_l + (X_{all} X_f) \Rightarrow$  transient reactance

The reactance under steady conditions is the synchronous reactance.

$$X_d'' < X_d' < X_d$$

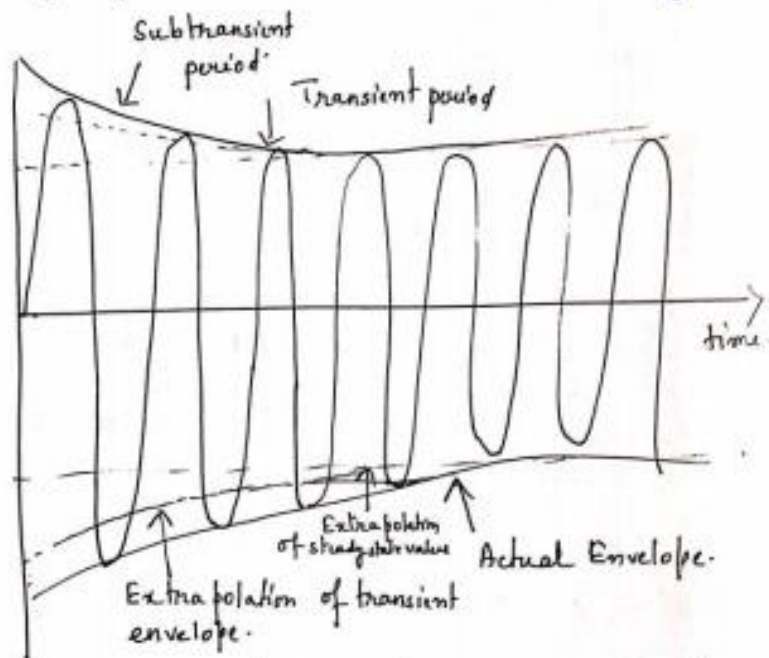Machine offers a time varying reactance which changes from  $X_d''$  to  $X_d'$  and finally to  $X_d$ .




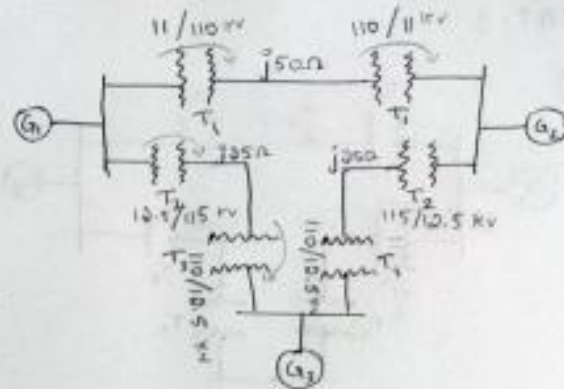a) Symmetrical short circuit armature current in synchronous machine.



IAT-1


- Ⓕ  $G_1 = 50 \text{ MVA}, 13.8 \text{ kV}, X'' = 0.15 \text{ pu}$
- $G_2 = 40 \text{ MVA}, 13.2 \text{ kV}, X'' = 0.2 \text{ pu}$
- $G_3 = 30 \text{ MVA}, 11 \text{ kV}, X'' = 0.25 \text{ pu}$
- $T_1 = 45 \text{ MVA}, 11 \text{ kV } \Delta / 110 \text{ kV Y}, X = 0.1 \text{ pu}$
- $T_2 = 25 \text{ MVA}, 10.5 \text{ kV } \Delta / 115 \text{ kV Y}, X = 0.15 \text{ pu}$
- $T_3 = 40 \text{ MVA}, 12.5 \text{ kV } \Delta / 110 \text{ kV Y}, X = 0.1 \text{ pu}$



Determine reactance diagram based on 50 MVA and 13.8 kV as base quantities in generator 1.

Sol<sup>n</sup>:-

Reactance Diagram

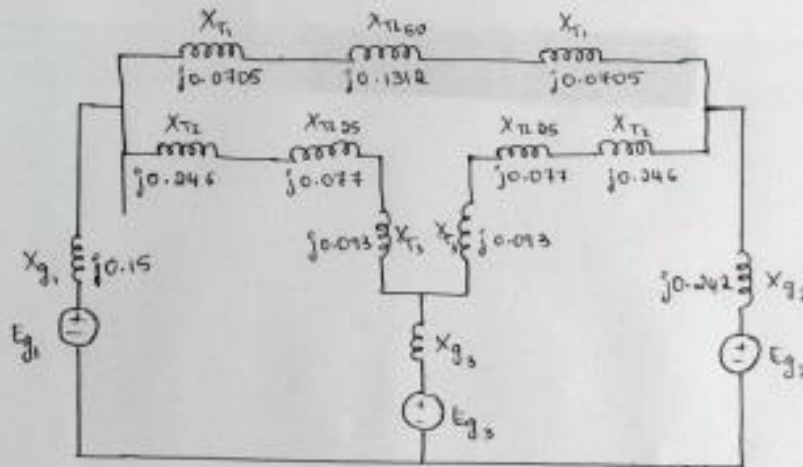

Base values

Base power of  $G_1$ ,  $(\text{MVA})_B = 50 \text{ MVA}$

Base voltage  $(\text{kV})_B = 13.8 \text{ kV}$

Base voltages

(i)  $(\text{kV})_B$  for 50 MVA TL = Base voltage of  $G_1$  x Transformation Ratio of  $T_1$

$$HT = 13.8 \times \frac{110}{11} \frac{kV}{kV}$$

$$(KV)_{B_{500}} = 138 \text{ KV}$$

$$\begin{aligned} \text{(i) } (KV)_B \text{ for } 25 \Omega \text{ TL} &= (KV)_{B_{500}} \times \text{TR of } T_2 \\ &= 13.8 \times \frac{115}{10.5} \frac{\text{HV}}{\text{LV}} \end{aligned}$$

$$(KV)_{B_{250}} = 127 \text{ KV}$$

$$\begin{aligned} \text{(ii) } (KV)_B \text{ for Generator 2} &= (KV)_{B_{500}} \times \text{TR} \\ &= 138 \times \frac{11}{110} \frac{\text{LV}}{\text{HV}} \end{aligned}$$

$$(KV)_{B_{G2}} = 13.8 \text{ KV}$$

$$\begin{aligned} \text{(iv) } (KV)_B \text{ for Generator 3} &= (KV)_{B_{250}} \times \text{TR of } T_3 \\ &= 127 \times \frac{12.5}{110} \frac{\text{LV}}{\text{HV}} \end{aligned}$$

$$(KV)_{B_{G3}} = 14.43 \text{ KV}$$

Reactances:

$$X_{pu, \text{new}} = X_{pu, \text{old}} \times \frac{(MVA)_{B, \text{new}}}{(MVA)_{B, \text{old}}} \times \frac{(KV)_{B, \text{old}}^2}{(KV)_{B, \text{new}}^2}$$

(i) Generator 1

$$X_{G1, \text{new}} = X_{G1, \text{old}} \times \frac{(MVA)_{B, \text{new}}}{(MVA)_{B, \text{old}}} \times \frac{(KV)_{B, \text{old}}^2}{(KV)_{B, \text{new}}^2}$$

$$= j0.15 \times \frac{50}{50} \times \frac{13.8^2}{13.8^2}$$

$$X_{G1, \text{new}} = j0.15$$

(ii) Generator 2

$$X_{G2, \text{new}} = 0.2j \times \frac{50 \text{ [new MVA]}}{40 \text{ [old MVA]}} \times \frac{13.8^2 \text{ [old KV]}}{13.8^2 \text{ [new base KV]}}$$

$$X_{G2, \text{new}} = j0.2287$$

(iii) Generator 3

$$X_{G_3, \text{new}} = j 0.25 \times \frac{50 \text{ [Base MVA of } G_3]}{30 \text{ [MVA of } G_3]} \times \frac{11^2 \text{ [old vlg - vlg of } G_3]}{14.43^2 \text{ [new vlg - base vlg of } G_3]}$$

$$X_{G_3, \text{new}} = j 0.242$$

(iv) Transformer 1,  $T_1$

$$X_{T_1, \text{new}} = j 0.1 \text{ (old)} \times \frac{50 \text{ [new-base MVA of } G_1]}{45 \text{ [old-MVA of } T_1]} \times \frac{11^2 \text{ [old-LT side vlg of } T_1]}{13.8^2 \text{ [new-LT side-base vlg of } T_1]}$$

$$X_{T_1, \text{new}} = j 0.0705$$

$$\text{(or)} \frac{110^2 \text{ (old-HT side vlg of } T_1)}{138^2 \text{ (new-HT side base vlg of } T_1)}$$

(v) Transformer 2,  $T_2$

$$X_{T_2, \text{new}} = j 0.15 \text{ (old)} \times \frac{50 \text{ [new-base MVA of } G_1]}{25 \text{ [old-MVA of } T_2]} \times \frac{12.5^2 \text{ [old-LT side vlg of } T_2]}{13.8^2 \text{ [new-LT side base vlg of } T_2]}$$

$$X_{T_2, \text{new}} = j 0.246$$

$$\text{(or)} \frac{115^2 \text{ (old-HT side of } T_2)}{127^2 \text{ (new-HT side base of } T_2)}$$

(vi) Transformer 3,  $T_3$

$$X_{T_3, \text{new}} = j 0.1 \times \frac{50 \text{ (base of } G_1)}{40 \text{ [old-MVA of } T_3]} \times \frac{12.5^2 \text{ [old-LT side of } T_3]}{14.43^2 \text{ [new-LT side base vlg of } T_3]}$$

$$\text{(or)} \frac{110^2 \text{ (HT side } T_3)}{127^2 \text{ (HT side base of } T_3)}$$

(vii) Transmission Line

$$X_{TL} = X(\%) \times \frac{\text{MVA}}{KV_A^2}$$

$$X_{TL|50A} = \frac{50 \times 50}{138^2 \text{ (base vlg of } j2T)} \quad \left| \quad X_{TL|20A} = \frac{20 \times 50}{127^2 \text{ (base vlg of } j2T)}$$

$$X_{TL|50A} = j 0.1312$$

$$X_{TL|20A} = j 0.077$$