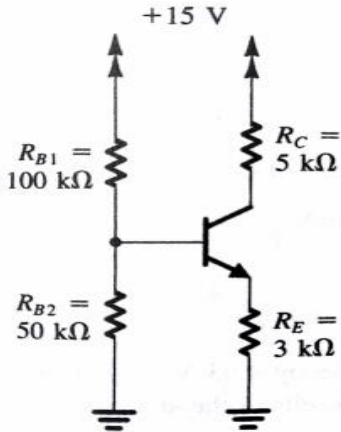
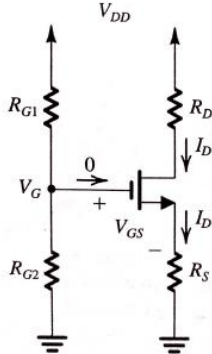


Internal Assessment Test - I

Sub:	Analog Circuits	Code:	18EC42
Date:	19/05/2021	Duration:	90 mins
		Max Marks:	50
		Sem:	4 <sup>th</sup>
		Branch:	ECE
Answer Any FIVE FULL Questions			

	Marks	OBE	
		CO	RBT
1. With the help of necessary circuit diagrams and design equations, explain the classical discrete biasing (voltage divider biasing) of BJT. How does $R_E$ provide a negative feedback action to stabilise the bias current.	[10]	CO1	L2
2. a) Why biasing a MOSFET amplifier circuit by fixing $V_{GS}$ is not considered as a good technique? b) With the help of necessary circuit diagrams and design equations, explain MOSFET biasing circuit by fixing $V_G$ and connecting a resistance in the source.	[04] [06]	CO1	L2
3. Calculate Thevenin equivalent voltage and resistance and hence draw the equivalent circuit. Find $I_C, I_B, I_E, V_B, V_C$ . Assume $\beta=100, V_{BE}=0.7V$	[10]	CO1	L3
			
4. With the small signal equivalent model of MOSFET, derive an expression for the voltage gain and transconductance, $g_m$ of MOSFET.	[10]	CO2	L2
5. Considering the conceptual circuit of Common Emitter BJT Amplifier, derive the following parameters; $g_m, r_e, r_{\pi}$ and $A_v$ . Draw the hybrid $\pi$ model.	[10]	CO2	L2
6. Design a MOS Amplifier (by fixing gate voltage), for the circuit below, given the specifications: $I_D = 0.5mA, V_t = 1V, K_n' W/L = 1mA/V^2, V_{DD} = 15V$ . Calculate the percentage change in the value of $I_D$ obtained when the MOSFET is replaced with another unit having $V_t = 1.5V$ . Consider $\lambda = 0$ .	[10]	CO2	L3
			

7.	Define the following characteristic parameters of Amplifiers using necessary circuit diagram. $A_v$ , $A_{vo}$ , $G_v$ , $G_{vo}$ , $G_m$ , $R_i$ , $R_{in}$ and $R_{out}$	[10]	CO2	L2
8.	With a neat circuit diagram and ac equivalent circuit, derive the expressions for Voltage gains $A_v$ , $A_{vo}$ , $G_v$ , and Output resistance $R_{out}$ for a Common source amplifier without source resistance.	[10]	CO2	L3

**IAT-1 (19/05/2021)**

**Analog Circuits Scheme**

**4<sup>th</sup> Sem**

Q-1 Diagram Voltage divider- 2 Marks

Explanation-6 Marks

Explanation of RE stabilization-2 marks

Q-2(a) Explanation-4 Marks

Q-2(b) Circuit Diagram-2 Marks

Explanation- 4 Marks

Q-3 Rth-1 marks

Vth-1 marks

Equivalent circuit -3 Mark

Ic, Ib, IE, VB, VC----- 5 marks (Each carries 1 mark)

Q-4 Small signal model-2 marks

Voltage gain-4 Marks

Transconductance-4 marks

Q-5 Circuit diagram-1 Marks

Gm, re, rpi, Av---8 Marks

Hybrid pi model-1 marks

Q-6 RD, RS, RG1, RG2---8 Marks

% change in ID= 2 marks

Q-7 Diagram -2 marks


Each parameter- 1 mark each (8x1= 8 marks)

Q-8 Circuit-2 marks


Each parameter - 2 mark each (4x2=8 marks)



→

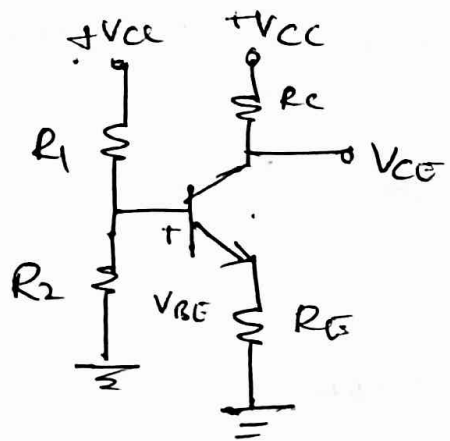

(a)

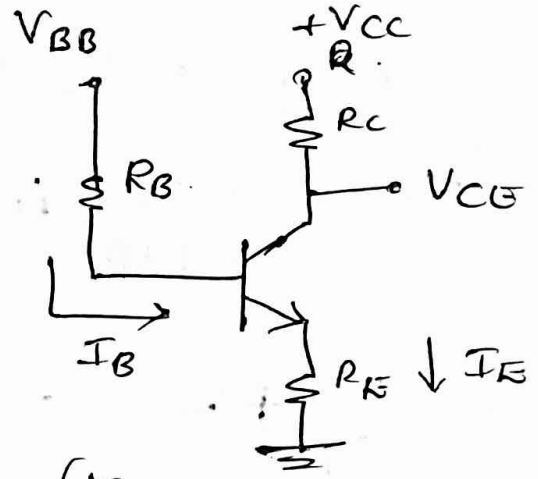

(b)

Fig (a) shows arrangement used for classical transistor amplifier biasing.

→ A fraction of  $V_{ce}$  is applied at base by using voltage divider at  $R_1$  &  $R_2$

→

$$\frac{1+\beta}{1+\beta}$$

Putting  $I_B$  from eqn 4 into ③ we have

$$V_{BB} = \frac{I_E}{(1+\beta)} R_B + V_{BE} + I_E R_E$$

$$I_E \left( \frac{R_B}{1+\beta} + R_E \right) = V_{BB} - V_{BE}$$

$$\Rightarrow \boxed{I_E = \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{1+\beta}}}$$

→ ⑤



NOTE: In order to make  $I_E$  insensitive

→ If  $F_{IS}$  is small, base voltage is determined by voltage divider  $R_1$  &  $R_2$  & it remains constant.

→ So  $\uparrow$  in  $V_{BE}$  result in decrease in  $V_{CE}$ .

→ This in turn reduce collector and emitter current.
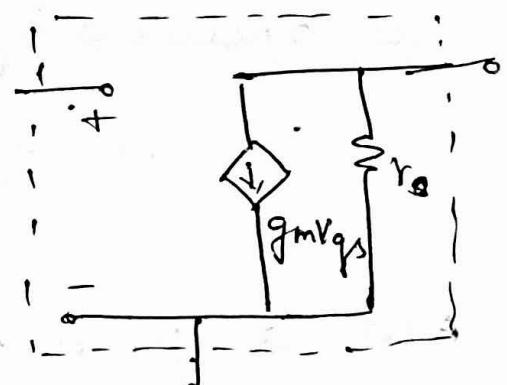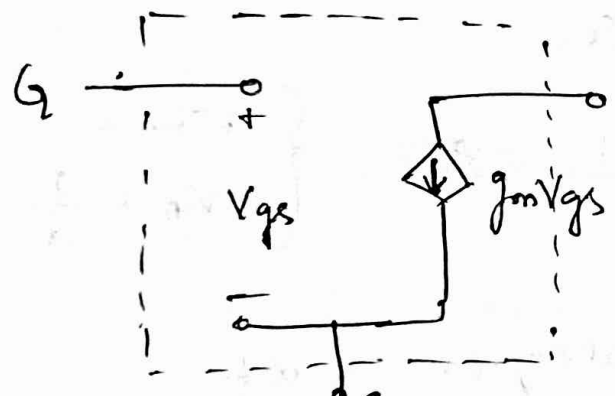
#### 4) Small signal equivalent of MOSFET



- (i) Replace MOSFET by equivalent circuit as shown
- (ii) Ideal const, dc vty sources are replaced by short circuit.
- (iii) Constant dc current if present are replaced by an open circuit.



⇒ Fig (a) circuit has prob, that drain current in sat, is independent of drain vty.

→ But drain current is depends on  $V_{os}$  which is modeled by  $r_o$ .


$$r_o = \frac{|V_A|}{I_D} \rightarrow 1 \quad \left\{ \begin{array}{l} \text{where} \\ V_A = \frac{1}{\lambda} \end{array} \right.$$

For a given technology.



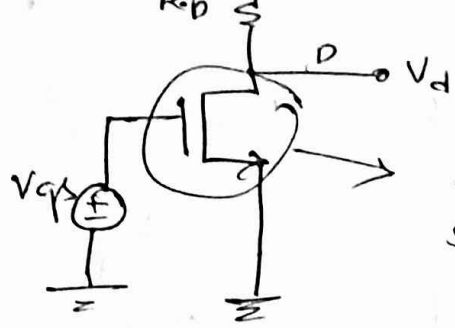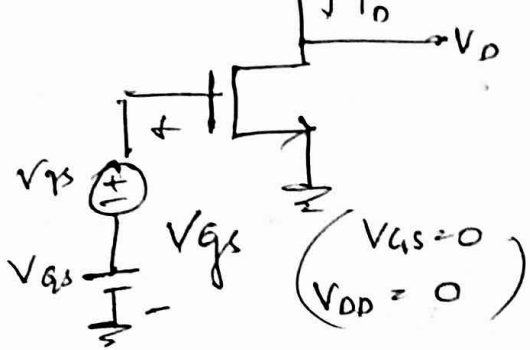

Replace by  
Small signal  
model.

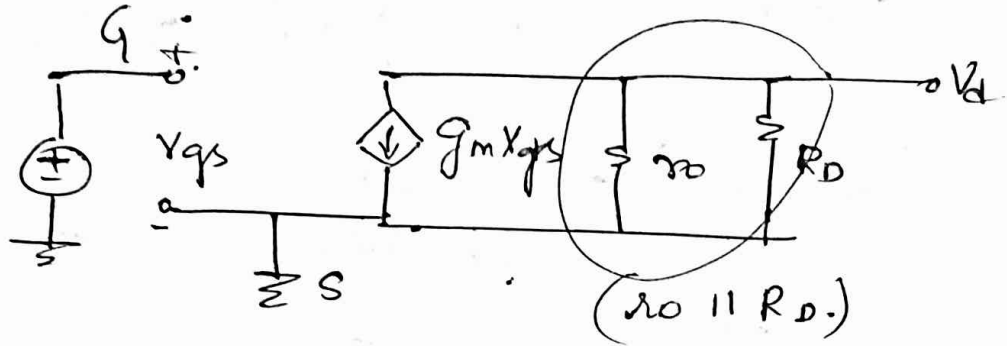

Resultant circuit

Voltage gain ( $A_v$ ) =  $\frac{V_d}{V_{qs}}$

$$g_m \propto kn' \quad , \quad g_m \propto \frac{W}{L} \quad , \quad g_m \propto V_{ov} \quad \& \quad (V_{GS} - V_T)$$

→  $g_m$  increased by large  $W$  & small  $L$

→  $g_m$  ↑ sed by increasing  $V_{GS}$


$$\text{We have, } I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_T)^2$$

$$\Rightarrow (V_{GS} - V_T)^2 = \frac{2I_D L}{k_n' W}$$

$$\Rightarrow \boxed{V_{GS} - V_T = \sqrt{\frac{2I_D L}{k_n' W}}}$$

But subr values,

$g_m$  ...

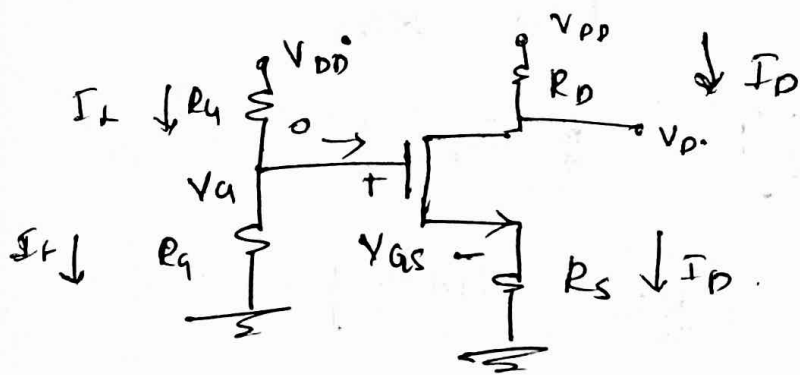

$$\left[ \begin{aligned} I_D R_D &= \frac{V_{DD}}{3} = \frac{15}{3} = 5V \\ \text{So } V_D &= 15 - 5 = 10V \end{aligned} \right.$$

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{15 - 10}{0.5 \times 10^{-3}} = \underline{\underline{10 \text{ k}\Omega}}$$

By thumb rule

$$R_S = \frac{V_S}{I_D} = \frac{5}{0.5 \times 10^{-3}} = \underline{\underline{10 \text{ k}\Omega}}$$

$$\left[ V_S = \frac{V_{DD}}{3} = 5V \right]$$

$$I_D = \frac{1}{2} K_n \frac{W}{L} (V_{GS} - V_T)^2$$

$$\boxed{8R_{G2} = 7R_{G1}} \quad | \quad \boxed{R_{G1} = \frac{8}{7} R_{G2}}$$

Let  $\boxed{R_{G2} = 7M\Omega}$   $\quad$   $\boxed{R_{G1} = 8M\Omega}$


$\therefore$  change in  $I_D = ?$   $V_t = 1.5$  e  $4mA/V_2$

$$I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2$$

$$I_D = \frac{1}{2} \times 10^{-3} \times (V_{GS} - 1.5)^2$$


$$2I_D = (7 - 10I_D - 1.5)^2 = (5.5 - 10I_D)^2$$
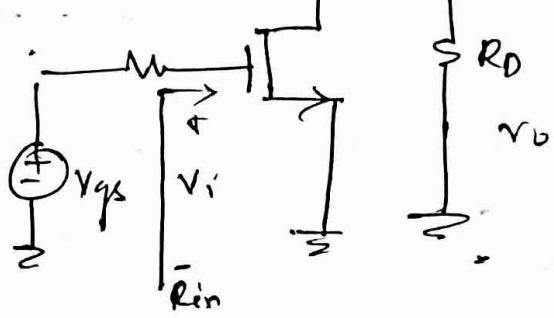
$$2I_D = \left( \frac{11 - 20I_D}{2} \right)^2$$



$R_o$ .

as Fig (a).  
CS fed. with  $V_{gs}$

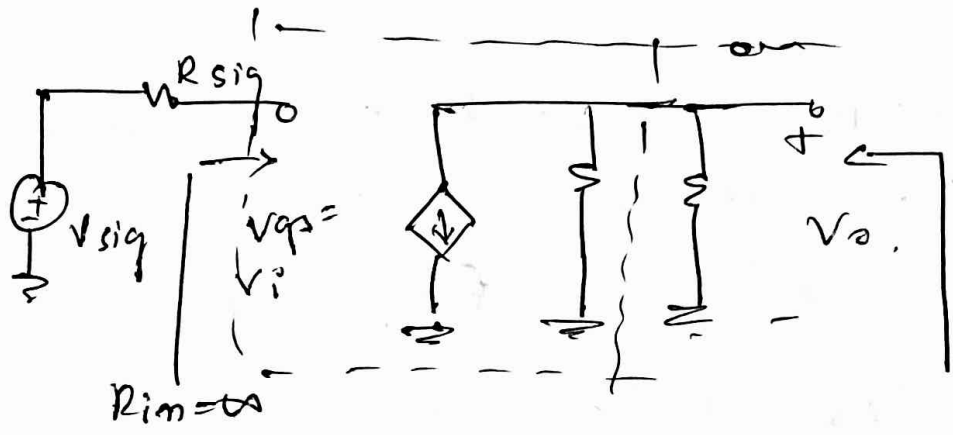

$$R_D \parallel r_o = R_D$$

Fig (b): CS amplifier with MOSFET replaced by hybrid  $\pi$  model

$$\boxed{A_{v_o} = \frac{v_o}{v_i} = -g_m (R_D \parallel r_o)} \rightarrow (3)$$

→  $R_D$  is usually much lower than  $r_o$  & effect of reducing  $|A_{v_o}|$  is slight. Thus

$$\rightarrow \boxed{A_{v_o} \approx -g_m R_D} \rightarrow (4)$$

$R_o$  :- o/p resistance  $R_o$  seen back into o/p terminals with  $v_i = 0$ .

$v_{gs} = 0$  & thus  $g_m \& v_{gs} = 0$

Thus,  $\boxed{R_o = R_D \parallel r_o} \rightarrow 5$

$$\boxed{R_o = R_D} \rightarrow (6)$$

( $R_D$  smaller than  $r_o$ )

→ If a load resistance  $R_L$  is connected to the o/p terminal of amplifier, so  $R_L$  will be placed.

$$A_v = -g_m (R_D \parallel R_L \parallel r_o) \rightarrow \textcircled{2}$$

→ As  $v_i = v_{sig}$ , Overall voltage gain

$$G_v = \frac{V_o}{V_{sig}} = \frac{V_o}{v_i} = -g_m (R_D \parallel R_L \parallel r_o)$$

$$G_v = -g_m (R_D \parallel R_L \parallel r_o) \rightarrow \textcircled{3}$$

$R_1 + R_2$

$$V_B = V_{CC} \times \frac{R_{B2}}{R_{B1} + R_{B2}} = 15 \times \frac{50 \times 10^3}{(100 + 50) \times 10^3}$$

$$\boxed{V_B = 5V}$$

$$\text{WKT, } R_B = R_{B1} \parallel R_{B2} \Rightarrow \frac{100 \times 50 \times 10^3}{(100 + 50) \times 10^3} = \underline{\underline{33.33 \text{ k}\Omega}}$$

$$\text{By KVL, } I_E = \frac{V_{BB} - V_{BE}}{R_E + \left(\frac{R_B}{\beta + 1}\right)}$$

Subst<sup>n</sup>

$$I_E = \frac{.5 - 0.7}{\quad}$$



$$V_{CC} = I_C R_C + V_{CE} + I_E R_E$$

$$V_{CC} = I_{CC} R_C + V_C$$

$$\begin{aligned} V_C &= V_{CC} - I_C R_C \\ &= 15 - 1.29 \times 5 \end{aligned}$$

$$V_C = \underline{\underline{8.55V}}$$

$$\boxed{V_{BB} = V_B = 5V}$$

$$I_B = \frac{I_C}{\beta + 1}$$

$$I_B = \frac{1.29 \times 10^{-3}}{100 + 1} = \underline{\underline{0.012 \text{ mA}}}$$