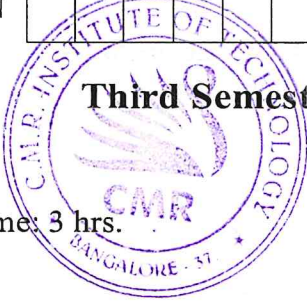


USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

10CS32



Third Semester B.E. Degree Examination, July/August 2021
Electronic Circuits

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions.

- 1
 - a. Which is the suitable position of operating point for the faithful amplification? Justify your answer. (04 Marks)
 - b. Derive the operating point equation for emitter bias configuration. (08 Marks)
 - c. Sketch the gate triggering and V-I characteristics of silicon controlled rectifier (SCR). (04 Marks)
 - d. Define the thermal runaway process of transistor with typical power derating curve of silicon transistor. (04 Marks)

- 2
 - a. List out the difference between JFET and MOSFET. (04 Marks)
 - b. With neat sketches, explain the working of N-channel D-MOSFET. (06 Marks)
 - c. Fig. Q2 (c) shows a circuit using E-MOSFET. Given that threshold voltage for MOSFET is 2V and $I_{D(ON)} = 6 \text{ mA}$ for $V_{GS(ON)} = 5 \text{ V}$. Determine the values of operating point. (10 Marks)

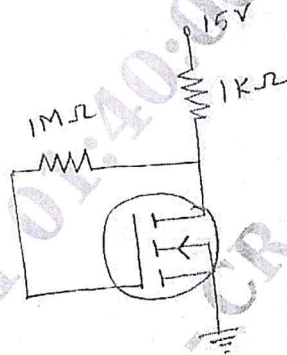


Fig. Q2 (c)

- 3
 - a. Explain the construction and working of photo transistor. Also mention its applications. (06 Marks)
 - b. Explain the working of Cathode Ray Tube (CRT) with a neat diagram. What are the advantages and disadvantages of CRT? (07 Marks)
 - c. A photodiode has a noise current of 1fA, responsivity figure of 0.5 A/W, active area of 1 mm^2 and rise time of 3.5 ns. Determine its
 - (i) Noise equivalent power (NEP)
 - (ii) Detectivity
 - (iii) D^* (DEE-STAR)
 - (iv) Quantum efficiency at 850 nm. (07 Marks)

- 4
 - a. Derive the expression for current gain (A_i), input impedance (Z_i), voltage gain (A_v) and output admittance (Y_o) for a transistor amplifier using h-parameter model. (12 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

- b. Fig. Q4 (b) shows a darlington amplifier. The two transistors Q_1 and Q_2 are identical and the h-parameters for the transistors are $h_{ie} = 1 \text{ K}\Omega$, $h_{fe} = 100$ and $h_{oe} = 40 \times 10^{-6} \text{ mho's}$. The values of voltages $V_{CC} = 15 \text{ V}$, $V_{BE1} = 0.7 \text{ V}$ and $V_{BE2} = 0.7 \text{ V}$. Determine the following :
- (i) Input impedance (ii) Output impedance (iii) Voltage gain
 (iv) Current gain. (08 Marks)

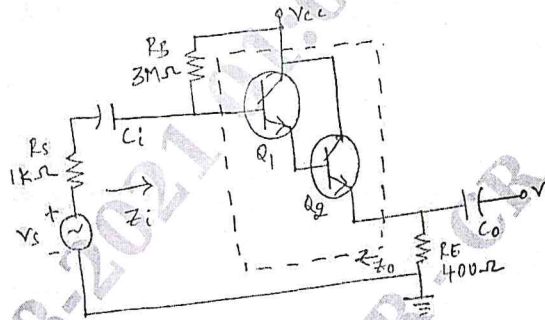


Fig. Q4 (b)

- 5 a. What are the advantages of negative feedback? (05 Marks)
 b. Derive the expression for voltage gain input resistance and output resistance in a voltage serial feedback topology. (10 Marks)
 c. Refer to the Fig. Q5 (c) of op-amp based inverting amplifier circuit. Identify the type of negative feedback. Determine the transimpedance gain, input impedance and output impedance parameters of op-amp are $100 \text{ M}\Omega$, $10 \text{ M}\Omega$ and 100Ω respectively. (05 Marks)

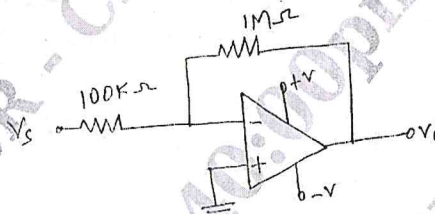


Fig. Q5 (c)

- 6 a. What are sinusoidal oscillators? Explain the barkhausen criterion for sustained oscillations. (07 Marks)
 b. Explain the operation of 555 timer as an Astable multivibrator. (05 Marks)
 c. Explain the working of RC low pass and RC high pass circuits. (08 Marks)
- 7 a. Define the terms load regulation, line regulation and output resistance for a voltage regulator. (06 Marks)
 b. Design a power transformer with a multiple output secondary and the following input and output specifications:
 (i) Primary voltage : 220 V , 50 Hz
 (ii) Secondary voltage : (a) $120 - 0 - 12 \text{ V}$ at 100 mA and (b) 5 V at 1 A .
 Assume $B = 60,000$ lines per square inch for the chosen core material and an efficiency of 90% . (07 Marks)
 c. With a neat circuit, explain the operation of buck or step down regulator. (07 Marks)
- 8 a. Explain the working of an op-amp window comparator. (07 Marks)
 b. Explain the working of the following :
 (i) Current to voltage converters. (06 Marks)
 (ii) Voltage to current converters. (07 Marks)
 c. Explain the working of relaxation oscillator circuit using op-amp. (07 Marks)