

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--

15EC73

## Seventh Semester B.E. Degree Examination, July/August 2021 Power Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any **FIVE** full questions.

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and / or equations written eg,  $42+8 = 50$ , will be treated as malpractice.

1. a. What is Power Electronics? With the help of block diagram explain it. Explain any four applications of power electronics. (06 Marks)  
b. With the transient model of MOSFET explain switching its characteristics. (06 Marks)  
c. Compare between Bipolar Junction Transistor (BJT) and MOSFET. (04 Marks)
  
2. a. What are the peripheral effects of power electronic converter system? (04 Marks)  
b. Explain briefly any two types of power electronic converters. (04 Marks)  
c. Explain  $\frac{di}{df}$  and  $\frac{dv}{dt}$  protection for transistor. (08 Marks)
  
3. a. The SCR shown in Fig.Q3(a) has latching current of 40mA and is triggered by the pulse width of 50  $\mu$ sec. Determine whether the SCR turn ON or not.
  
4. a. Explain class B LC communication with necessary circuit diagram, waveforms and equations. (08 Marks)  
b. A UJT is used to trigger the thyristor whose minimum gate triggering voltage is 6.2V. The UJT ratings are :  $\eta = 0.66$ ,  $I_p = 0.5\text{mA}$ ,  $I_v = 3\text{mA}$ ,  $R_{B_1} + R_{B_2} = 5\text{k}\Omega$ , leakage current = 3.2mA,  $V_p = 14\text{V}$  and  $V_v = 1\text{V}$ . Oscillator frequency is 2KHz and capacitor  $C = 0.04 \mu\text{F}$ . Design the complete circuits. (08 Marks)
  
5. a. Explain the working of single phase half wave controlled rectifier connected to resistive load. Derive expression for the average DC output voltage and rms value of output voltage. (08 Marks)  
b. With the neat circuit diagram and relevant waveforms explain the working of ON-OFF control for single phase AC voltage. Derive expression for rms output voltage. (08 Marks)

- 6 a. Explain the working of single phase dual converter with neat circuit diagram. Draw relevant waveforms. (08 Marks)
- b. For the single phase bidirectional AC voltage controller, delay angles of thyristors  $T_1$  and  $T_2$  are equal to  $\alpha_1 = \alpha_2 = \frac{2\pi}{3}$ . The input is  $V_s = 120\sqrt{2} \sin 314f$ , 50Hz. Calculate :
- rms output voltage
  - input power factor
  - average current through thyristors  $I_A$  and
  - rms current of thyristors. (Fig. Q6(b)).

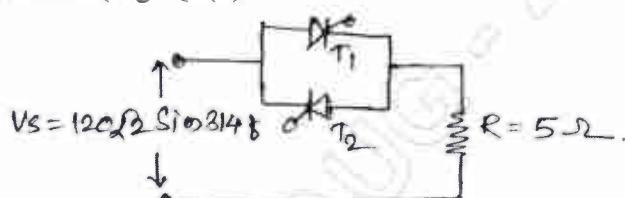


Fig.Q6(b)

(08 Marks)

- 7 a. Explain the working of stepdown chopper for resistive load with circuit diagram and waveform. Drive the expressions for average output voltage  $V_{0(av)}$ , rms output voltage  $V_{0(rms)}$  and output power. (08 Marks)
- b. With the help of circuit diagram and waveforms explain the working of boost regulator. Derive the expression for peak to peak ripple output current and peak to peak ripple output voltage. (08 Marks)
- 8 a. Briefly explain the classification of choppers with circuit diagram, waveforms and quadrant diagram. (08 Marks)
- b. Input to the step-up chopper is 200V. The output required is 600V. If the conduction time of thyristor is 200μsec. Compute :
- Chopping frequency
  - If pulse width is halved for constant frequency find the new output voltage. (08 Marks)
- 9 a. Explain the operation of single phase full bridge invertors supplying resistive load. Derive an expression for output RMS voltage. (08 Marks)
- b. Explain voltage control in inverter by single pulse width modulation and sinusoidal pulse width modulation. (08 Marks)

**OR**

- 10 a. With neat circuit diagram and waveforms explain transistorized current source inverter. (08 Marks)
- b. Write short note on solid state relays, and microelectronic relays. (08 Marks)

\* \* \* \* \*





Signature of Scrutinizer

Scheme & Solution

Subject Title: Power Electronics

Subject Code: 15EC73

Question Number	Solution	Marks Allocated
Q. 1 a.	<p>Definition of power electronics.</p> <p>Block diagram of power electronics and explanation</p> <p>Four applications of power electronics</p>	1
b.	<p>Transient or switching model &amp; explanation.</p> <p></p> <p>switching characteristics</p> <p></p> <p>Explanation of <math>t_{d(on)}</math>, <math>t_r</math>, <math>t_{d(off)}</math> &amp; <math>t_f</math>.</p> $t_{d(on)} = t_{d(on)} + t_r$ $t_{d(off)} = t_{d(off)} + t_f$	3 2 2.
c.	<p>Compare BJT &amp; MOSFET -</p> <p>(At least 6 different points)</p>	4
Q. 2. a.	<p>Peripheral effects -</p> <p>Explanation channel contention -</p> <p>Because of high switching - voltage &amp; current pulses, spikes produced, harmonics induced in power supply, RFI &amp; EMI increased -</p> <p>Block dia with with O/p &amp; C/p filter to reduce the above effect.</p>	3 2.

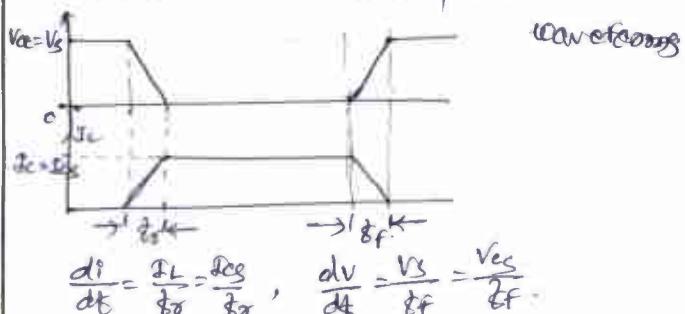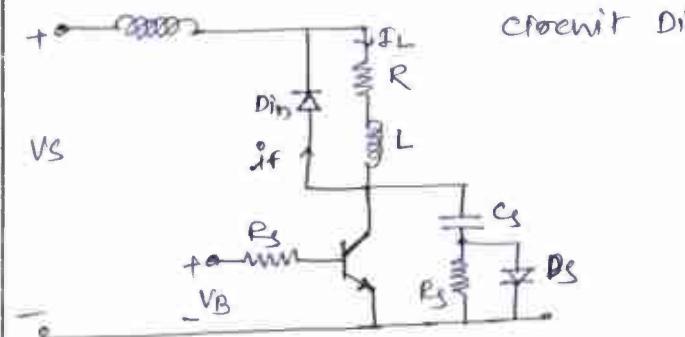Question Number	Solution	Marks Allocated
Q.2.b.	Explanation of any two types of power converter with relevant circuit diagrams and waveforms. ( 2 marks for one converter type)	4
Q.2.c.	<p><math>\frac{di}{dt}</math> and <math>\frac{dv}{dt}</math> protection.</p>  $\frac{di}{dt} = \frac{I_L}{t_0} = \frac{V_S}{R}, \quad \frac{dv}{dt} = \frac{V_S}{t_F} = \frac{V_S}{L}$ <p>Circuit Diagram</p> 	2
Q.3.a.	<p>Explanation with equations for:</p> $L_S = \frac{V_S t_0}{I_L}$ $C_S = \frac{I_L t_F}{V_S}$ $R_S = 2 \sqrt{L_S C_S} \quad \text{&} \quad R_g = \frac{1}{3 f_S C_S}$ $i(t) = \frac{V_S}{R} (1 - e^{-\frac{t}{R_L}})$ <p>for pulse width 50ms <math>i(t) = 10 \text{ mA}</math></p> <p>SCR current is less than latching current of hence SCR will not trigger.</p>	4 1 2 1

Question Number	Solution	Marks Allocated
Q.3.b.	<p>Two transistor model.</p> $I_K = I_a + I_B$ $I_B1 = I_B2 \quad \text{if} \quad I_C1 = I_C2$	2.
C.	<p>Proof for. <math>I_a = \frac{I_g + I_{C01} + I_{C02}}{1 - (\alpha_1 + \alpha_2)} \approx \frac{I_g}{1 - (\alpha_1 + \alpha_2)}</math></p> <p>Full wave RC - Averaging circuit</p> <p>Circuit Diagram:</p> <p>vs</p> <p><math>V_o</math></p> <p><math>R_L</math></p> <p><math>D_1, D_2, D_3, D_4</math></p> <p><math>R</math></p> <p><math>C</math></p> <p>AC Supply vs.</p> <p>2</p> <p>vs</p> <p>Rectified voltage</p> <p><math>V_o</math></p> <p><math>V_C</math></p> <p><math>U_{gm10}</math></p> <p>2</p> <p>Explanation with eqn <math>Re &gt; \frac{0.157}{2\pi f}</math></p> <p>4 ✓</p>	4.

Question Number	Solution	Marks Allocated
Q.4.a.	<p>Class B L C commutation.</p> <p>Circuit Diagram &amp; Waveforms.</p> <p>Explanations with equations for:</p> $I(t) = \frac{Edc}{\sqrt{L/C}} \sin(\omega_0 t)$ $\omega_0 = 1/\sqrt{LC}$ $I_{peak} = \frac{Edc}{\sqrt{L/C}} = 2I_L$ $t_{off} = \frac{\pi}{2} \sqrt{LC}$	4.
Q.4.b.	$R_C = 11.6 \text{ k}\Omega \quad (\tau = R_C C \ln(\frac{1}{1-\eta}))$ $V_{BB} = 20V \quad (V_P = \eta V_{BB} + V_D)$ $R_2 = 265\Omega \quad (R_2 = \frac{\eta (R_{B2} + R_{B1})}{V_{BB}})$ $R_1 = 985\Omega \quad (V_{BB} = I_{leakage}(R_1 + R_2 + R_{B1} + R_{B2}))$ $R_{Cmax} = 12 \text{ k}\Omega \quad (R_{Cmax} = \frac{V_{BB} - V_P}{I_P})$ $R_{Cmin} = 6.33 \text{ k}\Omega \quad (R_{Cmin} = \frac{V_{BB} - V_D}{I_V})$ <p>Circuit Dia</p>	1 1 1 1 1 1 2.

Question Number	Solution	Marks Allocated
Q.5 a. Single phase half wave controlled rectifier.	<p><math>V_s = V_m \sin(\omega t)</math></p>	3
Circuit Diagrams.	<p>Waveforms</p>	5
Expressions proof for.	$V_d(\text{av}) = \frac{V_m}{2\pi} (1 + \cos \alpha)$	1
	$V_{d(\text{rms})} = \frac{V_m}{2} \left[ \frac{\pi - \alpha + \sin \alpha \cos \alpha}{2} \right]^{1/2}$	2.
b. Single phase on-off AC voltage controller.	<p>Circuit Dia-</p>	5.
		1
Waveforms for AC sp., trigger pulses, output voltage & output current for n cycles ON & m cycles off		2.
Proof for	$V_{d(\text{rms})} = \frac{V_m}{\sqrt{2}} \sqrt{K} \quad K = \frac{n}{n+m}$	5.
	$V_{d(\text{rms})} = V_{s(\text{rms})} \sqrt{K}$	1
Q.6. a. Single phase dual converter.		2
Circuit Diagrams.	<p>4 Quadrant</p>	1

Question Number	Solution	Marks Allocated
Q.6 a.	<p>Waveforms:</p> <p>Explanations with equations</p> $V_{01} = \frac{2V_m}{\pi} \cos \alpha_1, \quad V_{02} = \frac{2V_m}{\pi} \cos \alpha_2$ $\alpha_2 = \pi - \alpha_1$ $i_s = \frac{2V_m}{\omega L_s} (\cos \alpha_1 - \cos \alpha_2)$	2
Q.6. b.	$V_{0rms} = V_m \sqrt{\frac{\pi - \lambda + \frac{\sin 2\lambda}{2}}{2\pi}} = 53V$ $I_{0rms} = \frac{V_{0rms}}{R} = 10.6A$ $\text{Active power} = I_{0rms}^2 R = 561.8W$ $\text{Total rms input power} = V_{0rms} \cdot I_{0rms} = 1272VA$ <p>Power factor = <math>\frac{\text{Active power}}{\text{Total rms S/P power}} = 0.4416</math></p> <p>OR = 44.16% lagging</p> $I_T(\text{av}) = \frac{V_m}{2\pi R} (1 + \cos \lambda) = 2.7A$ $I_T(\text{rms}) = \frac{I_{0rms}}{\sqrt{2}} = 7.49A$	3

Subject Title:

Subject Code:

Question Number	Solution	Marks Allocated
Q.7. a.	<p>Step down chopper for resistive load.</p> <p>Circuit Diagrams and waveforms.</p> $V_o(\text{avg}) = k \cdot V_s$ $k = \text{duty cycle}$ <p>RMS output voltage <math>V_{o(\text{rms})} = \sqrt{k} V_s</math></p> <p>Output power <math>P_o = \frac{k V_s^2}{R}</math></p>	2 2 2 2
b.	<p>Boost Regulator</p> <p>Circuit Diagram</p> <p>Waveforms</p> <p>Explanation with expressions.</p> $V_o(\text{avg}) = \frac{V_s}{1-k}$ $I_o(\text{ripple}) = \frac{V_s k}{fL}$ $V_o(\text{ripple}) = \frac{I_o(\text{avg}) k}{fC}$	2 2 4
Q.8. a.	<p>Chopper classification:</p> <p>First quadrant, second quadrant, first and second quadrant, third and fourth quadrant, &amp; four quadrant converters.</p> <p>Explanation with</p> <p>Quadrant diagrams waveforms &amp; explanations.</p> <ul style="list-style-type: none"> <li>- II -      1st, 2nd quadrant</li> <li>- + -      1st &amp; 2nd quadrant</li> <li>- II -      3rd &amp; 4th quadrant</li> <li>- + -      Four quadrant</li> </ul>	2 2 2 2

## Subject Title:

## Subject Code:

Question Number	Solution	Marks Allocated
Q-8.b.	$V_o(\text{av}) = \frac{V_s}{1-K}$ , $K = 0.6667$ , $f = \frac{K}{T_{on}} = 3.3 \text{ kHz}$ , $K = \frac{T_{on}}{T} = 0.333$ , $V_o(\text{av}) = 300 \text{ V}$ .	2 2 2 2 2
Q-9.a.	single phase full bridge inverter Circuit diagram. Waveforms. Explanations Expression for $V_{o(\text{rms})} = V_s$	2 2 2 2 2
b.	Voltage control in inverter. i) single pulse width modulation. Waveforms & explanations Expression for $V_{o(\text{rms})} = V_s \sqrt{P_f}$ ii) Sineoidal pulse width modulation. Waveforms & explanations Explanations with <del>no</del> equations - $m_f = \frac{V_o}{V_c}$ , Number of pulses = $\frac{m_f}{2}$ , $V_{o(\text{rms})} = V_s \sqrt{\sum_{n=1}^{m_f} \frac{P_n}{\pi}}$	2 2 2 2 2 2
Q-10.a.	Transistorized current source inverter. Circuit diagram Waveforms. Explanations.	2 3 3
b.	Brief explanation of merits dia. of solid state relays Brief explanation with circuit diagram of microelectromechanical relays.	4 4