



CMR Institute of Technology, Bangalore
DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING
II - INTERNAL ASSESSMENT

Semester: 6-CBCS 2018
 Subject: POWER SYSTEM ANALYSIS - I (18EE62)
 Faculty: Ms Keka Mukhopadhyaya

Date: 22 Jun 2021
 Time: 09:00 AM - 10:30 AM
 Max Marks: 50



Instructions to Students :

Answer Any FIVE FULL Questions.
 Assume Data wherever necessary.


Answer any 5 question(s)

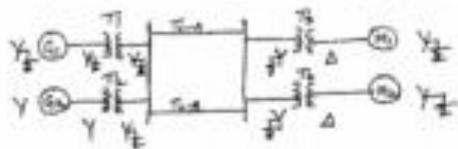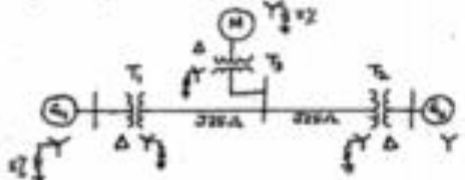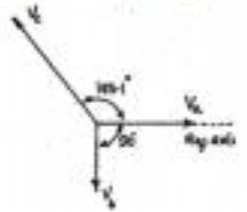
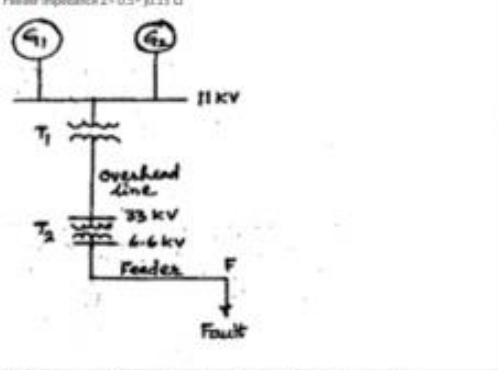
Q.No	Marks	CO	PO	BT/CL
1 a	5	CO3	PO1,PO2,PO3,PO4,PO6,PO7,PO12	L1
b	5	CO3	PO1,PO2,PO3,PO4,PO6,PO7,PO12	L2
2	10	CO3	PO1,PO2,PO3,PO4,PO6,PO7,PO12	L3
3 a	5	CO3	PO1,PO2,PO3,PO4,PO6,PO7,PO12	L2
b	5	CO3	PO1,PO2,PO3,PO4,PO6,PO7,PO12	L3
4	10	CO3	PO1,PO2,PO3,PO4,PO6,PO7,PO12	L4
5 a	5	CO3	PO1,PO2,PO3,PO4,PO6,PO7,PO12	L3

For the power system shown in the figure, draw the positive, negative and zero sequence networks. The ratings of power system components are as follows:
 Generator G1: 25MVA, 11kV, $X_1 = 0.2 \text{ pu}$, $X_2 = 0.15 \text{ pu}$, $X_0 = 0.03 \text{ pu}$
 Generator G2: 15MVA, 11kV, $X_1 = 0.2 \text{ pu}$, $X_2 = 0.15 \text{ pu}$, $X_0 = 0.03 \text{ pu}$
 Motor M: 25 MVA, 11kV, $X_1 = X_2 = 0.2 \text{ pu}$, $X_0 = 0.1 \text{ pu}$
 Transformer T1: 25 MVA, 11Δ/120 Y kV, X=10%
 Transformer T2: 12.5 MVA, 11Δ/120 Y kV, X=30%
 Transformer T3: 50 MVA, 120 Y/11Δ kV, X=10%
 X_n for T1, T2, T3 is 5% of the respective transformer ratings.
 Choose a base of 50 MVA, 11kV in Generator G1 circuit.




The original set of voltage phasors $V_a = 4 \angle 0^\circ$ degree, $V_b = 3 \angle -90^\circ$ degree, $V_c = 5 \angle 143.1^\circ$ degree as shown in figure. Find all the components for the positive, negative and zero sequence systems. Draw the corresponding phasor.



<p>b</p>	<p>Draw the zero sequence network for following configuration of three phase transformers.</p> 	<p>5</p>	<p>CO3 PO1,PO2,PO3,PO4,PO6,PO7,PO12</p>	<p>L1</p>
<p>6</p>	<p>For the radial network shown in the figure, a three phase fault occurs at point F. Determine the fault current. Choose the generator ratings as the base values.</p> <p>Generator G1: 10 MVA, 11kV, $X''=20\%$ Generator G2: 10 MVA, 11kV, $X''=12.5\%$ Transformer T1: 10 MVA, 11/33kV, $\alpha=10\%$ Transformer T2: 10 MVA, 11/33kV, $\alpha=8.7\%$ Over head line impedance $Z=6+j10 \Omega$ Feeder impedance $Z=0.5+j0.13 \Omega$</p> 	<p>10</p>	<p>CO2 PO1,PO2,PO6,PO7,PO12</p>	<p>L4</p>
<p>7</p>	<p>a Derive the expression for three phase power in terms of sequence components.</p>	<p>5</p>	<p>CO3 PO1,PO2,PO3,PO4,PO6,PO7,PO12</p>	<p>L2</p>
<p>b</p>	<p>Discuss briefly the major points need to consider to select a circuit breaker.</p>	<p>5</p>	<p>CO2 PO1,PO2,PO6,PO7,PO12</p>	<p>L1</p>

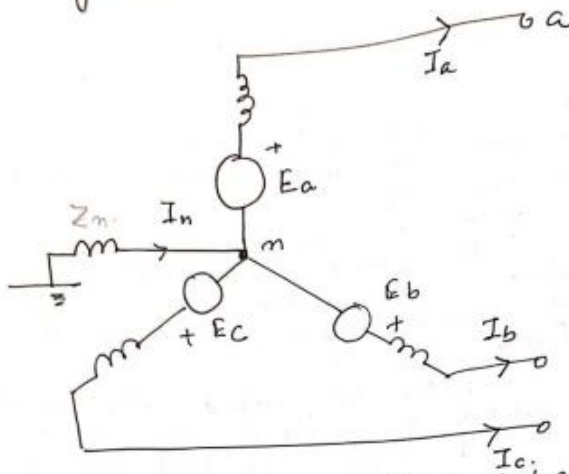Sequence Impedances And Networks Of Synchronous Machine.



Three-phase sym. gen with grounded neutral.

Fig shows an unloaded sym. machine (G/M), grounded through a reactor (impedance Z_n).

E_a , E_b and E_c are the induced emfs of the ϕ .

When a fault takes place at machine terminals, currents I_a , I_b and I_c flow in the lines.

Whenever the fault involves ground, current $I_n = I_a + I_b + I_c$ flows to neutral from ground via Z_n .

Unbalanced line currents can be resolved into their symmetrical components I_{a1} , I_{a2} and I_{a0} .

Because of winding symmetry currents of a particular seq. produce voltage drops of that seq. only.

Therefore, there is no coupling betn the eq. circuit of various sequences.

and.
Positive Sequence Impedance Network

Since synchronous machine is designed with symmetrical winding, it induces emfs of positive seq. only. i.e. no negative or zero sequence voltages are induced in it.

- \Rightarrow When machine carries positive sequence currents only \Rightarrow balance mode.
- \Rightarrow The armature reaction field caused by positive seq. currents rotates at syn speed in the same direction as the rotor (i.e. it is stationary w.r.t field excitation).
- \Rightarrow The machine equivalently offers a direct axis reactance (X_d) whose value reduces to X_d'' to X_d' and then finally X_d as short circuit transient progresses in time.

If armature resistance is assumed negligible, the +ve seq. impedance of the machine is


$$Z_1 = jX_d'' \text{ (if 1 cycle of transient is of interest)}$$

$$= jX_d' \text{ (if 2-4 cycle " " " ")}$$


$$= jX_d \text{ (if steady state value is of interest)}$$

If the machine short circuit takes place from unloaded conditions, the terminal voltage constitutes the +ve sequence voltage.

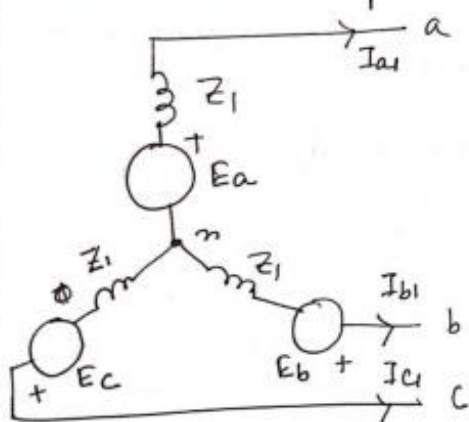If short circuit occurs from loaded conditions, the voltage behind appropriate reactance (subtransient, transient or synchronous) constitutes the positive sequence voltage.



3 ϕ Model.

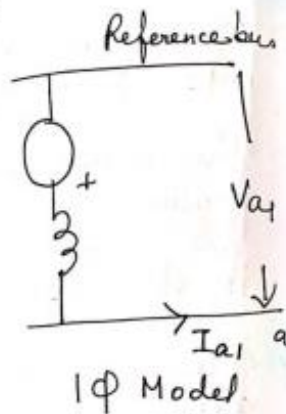

1 ϕ Model.

Positive Seq. Network of Syn Machine.

- * Z_n does not appear in the model as $I_n = 0$ for positive seq. currents.
- * Balanced network can be represented by 1 ϕ .
- * Ref bus for +ve seq. network is at neutral potential.
- * No current flows from ground to neutral so neutral at ground potential.

$$V_{a1} = E_{a1} - Z_1 I_{a1} \quad \text{--- 17}$$


Negative Sequence Impedance and Network

- * Sym M/c has zero -ve seq. induced voltages
- * With the flow of -ve seq. currents in the stator a rotating field is created which rotates in the opposite direction to that of the +ve seq. field at therefore at double sym. speed w.r.t rotor.
 Currents at double the stator frequency are induced in rotor field and damper winding.
- * In sweeping over the rotor surface, the -ve seq. mmf is alternately


presented with reluctance σ σ -
axis.

* The negative seq. impedance presented by the machine with consideration given to damper windings, is defined as

$$Z_2 = j \frac{X_q' + X_d'}{s} ; |Z_2| < |Z_1|$$

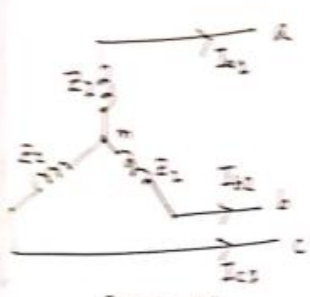

3 ϕ Model

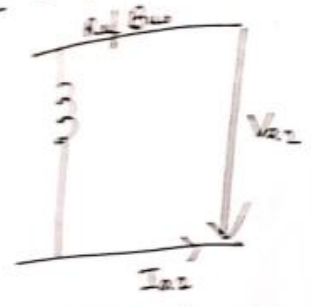

1 ϕ Model

Negative sequence network of a synchronous motor at Ref bus is at neutral potential, same as ground potential.

$$V_{n2} = -I_{a2} E_2$$


Zero Sequence Impedance and Network:

No zero seq. voltages are induced in a syn M/c.

The flow of zero seq. currents creates three mmfs which are in time phase but are distributed in space phase by 120° .

The resultant air gap field caused by zero seq. currents is zero.

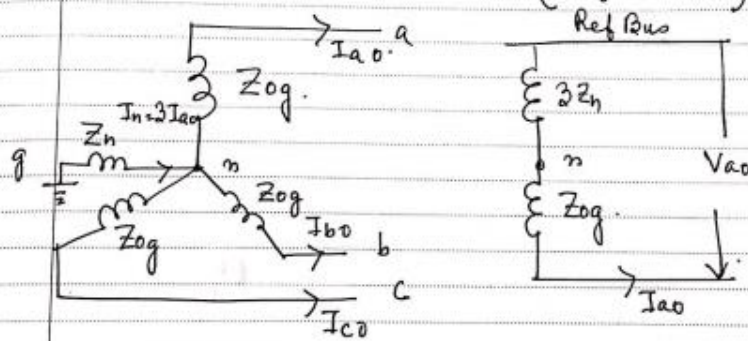Rotor windings present leakage reactance to the flow of zero seq. currents ($Z_{og} \ll Z_2 \ll Z_1$).



3 ϕ Model

1 ϕ Model

$$V_{a0} = -3Z_n I_{a0} - Z_{og} I_{a0}$$

$$= - (3Z_n + Z_{og}) I_{a0}$$


$Z_{og} \Rightarrow$ zero seq. imp | phase of the machine.

Since 1 ϕ zero seq. network carries only per phase zero seq. current.

Zero seq. impedance $Z_0 = 3Z_n + Z_{og}$
in order to have same ref voltage from a to ref bus.
Ref bus \rightarrow ground potential

$$V_{a0} = -Z_0 I_{a0}$$

1b

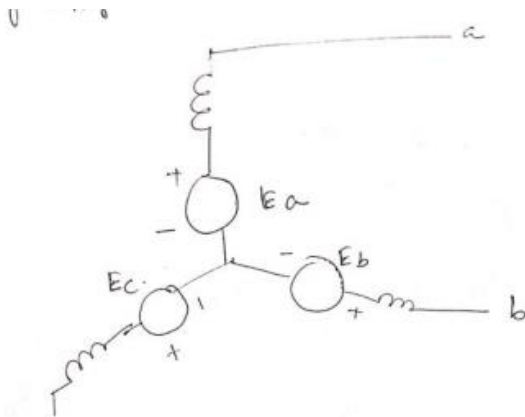

$E_a = V_p \angle 0^\circ$, $E_b = V_p \angle -120^\circ$, $E_c = V_p \angle +120^\circ$
 the seq. components of voltages are.

$$E_{a0} = \frac{1}{3} (E_a + E_b + E_c)$$

$$= \frac{1}{3} [V_p \angle 0^\circ + V_p \angle -120^\circ + V_p \angle 120^\circ]$$

$$= \frac{1}{3} [V_p - 0.5V_p - j0.866V_p - 0.5V_p + j0.866V_p]$$

$$= 0$$

$$E_{a1} = \frac{1}{3} [E_a + \alpha E_b + \alpha^2 E_c]$$

$$= V_p = E_a$$

$$E_{a2} = \frac{1}{3} [E_a + \alpha^2 E_b + \alpha E_c] = 0$$

2.

② Base power = 50 MVA

Base voltage in Generator $G_1 = 11 \text{ kV}$

Base voltage of j25 TL = Base vlg of $G_1 \times$ Transformation ratio

$$= 11 \times \frac{120}{11}$$

$$(KV)_{BTL} = 120 \text{ kV}$$

Base voltage of Motor = $(KV)_{BTL} \times TR$

$$= 120 \times \frac{11}{120}$$

$$(KV)_{BM} = 11 \text{ kV}$$

Base voltage of Generator $G_2 = (KV)_{BTL} \times TR$

$$= 120 \times \frac{11}{120}$$

$$(KV)_{BG_2} = 11 \text{ kV}$$

(i) Reactances of Generator 1:

Positive seq reactance $X_1(G_1) = X_1 \times \frac{(MVA)_{B, \text{new}}}{(MVA)_{B, \text{old}}} \times \frac{(KV)_{B, \text{old}}^2}{(KV)_{B, \text{new}}^2}$

$$= j0.2 \times \frac{50}{25} \times \frac{11^2}{11^2}$$

$$X_1(G_1) = \underline{j0.4}$$

Negative seq reactance $X_2(G_1) = X_2 \times \frac{(MVA)_{B, \text{new}}}{(MVA)_{B, \text{old}}} \times \frac{(KV)_{B, \text{old}}^2}{(KV)_{B, \text{new}}^2}$

$$= j0.15 \times \frac{50}{25} \times \frac{11^2}{11^2}$$

$$X_2(G_1) = \underline{j0.3}$$

Generator neutral reactance X_n

$$X_n(G_1) = j0.05 \times \frac{50}{25} \times \frac{11^2}{11^2}$$

$$X_n(G_1) = j0.1$$

$$3 X_n(G_1) = \underline{j0.3}$$

(ii) Reactance of Generator 2

$$X_1(G_2) = X_1 \times \frac{(MVA)_{B, \text{new}}}{(MVA)_{B, \text{old}}} \times \frac{(kV)_{B, \text{old}}^2}{(kV)_{B, \text{new}}^2}$$
$$= j0.2 \times \frac{50}{15} \times \frac{11^2}{11^2}$$

$$X_1(G_2) = \underline{j0.667}$$

$$X_2(G_2) = X_2 \times \frac{50}{15} \times \frac{11^2}{11^2}$$

$$= j0.15 \times \frac{50}{15}$$

$$X_2(G_2) = \underline{j0.5}$$

$$X_0(G_2) = X_0 \times \frac{50}{15} \times \frac{11^2}{11^2}$$

$$= j0.03 \times \frac{50}{15}$$

$$X_0(G_2) = \underline{j0.1}$$

(ii) Reactance of Transformer 1:

$$\begin{aligned}X_1(T_1) = X_2(T_1) = X_{OT}(T_1) &= X_1 \times \frac{(MVA)_{B, \text{new}}}{(MVA)_{B, \text{old}}} \times \frac{(KV)_{B, \text{old}}^2}{(KV)_{B, \text{new}}^2} \\&= j0.1 \times \frac{50}{25} \times \frac{11^2}{11^2} \\&= \underline{j0.2}\end{aligned}$$

Transformer neutral reactance

$$X_n(T_1) = j0.05 \times \frac{50}{25} \times \frac{11^2}{11^2}$$

$$X_n(T_1) = j0.1$$

$$3X_n(T_1) = \underline{j0.3}$$

(iv) Reactance of Transformer 2:

$$\begin{aligned} X_1(T_2) = X_2(T_2) = X_{0r}(T_2) &= j0.1 \times \frac{50}{12.5} \times \frac{11^2}{11^2} \\ &= \underline{j0.4} \end{aligned}$$

Transformer neutral reactance

$$X_n(T_2) = j0.05 \times \frac{50}{12.5} \times \frac{11^2}{11^2}$$

$$X_n(T_2) = j0.2$$

$$3X_n(T_2) = \underline{j0.6}$$

(v) Reactance of Transformer 3:

$$\begin{aligned} X_1(T_3) = X_2(T_3) = X_{0r}(T_3) &= j0.1 \times \frac{50}{10} \times \frac{11^2}{11^2} \\ &= \underline{j0.5} \end{aligned}$$

Transformer neutral reactance

$$X_n(T_3) = j0.05 \times \frac{50}{10} \times \frac{11^2}{11^2}$$

$$X_n(T_3) = j0.25$$

$$3X_n(T_3) = \underline{j0.75}$$

(vi) Reactance of Motor:

$$X_1(M) = X_2(M) = j 0.2 \times \frac{50}{25} \times \frac{11^2}{11^2}$$

$$X_1(M) = X_2(M) = \underline{j 0.4}$$

$$X_0(M) = j 0.1 \times \frac{50}{25} \times \frac{11^2}{11^2}$$

$$X_0(M) = \underline{j 0.2}$$

Motor neutral reactance

$$X_n(M) = j 0.05 \times \frac{50}{25} \times \frac{11^2}{11^2}$$

$$X_n(M) = j 0.1$$

$$3X_n(M) = \underline{j 0.3}$$

(v) Reactance of Transmission line


$$X_1(TL) = X_2(TL) = X(\Omega) \times \frac{(MVA)_R}{(kV)_R^2}$$
$$= j 25 \times \frac{50}{120^2}$$

$$X_1(TL) = X_2(TL) = \underline{j 0.086}$$


$$X_0(TL) = 3 X_1(TL) = 3 \times j 0.086$$

$$X_0(TL) = \underline{j 0.26}$$


Positive sequence network

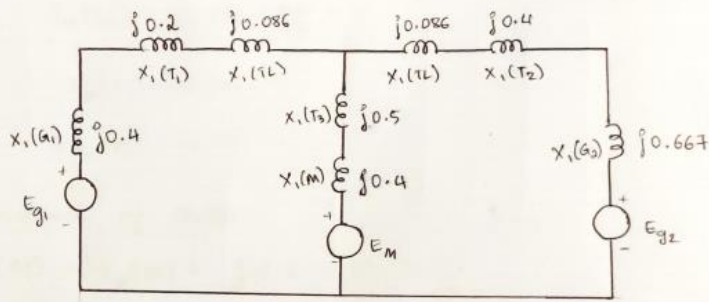


Negative sequence network

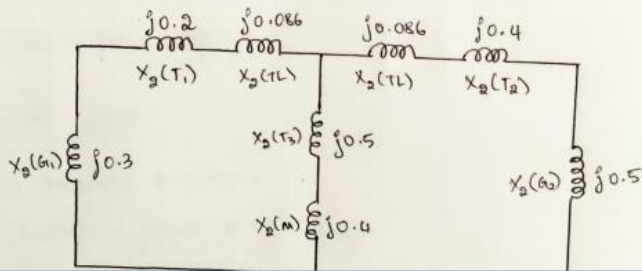

Zero sequence network

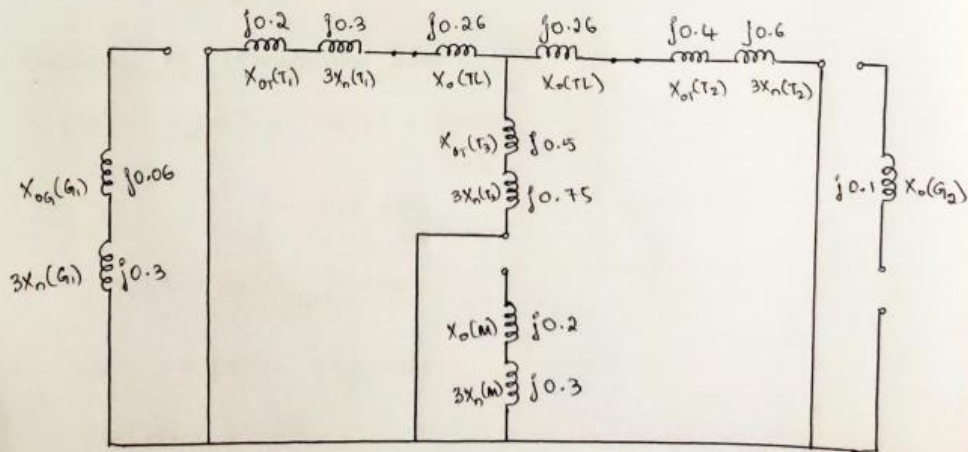

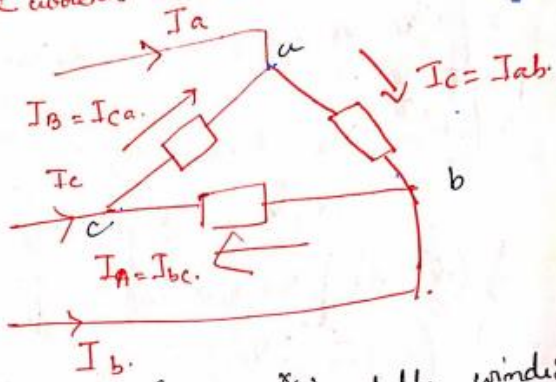same Relation between seq. Components
 Δ connection
 3 phase currents in delta connected system.



phase currents (currents in delta windings) are I_{ab} , I_{bc} and I_{ca} .

$$I_{ab} = I_c, \quad I_{bc} = I_a, \quad I_{ca} = I_b.$$

Applying KCL

$$\left. \begin{aligned} I_a &= I_c - I_b \\ I_b &= I_a - I_c \\ I_c &= I_b - I_a \end{aligned} \right\}$$

Document No.

Page No.



Seq. component of line current are.

$$I_{a1} = \frac{1}{3} [I_a + \alpha I_b + \alpha^2 I_c]$$

$$= \frac{1}{3} [I_c - I_b + \alpha (I_a - I_c) + \alpha^2 (I_b - I_a)]$$

$$= \frac{1}{3} \left[\alpha (I_a + \alpha I_b + \alpha^2 I_c) - \alpha^2 (I_a + \alpha I_b + \alpha^2 I_c) \right]$$

$$= \frac{1}{3} (\alpha - \alpha^2) (I_a + \alpha I_b + \alpha^2 I_c)$$

$$I_{a1} = \frac{1}{3} j\sqrt{3} \times 3 I_{A1}$$

$$I_{a2} = \frac{1}{3} (I_a + \alpha^2 I_b + \alpha I_c)$$

$$= \frac{1}{3} [I_c - I_b + \alpha^2 (I_a - I_c) + \alpha (I_b - I_a)]$$

$$= \frac{1}{3} \left[\alpha^2 (I_a + \alpha I_b + \alpha^2 I_c) - \alpha (I_a + \alpha I_b + \alpha^2 I_c) \right]$$

$$= \frac{1}{3} (\alpha^2 - \alpha) (I_a + \alpha I_b + \alpha^2 I_c)$$

$$I_{a2} = \frac{1}{3} (-j\sqrt{3}) (3 I_{A2})$$

∴ line currents in delta system is $\sqrt{3}$ times the phase currents.

The +ve seq. line current leads the respective phase currents by 90° whereas the -ve seq. line current lags the -ve seq. phase currents by 90° .

Zero seq. component of line current

$$I_{A0} = \frac{1}{3} (I_A + I_B + I_C)$$


$$= \frac{1}{3} [(I_C - I_B) + (I_A - I_C) + (I_B - I_A)]$$

$$= 0$$

though $I_{A0} = 0$ does not mean $I_{A0} = 0$

3b

3b)

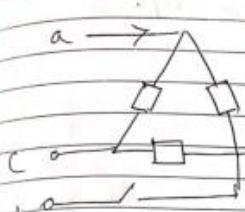

$I_a = 15 / 0^\circ \text{ A}$
 $I_c = 15 / -180^\circ \text{ A}$
 $I_b = 0$

In a 2 wire system $I_a + I_b + I_c = 0$
 but $I_b = 0$ ∴ $I_a = -I_c$

+ve sequence component of line current is

$$I_{A1} = \frac{1}{3} (I_a + \alpha I_b + \alpha^2 I_c)$$




$$= \frac{1}{3} [15 / 0^\circ + 15 / -180^\circ + 240^\circ] = 8.66 / 30^\circ \text{ A}$$

$$I_{A2} = \frac{1}{3} (I_a + \alpha^2 I_b + \alpha I_c)$$

$$= \frac{1}{3} [15 / 0^\circ + 15 / -180^\circ + 120^\circ] = 8.66 / -30^\circ \text{ A}$$

$$I_{A0} = 0$$

(4)

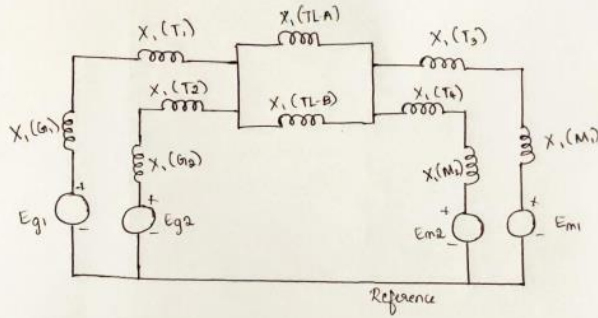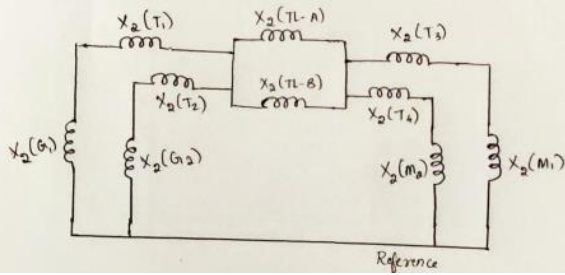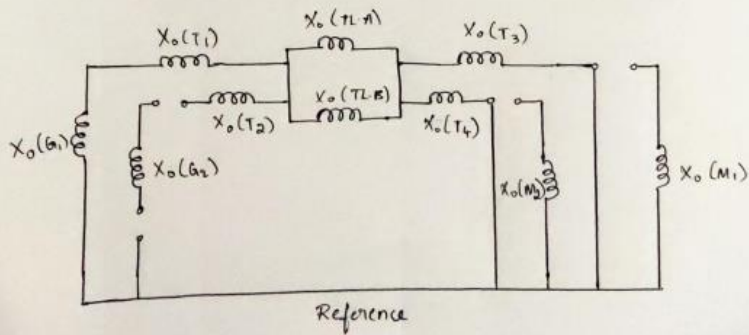Positive sequence networkNegative sequence networkZero sequence network

$$5a) \quad V_a = 4 \angle 0^\circ \text{ V}$$

$$V_b = 3 \angle -90^\circ \text{ V}$$

$$V_c = 8 \angle 143.1^\circ \text{ V}$$

$$V_{a0} = \frac{1}{3} (V_a + V_b + V_c) = 1.00 \angle 143.09^\circ \text{ V}$$

$$= \frac{2.72}{3} \angle -107.07^\circ \text{ V} \quad V_{b0} = 143.09^\circ \text{ V}$$

$$V_{c0} = 143.09^\circ \text{ V}$$

$$V_{b0} = 2.72 \angle -107.07^\circ \text{ V}$$

$$V_{c0} = 2.72 \angle -107.07^\circ \text{ V}$$

$$V_{a1} = \frac{1}{3} (V_a + \alpha V_b + \alpha^2 V_c)$$

$$= \frac{1}{3} (4 \angle 0^\circ + 3 \angle 120^\circ + 8 \angle 383.1^\circ) \text{ V}$$

$$= 4.9 \angle 18.31^\circ \text{ V}$$

$$V_{b1} = 4.9 \angle 258.31^\circ \text{ V}$$

$$V_{c1} = 4.9 \angle 138.31^\circ \text{ V}$$

$$V_{a2} = \frac{1}{3} (V_a + \alpha^2 V_b + \alpha V_c)$$

$$= \frac{1}{3} (4 \angle 0^\circ + 3 \angle 150^\circ + 8 \angle 263.1^\circ) \text{ V}$$

$$= 3.3 \angle 266.2^\circ \text{ V} \quad 2.15 \angle -86.0^\circ \text{ V}$$



$$V_{b2} = 3.3 \angle 146.2^\circ \text{ V}$$

$$V_{b2} = 2.15 \angle 34^\circ \text{ V}$$


$$V_{c2} = 2.15 \angle 154^\circ \text{ V}$$

$$V_{c2} = 3.3 \angle 266.2^\circ \text{ V}$$


V_{a1}

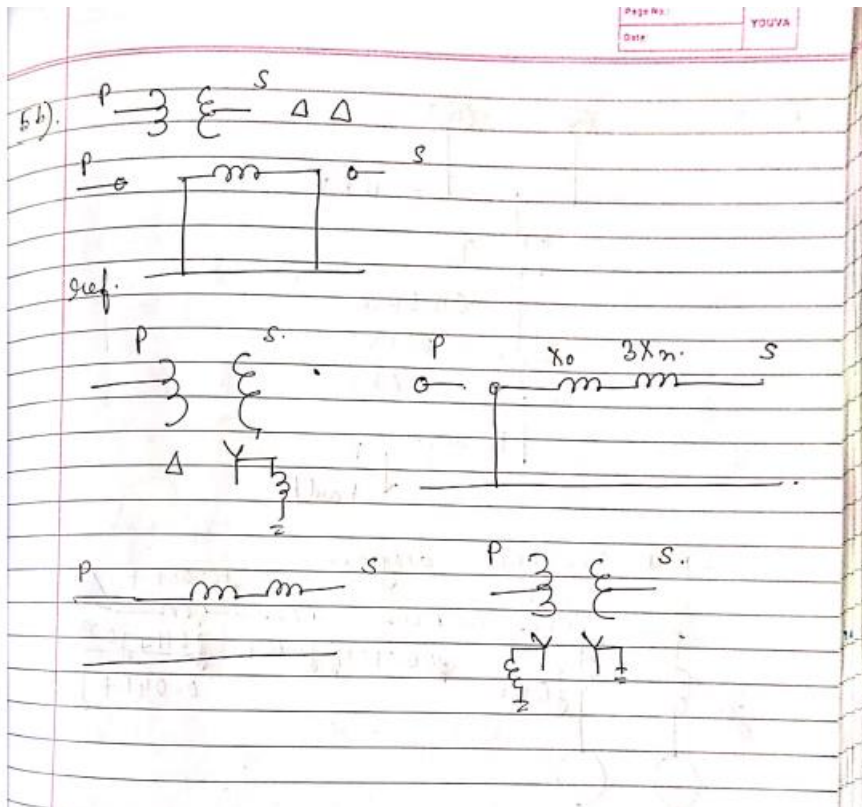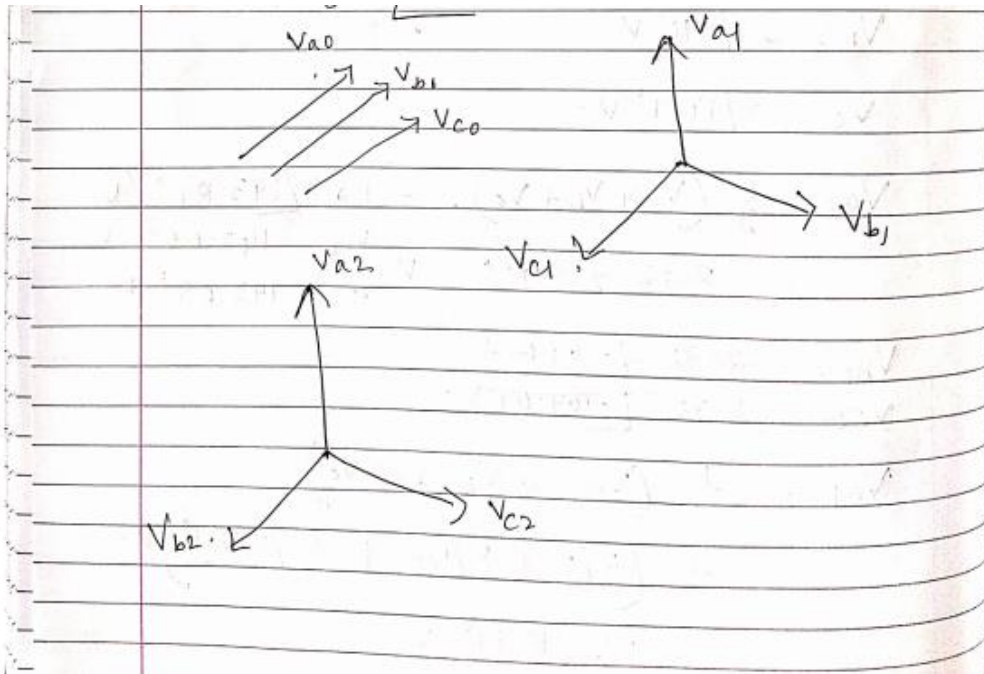

6.

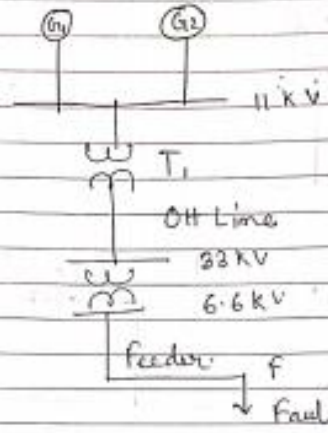

p.u reactance diagram

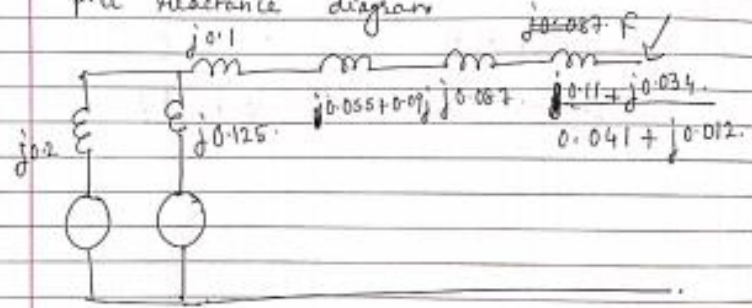


$$X_{OH} (pu) = \frac{(6 + j10) \times 10}{33^2}$$

$$X_{feeder} (pu) = \frac{(0.5 + j0.15) \times 10}{6.6^2}$$

$$Z_{TH} = (j0.211 + j0.1125) + (j0.1 + j0.055 + j0.09 + j0.087 + j0.041 + j0.012)$$

$$= Z_{TH} = 0.096 + 0.3659j$$
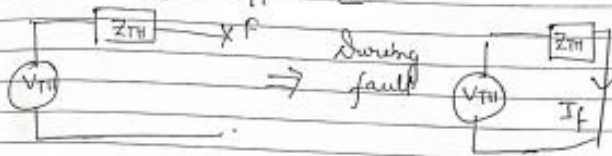
$$V_{TH} = V_{pf} = \frac{11}{11} = 1 \angle 0^\circ$$



$$I_f = \frac{1 \angle 0^\circ}{0.096 + 0.3659j}$$

$$= 2.64 \angle -75.3^\circ \text{ pu.}$$

$$\text{Base current } I_B = \frac{(MVA)_B \times 10^6}{\sqrt{3} (kV)_B \times 10^3}$$

$$= \frac{10 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 524.86 \text{ A}$$

$$I_f = I_B \times (I_f)_{pu} = 524.86 \times 2.64 \angle -75.3^\circ$$

$$= 1385.64 \angle -75.3^\circ \text{ A}$$

Complex Power in terms of symmetrical components

The total complex power flowing into a 3 ϕ circuit is

$$S = P + jQ = V_a I_a^* + V_b I_b^* + V_c I_c^*$$

S \Rightarrow total complex power

P \Rightarrow active power,

Q \Rightarrow reactive power.

$$S = P + jQ = [V_a \ V_b \ V_c] \begin{bmatrix} I_a^* \\ I_b^* \\ I_c^* \end{bmatrix}$$

$$[V_a \ V_b \ V_c] = \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix}^T \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}$$

$$= \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix}^T \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}$$

$$\{ [A] [B] \}^T = [B]^T [A]$$



$$\begin{bmatrix} I_a^* \\ I_b^* \\ I_c^* \end{bmatrix} = \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}^* = \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}^*$$

$$\begin{aligned} ([A][B])^* &= [A]^* [B]^* \\ &= \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix}^* \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}^* \end{aligned}$$

$$\alpha^* = \alpha^2$$

$$(\alpha^2)^* = \alpha$$

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}^*$$

$$\therefore S \pm P + jQ = \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix}^T \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}^*$$

$$= \begin{bmatrix} V_{a0} & V_{a1} & V_{a2} \end{bmatrix} \begin{bmatrix} 3 & 0 & 0 \\ 0 & 3 & 0 \\ 0 & 0 & 3 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}^*$$

$$S = P + jQ = 3 \left\{ V_{a0} I_{a0}^* + V_{a1} I_{a1}^* + V_{a2} I_{a2}^* \right\} V_A$$

Two factors are of utmost importance of selection of CB.

1) The maximum instantaneous current that a breaker must withstand (called momentary duty of CB)

2) The total current when the breaker contacts part (called interrupting current)



Two of the CB ratings which require the computation of SC current are: rated momentary current and rated symmetrical interrupting current.

* Symmetrical SC current is obtained by using subtransient reactance for synchronous machines.

Momentary (r.m.s) current is then calculated by multiplying the symmetrical momentary current by a factor of 1.6 to account for the presence of DC offset current.

* Symmetrical current to be interrupted is computed by using X_d'' for syn gen and X_d' for syn motors — induction motors are neglected.

DC offset value to be added to obtain the current to be interrupted is accounted for by multiplying the symmetrical SC current by a factor as follows:

CB speed	Multiplying factor
8 cycles or slower	1.0
5 cycles	1.1
3 cycles	1.2
2 cycles	1.4