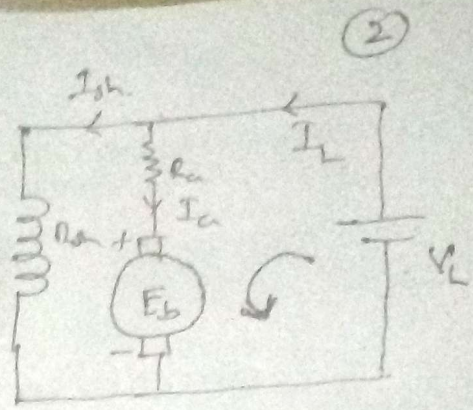


4b.  $V_L = 250V \mid P = 6 \mid Z = 220$   
 $R_a = 0.2 \Omega \mid I_a = 13.3A \mid A = 2$   
 $N = 908 \text{ RPM}$



$$+V_L - I_a R_a - E_b = 0$$

$$E_b = V_L - I_a R_a = 247.34V$$


$$E_b = \frac{N \phi Z P}{60A} \rightarrow \phi = \frac{E_b 60A}{N Z P} = \frac{29680.8}{1198560} = 0.024 \text{ Wb}$$

5b.  $R = 100 \Omega \mid C = 25 \times 10^{-6} F \mid L = 0.15 H$

$$V = 220V \mid f = 50 \text{ Hz}$$

$$X_L = 2\pi f L = 47.1 \Omega$$
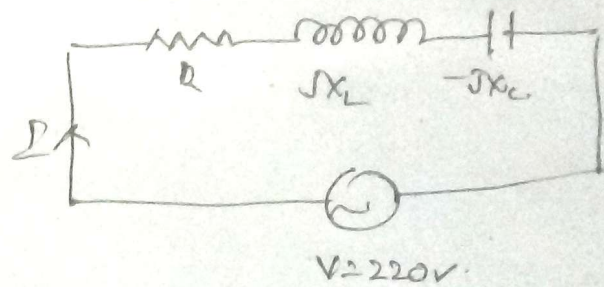
$$X_C = \frac{1}{2\pi f C} = 127.38 \Omega$$



$$1.337 + j1.07$$

$$* Z = R + j(X_L - X_C) = (100 - j80.28) \Omega$$


$$* |I| = \frac{|V|}{|Z|} = \frac{220}{124} \quad \left| \quad I = \frac{V}{Z} = 1.715 \angle 38.75^\circ \text{ A}$$

$$* \text{Complex power (S)} = VI^* = 294.14 - j235.4 = (\bar{P} - j\bar{Q}) \text{ VA}$$

$$* \text{power factor } \cos \phi = \cos(38.75^\circ) = 0.779$$



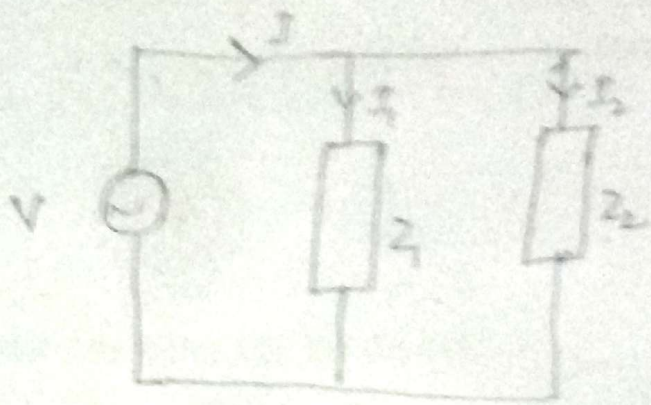6b.  $V = 200 \angle 0^\circ \text{ V}$   
 $f = 50 \text{ Hz}$   
 $Z_1 = (150 - j157) \Omega$   
 $Z_2 = (100 + j110) \Omega$



\*  $I_1 = \frac{V}{Z_1} = 0.92 \angle -47.3^\circ \text{ A} = 0.676 + j0.665 \text{ A}$   
 \*  $I_2 = \frac{V}{Z_2} = 1.34 \angle -47.7^\circ \text{ A} = 0.90 - j0.99 \text{ A}$   
 \*  $J = I_1 + I_2 = 2.02 \angle -38^\circ \text{ A} = (2.02 - j0.135) \text{ A}$   
 \* power  $S = V J^* = (404 + j227) \text{ VA} = (P + jQ) \text{ VA}$

7c.  $p = 6$  |  $\text{\textcircled{Y}}$ -connected | slots = 90 |  
 cond / slot = 12 |  $N_s = 1000 \text{ RPM}$  |  $\phi = 0.5 \text{ Wb}$  |  
 $k_w = 0.97$

$E_p = 4.44 \phi f T_p k_w$  |  $E_L = \sqrt{3} E_p$

$T_p = \frac{12 \times 90}{6} = 180$  |  $f = \frac{N_s}{120} = 50 \text{ Hz}$

$E_p = 19380.6 \text{ V}$  |  $E_L = 33528.438 \text{ V}$



80.  $V_L = 400V \mid I_L = 10A \mid \cos\phi = 0.7$

$\rightarrow \phi = 45.57^\circ$

④ connected;

$V_L = V_p = 400V$

(i)  $I_p = I_L / \sqrt{3} = 5.77A$

(ii)  $S = P + jQ = \sqrt{3} V_L I_L \cos\phi + j\sqrt{3} V_L I_L \sin\phi$   
 $= (3997.27 + j2854.69) VA$

(iii)  $Q = \sqrt{3} V_L I_L \sin\phi = 2854.69 VAR$

95.  $\eta_{max} = \frac{x^* |V_2| (I_{2FL}) \cos\phi}{x^* |V_2| (I_{2FL}) \cos\phi + 2W_i} \quad \left. \begin{array}{l} x^* \geq 1 \\ |V_2| (I_{2FL}) = 25 \times 10^3 VA \\ \cos\phi = 1 \end{array} \right\} = 0.98$

$25 \times 10^3 = 0.98 (25 \times 10^3) + 1.96 W_i$

$W_i = 255 W$

$x^* = \sqrt{\frac{W_i}{(W_{cu})_{FL}}} \Rightarrow (k_{cu})_{FL} = 255 W$

CASE (i): -  $x_1 = 0.75 \mid \cos\phi_1 = 0.9 \mid \eta_1 = ?$

$\eta_1 = \frac{x_1 |V_2| (I_{2FL}) \cos\phi_1}{x_1 |V_2| (I_{2FL}) \cos\phi_1 + W_i + x_1^2 (k_{cu})_{FL}} = 97.33\%$



CASE (ii) : —  $x_2 = 0.5$  |  $\cos\phi_2 = 0.8$  |  $\eta_2 = ?$

$$\eta_2 = \frac{x_2 |V_2| (I_{2FL} | \cos\phi_2)}{x_2 |V_2| (I_{2FL} | \cos\phi_2 + kI_1 + x_2^2 (1-k) P_L)} = 96.91\%$$

CASE (iii) : —  $x_3 = 0.25$  |  $\cos\phi_3 = 0.6$  |  $\eta_3 = ?$

$$\eta_3 = \frac{x_3 |V_2| (I_{2FL} | \cos\phi_3)}{x_3 |V_2| (I_{2FL} | \cos\phi_3 + kI_1 + x_3^2 (1-k) P_L)} = 93.26\%$$

9C.  $P = 6$  |  $f = 50\text{Hz}$  |  $S_{NL} = 0.01$  |  $S_{FL} = 0.03$

(i)  $N_s = \frac{120f}{p} = 1000\text{RPM}$

(ii)  $(N_r)_{NL} = (1 - S_{NL}) N_s = 990\text{RPM}$

(iii)  $(N_r)_{FL} = (1 - S_{FL}) N_s = 970\text{RPM}$

(iv)  $(f_r)_{NL} = Sf = f = 50\text{Hz}$  @ standstill

(v)  $(f_r)_{FL} = (S_{FL})f = 1.5\text{Hz}$

10C. Rating =  $20\text{kVA} = 20 \times 10^3 \text{VA}$  |  $N_1 = 1000$  |  $N_2 = 2500$  |  $g = 0.01 \text{m}^2$

$V_1 = E_1 = 550\text{V}$



(g)

$$V = E = 4.4 \text{ kV} = 4400 \text{ V}$$

$$Q_m = \frac{V}{4.4 \text{ kV}} = 0.0024 \text{ kWh}$$

$$B_m = \frac{Q_m}{\alpha} = 0.2477 \text{ T}$$

(h)

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} \rightarrow E_2 = E_1 \left( \frac{N_1}{N_2} \right) = \frac{4400}{1.375} = 3200 \text{ V}$$


(i)

$$N_1 I_{1PL} = N_2 I_{2PL} = 20 \times 10^3 \text{ kVA}$$

$$I_{1PL} = 3636 \text{ A} \quad | \quad I_{2PL} = 14.54 \text{ A}$$



1c.  $I_1 = 10A \quad | \quad \Delta t = 0.01s$

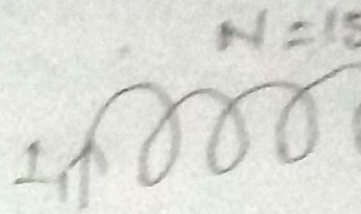

(i) Self inductance;  $L = \frac{N\Phi}{I_1} = 0.15H$

(ii) Induced emf;  $E = L \frac{\Delta I}{\Delta t} \quad \left| \begin{array}{l} \Delta I = 10 - 0 \\ \Delta t = 0.01s \end{array} \right.$


$E = 300V$

2b. CASE (i):

$$P_1 = \frac{V^2}{R_1} = V I_1 = 600W$$

$$I = I_1 + I_2 \quad | \quad I_1 = 6A \quad | \quad I_2 = 4A$$

$$R_1 = \frac{V}{I_1} = 16.66\Omega \quad | \quad R_2 = \frac{V}{I_2} = 25\Omega$$

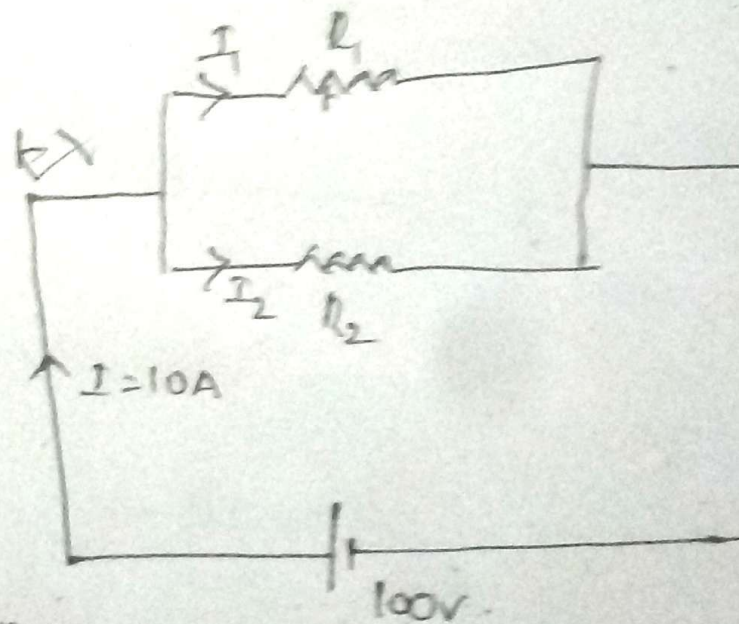

CASE (ii):

$$I = \frac{V}{R_1 + R_2} = 2.40A$$

