

--	--	--	--	--	--	--	--	--	--

Seventh Semester B.E. Degree Examination, Dec.2017/Jan.2018

Industrial Drives and Applications

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1
 - a. Briefly explain the different power modulators that used in drive system. (06 Marks)
 - b. With the help of quadrantal diagram, explain four-quadrant operation of a motor driving a hoist load. (10 Marks)
 - c. Define active load torque and passive torque. Give an example. (04 Marks)
- 2
 - a. Explain the steady state stability in the drive system. (05 Marks)
 - b. Explain standard classes of motor duty with load diagram. (08 Marks)
 - c. A motor has heating-time constant of 70 min and a cooling time constant of 90 min. When run continuously on full load of 400 kW, final temperature rise is 50°C.
 - i) When used in short time periodic duty cycle consisting of loaded period of 10 min followed by no-load period long enough for the motor to cool down. What will be the maximum load that motor can carry?
 - ii) Determine the maximum load the motor can deliver when subjected to intermittent periodic load cycle consisting of a load period of 10 min followed by a no-load period of 15 min. (07 Marks)
- 3
 - a. Explain the dynamic braking of separately excited DC motor. (06 Marks)
 - b. A 220 V, 200 A, 800 rpm separately excited DC motor has an armature resistance of 0.06 Ω. The motor armature is fed from a variable voltage source with an internal resistance of 0.04 Ω. Calculate internal voltage of the variable voltage source when the motor is operating in regenerative braking at 80% of the rated motor torque and 600 rpm. (06 Marks)
 - c. Explain the operation of continuous conduction mode of a single-phase fully controlled rectifier control of separately excited DC motor. (08 Marks)
- 4
 - a. A 220 V, 1500 rpm, 10 A separately excited dc motor is fed from a single-phase fully controlled rectifier with an AC source voltage of 230 V, 50 Hz, $R_a = 2 \Omega$. Conduction can be assumed to be continuous, calculate firing angle for:
 - i) Half the rated motor torque and 500 rpm
 - ii) Rated motor torque and -1000 rpm. (08 Marks)
 - b. Explain the multiquadrant operation of a separately excited DC motor using single-phase fully controlled rectifier with a reversing switch. (06 Marks)
 - c. Explain the regenerative braking of separately excited DC motor by chopper control. (06 Marks)

PART - B

- 5
 - a. What is single phasing? Explain the operation of a 3-phase induction motor with unbalanced voltages. (07 Marks)

- b. A 2200 V, 50 Hz, 3 phase, 6 pole, Y connected, squirrel cage induction motor has following parameters: $R_s = 0.075 \Omega$, $R'_r = 0.12 \Omega$, $X_s = X'_r = 0.5 \Omega$. The combined inertia of motor and load is 100 kg-m^2 . Calculate time taken and energy dissipated in the motor during starting. (08 Marks)
- c. Explain the reverse voltage braking (plugging) of an induction motor. (05 Marks)
- 6 a. Explain the available frequency control of an induction motor and mention any two features. (07 Marks)
- b. Explain the operation of a voltage source inverter fed induction motor drive. (07 Marks)
- c. Explain the static rotor resistance control. (06 Marks)
- 7 a. Explain pull-in process in synchronous motor operation from fixed frequency supply. (05 Marks)
- b. Explain the modes of variable frequency control of synchronous motors. (05 Marks)
- c. Explain the operation of self controlled synchronous motor drive employing load commutated thyristor inverter. (10 Marks)
- 8 a. With schematic diagram, explain the paper mill drive. (10 Marks)
- b. With schematic diagram, explain the cement mill. (10 Marks)

higher (ratings), speed, torque and power ratings.
Synchronous Motor :- (high full-load η and PF).

- ↳ Wound field
- ↳ Perm Magnet . PM

- * Compared to squirrel cage motor, wound field syn motors are high cost and needs more maintenance.
- * PM syn motors have all the adv of squ cage motor but available at lower power ratings.
- Stepper motor is popular for position control.
- SRM " " speed control.

POWER MODULATORS

- 1) Converters
- 2) Variable impedances
- 3) Switching ckt's.

The need for converter arises when the available electric power is diff than that required by the motor.

- 1) Fixed voltage fixed freq AC
 - 2) Fixed voltage dc.
- } Types of power source.

Types of converters :-


- 1) AC to DC converters
- 2) ac voltage controllers or ac regulators
- 3) Choppers or dc-dc converters
- 4) inverters (or) dc to ac converters
- 5) Cyclo converters.



AC to DC Converters


①

Fixed voltage
dc

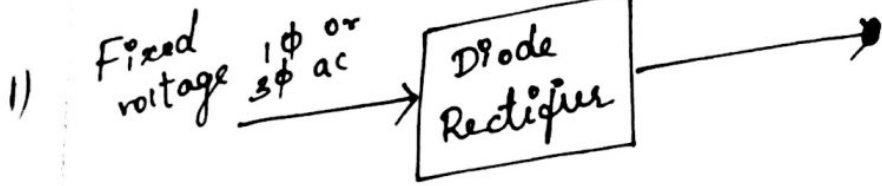


2)

Variable voltage
dc.

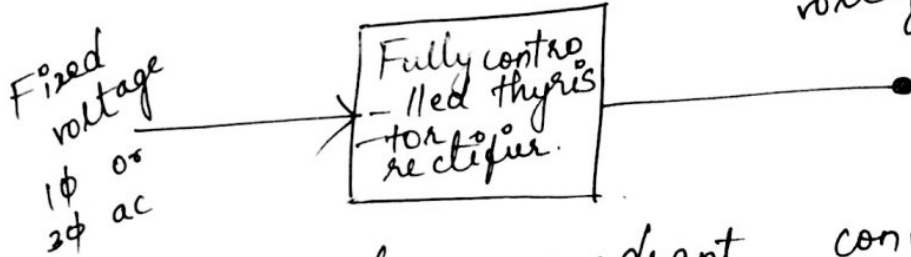

→ This is a two-quadrant converter.
i.e. capable of providing variable dc voltage
of either polarity with +ve current.


3)


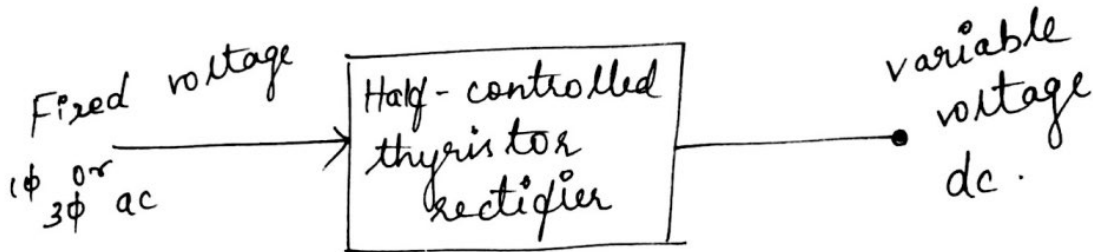


→ single quadrant converter.


(2) and (3) produces harmonics on both ac
and dc side \therefore low PF at low dc voltages.

4)

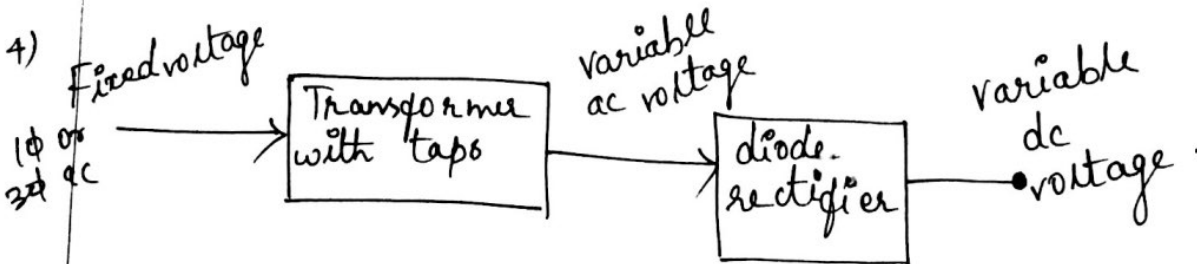


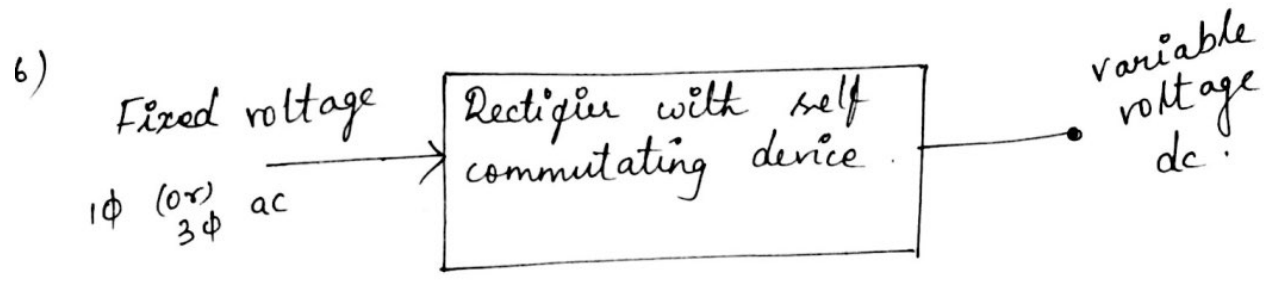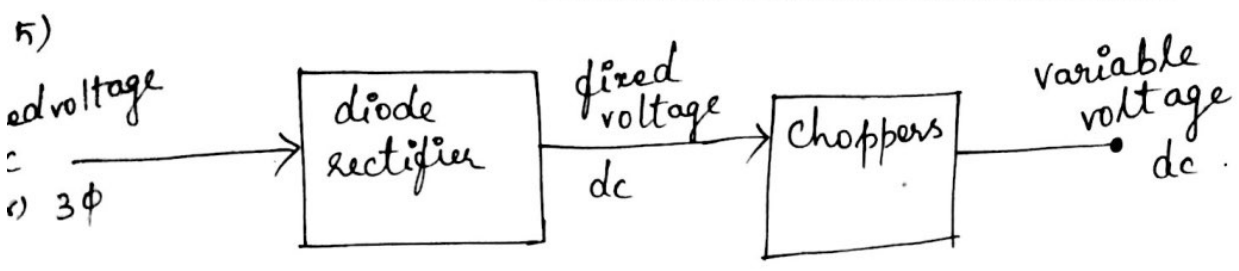

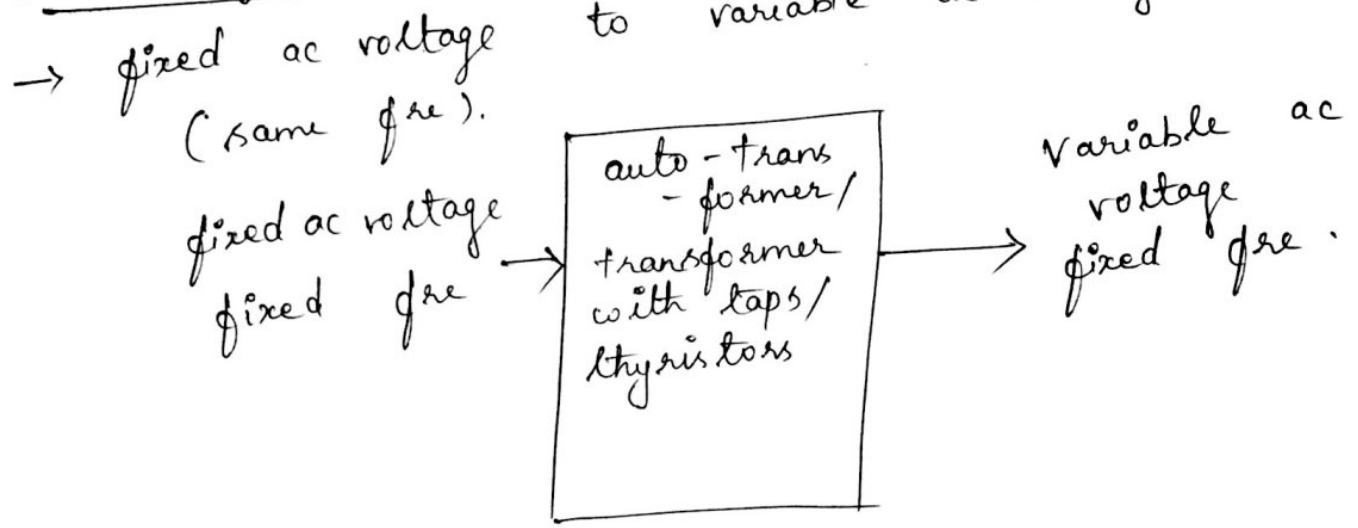AC voltage converters / ac regulators :-
to variable ac voltage.




Choppers or dc-dc converters :-

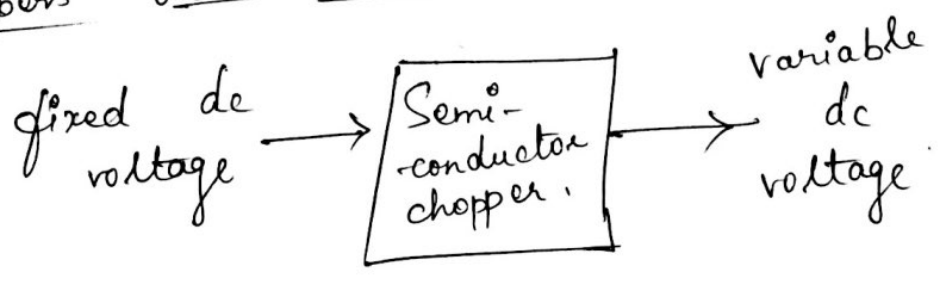




(A) Inverters

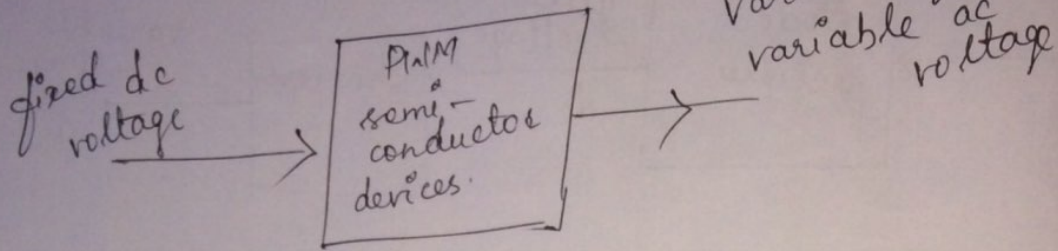

(B) Cyclo-converter

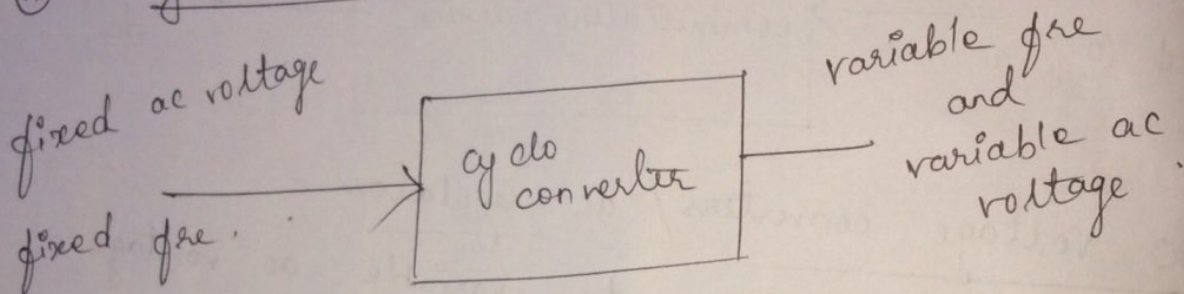

Variable Impedances :-

variable resistors - dynamic braking of drives
- control of low cost ac and dc drives.

Resistors are employed along with semi-conductor switch.

Inductors are used for limiting starting current of ac motors.

Old drives - reactors are used for control of induction motors.

(i) for changing motor connections to change its quadrant of operation

FB	FM
RM	RB

(ii) for changing motor ext parameters for auto-matic starting and braking control.

(iii) for operating motors and drives for pre-determined sequence.

(iv) provide interlocking to prevent mal-operation


eg

(v) disconnect motor during abnormal working conds

Control Unit

Switches - electro-magnetic relays called contactors.
- thyristor switches.

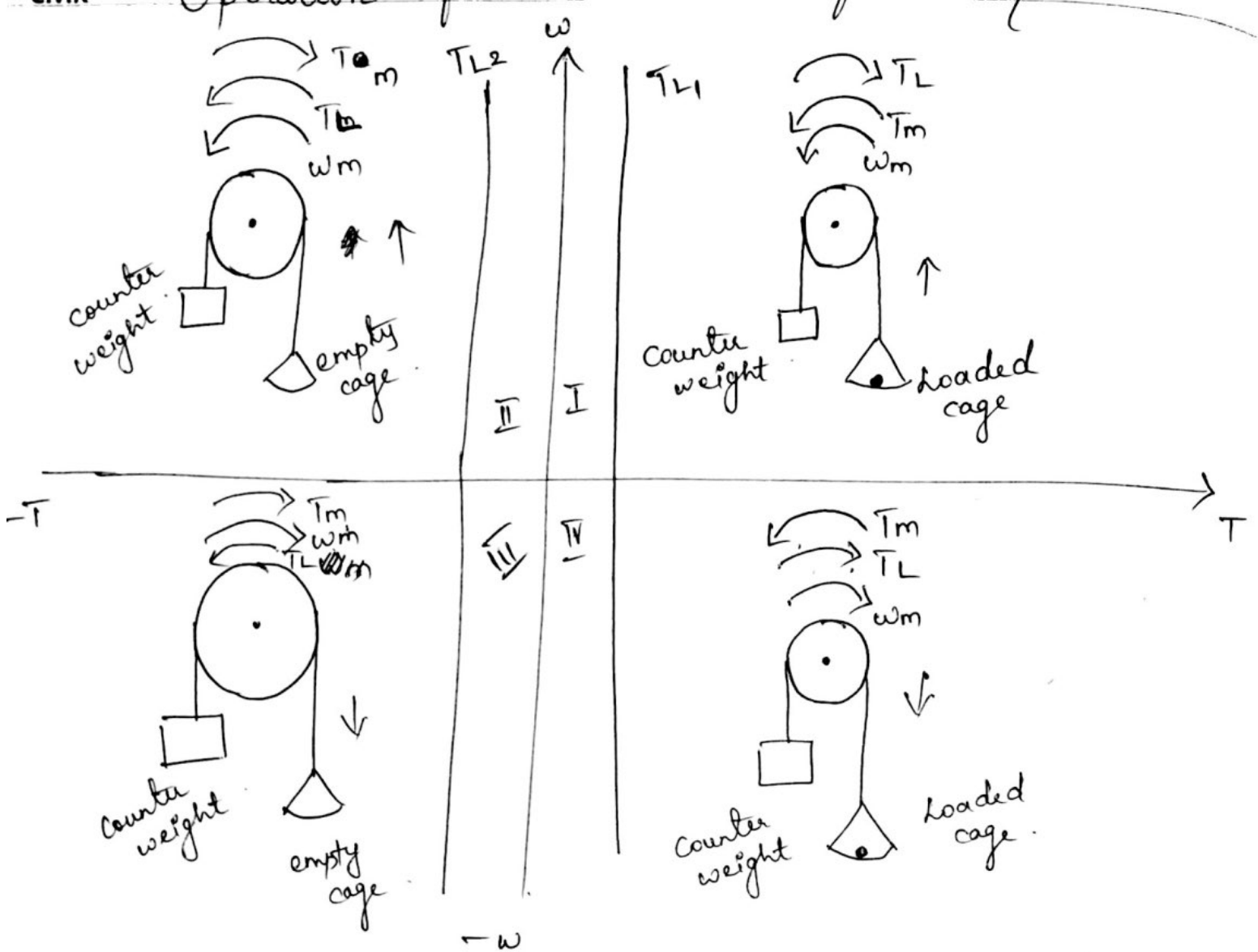For sequencing and interlocking operations, PLCs are employed.



- A hoist consists of a rope wound on a drum coupled to a motor shaft.
- One end of the rope is connected to cage (used for transporting material) and other end has a counter weight.
- Weight of the counter weight is chosen higher than the empty cage and but lower than a fully loaded cage.
- the load torque of the hoisting mechanism is of active type and assumed to be constant due to

Load torque T_L represents the N-T char of hoist loaded hoist. T_L is the diff of torque b/w loaded counter weight.

Load torque T_{L2} (II & III) represents the N-T char of an empty hoist. This torque is due to diff in torque of counter weight and empty hoist. This is -ve bcoz the counter weight is always higher than the empty cage.

Quadrant I

Hoist requires the movement of the cage upward which corresponds to the +ve motor speed which is in CCW direction. It will be obtained if motor produce +ve torque in CCW direction (equal to T_L). Since developed power is +ve, this is forward motoring operation.

Quadrant ~~III~~ IV

when the cage has to be lowered. Since counter weight is greater than $<$ loaded cage, the hoist moves down due to gravity. To limit the speed within safe limit, the motor has to produce +ve torque, in CCW direction (equal to T_L).

When empty cage has to be moved up.
Since counter weight is heavier than empty cage, it is able to pull it up. To limit the speed within safe limit, motor must produce a braking torque (equal to T_{L2}) in clockwise direction. $\omega \rightarrow +ve$, $T_m = -ve$, $P = -ve$
 \therefore forward braking.

Quadrant III:-

When empty cage has to be lowered.
empty cage has lesser weight than counter weight, the T_m will be in cw dir.
 $\omega_m = -ve$, $T_m = -ve$, $P = +ve$.

\therefore Reverse motoring.

EQUIVALENT VALUES OF DRIVE PARAMETERS.

\rightarrow diff parts of load may be coupled thro diff mechanisms (eg:- gears, v-belts and crankshaft).

Finding the equivalent moment of inertia J of motor-load system and equivalent torque components.

Classification of load torque.



Active load torque:-

load torque which has the potential to drive the motor under equilibrium conditions - such load torques retain the sign when the drive rotation is changed (reversed).

Eg:- Torque due to gravity, due to tension, due to compression and torsion.

Passive load torque:-

load torques which always oppose the motion and change their sign on the reversal of motion are called passive load torques.

Eg:- torque due to friction and cutting.



Stability :-


The system is said to be stable if it retains its original position or in equilibrium position ^{after} the disturbance period and this ~~original~~ ^{equilibrium} position may be a new position or original position.

The system is unstable if it comes to rest or has continuous ↑ in speed following the disturbance i.e. the system cannot achieve its new equilibrium position.

In practice, it is necessary to consider two types of disturbance:

- 1) Changes from the state of equilibrium take place slowly and the effect of either the inertia of the rotating mass or that of inductance is insignificant.
- 2) Sudden and fast changes from the equilibrium state, as a result of which the effect of neither the inertia nor the inductance can be ignored.

Case A)

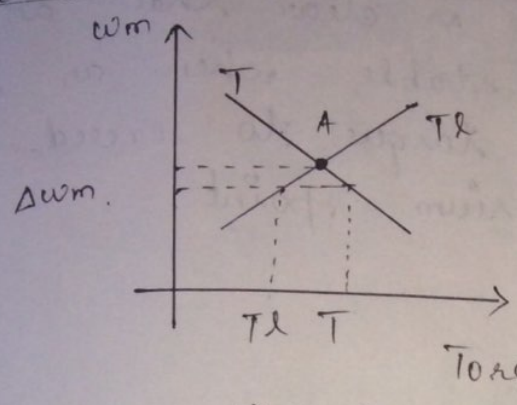


A - equilibrium or steady state position.

- Let the disturbance causes a reduction of $\Delta\omega_m$ in speed.
- At new speed, $T > T_L$ ∴ drive accelerates and speed ↑.
- ↑s. ∴ operation will be restored to A.
- Similarly increase in $\Delta\omega_m$ will make $T < T_L$.
- $T_L > T$, ∴ drive decelerates and speed ↓s.


Thus operation is restored to A. Hence the drive is steady state at pt A.

We can do the similar analysis for the following cases.

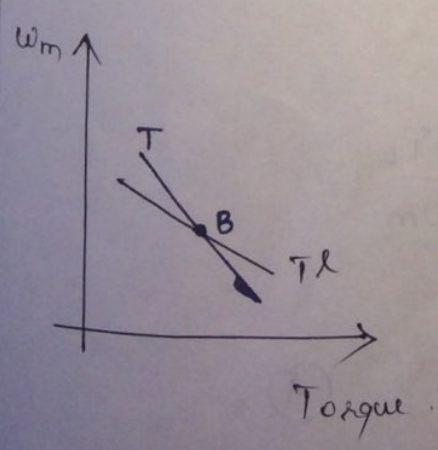
It is found that pts A and C are stable and B and D are unstable.



(B)

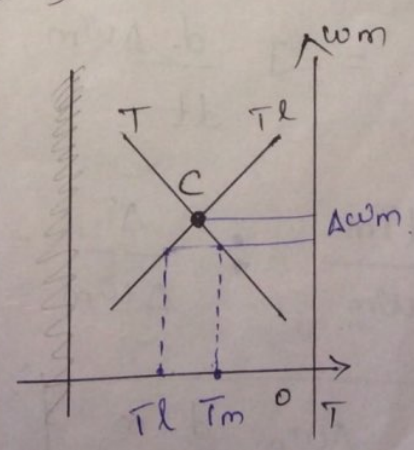

$T_m > T_L$

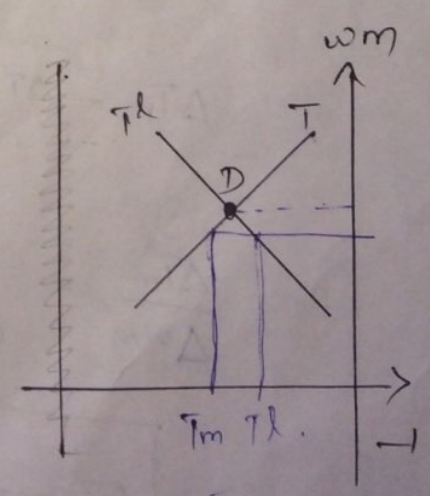



$T > T_m$

According to IS - there are eight standard classes of duty.

- (1) Continuous duty
- (2) Short time duty
- (3) Intermittent periodic duty
- (4) Intermittent periodic duty with starting
- (5) Intermittent periodic duty with starting and braking.
- (6) Continuous duty with intermittent periodic loading
- (7) Continuous duty with starting and braking.
- (8) Continuous duty with periodic speed changes.

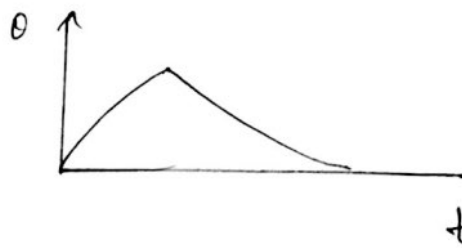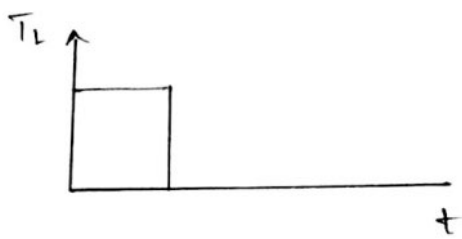1) Short Time Duty :-

Eg:- Drives for household applications, Crane drives, many m/c tool drives for position control.




→ time of drive operation less than heating time const and m/c is allowed to cool off to ambient temp (before the motor operates again)



't

curves, connecting 1 1 -


3) Intermittent periodic duty

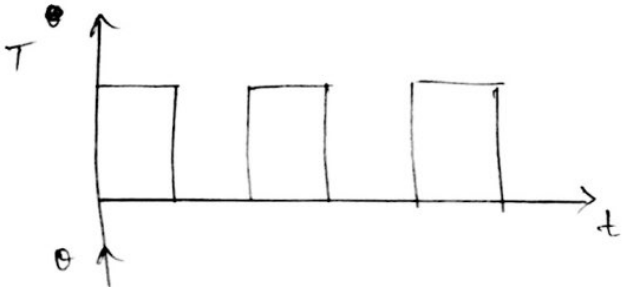


* consists of periodic duty cycle - period of running at const load and a rest period.
* the running period and being too

intermittent periodic duty with starting and braking (6)

eg:- m/c tool drives

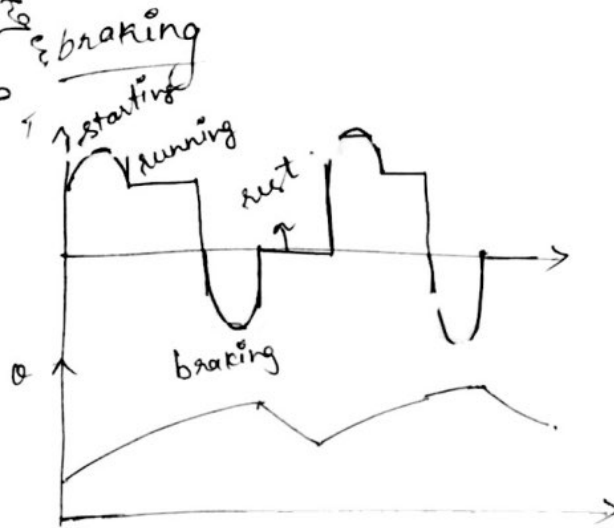

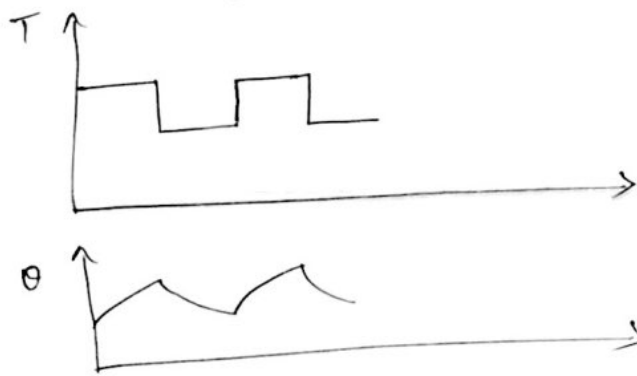6) Continuous duty with intermittent perioding loading




* consists of a period of starting running at const load and a period of no-load running.

* pressing, cutting, shearing and drilling m/c

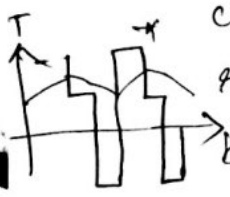7) Continuous duty with starting and braking

consists of a period of starting, a period of running at const load and a period of electrical braking (no rest) eg:- blooming mill.




8) Continuous duty with periodic speed changes

* a period of running at one load and speed and another period of running at diff speed and load.

$$\therefore \theta = \theta_2 e^{-t/\tau}$$

D) A motor operates on a periodic duty cycle which it is clutched to its load for 10 min, declutched to run on no-load for 20 min. Max temp rise is 40°C . Heating and cooling time constants are equal and have a value of 60 min. When the load is declutched continuously the temp rise is θ_2 . Find

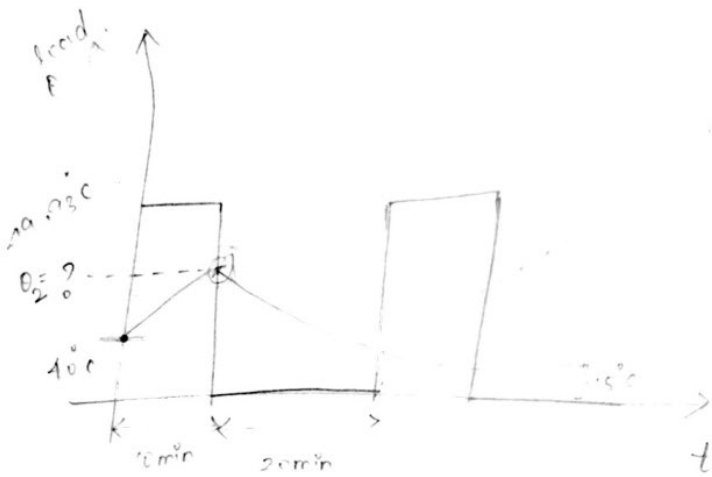- (i) max temp during the duty cycle.
- (ii) temp when the load is clutched continuously.



heating

$$\theta = \theta_{ss} (1 - e^{-t/\tau}) + \theta_1 e^{-t/\tau}$$

θ_1 - initial temp rise.

$$\theta = \theta_{ss} (1 - e^{-10/60}) + 40 e^{-10/60}$$

$$\theta = \theta_{max} (0.1535) + 33.86$$

$$\theta = 0.15 \theta_{max} + 33.86 \quad \text{--- (1)}$$

$$\theta = \theta_{ss} (1 - e^{-t/\tau}) + \theta_2 e^{-t/\tau}$$

$$\theta = 15 \left(1 - e^{-20/60} \right) + \theta_2 e^{-20/60}$$

$$40 = 4.25 + \theta_2 (0.716)$$

$$0.716 \theta_2 = 35.75$$

$$\boxed{\theta_2 = 49.93^\circ \text{C}}$$

Take ①

$\theta = \theta_2$ b'coz mean temp during heating

$$49.93 = \theta_{max} (0.1535) + 33.86$$

$$0.1535 \theta_{max} = 16.07$$

$$\boxed{\theta_{max} = 104.69}$$

dubay

②

A motor operates on a periodic duty cycle consisting of a loaded period of 20 min and a no-load period of 10 min. The max temp rise is 60°C . Heating and cooling time const are 70 and 70 min, when operating continuously on no-load the temp rise is 10°C . Find.

- 1) Min temp during the duty cycle.
- 2) Temp when the motor is loaded continuously

θ - mean temp
rise
at particul.
time

$\theta = 40^\circ$
during cooling



RB - not possible in series motor $\because E = k\phi\omega$

$\phi \rightarrow$ fun of $I_a \downarrow$
 $\omega_{\text{nom}} = \frac{V}{k\phi I_a} - \frac{R_a}{k\phi I_a}$


Dynamic or Rheostatic Braking

- Motor armature is disconnected from source and connected across a resistance R_B .
- The generated energy will be dissipated in R_B and R_a .


Separately Excited

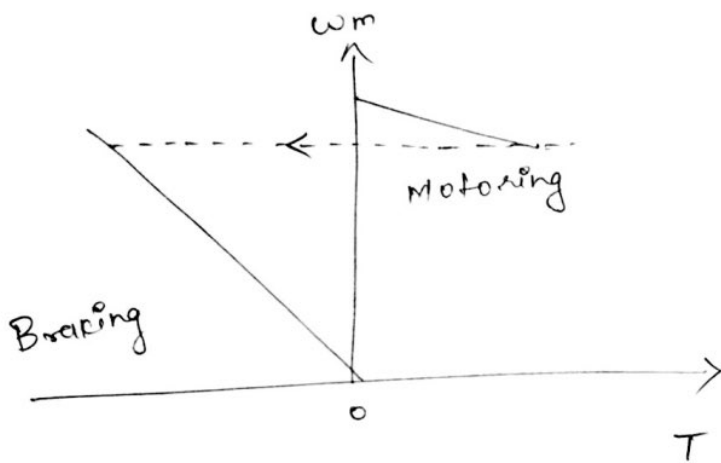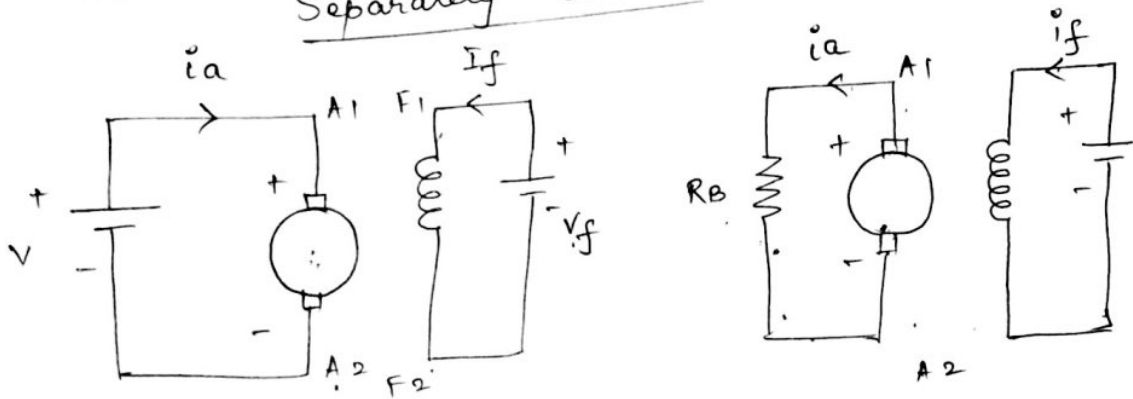


Series Motor

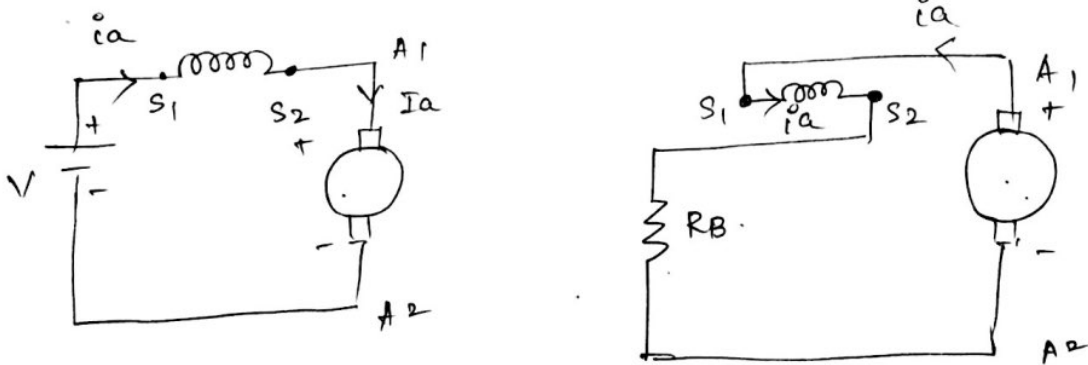

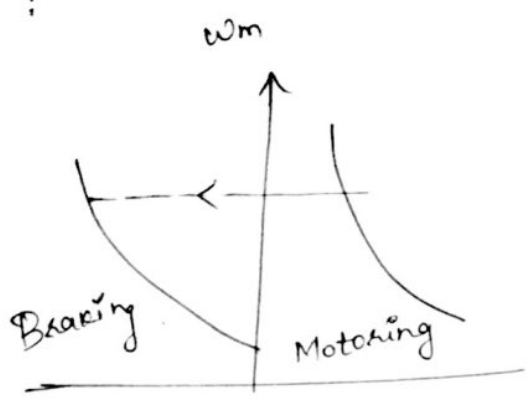$V = E + I_a R_a$
 $E > V \Rightarrow I_a$
 $V = E - I_a R_a$



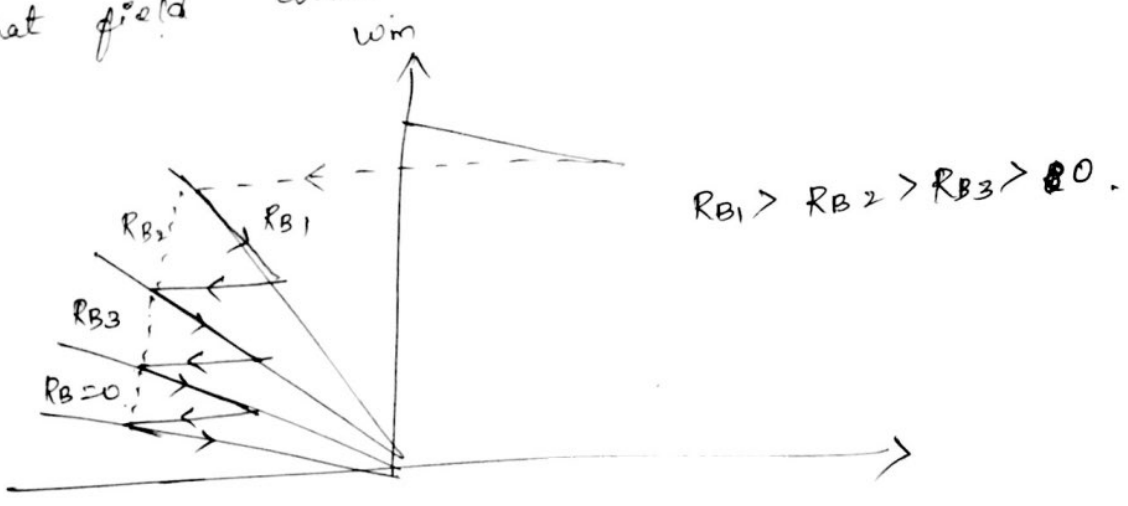In series m/c, the field connection is reversed so that field assists the residual magnetism.



$R_{B1} > R_{B2} > R_{B3} > 0$

When fast braking is needed - R_B consists of few sections. As the speed \downarrow , sections are cut-out to maintain a high avg torque.


Plugging

Separately excited:-

- > supply voltage is reversed so that it assist the back emf in forcing arm current in reverse direction.
- > R_B is connected in series with arm to


14 Turny controlled Rectifier control of
dc. separately excited motor

Qm

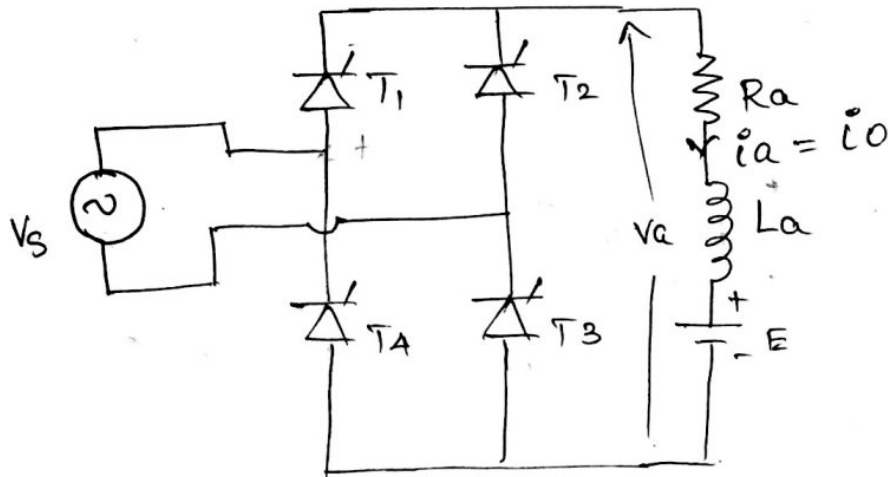

CONTROLLED rectifier fed dc drives are known as static Ward - Leonard drives.

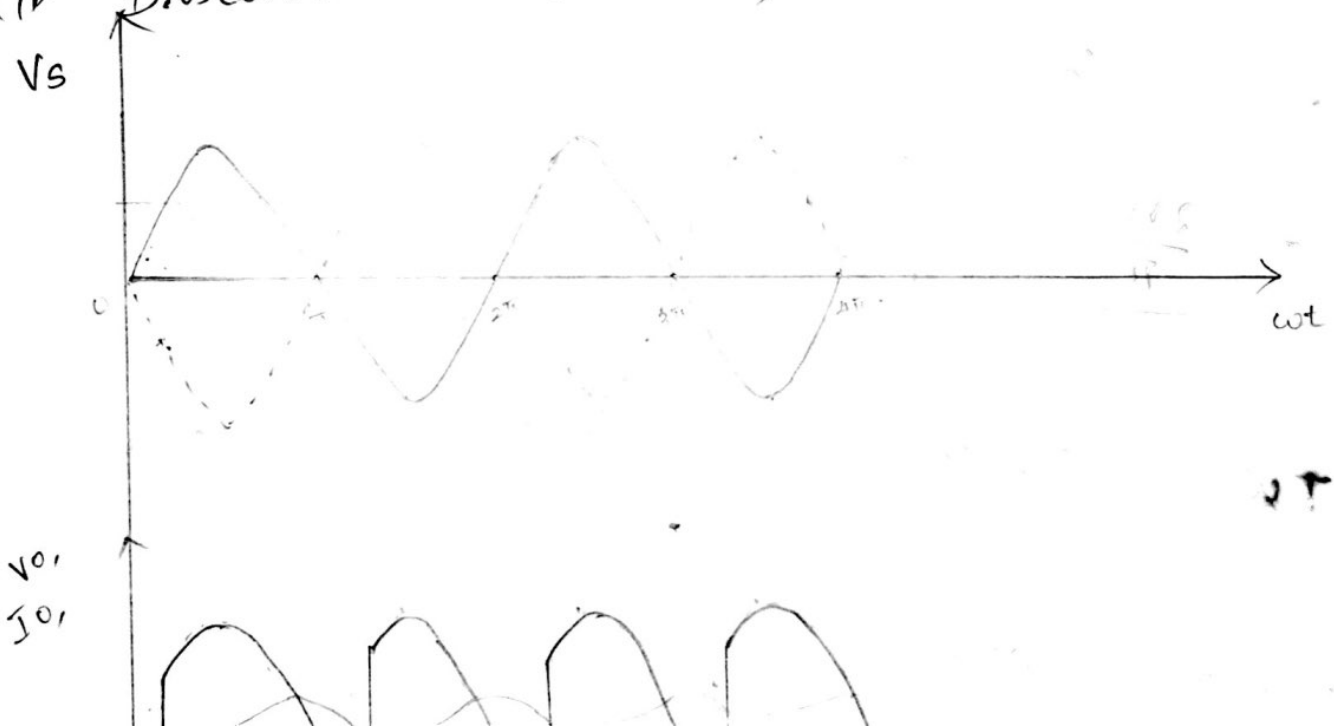- (i) Continuous (current) mode
- (ii) Discontinuous (current) mode



Continuous mode.

$$V_s = V_m \sin \omega t$$

F. r.m.s

$$V_a = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} v_s \, d\omega t$$

$$= \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \, d\omega t$$

$$= \frac{V_m}{\pi} (-\cos \omega t)_{\alpha}^{\pi+\alpha}$$

$$= \frac{V_m}{\pi} (-\cos(\pi+\alpha) + \cos \alpha)$$

$$= \frac{V_m}{\pi} (\cos \alpha + \cos \alpha)$$

$$\boxed{V_a = \frac{2V_m}{\pi} \cos \alpha}$$

①

$$i_a = \frac{T}{k^2}$$

sep ext

$$T \omega_m = E I \alpha$$

⊗

$$E = k_e \phi \omega_m$$

$$= k \omega_m$$


$$T = k i_a$$

$$V - i_a R_a = k \omega_m$$

$$\omega_m = \frac{V - i_a R_a}{k} = V -$$

$$\boxed{\omega_m = \frac{2V_m \cos \alpha}{\pi k} - \frac{R_a T}{k^2}}$$

②

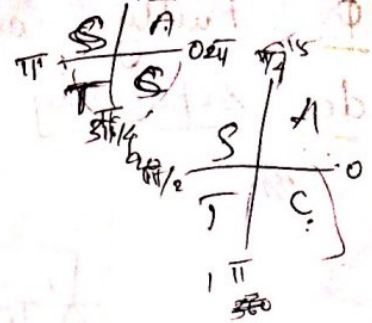

$$V_a = \frac{1}{\pi} \left[\int_{\alpha}^{\beta} v_a + \int_{\beta}^{\pi+\alpha} E \right] dt$$

$$= \frac{1}{\pi} \left[\int_{\alpha}^{\beta} v_m \sin \omega t dt + \int_{\beta}^{\pi+\alpha} E dt \right]$$

$$= \frac{1}{\pi} \left[v_m (-\cos \omega t) \Big|_{\alpha}^{\beta} + E (\omega t) \Big|_{\beta}^{\pi+\alpha} \right]$$

$$= \frac{1}{\pi} \left[v_m (-\cos \beta + \cos \alpha) + E (\pi + \alpha - \beta) \right]$$

$$V_a = \frac{v_m (\cos \alpha - \cos \beta) + (\pi + \alpha - \beta) E}{\pi}$$




$$\uparrow T = k i_a$$

$$\omega_m = \frac{V - i_a R_a}{k}$$

$$= \frac{v_m (\cos \alpha - \cos \beta) + (\pi + \alpha - \beta) E}{\pi k} - \frac{i_a R_a}{k}$$

$$\omega_m = \frac{v_m (\cos \alpha - \cos \beta) + (\pi + \alpha - \beta) k \omega_m}{\pi k} - \frac{R_a T}{k^2}$$
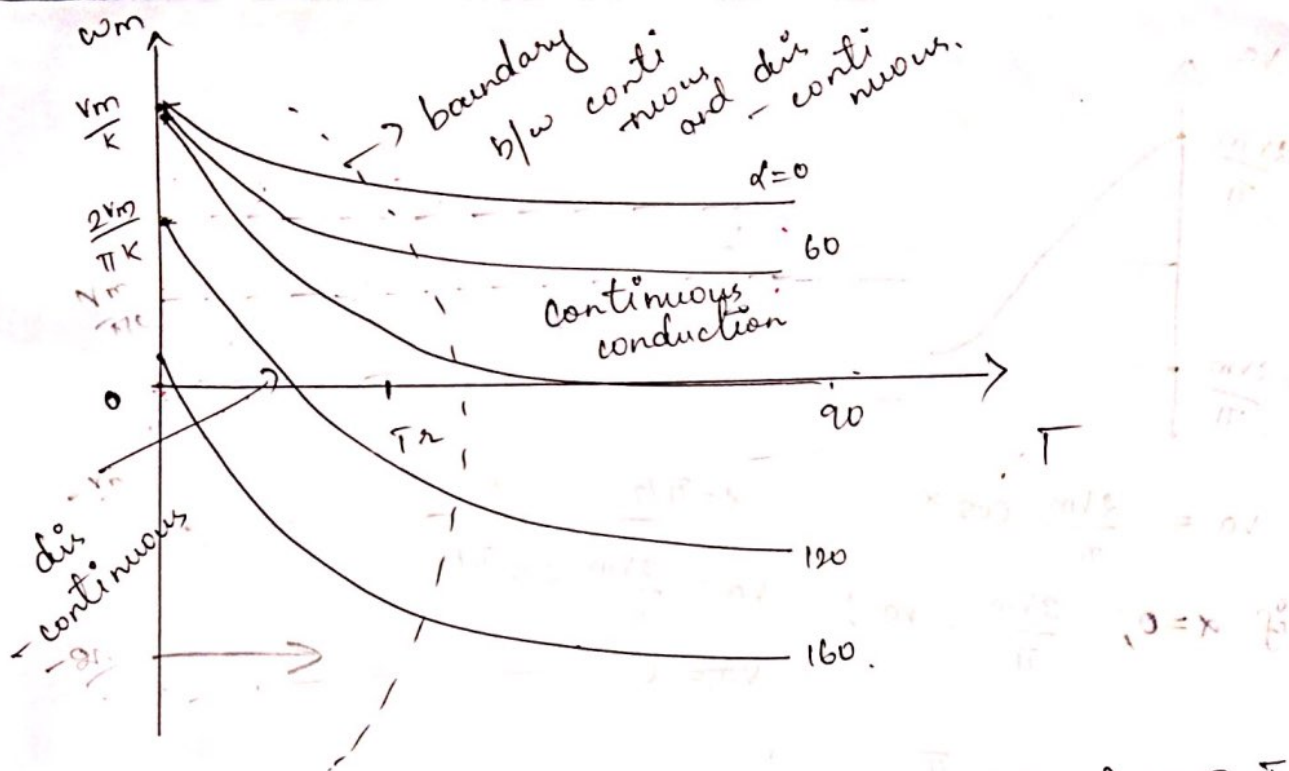
$$\omega_m \cdot \frac{\pi k}{\pi k} - \frac{k \omega_m (\pi + \alpha - \beta)}{\pi k} = \frac{v_m (\cos \alpha - \cos \beta)}{\pi k} - \frac{R_a T}{k^2}$$



$$I_m \left[1 - \frac{(\pi + \alpha - \beta)}{\pi} \right] = \frac{V_m (\cos \alpha - \cos \beta)}{\pi K} - \frac{R_a T}{K^2}$$


$$I_m \frac{-(\alpha - \beta)}{\pi} = \frac{V_m (\cos \alpha - \cos \beta)}{\pi K} - \frac{R_a T}{K^2}$$

$$I_m \frac{\pi}{\pi(\alpha - \beta)} = \frac{V_m (\cos \alpha - \cos \beta)}{K(\alpha - \beta)} - \frac{R_a T}{K^2}$$

$$I_m \frac{(\beta - \alpha)}{\pi} = \frac{V_m (\cos \alpha - \cos \beta)}{\pi K} - \frac{R_a T}{K^2}$$

$$I_m = \frac{V_m (\cos \alpha - \cos \beta)}{K(\beta - \alpha)} - \frac{R_a T \pi}{K^2 (\beta - \alpha)}$$

$$E = \frac{2}{\pi} V_m$$

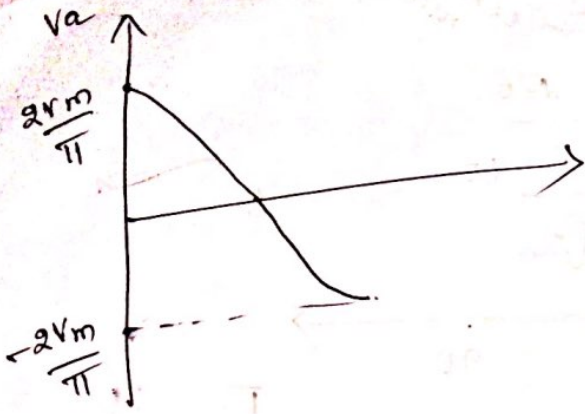

$$V_a = \frac{2V_m}{\pi} \cos \alpha$$

$$\alpha = \pi/2$$


$$V_a = \frac{2V_m}{\pi} \cos \pi/2$$

$$V_a = 0$$


if $\alpha = 0$, $\frac{2V_m}{\pi} = V_a$;

$$\alpha > 90; \alpha = \pi$$
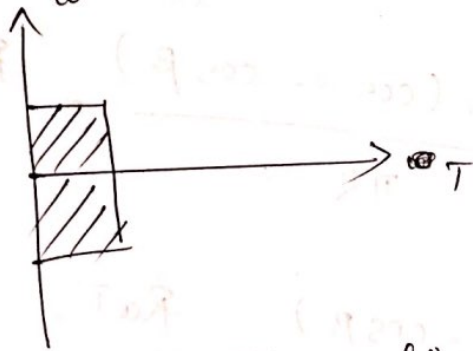
$$V_a = \frac{2V_m}{\pi} \cos \pi = -\frac{2V_m}{\pi}$$



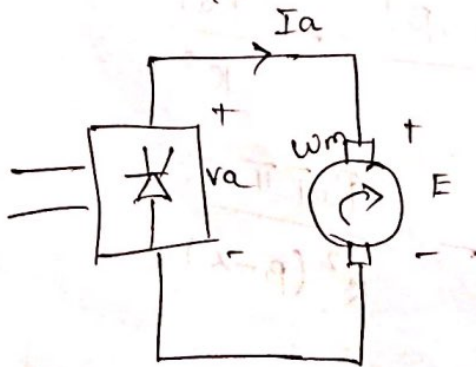
fully-controlled rectifier operates in I and II quadrant.



~~alpha > 90~~

$$\alpha < 90, \omega_m > 0$$

+

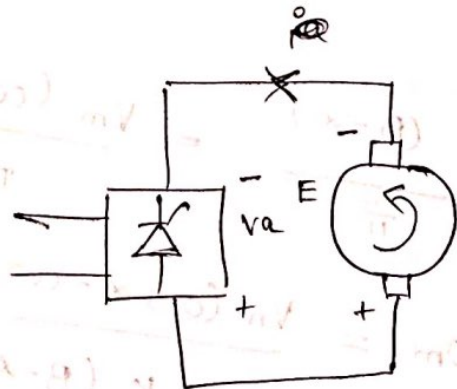

$$\alpha > 90, \omega_m < 0.$$

① A $200V$, 875 rpm , $150A$ separately excited dc motor has an arm resistance of 0.06Ω . It is fed from a 1ϕ fully controlled rectifier with an ac source voltage of $220V$, 50Hz . Assume continuous conduction, calculate

- (i) α for rated motor torque and 600 rpm
 (ii) α for rated motor torque and 750 rpm
 (iii) motor speed for $\alpha = 160^\circ$ and rated torque.

(i) E_1 - rated $E_1 = V - i_a R_a = 200 - (150 \times 0.06) = 191V$.

$E_1 = 191V$, $N_1 = 875 \text{ rpm}$.

$E_2 = ?$, $N_2 = 750 \text{ rpm}$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$E_2 = E_1 \frac{N_2}{N_1} = 191 \times \frac{750}{875} = 163.71V$$

$$\frac{2V_m \cos \alpha}{\pi} = V_a$$

$$V_a = E_2 + i_a R_a = 163.71 + (150 \times 0.06) = 172.71$$

$$V_m = \frac{220\sqrt{2}}{\sqrt{2}} = 220\sqrt{2} = 311.13V$$

$$\cos \alpha = \frac{V_a \pi}{2V_m} = \frac{172.71 \pi}{2 \times 311.13} = 0.8719$$

$$\alpha = 29.31^\circ$$

(ii) E_2 at -500 rpm , $= 191 \times \frac{-500}{875} = -109.14$

$$V_a = E_2 + i_a R_a \Rightarrow -109.14 + (150 \times 0.06) = -100.14$$

$$\cos \alpha = \frac{-100.14 \pi}{2 \times 311.13} = -0.5055$$

$$\alpha = 120.369^\circ$$

(iii) $\alpha = 160^\circ$,

$$\frac{2V_m \cos \alpha}{\pi} = V_a$$

$$V_a = \frac{2(311.13) \cos 160}{\pi} = -186.12 \text{ V}$$

$$E_2 = V_a - I_a R_a \quad E_2 = -186.12 - (150 \times 0.06)$$

$$E_2 = -195.12 \text{ V}$$

$$E_2 = E_1 \frac{N_2}{N_1} \quad ; \quad N_2 = \frac{E_2 N_1}{E_1} = \frac{-195.126}{191} \times 875$$

$$N_2 = -893.90 \text{ rpm}$$

(exercise)
5.36
G.K. Dubey

② A 220V, 1500 rpm, 10A sep exc dc motor is fed from a 1 ϕ FOC with an ac source voltage of 230V, 50Hz. $R_a = 2\Omega$. Conduction can be assumed to be continuous

calculate firing angle for
(i) half the rated motor torque and 500 rpm.

(ii) rated motor torque and (-1000) rpm.

(i) half the rated motor torque,

$$T \propto I_a$$

$$\therefore I_a \Rightarrow I_a/2 \Rightarrow 5 \text{ A}$$

$$E_1 = V - I_a R_a = 220 - (10 \times 2) = 200 \text{ V}$$

$$E_2 = \frac{N_2}{N_1} \times E_1 = \frac{500}{1500} \times 200 = 66.67 \text{ V}$$

$$V_a = E_2 + I_a R_a = 66.67 + (5 \times 2) = 76.67 \text{ V}$$

$$\frac{2V_m \cos \alpha}{\pi} = V_a$$

$$\cos \alpha = \frac{V_a \times \pi}{2V_m} = \frac{76.67 \times \pi}{2 \times 230 \times \sqrt{2}} = 0.3702$$


$$\alpha = 68.86^\circ$$

Multi-quadrant operation of separately excited dc motor fed from fully controlled rectifier.

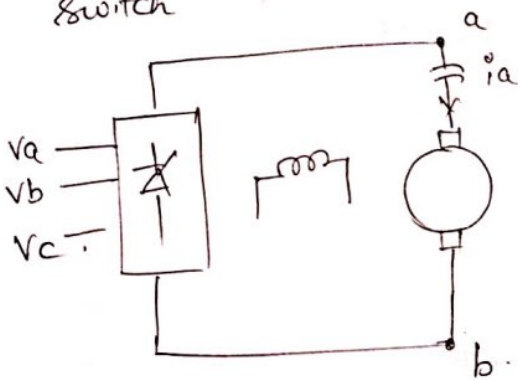- a) 1ϕ fully controlled rectifier with a reversing switch
- b) Dual converter
- c) 1ϕ fully controlled rectifier in the armature with field current reversal.


Fully controlled converter - quadrant I & IV

1ϕ fully controlled rectifier with a reversing switch




→ Reversing switch R_s is used to reverse the arm connection w.r.t to rectifier

→ $i_{ce} \rightarrow$ I and IV


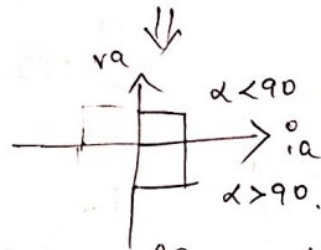


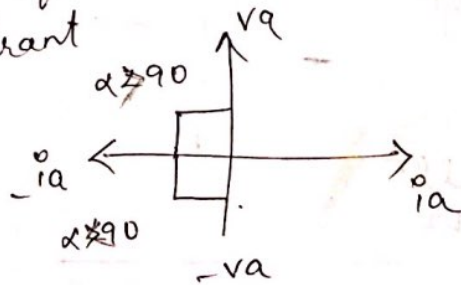→ The reversal of armature connection provides II and III quadrant



The switch can be relay-operated contactor with 2 normally NO and NC closed contactors. (fig a)


using thyristors ^{or} fig (b)

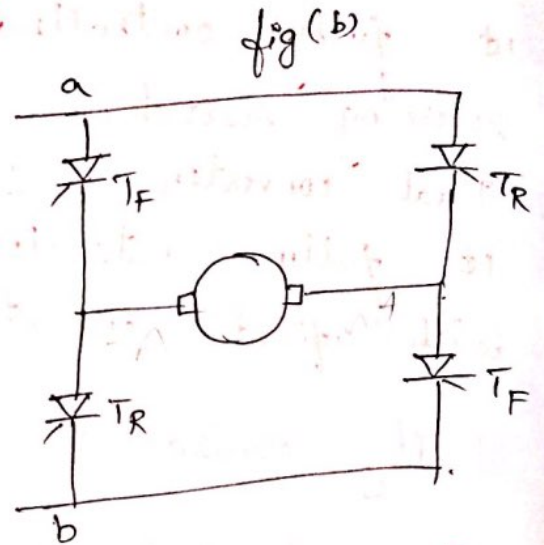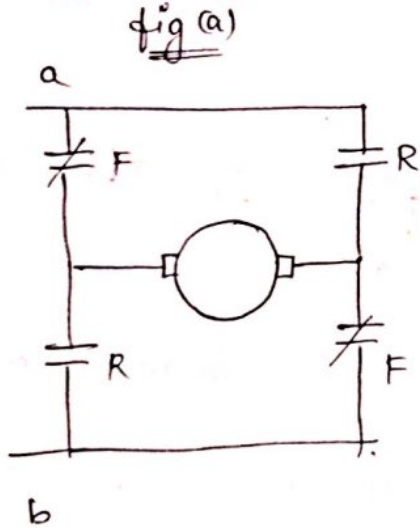

NO - a - F - M - F - b \Rightarrow I & IV
 relay operates NC - a - R - M - R - b

T_F-ON (T_R-OFF) - I & IV
 T_R-ON (T_F-OFF) - III & II

Dual Converter:-

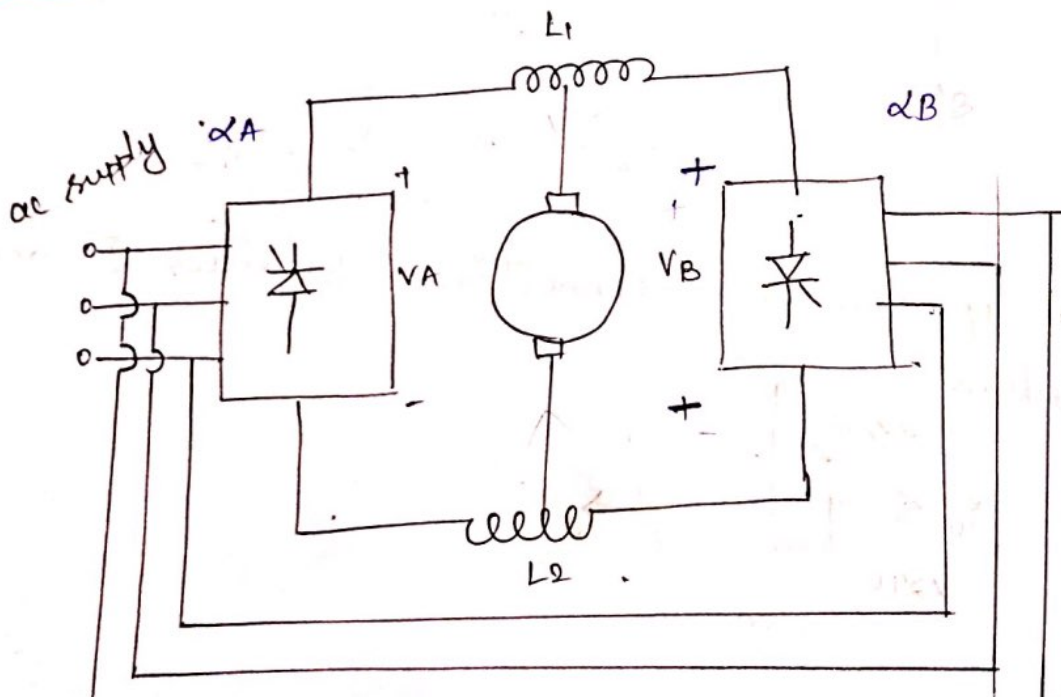

→ 2 fully controlled converters connected in anti-parallel across the armature.

→ Rectifier A - +ve current and +VA and -VA


∴ I and IV quadrant

→ Rectifier B - -ve current and +VB and -VB

∴ II and III quadrant


E =

Refer Bimbra.

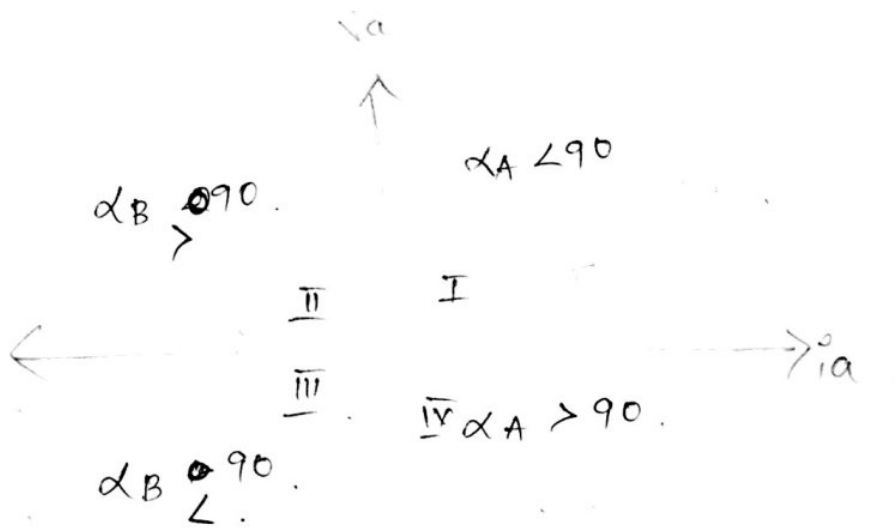

i) circulating current mode / simultaneous mode.
 $\alpha_A + \alpha_B = 180$.


Field current Reversal

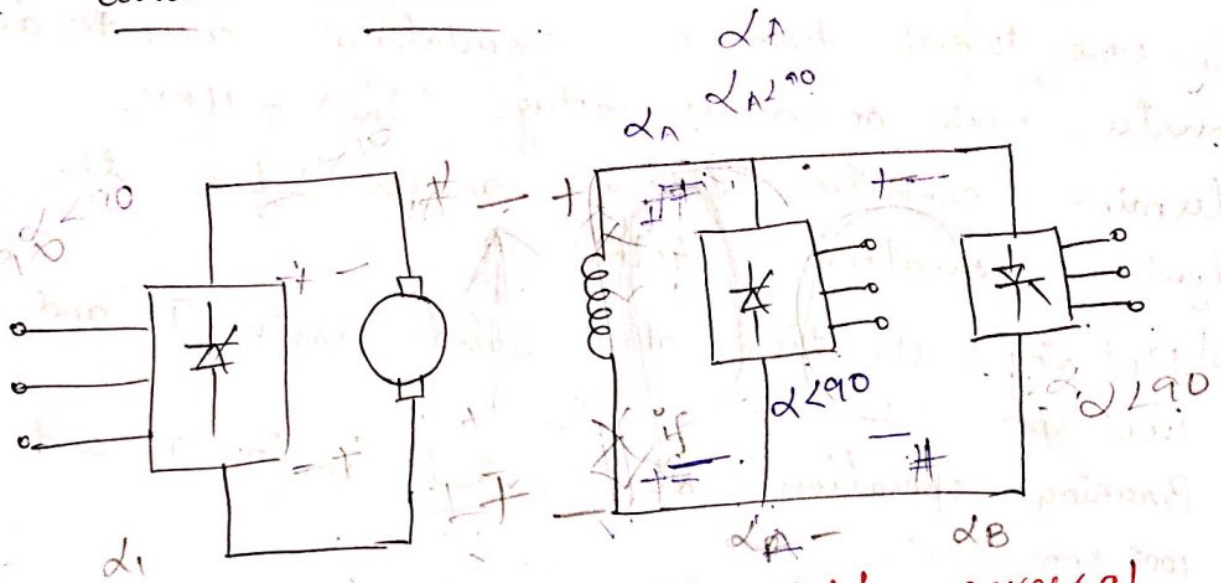


Four quadrant drive with field reversal.

- * With I_f in one direction, \rightarrow Quadrants I and IV
- * When I_f is reversed \rightarrow Quadrants II and III.

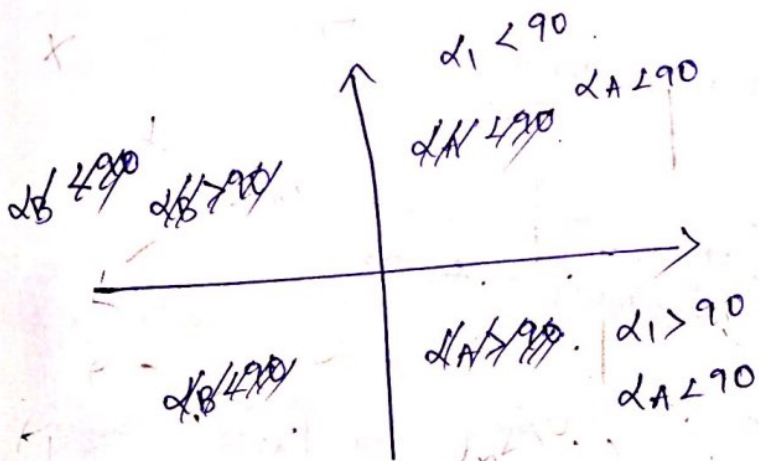\rightarrow The dual converter operates with non-simultaneous control.



Regenerative Braking

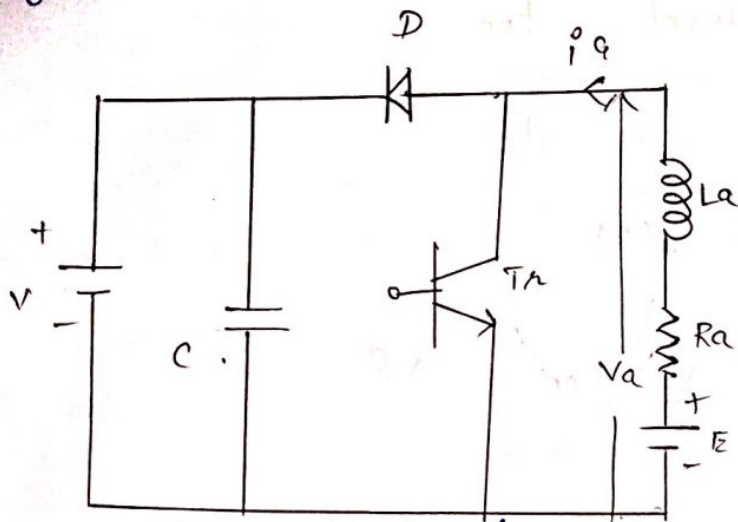

Energy Storage interval

→ When T_r is on ($0 \leq t \leq t_{on}$), the o/p voltage

is zero. $V_o = V_a = 0$

→ Though $V_a = 0$, voltage E drives current thro L_a and T_r .

→ L_a stores energy during t_{on} .

→ i_a ↑ from i_{a1} to i_{a2} .


Duty interval = ($t_{on} \leq t \leq T$)

→ When T_r is off, $V_o = E + L_a \frac{di_a}{dt} = V$

$\therefore V > V_a$


bcz of this, D is forward biased and begins conduction, thus allowing power flow to the source.

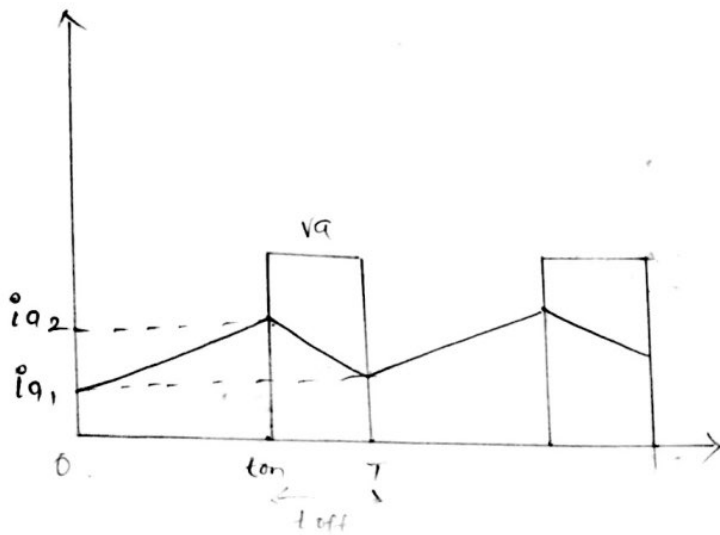→ i_a flows thro D , and source V and reduces from i_{a2} to i_{a1} .



$$\delta = \frac{\text{duty interval}}{T} = \frac{t_{\text{on}}}{T} = \frac{T - t_{\text{off}}}{T}$$

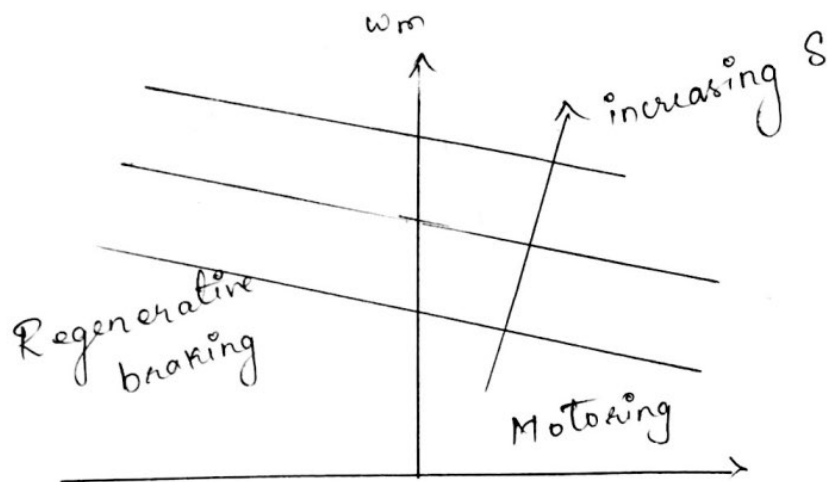$V_a = \frac{1}{T} \int_{t_{\text{on}}}^T v \, dt = \frac{V}{T} (T - t_{\text{off}})$



$$V_a = V \left(1 - \frac{t_{\text{off}}}{T}\right) = V(1 - \delta) \quad \text{where } \delta = 1 - \frac{t_{\text{off}}}{T}$$

$$E_g = K \omega_m$$

$$T = -K I_a \quad (\because I_a \text{ is reversed})$$

$$\omega_m = \frac{V_a + I_a R_a}{K} = \frac{V(1 - \delta) + R_a I_a}{K}$$

$$\omega_m = \frac{V\delta + R_a I_a}{K}$$

1a) Operation with unbalanced source voltage, and single phasing

Let V_a, V_b and V_c be unbalanced supply voltage.

This set of unbalanced voltages can be resolved into 3 ϕ balanced +ve sequence V_p , -ve sequence V_n and zero sequence V_0 (symmetrical components relationships)

$$V_p = \frac{1}{3} [V_a + \alpha V_b + \alpha^2 V_c]$$

$$V_n = \frac{1}{3} [V_a + \alpha^2 V_b + \alpha V_c]$$

$$V_0 = \frac{1}{3} [V_a + V_b + V_c]$$

$$\alpha = e^{j120} \Rightarrow \cos 120 + j \sin 120.$$

Assume m/c without neutral connection.

- +ve sequence voltage have same phase sequence, as that of original system.
- -ve sequence voltage - opposite phase sequence.
- in the absence of neutral connection, zero sequence line voltages are zero.

Calculate motor performance for +ve and -ve sequence separately.

* Resultant performance of motor can be obtained by using super-position principle.

POSITIVE SEQUENCE

→ +ve sequence voltage produce an air-gap flux which rotates at syn speed in forward direction.

Let ω_m - forward direction.

$$s = \frac{\omega_{ms} - \omega_m}{\omega_{ms}}$$

$$\omega_m = s\omega_{ms} \quad s\omega_{ms} = \omega_{ms} - \omega_m$$

$$\omega_m = \omega_{ms} - s\omega_{ms}$$

$$\boxed{\omega_m = \omega_{ms}(1-s)} \quad \text{--- (1)}$$

Equivalent ckt are same,

$$\therefore I_{sp}' = \frac{V_p}{(R_s + \frac{R_r'}{s}) + j(X_s + X_r')} \quad \text{--- (2)}$$

$$T_p = \frac{3}{\omega_{ms}} \left[\frac{V_p^2 \frac{R_r'}{s}}{(R_s + \frac{R_r'}{s})^2 + (X_s + X_r')^2} \right] \quad \text{--- (3)}$$

NEGATIVE SEQUENCE

-ve sequence produces air gap flux which rotates at syn speed in reverse direction.

$$s_n = \frac{-\omega_{ms} - \omega_m}{-\omega_{ms}}$$

$$= \frac{-\omega_{ms} - [\omega_{ms}(1-s)]}{-\omega_{ms}} \quad \leftarrow \text{using (1)}$$

$$= \frac{-W_{ms} - W_{ms} + W_{ms} s}{-W_{ms}} = 1 + 1 - s = 2 - s$$

$$\therefore \boxed{S_n = 2 - s} \quad \text{--- (4)}$$


Egn (4) represents slip for -ve sequence.
 Replace s by $(2-s)$ in rotor current and torque equations.

$$I_{rn} = \frac{V_n}{R_s + \frac{R_r'}{(2-s)} + j(X_s + X_r')} \quad \text{--- (5)}$$

$$T_n = \frac{3}{W_{ms}} \left[\frac{V_n^2 R_r' / (2-s)}{\left[R_s + \frac{R_r'}{(2-s)} \right]^2 + (X_s + X_r')^2} \right] \quad \text{--- (6)}$$

Rotor current $\Rightarrow I_r' = I_{rp}' + I_{rn}'$
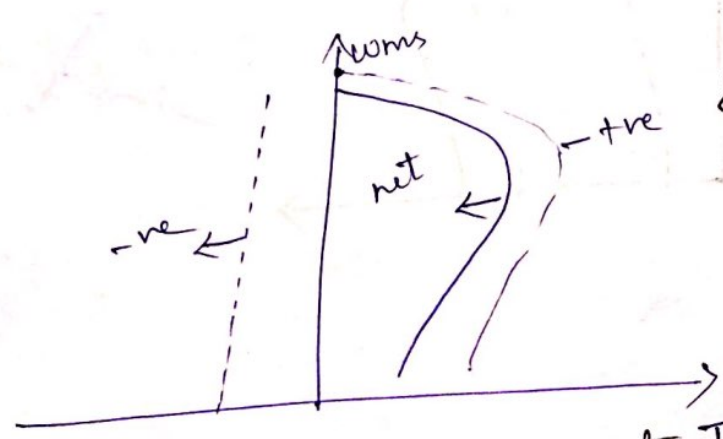
$$T = T_p + T_n = \frac{3}{W_{ms}} \left[\frac{V_p^2 R_r' / s}{\left(R_s + \frac{R_r'}{s} \right)^2 + (X_s + X_r')^2} + \frac{V_n^2 R_r' / (2-s)}{\left[R_s + \frac{R_r'}{(2-s)} \right]^2 + (X_s + X_r')^2} \right]$$



Torque capacity is reduced and cu losses are increased to satisfy load demand, motor will draw more current from the supply.

\therefore to prevent burning of the motor, it is not allowed to run for prolonged period when voltage unbalance is $> 5\%$.

$$T_{max} = \frac{3 I_r^2 R_r' / S_m}{\omega_{ms}} \quad S = S_m = \frac{-R_r'}{\sqrt{R_s^2 + (X_s + X_r')^2}}$$

A 400V, λ -connected 3 ϕ , 6-pole, 50Hz IM has following parameters referred to stator
 $R_s = R_r' = 1\Omega$, $X_s = X_r' = 2\Omega$.

For regenerative braking, determine.

- (i) max torque (overhauling) it can hold and range of speed for safe operation.
- (ii) speed at which it can hold an overhauling load with a torque of 100N-m.

$$N_s = \frac{120 \times 50}{6} = 1000$$

$$\omega_{ms} = \frac{2\pi \times 1000}{60} = 104.71 \text{ rad/sec}$$

$$N_s = \frac{120f}{P}$$

$$\frac{2\pi N_s}{60} = \omega_{ms}$$

$$\frac{120f \times 2\pi \times N_s}{60}$$

$$N_s = \frac{60 \times \omega_{ms}}{2\pi}$$

$$= \frac{30 \omega_{ms}}{\pi}$$

$$S_m = \frac{-R_r'}{\sqrt{R_s^2 + (X_s + X_r')^2}} = \frac{-1}{\sqrt{1 + (2+2)^2}}$$

$$= \frac{-1}{4.123} = -0.2425$$

$S_m = -0.2425$

$$I_r' = \frac{V^2}{\left(R_s + \frac{R_r'}{s}\right)^2 + (X_s + X_r')^2} = \frac{(400/\sqrt{3})^2}{\left[1 + \frac{1}{(-0.2425)}\right]^2 + (2+2)^2}$$

$$= \frac{53\,333.33}{9.7575 + 16} = 2070.594 \text{ A}$$

$$I_r' = 45.5 \text{ A}$$

$$T_{\max} = \frac{3 I_r'^2 R_r'}{s} = \frac{3 \times (45.5)^2 \times 1}{(-0.2425)} = -244.59$$

Wms 104.71

$$T_{\max} = -244.59 \text{ Nm}$$

$$N_m \omega_m = (1-s) \omega_{ms} = [1 - (-0.2425)] 1000$$

$$= 1.2425 (1000)$$

$$N \omega_m = 1242.5 \text{ rpm}$$

(ii) $T_{\max} = 100 \text{ Nm}$

$$T = \frac{3 R_r'}{s} \frac{V^2}{\left(R_s + \frac{R_r'}{s}\right)^2 + (X_s + X_r')^2}$$

$$100 = \frac{3 (1)}{104.71 (s)} \left[\frac{(400/\sqrt{3})^2}{\left(1 + \frac{1}{s}\right)^2 + 16} \right]$$

$$100 = \frac{0.02}{s} \left[\frac{230.9^2}{1 + \frac{1}{s^2} + \frac{2}{s} + 16} \right]$$

→ Inner current loop is provided to limit the converter & motor current or torque below a safe limit.

Supply Frequency Control (V/f const)

$$N = N_s (1-s)$$

$$= \frac{120f}{P} (1-s)$$

f changes $\rightarrow N_s$ changes $\rightarrow s$ changes $\rightarrow N$ changes.

Let E_1 be the induced voltage in stator winding of IM

$$E_1 = 4.44 f \phi T K$$

K - winding factor

T - no of turns in stator winding

f - i/p supply freq.

$$E_1 \propto f \phi$$

$$\frac{E_1}{\phi} \propto f$$

$f \downarrow$, E_1 - const, $\phi \uparrow$

→ The increase in flux will saturate the motor
 → This will \uparrow , magnetizing current, distort line voltage and current, \uparrow I_s cu loss and core loss, produces noise.

→ $\therefore \uparrow$ in flux is undesirable from the consideration of saturation effects.

∴ the variable f_{sc} comes out at rated f_{sc} in generally varying terminal voltage with f_{sc} plus by varying ratio is maintained const. such that $\frac{V}{f}$ and f_{sc} .

For rated voltage and f_{sc} ,

$$T_{\text{more}} = \frac{3}{2I_{\text{rms}}} \left[\frac{V^2}{R_s \pm \sqrt{R_s^2 + (X_s + X_s')^2}} \right] \quad \text{--- (1)}$$

$$I_{\text{rms}} = \frac{4\pi f}{P} ; X_s = 2\pi f L_s, X_s' = 2\pi f L_s'$$

$$= \frac{3}{2 \left(\frac{4\pi f}{P} \right)} \left[\frac{V^2}{R_s \pm \sqrt{R_s^2 + (2\pi f L_s + 2\pi f L_s')^2}} \right]$$

$$= \frac{3P}{8\pi f} \left[\frac{V^2}{R_s \pm \sqrt{R_s^2 + 4\pi^2 f^2 (L_s + L_s')^2}} \right]$$

$$= K \frac{V^2}{f \times f} \left[\frac{1}{R_s \pm \sqrt{R_s^2 + 4\pi^2 (L_s + L_s')^2}} \right]$$

$$= K \left[\frac{\left(\frac{V}{f} \right)^2}{\frac{R_s}{f} \pm \sqrt{\left(\frac{R_s}{f} \right)^2 + 4\pi^2 (L_s + L_s')^2}} \right] \quad \text{--- (2)}$$


When f is not low,

$$\frac{R_s}{f} \ll 2\pi (L_s + L_s')$$


$$T_{max} = \pm K \left(\frac{V}{f} \right)^2 \frac{1}{8\pi (L_s + L_r)}$$

(3)

$$T_{max} \propto \frac{K}{f}$$

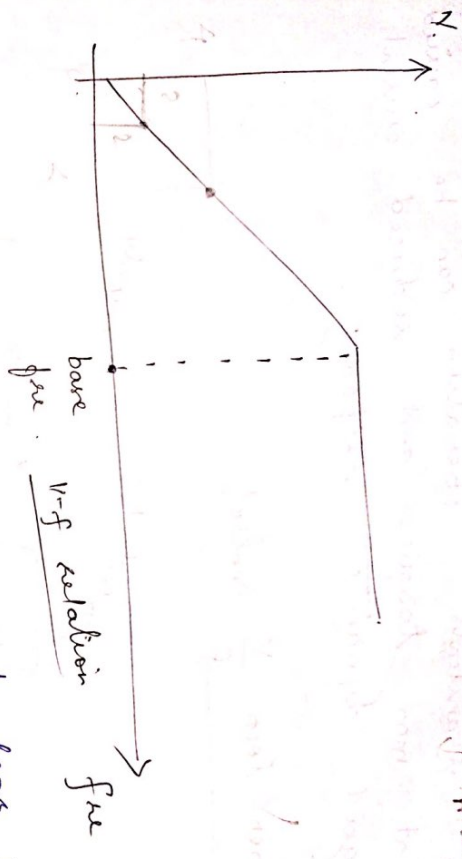

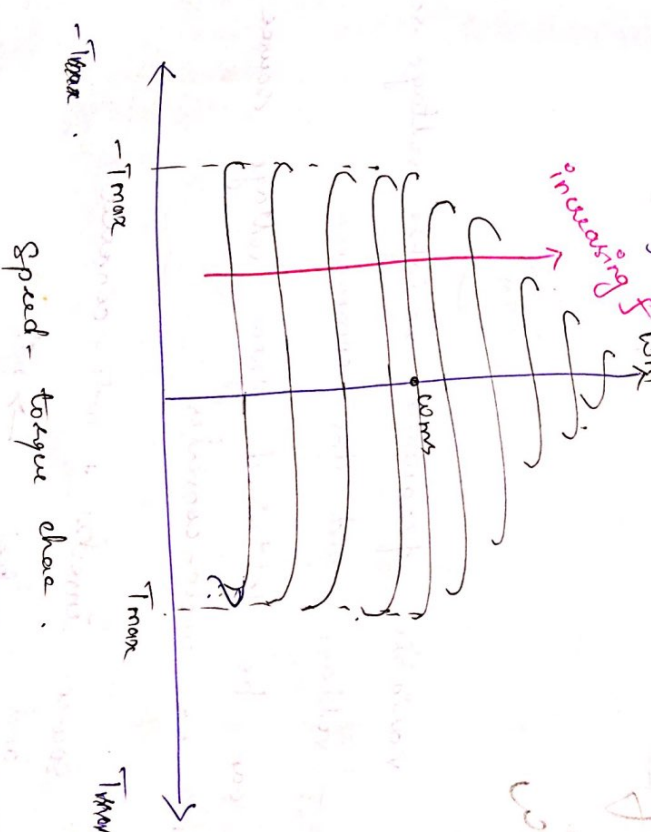→ with const $\frac{V}{f}$ ratio, motor develops max torque




with const $\frac{V}{f}$ ratio, motor develops max torque

Advantages :-

- Speed control and braking available from 300 to above base speed. operation can be carried out during at max torque and reduced current return good dynamic response.

Open-loop $\frac{V}{f}$ control

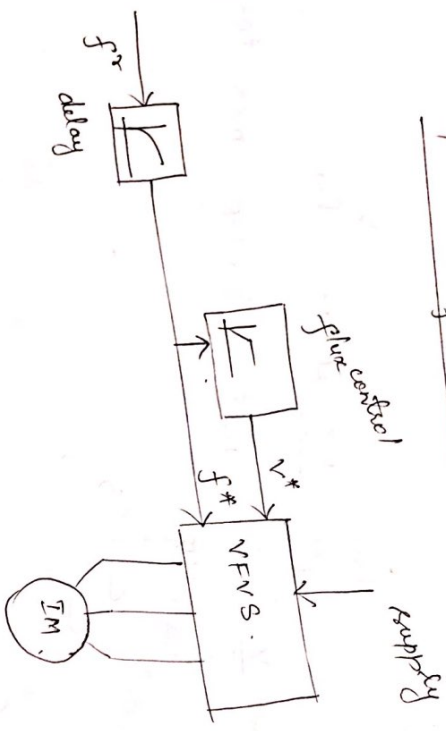

VENS - variable frequency variable voltage source
 V^* , f^* - voltage and frequency commands.

VENS - can be obtained from voltage source inverter or cyclo-converter.


Voltage source inverter + cyclo-converter and closed-loop control → ppt
 current source inverter

Voltage Source Inverter Control :- VSI

Variable frequency and variable voltage supply for IM control can be obtained either from a voltage source inverter (VSI) or a cycloconverter.

VSI IM Drives :-

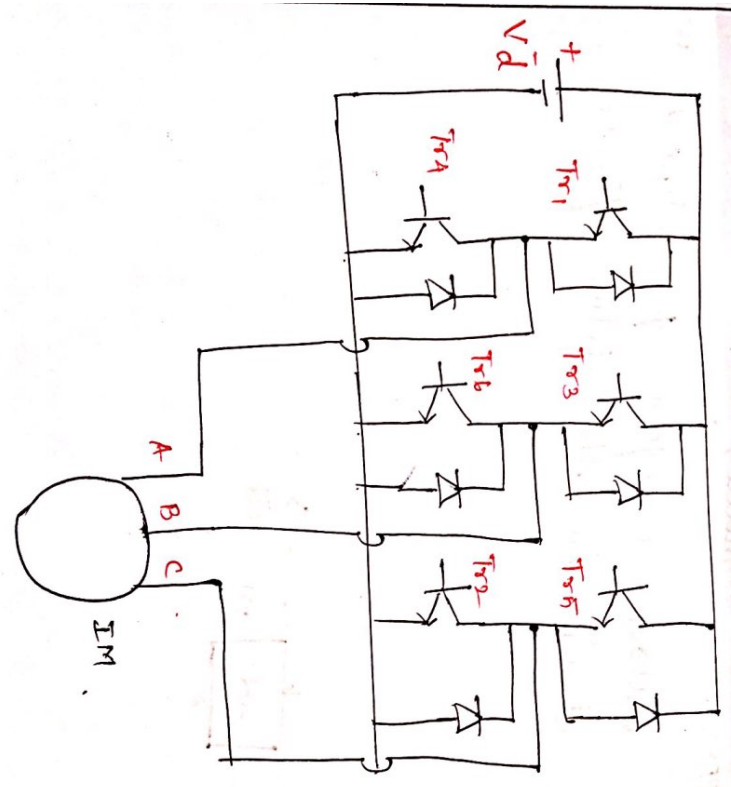⇒ VSI allows a variable frequency from dc supply transistor inverter fed IM drive is shown in the below figure.




⇒ instead of transistors, any other self commutated devices [MOSFET (low voltage and low power), IGBT, GTO, IGBT - high power level can be used].

⇒ VSI can be operated as stepped wave inverter or a PWM inverter.

* For a given time period T (one cycle), each device is on for $T/2$ duration, in which all the devices are switched in the sequence of their numbers with a time difference of $T/6$.

* frequency is varied by varying T and o/p voltage is varied by varying dc ip voltage (chopper is required).

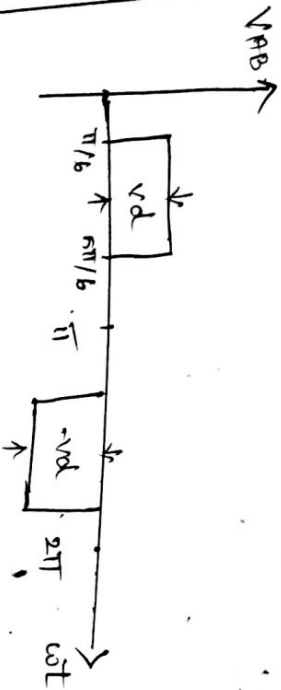The line voltage waveform for stepped wave inverter is shown in the below figure.



The o/p line voltage and phase voltage are given by following expressions :-

$$V_{AB} = \frac{2\sqrt{3}}{\pi} V_d \left[\sin \omega t - \frac{1}{5} \sin 5\omega t - \frac{1}{7} \sin 7\omega t + \frac{1}{11} \sin 11\omega t + \frac{1}{13} \sin 13\omega t \dots \right]$$

$$V_{AN} = \frac{2V_d}{\pi} \left[\sin \omega t + \frac{1}{5} \sin 5\omega t + \frac{1}{7} \sin 7\omega t \dots \right]$$

The rms value of fundamental phase voltage,

$$V = \frac{V_{AN}}{\sqrt{2}} = \frac{\sqrt{2}}{\pi} V_d$$

Drawbacks of stepped wave inverter fed IM drive :-

[Large harmonics of low frequency] High motor

i) Large amt of low freq harmonics - High motor losses due to motion of the rotor


ii) Results in jerky torque. Torque is more at low harmonic pulsating current component - limiting

iii) Harmonic results in overheating - 40% of rated value speeds - results in around 40% of rated value lowest speeds mentioned drawbacks are

All the above pulse width modulation

eliminated using technique

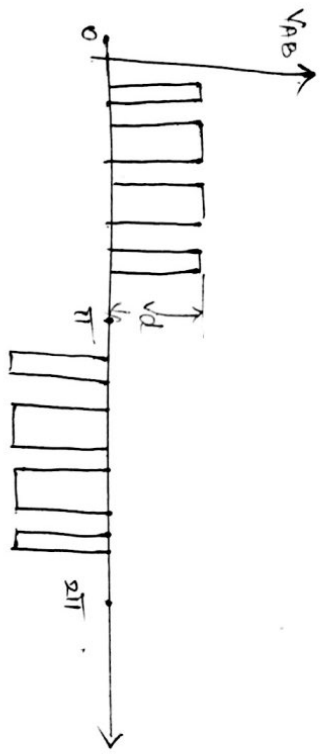The line voltage for PWM inverter is shown below,







Since o/p can be directly varied by PWM, no arrangement is required for variation of i/p voltage.

The fundamental component of o/p voltage is given by

$$V = \frac{m V_d}{2\sqrt{2}}$$

where "m" is the modulation index.

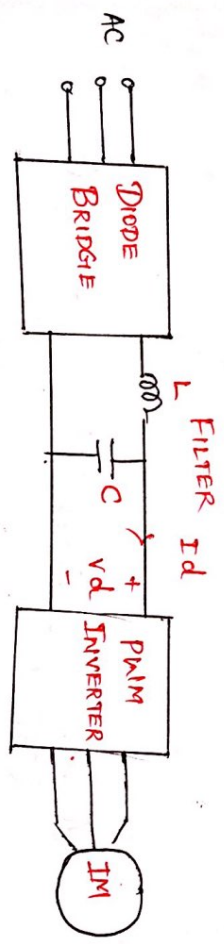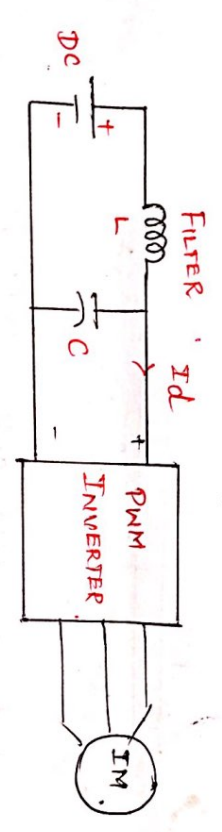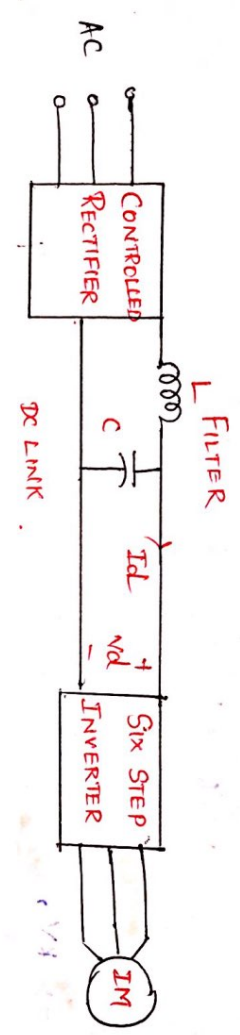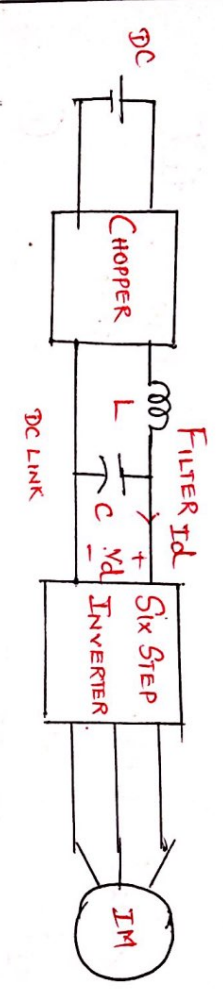The various configurations of VSI connected IM drives are shown below,




-x- for braking and multiquadrant operation of VSI IM drive refer slides (PPT).

$$T \propto \frac{V^2 R_s'}{s}$$

$$T \propto \frac{R_s'}{s}$$

$R_s' \uparrow$, to maintain const torque, $s \uparrow$, $N \downarrow$.

Static Potor Resistance Control

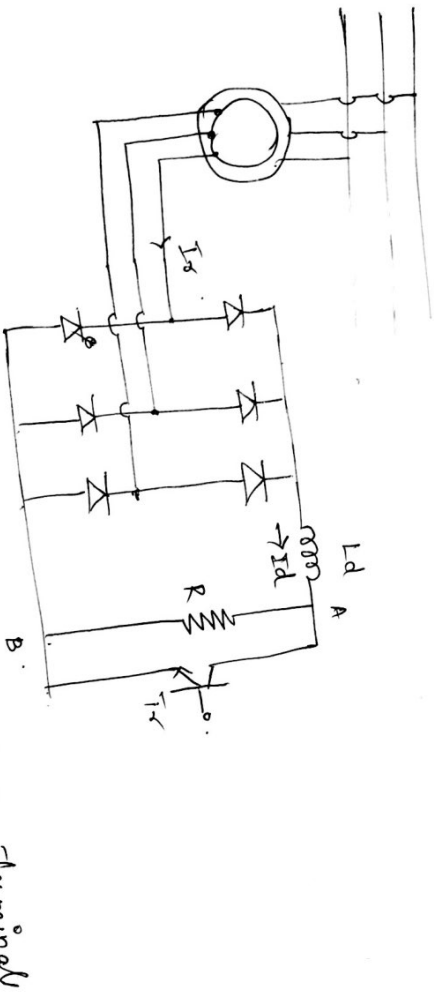

→ The value of R_{AB} across A and B terminal can be varied by varying the duty ratio

of T_1 .
 → Thus rotor ckt resistance is varied.
 → L_d is to reduce ripple and dis continuity in the dc link current.

$$R_{AB} = (1 - \beta) R$$

$$s = \frac{T_m}{T}$$

$$s = 0 \rightarrow R$$

$$s = 1 \rightarrow R_{AB} = 0$$

power consumed by R_{AB}
 $P_{AB} = I_d^2 R_{AB} = I_d^2 R(1-s)$

$$I_s = \sqrt{\frac{3}{2}} I_d$$

$$I_d^2 = \frac{2}{3} I_s^2$$


$$P_{AB} = I_d^2 R(1-s) = \frac{2}{3} I_s^2 R(1-s)$$

$$P_{AB} \text{ per phase} = \frac{1}{2} I_s^2 R(1-s)$$

$$\begin{aligned} \text{Total a.c. } P \text{ per phase} &= P_{sT} \\ &= R_s + 0.5R(1-s) \end{aligned}$$

when $s = 1$, $R_{sT} = R_s$
 $s = 0$, $R_{sT} = R_s + 0.5R$

Closed Loop Speed Control

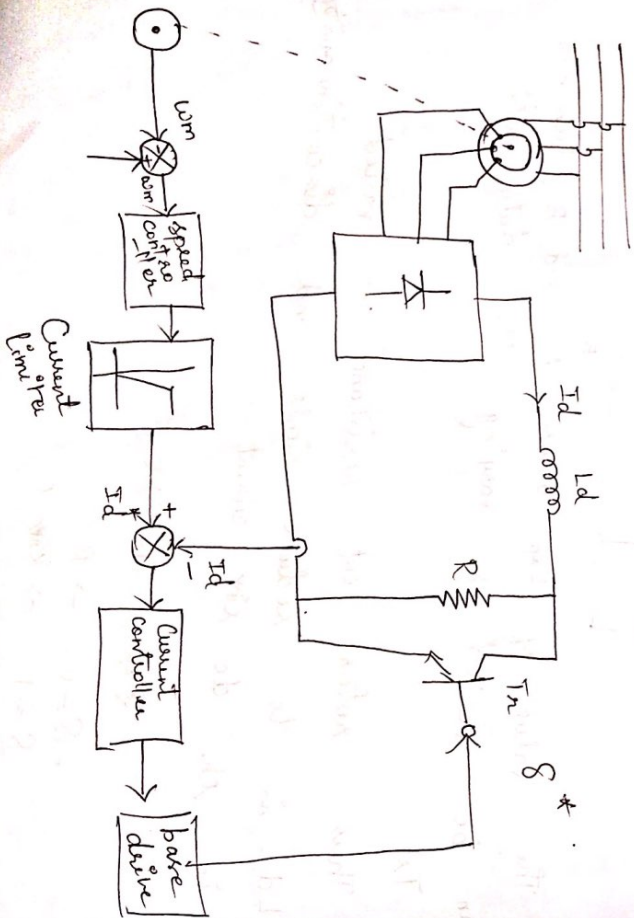

The process of pulling rotor into step with the rotating field is called pull in or synchronisation.

Starting :-

1) start syn motor as IM with field unexcited

Pull in :- already defined,

→ things to note

→ starting current can be high (starters)

→ during acc as an IM, becoz of large no of turns in field winding, the induced voltage may reach several thousands - insulation breakdown - to avoid this situation, field ckt should be closed thro small discharge R before dc excitation.


Transients :

steady state stability

dynamic stability

$$T = T_{max} \sin \delta$$
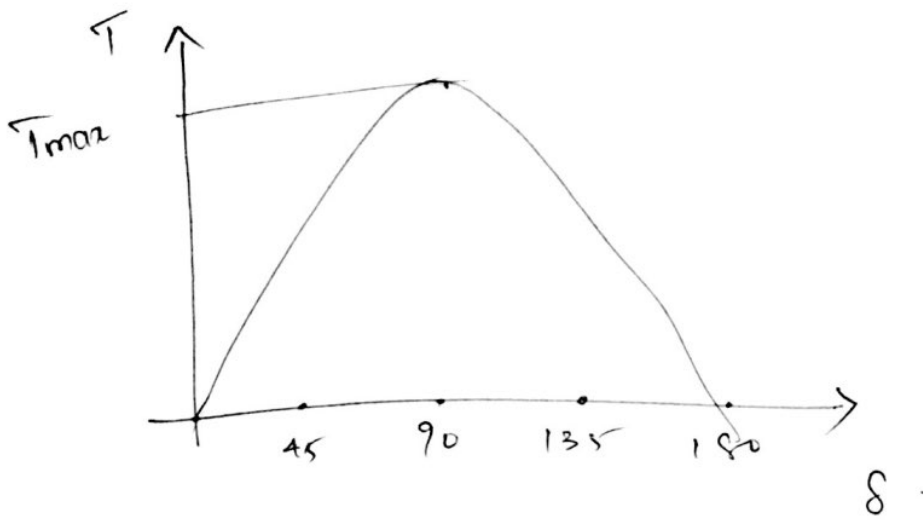
$$T_{max} = \frac{3VE}{\omega_{ms} X_s}$$



$$T_m = T_L + J \frac{d\omega_m}{dt} = 0$$

T_L is slowly applied.

Dynamic Stability

$$T = T_{max} \sin \delta$$

$$T_{max} = \frac{3VEI}{X_S \omega_{ms}}$$

$$T_m = T_L + J \frac{d\omega_m}{dt}$$


$$= T_L + T_a + T_d$$

T_a - acceleration torque - $K_j \frac{d^2 \delta}{dt^2}$

T_d - dyn damping u - $K_d \frac{d\delta}{dt}$

$$\therefore K_j \frac{d^2 \delta}{dt^2} + K_d \frac{d\delta}{dt} + T_L - T_{max} \sin \delta = 0.$$

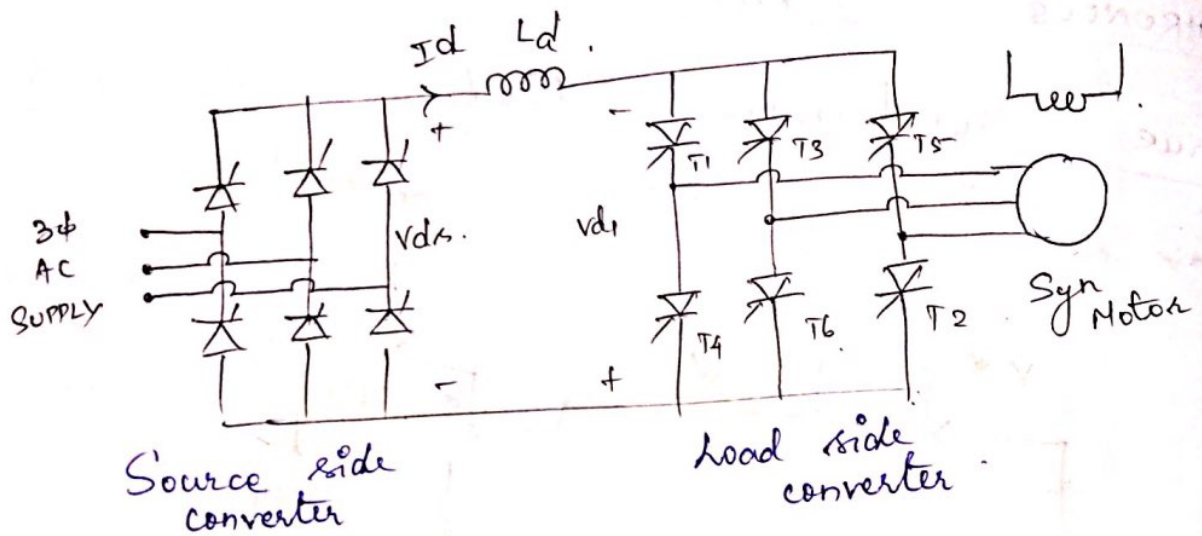Self-controlled synchronous motor drive
employing load commutated thyristor
inverter



Large power drives - wound field SM
 Medium power drives - PM SM

Source-side converter - line commutated thyristor converter.

↳ $0 < \alpha_s < 90$ - rectifier → (+ve) v_{ds} and (+ve) I_d


↳ $90 < \alpha_s < 180$ - inverter → (-ve) v_{ds} and (+ve) I_d

When synchronous motor operates in leading PF, the thyristors (load side) can be commutated by the motor induced voltages in the same way as thyristors of line-commutated converters.

Commutation of thyristors by induced load voltage is known as load commutation.

Motoring operation :- $0 < \alpha_s < 90$ & $90 < \alpha_L < 180$.

Regenerative braking :- $90 < \alpha_s < 180$ & $0 < \alpha_L < 90$.



* Speed can be changed by control of line side converter firing angle.

* When working as an inverter, the α has to be less than 180° to take care of commutation overlap.

$$\beta_l = 180^\circ - \alpha_l$$

β_l - commutation lead angle for load side converter.

$$\gamma = \beta_l - \mu$$

μ - commutation over-lap.

γ_{min} - thyristor under commutation can be reverse biased for this time duration.

$$I_s = \frac{\sqrt{6}}{\pi} I_d$$

