

Modified.

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EE35

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019

Digital System Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define canonical minterm form and canonical maxterm form. (05 Marks)
- b. Compare between prime implicant and essential prime implicant. Identify all the prime implicants and essential prime implicants of the following functions using k-map :
 $f(a, b, c, d) = \pi_M (0, 2, 3, 8, 9, 10, 12, 14)$. (07 Marks)
- c. Simplify the following boolean function using k-map, and implement by logic gates.
 $f(A, B, C, D, E) = \sum_m (3, 7, 10, 11, 12, 13, 14, 15, 17, 19, 21, 23, 25, 27, 28, 29, 31) + \sum_d (2, 6, 26, 30)$ (08 Marks)

OR

- 2 a. Convert the given boolean function into minterm canonical form.
 $f(a, b, c) = (\bar{a} + b)(b + \bar{c})$. (05 Marks)
- b. Simplify the following boolean function using k-map
 $f(P, Q, R, S) = \sum_m (0, 2, 4, 5, 6, 8, 10, 15) + \sum_d (7, 13, 14)$. (07 Marks)
- c. Using Quine – McCluskey method, obtain a minimal SOP expression for
 $f(a, b, c, d) = \sum_m (2, 3, 4, 5, 13, 15) + \sum_d (8, 9, 10, 11)$. (08 Marks)

Module-2

- 3 a. Design two bit magnitude comparator and draw the logic diagram. (10 Marks)
- b. Write a short note on encoders. (05 Marks)
- c. Design full adder using two numbers of 4:1 MUX. (05 Marks)

OR

- 4 a. Explain look ahead carry adder. (10 Marks)
- b. Implement following multiple output function using IC74138 and external gates. (05 Marks)
 $F_1 (A, B, C) = \sum_m (1, 4, 5, 7)$ and $F_2 (A, B, C) = \pi_m (2, 3, 6, 7)$.
- c. Design 16:1 multiplexer using 8:1 MUX. (05 Marks)

Module-3

- 5 a. Explain the working of master slave JK flip-flops with functional table and timing diagram. Show how race around condition is overcome. (08 Marks)
- b. Obtain characteristic equation of SR flip-flop. (05 Marks)
- c. Explain working of 3-bit binary ripple counter with the suitable logic and timing diagram. (07 Marks)

OR

- 6 a. Convert JK flip-flop to D flip flop. (05 Marks)
- b. Explain the 4 modes of operation of shift register with suitable logic diagram and truth table. (08 Marks)
- c. Design MOD – 6 synchronous counter using D flip-flop. (07 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-4

- 7 a. Analyze the following sequential circuit given in Fig Q7(a) and obtain excitation, transition and state table. Also write the state diagram.

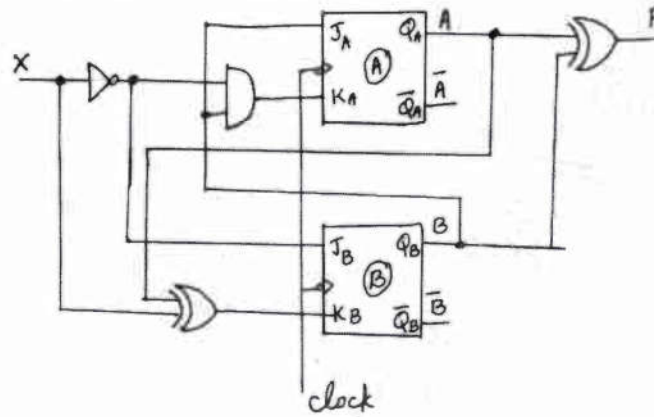


Fig Q7(a)

(12 Marks)

- b. Design a synchronous counter with the sequence 0, 1, 3, 7, 6, 4, 0 using JK flip-flop. (08 Marks)

OR

- 8 a. Design a clocked sequential circuit that operates according to the state diagram shown in Fig Q8 (a) implement the circuit using D flip flop.

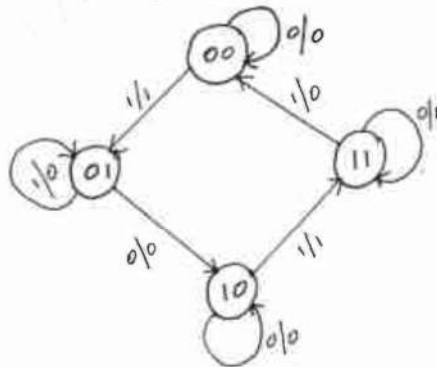


Fig Q8(a)

(12 Marks)

- b. With the help of block diagram explain Mealy and Moore model in a sequential circuit analysis. Give the example circuits. (08 Marks)

Module-5

- 9 a. Write the comparison between VHDL and verilog. (08 Marks)
 b. Explain the various data types available in VHDL. (06 Marks)
 c. Write HDL code of a 2×1 multiplexer – VHDL. (06 Marks)

OR

- 10 a. Write a data flow description for a full adder with active high enable in both VHDL and verilog. (08 Marks)
 b. Explain shift and rotate operators in HDL with an example. (08 Marks)
 c. Explain the structure of verilog module. (04 Marks)





Scheme & Solution

Signature of Scrutinizer

Subject Title: Digital System Design

Subject Code: 17EE35

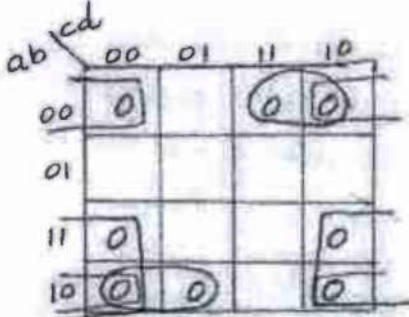
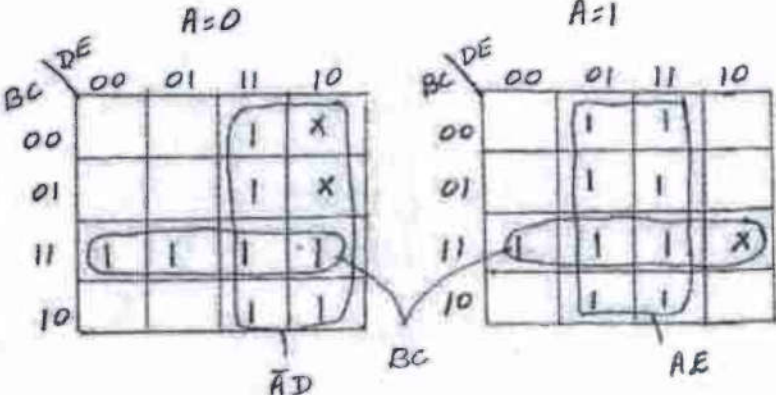
Question Number	Solution	Marks Allocated
1 (a)	Definition with example expression for canonical minterm form canonical maxterm form	-5M-
1 (b)	Comparison between prime implicant and essential prime implicant $f = \prod M(0, 2, 3, 8, 9, 10, 12, 14)$  Prime implicants & essential prime implicants: $(a+b+c)(\bar{a}+b+c)$ $(\bar{a}+d)(b+d)$	-2M- 5M-
1 (c)	 $f = \bar{A}D + BC + AE$ - logic diagram -	-4M- -2M- 2M


"APPROVED"

 Registrar (Evaluation)
 Visvesvaraya Technological University
 BELAGAVI - 590018

Question Number	Solution	Marks Allocated																																																																																														
(2) a.	$f(a,b,c) = (\bar{a}+b)(b+\bar{c})$ $= abc + ab\bar{c} + \bar{a}bc + \bar{a}b\bar{c} + \bar{a}\bar{b}\bar{c}$ $= \sum m(0, 2, 3, 6, 7)$	-5M-																																																																																														
(b)	<table border="1" data-bbox="251 451 617 787"> <tr> <td></td> <td>RS</td> <td>00</td> <td>01</td> <td>11</td> <td>10</td> </tr> <tr> <td>PQ</td> <td>00</td> <td>1</td> <td></td> <td></td> <td>1</td> </tr> <tr> <td></td> <td>01</td> <td>1</td> <td>1</td> <td>x</td> <td>1</td> </tr> <tr> <td></td> <td>11</td> <td></td> <td>x</td> <td>1</td> <td>x</td> </tr> <tr> <td></td> <td>10</td> <td>1</td> <td></td> <td></td> <td>1</td> </tr> </table> <p>answers:</p> <p>(1) $\bar{p}q + qs + \bar{q}\bar{s}$ OR</p> <p>(2) $\bar{p}q + qr + \bar{q}\bar{s}$ OR</p> <p>(3) $\bar{p}\bar{s} + qst + \bar{q}\bar{s}$</p>		RS	00	01	11	10	PQ	00	1			1		01	1	1	x	1		11		x	1	x		10	1			1	-5+2M-																																																																
	RS	00	01	11	10																																																																																											
PQ	00	1			1																																																																																											
	01	1	1	x	1																																																																																											
	11		x	1	x																																																																																											
	10	1			1																																																																																											
(c)	<p>Quine McCluskey method.</p> <table data-bbox="251 892 592 1438"> <tr> <td>①</td> <td>minterm</td> <td>binary</td> </tr> <tr><td></td><td>m₂</td><td>0010</td></tr> <tr><td></td><td>m₄</td><td>0100</td></tr> <tr><td></td><td>m₈</td><td>1000</td></tr> <tr><td></td><td>m₃</td><td>0011</td></tr> <tr><td></td><td>m₅</td><td>0101</td></tr> <tr><td></td><td>m₉</td><td>1001</td></tr> <tr><td></td><td>m₁₀</td><td>1010</td></tr> <tr><td></td><td>m₁₁</td><td>1011</td></tr> <tr><td></td><td>m₁₃</td><td>1101</td></tr> <tr><td></td><td>m₁₅</td><td>1111</td></tr> </table> <table data-bbox="682 892 1047 1543"> <tr> <td>②</td> <td>minterm</td> <td>binary</td> </tr> <tr><td></td><td>(2,3)✓</td><td>001-</td></tr> <tr><td></td><td>(2,10)✓</td><td>-010</td></tr> <tr><td></td><td>(4,5)</td><td>010-</td></tr> <tr><td></td><td>(8,10)✓</td><td>10-0</td></tr> <tr><td></td><td>(8,9)-</td><td>100-</td></tr> <tr><td></td><td>(3,11)✓</td><td>-011</td></tr> <tr><td></td><td>(5,13)</td><td>-101</td></tr> <tr><td></td><td>(9,13)✓</td><td>1-01</td></tr> <tr><td></td><td>(9,11)✓</td><td>10-1</td></tr> <tr><td></td><td>(10,11)✓</td><td>101-</td></tr> <tr><td></td><td>(13,15)✓</td><td>11-1</td></tr> <tr><td></td><td>(11,15)✓</td><td>1-11</td></tr> </table> <table data-bbox="292 1564 641 1795"> <tr> <td></td> <td>minterm</td> <td>binary</td> </tr> <tr><td></td><td>(2,3,10,11)</td><td>-01-</td></tr> <tr><td></td><td>(8,9,10,11)</td><td>10--</td></tr> <tr><td></td><td>(9,11,13,15)</td><td>1--1</td></tr> </table> <p>Prime implicants</p> <table data-bbox="771 1564 1112 1879"> <tr><td>$\bar{a}b\bar{c}$</td><td>(4,5)</td></tr> <tr><td>$b\bar{c}d$</td><td>(5,13)</td></tr> <tr><td>$\bar{b}c$</td><td>(2,3,10,11)</td></tr> <tr><td>$a\bar{b}$</td><td>(8,9,10,11)</td></tr> <tr><td>$a\bar{d}$</td><td>(9,11,13,15)</td></tr> </table>	①	minterm	binary		m ₂	0010		m ₄	0100		m ₈	1000		m ₃	0011		m ₅	0101		m ₉	1001		m ₁₀	1010		m ₁₁	1011		m ₁₃	1101		m ₁₅	1111	②	minterm	binary		(2,3)✓	001-		(2,10)✓	-010		(4,5)	010-		(8,10)✓	10-0		(8,9)-	100-		(3,11)✓	-011		(5,13)	-101		(9,13)✓	1-01		(9,11)✓	10-1		(10,11)✓	101-		(13,15)✓	11-1		(11,15)✓	1-11		minterm	binary		(2,3,10,11)	-01-		(8,9,10,11)	10--		(9,11,13,15)	1--1	$\bar{a}b\bar{c}$	(4,5)	$b\bar{c}d$	(5,13)	$\bar{b}c$	(2,3,10,11)	$a\bar{b}$	(8,9,10,11)	$a\bar{d}$	(9,11,13,15)	-5M-
①	minterm	binary																																																																																														
	m ₂	0010																																																																																														
	m ₄	0100																																																																																														
	m ₈	1000																																																																																														
	m ₃	0011																																																																																														
	m ₅	0101																																																																																														
	m ₉	1001																																																																																														
	m ₁₀	1010																																																																																														
	m ₁₁	1011																																																																																														
	m ₁₃	1101																																																																																														
	m ₁₅	1111																																																																																														
②	minterm	binary																																																																																														
	(2,3)✓	001-																																																																																														
	(2,10)✓	-010																																																																																														
	(4,5)	010-																																																																																														
	(8,10)✓	10-0																																																																																														
	(8,9)-	100-																																																																																														
	(3,11)✓	-011																																																																																														
	(5,13)	-101																																																																																														
	(9,13)✓	1-01																																																																																														
	(9,11)✓	10-1																																																																																														
	(10,11)✓	101-																																																																																														
	(13,15)✓	11-1																																																																																														
	(11,15)✓	1-11																																																																																														
	minterm	binary																																																																																														
	(2,3,10,11)	-01-																																																																																														
	(8,9,10,11)	10--																																																																																														
	(9,11,13,15)	1--1																																																																																														
$\bar{a}b\bar{c}$	(4,5)																																																																																															
$b\bar{c}d$	(5,13)																																																																																															
$\bar{b}c$	(2,3,10,11)																																																																																															
$a\bar{b}$	(8,9,10,11)																																																																																															
$a\bar{d}$	(9,11,13,15)																																																																																															

Question Number	Solution	Marks Allocated																																						
	Prime implicant table $Y = \bar{b}c + \bar{a}b\bar{c} + d$	-2M- -1M-																																						
3 (a)	<p style="text-align: center;"><u>Module 2</u></p> <p>2-bit comparator truth table</p> <p>K-map simplification</p> $(A > B) = A_0\bar{B}_1\bar{B}_0 + A_1\bar{B}_1 + A_1A_0\bar{B}_0$ $(A = B) = (A_0 \odot B_0) (A_1 \odot B_1)$ $(A < B) = \bar{A}_1\bar{A}_0B_0 + \bar{A}_0B_1B_0 + \bar{A}_1B_1$ <p>logic diagram - (2M)</p>	-2M- -6M- each - 2M.																																						
(b)	<p>Definition for encoder -</p> <p>Block diagram -</p> <p>Explanation -</p>	-1M- -2M- -2M-																																						
(c)	<p>Full adder</p> $\text{Sum} = \sum m(1, 2, 4, 7), \text{ carry} = \sum m(3, 5, 6, 7)$ <div style="display: flex; justify-content: space-around;"> <table border="1" style="margin-right: 20px;"> <caption>Sum</caption> <thead> <tr><th>D₀</th><th>D₁</th><th>D₂</th><th>D₃</th></tr> </thead> <tbody> <tr><td>\bar{A}</td><td>0</td><td>①</td><td>②</td><td>3</td></tr> <tr><td>A</td><td>④</td><td>5</td><td>6</td><td>⑦</td></tr> <tr><td></td><td>A</td><td>\bar{A}</td><td>\bar{A}</td><td>A</td></tr> </tbody> </table> <table border="1"> <caption>Carry</caption> <thead> <tr><th>D₀</th><th>D₁</th><th>D₂</th><th>D₃</th></tr> </thead> <tbody> <tr><td>\bar{A}</td><td>0</td><td>1</td><td>2</td><td>③</td></tr> <tr><td>A</td><td>4</td><td>⑤</td><td>⑥</td><td>⑦</td></tr> <tr><td></td><td>0</td><td>A</td><td>A</td><td>1</td></tr> </tbody> </table> </div>	D ₀	D ₁	D ₂	D ₃	\bar{A}	0	①	②	3	A	④	5	6	⑦		A	\bar{A}	\bar{A}	A	D ₀	D ₁	D ₂	D ₃	\bar{A}	0	1	2	③	A	4	⑤	⑥	⑦		0	A	A	1	-1M- -2M-
D ₀	D ₁	D ₂	D ₃																																					
\bar{A}	0	①	②	3																																				
A	④	5	6	⑦																																				
	A	\bar{A}	\bar{A}	A																																				
D ₀	D ₁	D ₂	D ₃																																					
\bar{A}	0	1	2	③																																				
A	4	⑤	⑥	⑦																																				
	0	A	A	1																																				

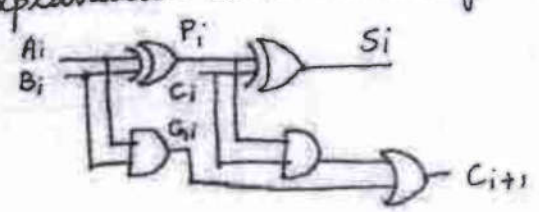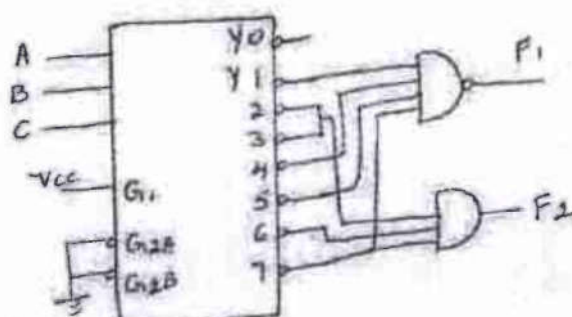Question Number	Solution	Marks Allocated															
(a)	<p>Explanation with the logic circuit</p>  <p> $P_i = A_i \oplus B_i$ $G_i = A_i B_i$ </p> <p>logic expressions</p> $C_1 = G_0 + P_0 C_0$ $C_2 = G_1 + P_1 C_1$ $C_3 = G_2 + P_2 C_2$ $C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 C_0$	-3M-															
(b)	<p>logic diagram of look ahead carry generator</p> 	-5M-															
(c)	<p>logic diagram 16:1 MUX using 8:1 MUX</p>	-5M-															
5 (a)	<p style="text-align: center;"><u>MODULE-3</u></p> <p>logic diagram of Master slave JK flip flop. functional table / truth table Timing diagram Explanation with race around condition</p>	-2M- -2M- -2M- -2M-															
(b)	<p>SR flip flop truth table</p> <p>K-map</p> <table border="1" data-bbox="406 1764 698 1911"> <tr> <td></td> <td>$\bar{R}Q^n$</td> <td>01</td> <td>11</td> <td>10</td> </tr> <tr> <td>S</td> <td>00</td> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>10</td> <td>1</td> <td>1</td> <td>x</td> </tr> </table> <p>$Q_{n+1} = S + \bar{R}Q^n$</p> <p>block diagram</p>		$\bar{R}Q^n$	01	11	10	S	00	0	1	0	1	10	1	1	x	-2M- -1M-
	$\bar{R}Q^n$	01	11	10													
S	00	0	1	0													
1	10	1	1	x													

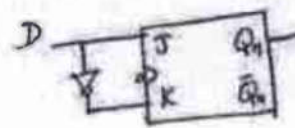Question Number	Solution	Marks Allocated																																																						
5.(c)	logic diagram 3-bit ripple counter truth table Explanation Timing diagram	-2M- -1M- -2M- -2M-																																																						
6(a)	Conversion table J K Flip flop to D flip flop. <table border="1" data-bbox="324 651 730 903"> <thead> <tr> <th>D</th> <th>Q_n</th> <th>Q_{n+1}</th> <th>J</th> <th>K</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>x</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>x</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>1</td> <td>x</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td>x</td> <td>0</td> </tr> </tbody> </table> $J = D, K = \bar{D}$ 	D	Q _n	Q _{n+1}	J	K	0	0	0	0	x	0	1	0	x	1	1	0	1	1	x	1	1	1	x	0	2+2+1																													
D	Q _n	Q _{n+1}	J	K																																																				
0	0	0	0	x																																																				
0	1	0	x	1																																																				
1	0	1	1	x																																																				
1	1	1	x	0																																																				
(b)	4 modes of operation (1) SISO (2) SIPO (3) PISO (4) PIPO explain with the logic diagram	2 Marks each. (2x4) M																																																						
(c)	$2^n \geq N, N=6, n=3$ flip flops required. <table border="1" data-bbox="324 1344 730 1722"> <thead> <tr> <th>Q_A</th> <th>Q_B</th> <th>Q_C</th> <th>Q_{A+1}</th> <th>Q_{B+1}</th> <th>Q_{C+1}</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>x</td> <td>x</td> <td>x</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td>x</td> <td>x</td> <td>x</td> </tr> </tbody> </table> $D = Q_{n+1}$ simplification using K-map. $D_A = Q_A \bar{Q}_C + Q_B Q_C, D_B = \bar{Q}_A \bar{Q}_B Q_C + Q_B \bar{Q}_C, D_C = \bar{Q}_C$ logic diagram -	Q _A	Q _B	Q _C	Q _{A+1}	Q _{B+1}	Q _{C+1}	0	0	0	0	0	1	0	0	1	0	1	0	0	1	0	0	1	1	0	1	1	1	0	0	1	0	0	1	0	1	1	0	1	0	0	0	1	1	0	x	x	x	1	1	1	x	x	x	→ 2M- -3M- -2M-
Q _A	Q _B	Q _C	Q _{A+1}	Q _{B+1}	Q _{C+1}																																																			
0	0	0	0	0	1																																																			
0	0	1	0	1	0																																																			
0	1	0	0	1	1																																																			
0	1	1	1	0	0																																																			
1	0	0	1	0	1																																																			
1	0	1	0	0	0																																																			
1	1	0	x	x	x																																																			
1	1	1	x	x	x																																																			

Q.No.

Marks

Module - 4

7
(a)

$F = A \oplus B$

$J_A = B, K_A = \bar{X}B$


$J_B = \bar{X}, K_B = X \oplus A$

$Q_A^+ = B\bar{A} + (X + \bar{B})A$

$Q_B^+ = \bar{X}\bar{B} + X \oplus A \cdot B$

Transition Table

Present state AB	Next state		output F
	X=0	X=1	
	A ⁺ B ⁺	A ⁺ B ⁺	
a	b	a	0
b	d	c	1
c	d	c	1
d	a	d	0

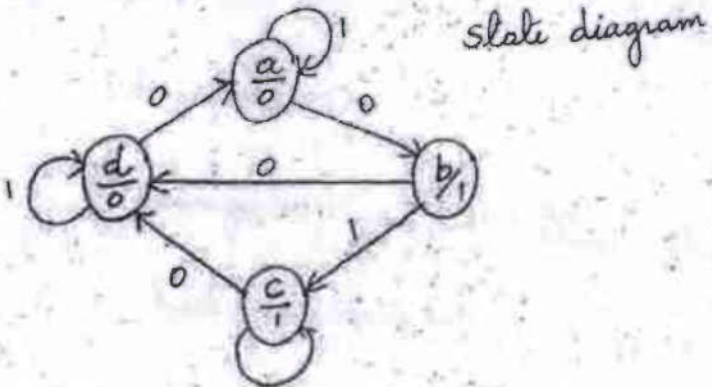

(b)

3 flip flops required

Excitation table →

K-map simplification: $J_A = B, K_A = \bar{B}, J_B = C, K_B = \bar{C}, J_C = \bar{A}, K_C = A$

logic diagram →

-2M-

-3M-

-5M-

-2M-

→ 3M-

→ 3M-

-2M-

Q.No.		Marks																																		
(8)	state table																																			
(a)	<table border="1" data-bbox="219 283 1015 619"> <thead> <tr> <th rowspan="2">Present state</th> <th colspan="2">Next state</th> <th colspan="2">output</th> </tr> <tr> <th>x=0</th> <th>x=1</th> <th>x=0</th> <th>x=1</th> </tr> </thead> <tbody> <tr> <td>AB</td> <td>A⁺B⁺</td> <td>A⁺B⁻</td> <td>Y</td> <td>Y</td> </tr> <tr> <td>00</td> <td>00</td> <td>01</td> <td>0</td> <td>1</td> </tr> <tr> <td>01</td> <td>10</td> <td>01</td> <td>0</td> <td>0</td> </tr> <tr> <td>10</td> <td>10</td> <td>11</td> <td>0</td> <td>1</td> </tr> <tr> <td>11</td> <td>11</td> <td>00</td> <td>0</td> <td>0</td> </tr> </tbody> </table>	Present state	Next state		output		x=0	x=1	x=0	x=1	AB	A ⁺ B ⁺	A ⁺ B ⁻	Y	Y	00	00	01	0	1	01	10	01	0	0	10	10	11	0	1	11	11	00	0	0	-4M-
Present state	Next state		output																																	
	x=0	x=1	x=0	x=1																																
AB	A ⁺ B ⁺	A ⁺ B ⁻	Y	Y																																
00	00	01	0	1																																
01	10	01	0	0																																
10	10	11	0	1																																
11	11	00	0	0																																
	<p>K-map simplification</p> $D_A = \bar{x}B + A\bar{B} \quad , \quad Y = x\bar{B}$ $D_B = \bar{x}AB + x\bar{A} + x\bar{B}$ <p>Sequential circuit diagram -</p>	-4M- -4M- -4M-																																		
(b)	<p>Mealy model explanation with block diagram & example logic circuit diagram</p> <p>Moose model explanation with block diagram & example logic circuit diagram</p>	-4M- -4M-																																		
9	<p style="text-align: center;">Module-5</p> <p>(a) Comparison between VHDL & Verilog. Explain by considering application, data type, ease of learning, libraries, operators, procedures, case sensitivity Comment: → each carries (1M)</p> <p>(b) VHDL data types Scalar type Composite type Access type File type Other types give examples</p>	-8M- -6M-																																		

(c) VHDL 2x1 multiplexer

```

library ieee;
use ieee.std_logic_1164.all;
entity mux2x1 is
port C, D0, D1, S, Enbae : in std_logic;
    Y : out std_logic);
end mux2x1;
architecture MUX of mux2x1 is
signal I1, I2, I3, I4 : std_logic;
begin
I1 <= not S after 10ns;
I2 <= not Enbae after 10ns;
I3 <= D0 and I1 and I2 after 10ns;
I4 <= D1 and S and I2 after 10ns;
Y <= I3 or I4 after 10ns;
end MUX;

```

S	Enbae	Y
x	1	0
0	0	D0
1	0	D1

Alternate methods such as structural description, process case, behavioral description can also be considered.

6M

10
(a)

VHDL data flow

```

entity full_add is
port (A, B, Cin, En : in bit;
    Sum, Cout : out bit);
end full_add;
architecture adder of full_add is

```

```

begin
Sum <= (A XOR B XOR Cin) and En;
Cout <= ((A and B) or (Cin and A) or (Cin and B)) and En;
end adder;

```

Verilog data flow

```

module full_add (A, B, Cin, En, Sum, Cout);
input A, B, Cin, En;
output Sum, Cout;
assign Sum = ((A ^ B) ^ Cin) & En;
assign Cout = ((A & B) | (Cin & A) | (Cin & B)) & En;
end module.

```

(b) Shift & rotate operators with examples

Dr. S.B. Shiva Kumar
Chairman
B.O.E (ETE)

structure of verilog module Explanation. *Mull*
 module <module name> <port list>;
 <declares>
 <module items>

Dr. S. Lakshmi
Associate Professor & Head
Dept. of Electrical & Electro
Institute of Technol
RRO 098