

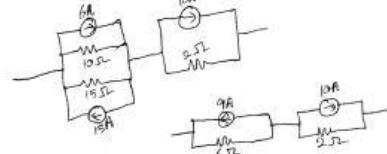
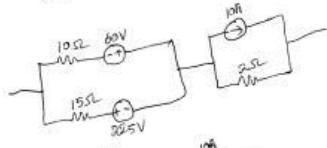
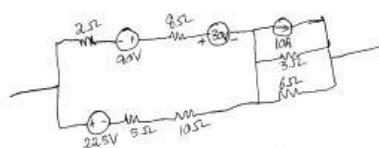


Module -1

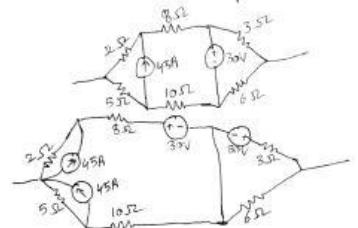- ① Reduce the network shown in Fig 1(a) to a single voltage source in series with a resistance using source shift and source transformation.



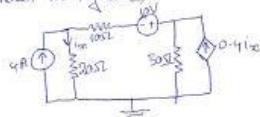- ② Find current in 30Ω resistor using nodal analysis for the circuit shown in Fig 2(a).



$$\text{KCL at Node } V_1: 4 - 1 - i_{12} - \frac{(V_1 - V_2)}{10} = 0$$

$$\begin{cases} i_{12} = \frac{V_1}{20} & \text{--- (2)} \\ 3 - \frac{V_1}{20} - \frac{V_1}{10} + \frac{V_2}{10} = 0 & \text{--- (3)} \\ -\frac{34}{20} + \frac{V_2}{10} = -3 & \text{--- (1)} \end{cases}$$

$$\text{KCL at Node 2: } 0.41i_{12} + 1 - \frac{(V_2 - V_1)}{10} - \frac{V_2}{30} = 0$$

$$\begin{cases} 0.41V_1 + 1 - \frac{V_2}{10} + \frac{V_1}{10} - \frac{V_2}{30} = 0 \\ \frac{0.4V_1}{10} + 1 - \frac{V_1}{10} - \frac{2V_2}{15} = 0 \end{cases}$$

$$\frac{3V_1}{30} - \frac{2V_2}{15} = -1 \quad \text{--- (3)}$$


$$V_1 = 62.5V$$

$$V_2 = 63.75V$$

$$\text{Current flowing in } 30\Omega \text{ resistor} = \frac{V_2}{30} = \frac{63.75}{30} = 2.125A$$

$$i_{12} = \frac{V_1}{20} = \frac{62.5}{20} = 3.125A$$

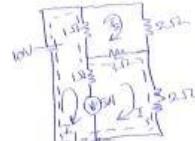- ③ Use mesh analysis to determine the 3 mesh currents I_1 , I_2 , and I_3 in the circuit shown in Fig 1(b).



Applying super mesh:

$$10V - (I_1 - I_2)1 - 3(I_1 - I_2) - 2I_3 = 0$$

$$10 - I_1 + I_2 - 3I_3 + 3I_2 - 2I_3 = 0$$

$$10 - I_1 + 4I_2 - 5I_3 = 0$$

$$I_1 - 4I_2 + 5I_3 = 10 \quad \text{--- (1)}$$

KVL at 2nd loop:

$$-(I_2 - I_1)1 - 2I_2 - (I_2 - I_3)3 = 0$$

$$-I_2 + I_1 - 2I_2 - I_2 + 3I_3 = 0$$

$$I_1 - 6I_2 + 3I_3 = 0 \quad \text{--- (2)}$$

$$I_1 - I_2 = 5A \quad \text{--- (3)}$$



Solving equations simultaneously (1), (2), (3)

$$I_1 = 15A \Rightarrow I_2 = 10A \quad I_1 = 18.75A$$

$$I_2 = 10A \quad I_2 = 10A$$

$$I_3 = 13.75A$$

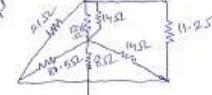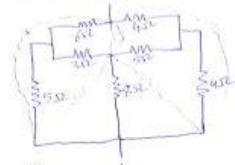
- ④ Find the equivalent resistance between a and b using star delta transformation for the network shown in Fig 2(b)(a).



$$\text{Req } R_a = 6 + 3 + \frac{6 \times 3}{3} = 12.6\Omega$$


$$R_b = 4 + 5 + \frac{4 \times 5}{5} = 11.2\Omega$$

$$R_c = 5 + 4 + \frac{5 \times 4}{4} = 14\Omega$$

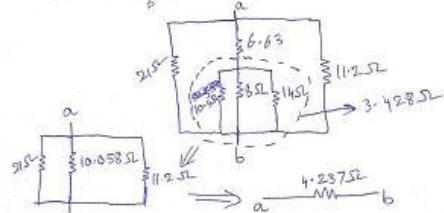

Module 2.

- 3a For the circuit shown in fig Q3(a), find the current I_x using superposition theorem

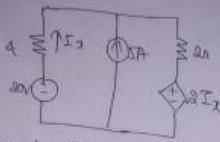

(Case 1: Due to 20V source only)

$$20 + (2I_x) = 6I_x$$

$$20 = 8I_x$$

$$I_x = \frac{20}{8} = 2.5A$$

(Case 2: Due to 5A only)

$$I_x = \frac{5 \times 2}{4+2} = \frac{10}{6} = 1.66A$$

(Case 3: Due to $2I_x$ only)

$$4I_x'' + 2I_x''' = -2I_x'''$$

$$8I_x''' = 0$$


$$I_x''' = 0$$

$$I_x = I_x' + I_x'' + I_x'''$$


$$= 2.5 + 1.66 + 0$$

$$I_x = 3.16A$$

- 3b Verify Reciprocity theorem by calculating I_1 for the network shown in fig Q3(b)

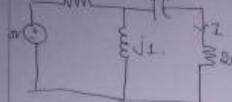

case 1:

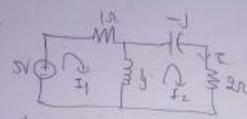

loop 1
5 = $I_1 + (I_1 - I_2)j$

loop 2
0 = $(1+j)I_1 - jI_2 \rightarrow 0$

$$0 = j(I_2 - I_1) + (-jI_1) + 2I_2$$

$$0 = jI_2 - jI_2 - jI_1 + 2I_2$$


$$0 = -jI_1 + 2I_2$$

$$I_1 - I_2 = \begin{bmatrix} 1+j & 5 \\ -j & 0 \\ 1+j & -j \\ -j & 2 \end{bmatrix}^{-1} \cdot \begin{bmatrix} 5j \\ 5j \end{bmatrix}$$

$$\Sigma = 24j\pi = 1.386 / 36.309A$$

$$\Sigma = 3.23 \angle -26.56^\circ A$$

Step 2

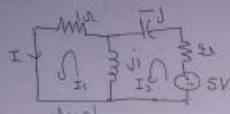

$$I_1 + (I_1 - I_2)j = 0$$

$$(1+j)I_1 - jI_2 = 0$$

Loop 3

$$5 = 2I_2 - jI_2 + (I_2 - I_1)j$$

$$5 = 2I_2 - jI_2 + jI_2 - I_1j$$

$$5 = -I_1j + 2I_2$$

$$I_1 = \frac{\begin{vmatrix} 0 & -j \\ 5 & 2 \end{vmatrix}}{\begin{vmatrix} 1+j & -j \\ -j & 2 \end{vmatrix}} = \frac{5j}{2+2j-j^2} = \frac{5j}{3+2j}$$


$$I_1 + I_2 = \frac{5j}{3+2j} \approx 1.38 \angle 63^\circ A$$

Hence Reciprocity theorem Verified

To obtain the Thevenin's equivalent of the circuit shown in Fig Q3(c)



Step 3: To find V_{TH}

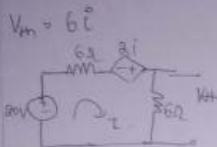

$$20 + 2I = 8I$$

$$20 + 2I = 12I$$

$$20 = 10I$$


$$I = 2A$$

$$\dot{I} = 2A$$

$$V_{TH} = 6 \times 2 = 12V$$

Step 4: To find R_{TH}

short circuit the open terminal pair

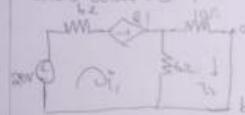

$$Z_{TH} = \frac{V_m}{I_m}$$

$$FVL @ \text{loop 1} \quad I = I_1 - I_2$$

$$20 + 2I = 6I_1 + 6I_2 - I_2$$

$$20 + 2I = 6I_1 + 5I_2$$

$$20 + 10I_1 - 4I_2 = 0$$

loop 2.

$$0 = 6(i_2 - i_1) + 10i_2$$

$$0 = 6i_1 + 10i_2 \rightarrow 0 \quad \text{②}$$

$$i = i_1 - i_2 \quad \text{③}$$


solving ① & ②

$$i_1 = 2.3 \text{ A} \quad i_2 = 0.883 \text{ A}$$


$$i_2 - i_1 = 0.883 \text{ A}$$

$$Z_{eq} = \frac{V_m}{I_{eq}} = \frac{12}{0.883} = 13.6 \Omega$$

Thevenin equivalent circuit

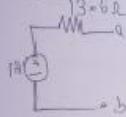

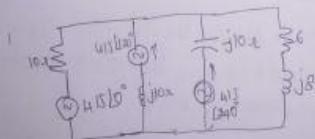- For the circuit shown in fig 4(a) find the current in $(6+j8) \Omega$ impedors using Millman's theorem



Using millman's theorem

$$Y_1 = \frac{1}{Z_1} = \frac{1}{10} = 0.1 \Omega^{-1}$$


$$V_m = \frac{V_1 Y_1 + V_2 Y_2 + V_3 Y_3}{Y_1 + Y_2 + Y_3} \quad Y_L = \frac{1}{Z_L} = \frac{1}{j10 \Omega} = -0.1j \Omega^{-1}$$

$$Z_m = \frac{1}{Y_1 + Y_2 + Y_3} \quad Y_3 = \frac{1}{Z_3} = \frac{1}{j10} = 0.1j \Omega^{-1}$$

$$V_m = \frac{415\angle 0^\circ + 415\angle 0^\circ + 415 \times 0.1 j_2}{0.1 + 0.1j - 0.1j} \quad 0.1 + 0.1j - 0.1j$$

$$V_m = 486.8 \text{ V}$$

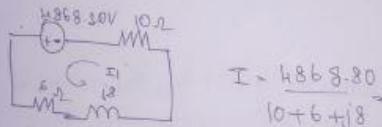
$$Z_m = \frac{1}{Y_1 + Y_2 + Y_3} = \frac{1}{0.1 + 0.1j - 0.1j} = 10 \Omega$$



$$I = \frac{486.8 \text{ V}}{10 + 6 + j8}$$

$$I = 27.21741 / -86.56^\circ \text{ A}$$

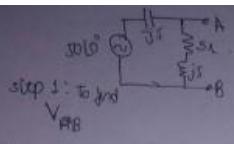- For the network shown in figure 4(b) determine Norton's equivalent circuit A-B finding current through impedors connected to the terminal A-B




$$V_m > V_{AB} = V(s+jj)$$

$$V_{AB}, \frac{50\angle 0^\circ \times (s+jj)}{s+5j-jj} = \frac{50}{8} (s+jj)$$


$$Y_{AB} = 50 + 50jV = 70.71 \angle 45^\circ V.$$

suppose to find $R_{th} = R_{AB}$

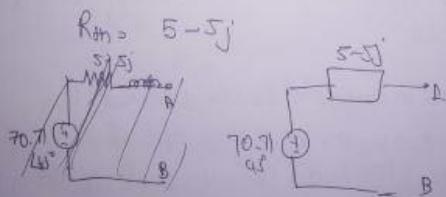
$$\begin{aligned} R_{AB} &= \frac{-js \times (s+jj)}{-js+j+sj} \\ &= \frac{-25j - 25j^2}{s} \\ &= \frac{5}{8} (-sj + 5) \end{aligned}$$



Nodal A equivalent circuit

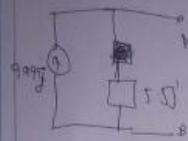

connecting 6-8j shunt to AB

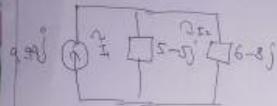

$$I_2 = \frac{9.99j \times (s-sj)}{s-sj+6-8j}$$

$$I_2 = \frac{9.99j \times (s-sj)}{11-16j} = 4.632 \angle 103.39^\circ A$$

to state and solve maximum power for any given load for AC circuit when both R_L and X_L are varying.

It states that the maximum power delivered by a source represented by the Thvenin's equivalent circuit is obtain when the load (R_L) is equal to thevenin's equivalent

$$Z_T = R + jX$$

$$Z_L = R_L + jX_L$$

$$I = \frac{V_m}{Z_T}$$

$$I = \frac{V_m}{R + jX + R_L + jX_L} = \frac{V_m}{R + R_L + j(X + X_L)}$$

$$P_L = I^2 R_L$$

$$I^2 = \frac{V_m^2}{(R + R_L)^2 + (X + X_L)^2}$$

$$P_L = \frac{V_m^2 R_L}{(R + R_L)^2 + (X + X_L)^2}$$

Maximum condition

$$\frac{\partial P_L}{\partial R_L} > 0 \quad \frac{\partial P_L}{\partial X_L} > 0$$

$$\frac{\partial P_L}{\partial X_L} = \frac{\partial}{\partial X_L} \left(\frac{V_m^2 R_L}{(R+R_L)^2 + (X+X_L)^2} \right) > 0$$

$$\frac{\partial P_L}{\partial X_L} = \frac{-2V_m^2 R_L (X+X_L)}{(R+R_L)^2 + (X+X_L)^2}$$

$$-2V_m^2 R_L (X+X_L) > 0$$

$$X+X_L > 0$$

$$\boxed{X = -X_L}$$

$$\frac{\partial P_L}{\partial R_L} = \frac{\partial}{\partial R_L} \left(\frac{V_m^2 R_L}{(R+R_L)^2 + (X+X_L)^2} \right) = \frac{(R+R_L)^2 + (X+X_L)^2 - V_m^2 R_L^2 (R+R_L)}{(R+R_L)^2 + (X+X_L)^2} > 0$$

$$\frac{\partial P_L}{\partial R_L} > 0 \Leftrightarrow V_m^2 ((R+R_L)^2) - 2R_L (R+R_L) > 0$$

$$\Rightarrow (R+R_L)^2 - 2R_L (R+R_L) > 0$$

$$= (R+R_L)^2 > 2R_L (R+R_L)$$

$$\Rightarrow R = R_L$$

$$P_{max} = I^2 R_L = \frac{V_m^2}{\sqrt{\frac{(R+R_L)^2}{R_L} + \frac{(X+X_L)^2}{-X_L}}} = \frac{I^2 R_L}{\sqrt{\frac{(R+R_L)^2}{R_L} + \frac{(X+X_L)^2}{-X_L}}}$$

$$P_{max} = \frac{V_m^2 R_L}{4 R_L^2} = \frac{V_m^2}{4 R_L}$$


- Q3a) In the Network shown in fig Q3a(a), a steady state is reached with the switch b is open. At $t=0$, the switch b is closed. Obtain the initial values of (i) i_2 (ii) v_c

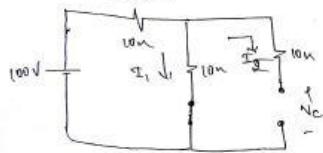(iii) v_c (iv) $\frac{di_2}{dt}$ (v) $\frac{dv_c}{dt} + 2 \frac{di_2}{dt}$ at $t=0^+$



Ans:

(ans(i)): At $t=0^-$, b is open, steady state is reached.



(i)

$$i_2(0^-) \times \frac{V}{10+10} = \frac{100}{20} = 5A = i_2(0^+)$$

$$(ii) i_2(0^+) = 0A.$$

$$(iii) v_c(0^-) = \frac{100[10]}{10+10} = 50V = v_c(0^+)$$

Differentiating eq (i)

$$0 = 10 \frac{di_2(0)}{dt} + \frac{1}{C} i_2(0)$$

At $t=0^+$

$$0 = 10 \frac{di_2(0^+)}{dt} + 10^6 i_2(0^+)$$

$$\frac{di_2(0^+)}{dt} = -\frac{10^6 \cdot 5}{10^2} = -\frac{10^6}{10^2} A/s$$

(iv) $t \rightarrow t \rightarrow \infty$,

$$i_2(\infty) = \frac{100}{10} = 10A$$

$$\frac{di_2(\infty)}{dt} = 0A/s.$$

Ans:

$$i_2(\infty) = 0$$


$$\frac{di_2(\infty)}{dt} = 0A/s.$$

- Q3b) In the Circuit of Fig Q3b(a) - the source voltage is $V(t) = 50 \sin 350t$. Using Laplace transform, determine the current when switch k is closed at $t=0$.

- (vi) ~~i_2~~ ~~v_c~~

(vii) At $t=0^+$, k is closed.

Circuit diagram:

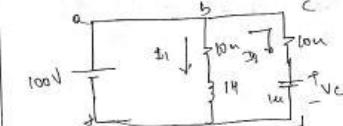

Applying KVL to the loop abcda

$$100 = 10I_1(0^+) + \frac{1}{C} \frac{di_2(0^+)}{dt} \quad \text{--- (1)}$$

$$100 = 10I_1(0^+) + \frac{1}{10} \frac{di_2(0^+)}{dt}$$

At $t=0^+$

$$100 = 10I_1(0^+) \Rightarrow \frac{di_2(0^+)}{dt}$$

$$\frac{di_2(0^+)}{dt} = 100 - 10I_1(0^+)$$

$$\frac{di_2(0^+)}{dt} = 50 A/s$$

Applying KVL to the loop abcda

$$100 = 10I_2(0^+) + \frac{1}{C} \int I_2(t) dt \quad \text{--- (2)}$$


$$100 = 10I_2(0^+) + 10^6 \int I_2(t) dt$$

$$\text{At } t=0^+ \frac{dI_2(0^+)}{dt} = \frac{100 - 50}{10} = 5A$$

$$\frac{dI_2(0^+)}{dt} = 5A$$

$$v_c(0^+) = V_c(0^+)$$

$$100 = 10I_2(0^+) + 5 \int I_2(t) dt$$

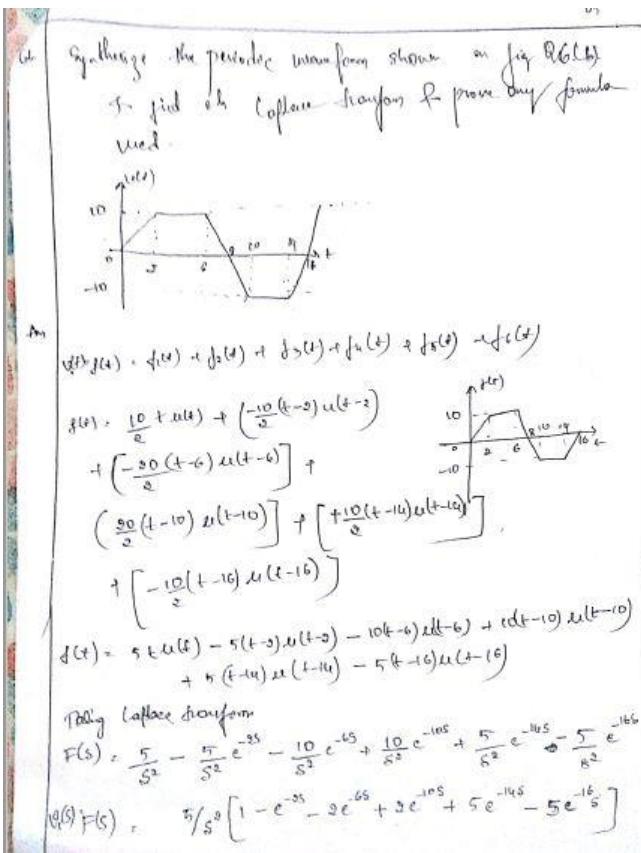

Module - 4.

Q. Bandwidth of series RLC circuit is defined as the band of frequencies over which the power in circuit is half of its max. value.

At resonance frequency, max. current I_0 is given by:

$$I_0 = \frac{V}{R}$$


At resonance frequency, Power in circuit is max. & given by:

$$P_0 = P_{max} = (I_0)^2 R$$

Half of max power is given by:-

$$P = \frac{P_0}{2} = \frac{I_0^2 R}{2} = \left(\frac{V}{\omega L}\right)^2 R$$

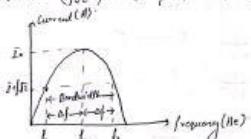: Frequency where power in circuit is half of max. value, current becomes $(\sqrt{\frac{1}{2}})$ times of its max. value.



At resonant frequency, power in circuit is given by P_0 . $P_{max} = (I_0)^2 R$

At frequency f_1 , power in circuit is half & it is given by $P = \frac{1}{2} (I_0)^2 R$.

Similarly, at frequency f_3 , power in circuit is half & it is given by $P = \frac{1}{2} (I_0)^2 R$.

Thus f_1 is lower half-power frequency &

f_3 is upper half-power frequency.

bandwidth = $(f_3 - f_1)$ Hz.

Now, current in series RLC circuit is given by:-

$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \rightarrow \text{Q}$$

The periodic function is given by

$$v(s) = \frac{V_0(s)}{1 - e^{js}}$$

where $T = 16$

$$V(s) = \frac{5/s^2 [1 - e^{-2s} - 2e^{-4s} + 2e^{-6s} + 5e^{-10s} - 5e^{-16s}]}{1 - e^{jws}}$$

We have used Ramp function & periodic function

Proof for ramp function & periodic function.

At half power point,

$$I = \frac{I_0}{\sqrt{2}} = \frac{1}{\sqrt{2}} \frac{V}{Z} \Rightarrow I_0 = \frac{V}{Z} \text{ at resonance.}$$

∴ equating eqn ① & eqn ②.

$$\frac{1}{\sqrt{2}} \frac{V}{R} = \frac{V}{\sqrt{R^2 + (\omega_L - \frac{1}{\omega_C})^2}}$$

$$\Rightarrow \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2} = \sqrt{2} R$$

Squaring both sides, we get:-

$$R^2 + (\omega L - \frac{1}{\omega C})^2 = 2R^2$$

$$\Rightarrow (\omega L - \frac{1}{\omega C})^2 = R^2$$

Above eq. is quadratic in ω , which gives 2 values of ω as ω_1 & ω_2 whose half power frequency (f_1 & f_2) are.

$$\therefore \omega_2 L - \frac{1}{\omega_2 C} = R \rightarrow \text{③}$$

$$\omega_1 L - \frac{1}{\omega_1 C} = -R \rightarrow \text{④}$$

Adding eqn ③ & ④-

$$\omega_2 L - \frac{1}{\omega_2 C} + \omega_1 L - \frac{1}{\omega_1 C} = 0$$

$$(\omega_2 + \omega_1)L - \left(\frac{1}{\omega_2} + \frac{1}{\omega_1} \right) \frac{1}{C} = 0$$

$$(\omega_2 + \omega_1)L = \left(\frac{1}{\omega_1} + \frac{1}{\omega_2} \right) \frac{1}{C} = \left(\frac{\omega_1 + \omega_2}{\omega_1 \omega_2} \right) \frac{1}{C}$$

$$\Rightarrow \omega_1 \omega_2 = \frac{1}{LC}$$

but from resonance condition, $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\therefore \omega_1 \omega_2 = \frac{1}{LC} (\omega_0)^2$$

$$\Rightarrow \omega_0 = \sqrt{\omega_1 \omega_2}$$

i.e., $f_1 f_2 = f_0^2$.

$$\therefore f_1 = \sqrt{f_0 f_2}$$

7) (a) $V(t) = 10 \cos(100t)$; $C = 10 \mu F \Rightarrow I = I_m$
 $\Rightarrow \omega = 1000$, $C = 10 \mu F \Rightarrow I = I_m/\sqrt{2}$

Find L, R & ω .

$$\omega = \frac{1}{\sqrt{LC}} \Rightarrow L = \frac{1}{\omega^2 C} = \frac{1}{(1000)^2 (10 \mu F)} = \frac{1}{10} = 0.1 H$$

When $C = 10 \mu F$,

$$I = \frac{I_m}{\sqrt{2}} = \frac{EV}{\sqrt{2}R} \quad [\because I_m = \frac{V}{R} \text{ at resonance}]$$

$$\therefore I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + X^2}} \rightarrow \textcircled{1}$$

equating $\textcircled{1}$ & $\textcircled{2}$:

$$\sqrt{R^2 + X^2} = \sqrt{L} R$$

Comparing L & R terms:

$$X^2 = R^2 \Rightarrow X = R$$

but $X_L = X_C - R$

$$\Rightarrow X_C = X_L + R$$

$$XL = \frac{1}{\omega C}$$

$$1000(0.1) = \frac{1}{1000(12 \mu F)} \times R$$

$$\therefore R = 20 \Omega$$

8) $\omega L \propto \varphi = \frac{(100)(0.1)}{20} \rightarrow \boxed{8.5}$

9. a. Z parameters of a network are obtained from an experiment. Explain how y parameters and ABCD parameters can be computed from experimental data.

Z parameters

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \rightarrow \textcircled{1}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \rightarrow \textcircled{2}$$

y parameters

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \rightarrow \textcircled{3}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \rightarrow \textcircled{4}$$

To obtain y parameters

From $\textcircled{1}$ & $\textcircled{2}$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$I_1 = \frac{V_1 Z_{12} - V_2 Z_{11}}{\Delta Z} \quad \Delta Z = Z_{11} Z_{22} - Z_{12} Z_{21}$$

$$I_2 = \frac{V_1 Z_{22} - V_2 Z_{12}}{\Delta Z}$$

$$I_1 = \frac{Z_{22} V_1 - (-Z_{12}) V_2}{\Delta Z} \rightarrow \textcircled{5}$$

$$I_2 = \frac{Z_{11} V_2 - Z_{21} V_1}{\Delta Z}$$

$$I_2 = \frac{Z_{11} V_2 - Z_{21} V_1}{\Delta Z}$$

$$I_2 = \left(-\frac{Z_{21}}{\Delta Z} \right) V_1 + \frac{Z_{11}}{\Delta Z} V_2 \rightarrow \textcircled{6}$$

7) (b) $R = 100 \Omega$; $L = 318 \mu H$; $f_r = 1 MHz$



$$\text{Here } f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = \frac{f_r^2}{L} \cdot \frac{1}{C}$$

$$f_r^2 = \frac{1}{4\pi^2} \left(\frac{1}{LC} - \frac{R^2}{L^2} \right)$$

$$+ C_r = \frac{1}{L \left(4\pi^2 f_r^2 + \frac{R^2}{L^2} \right)}$$

$$(318 \mu H) / (4\pi^2 (1 Hz)^2 + (100)^2)$$

$$\sqrt{C_r} = 7.6587 \times 10^{-11} F$$

$$\begin{aligned} L: 100 \Omega & \quad C: 7.6587 \times 10^{-11} F \\ C: 318 \mu H & \quad L: 318 \mu H \\ \therefore C_r = \frac{C_1 C_2}{C_1 + C_2} & \quad \left[\frac{3.947 \times 10^{-11}}{(1.756 \times 10^{10}) - (1.121 \times 10^{10})} \right] \\ & \quad 1.8057 \times 10^{10} \cdot \frac{(1.795 \times 10^{-11})}{(1.0007 \times 10^{-10})} \\ & \quad C_r = 7.6587 \times 10^{-11} F \end{aligned}$$

$$\therefore f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC_r}} = \frac{f_r^2}{LC_r} = \frac{1}{2\pi} \sqrt{\frac{1}{(318 \mu H)(7.6587 \times 10^{-11})}} = \frac{1000}{(318 \mu H)}$$

$$\therefore f_r = 2.099 \text{ Hz}$$

Compare $\textcircled{1}$ & $\textcircled{2}$ with $\textcircled{5}$ & $\textcircled{6}$

$$Y_{11} = \frac{Z_{22}}{\Delta Z} \quad Y_{12} = -\frac{Z_{12}}{\Delta Z}$$

$$Y_{21} = -\frac{Z_{21}}{\Delta Z} \quad Y_{22} = \frac{Z_{11}}{\Delta Z}$$

$$\therefore Y = \begin{bmatrix} Z_{22} & -Z_{12} \\ -Z_{21} & Z_{11} \end{bmatrix} \quad \text{opp}$$

ABCD parameters

$$V_1 = AV_2 - B I_2 \rightarrow \textcircled{7}$$

$$I_1 = CV_2 - DI_2 \rightarrow \textcircled{8}$$

From $\textcircled{7}$

$$V_2 = Z_{22} I_2 + Z_{12} I_1$$

$$I_1 = \frac{V_1}{Z_{21}} - \frac{Z_{22} I_2}{Z_{21}} \rightarrow \textcircled{9}$$

Sub $\textcircled{9}$ in $\textcircled{7}$

$$V_1 = Z_{11} \left(\frac{V_2}{Z_{21}} - \frac{Z_{22} I_2}{Z_{21}} \right) + Z_{12} I_2$$

$$V_{12} = \frac{Z_{11}}{Z_{21}} V_2 - \frac{Z_{11} Z_{22}}{Z_{21}} I_2 + Z_{12} I_2$$


$$V_1 = \frac{Z_{11}}{Z_{21}} V_2 + \left(Z_{21} Z_{12} - Z_{11} Z_{22} \right) I_2$$

$$V_1 = \frac{Z_{11}}{Z_{21}} V_2 + \left(\frac{Z_{11} Z_{22} - Z_{21} Z_{12}}{Z_{21}} \right) I_2 \rightarrow \textcircled{10}$$

Compare $\textcircled{5}$ & $\textcircled{6}$ with $\textcircled{7}$ & $\textcircled{8}$

$$T_2 = \begin{bmatrix} \frac{Z_{11}}{Z_{21}} & \frac{Z_{11} Z_{22} - Z_{21} Z_{12}}{Z_{21}} \\ \frac{1}{Z_{21}} & \frac{Z_{22}}{Z_{21}} \end{bmatrix}$$

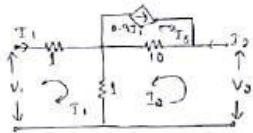Q(b) Find Z and Y parameters of the network shown in fig



→ apply KVL to loops

$$V_1 = 1I_1 + 1(I_1 + I_2)$$

$$V_1 = 0.9I_1 + I_1 = 0$$

$$I_3 = 0.9I_1$$

apply KVL to loops

$$V_2 = 10(I_2 + I_3) + 1(I_1 + I_2)$$

$$V_2 = 11I_2 + 10I_3 + I_1$$

$$V_2 = 11I_2 + 10(0.9I_1) + I_1$$

$$V_2 = -9I_1 + 11I_2 = 0 \quad \text{--- (1)}$$

Comparing (1) & (2)

$$V_1 = 2I_1 + Z_{12}I_2$$

$$V_3 = Z_{21}I_1 + Z_{32}I_2$$

$$Z_{11} = 0 \quad Z_{12} = 1 \quad Z_{21} = 9 \quad Z_{32} = 0$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{32} \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ 9 & 0 \end{bmatrix}$$

Y parameters

$$Y_{11} = \frac{Z_{22}}{Z_{11}Z_{22} - Z_{12}Z_{21}} = \frac{1}{9Y_{11} - 9Y_1} = 0.846 \text{ S}$$

$$Y_{12} = \frac{-Z_{12}}{Z_{11}Z_{22} - Z_{12}Z_{21}}$$

$$= \frac{1}{9Y_{11} - 9} = \frac{1}{18} = 0.056 \text{ S}$$

$$Y_{21} = \frac{-Z_{21}}{Z_{11}Z_{22} - Z_{12}Z_{21}} = \frac{-9}{18} = -0.692 \text{ S}$$

$$Y_{22} = \frac{Z_{11}}{Z_{11}Z_{22} - Z_{12}Z_{21}} = \frac{9}{18} = 0.167 \text{ S}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 0.846 & -0.056 \\ -0.692 & 0.167 \end{bmatrix} \text{ S}$$

Network Analysis

Module - 5 (Question - 10)

10)

- a) Find \mathbf{Z} and \mathbf{h} parameters for the following Network given.
-

Applying KVL to mesh 1:

$$V_1 - \frac{1}{s} Q_1 - 1(Q_1 + Q_2) = 0$$

$$V_1 - Q_1 \left(\frac{1}{s} + 1 \right) - Q_2 = 0$$

$$V_1 = \left(\frac{1}{s} + 1 \right) Q_1 + Q_2 \rightarrow \textcircled{1}$$

Applying KVL to mesh 2:

$$V_2 - \frac{1}{s} Q_2 - 1(Q_1 + Q_2) = 0$$

$$V_2 = -Q_1 + Q_2 \left(\frac{1}{s} + 1 \right) \rightarrow \textcircled{2}$$

We know the equations for \mathbf{Z} -parameters.

$$V_1 = Z_{11} Q_1 + Z_{12} Q_2, \quad V_2 = Z_{21} Q_1 + Z_{22} Q_2$$

Comparing these equations with eq $\textcircled{1}$ and $\textcircled{2}$

$$Z_{11} = \left(\frac{1}{s} + 1 \right) \Omega, \quad Z_{12} = 1 \Omega, \quad Z_{21} = \left(1 + \frac{1}{s} \right) \Omega, \quad Z_{22} = 1 \Omega$$

H-parameters in terms of Z-parameters

$$\text{we get } H_{11} = \frac{\Delta Z}{Z_{22}}, \quad H_{12} = \frac{Z_{12}}{Z_{22}}$$

$$H_{21} = \frac{1}{Z_{22}}, \quad H_{22} = -Z_{21}/Z_{22}$$

so we know,

$$Z_{11} = \frac{1}{s} + 1 \Omega, \quad Z_{12} = 1 \Omega, \quad Z_{21} = 1 + \frac{1}{s} \Omega$$

$$Z_{22} = 1 \Omega$$


$$H_{12} = \frac{1}{\frac{1}{s} + 1} = \frac{1}{\frac{1+s}{s}} \Rightarrow H_{12} = \frac{s}{s+1}$$

$$H_{21} = \frac{1}{Z_{22}} = \frac{1}{\frac{1}{s+1}} \Rightarrow H_{21} = s$$

$$H_{22} = -Z_{21}/Z_{22} = -\frac{1}{\frac{1+s}{s}} \Rightarrow H_{22} = -\frac{s}{s+1}$$

$$H_{11} = \frac{\left(\frac{1+s}{s} \right)^2 - 1}{\frac{1+s}{s}}$$

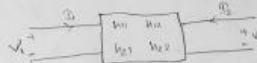
- 10) b) Write a note on hybrid parameters with its equivalent circuit



$$V_1 = h_{11} Q_1 + h_{12} Q_2$$

$$Q_2 = h_{21} Q_1 + h_{22} V_2$$

Equivalent circuit

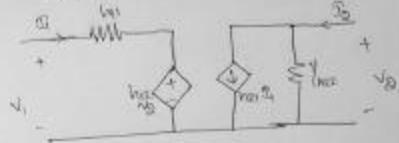

- 10) c) Explain symmetry and reciprocal property of 2-port network

Condition for Reciprocity:

If the ratio of voltage at one port to the current at the other port is same to the ratio of the position of voltage and current are interchanged then the network is said to be reciprocal.

Z-parameters : $Z_2 = -Z_{21}$

H-parameters : $h_{12} = -h_{21}$

T-parameters : $AD - BC = 1$

J-parameters : $J_{12} = J_{21}$

Condition for Symmetry:

Z-parameters : $Z_{11} = Z_{22}$

J-parameters : $J_{11} = J_{22}$

H-parameters : $\Delta h = 1 \quad (h_{11}h_{22} - h_{12}h_{21} = 1)$