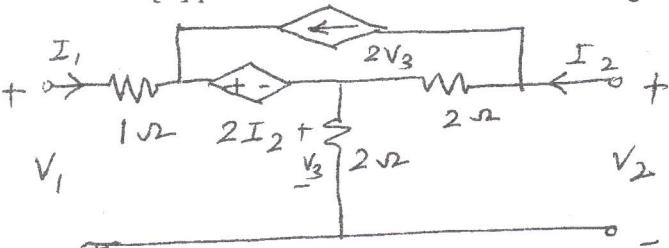
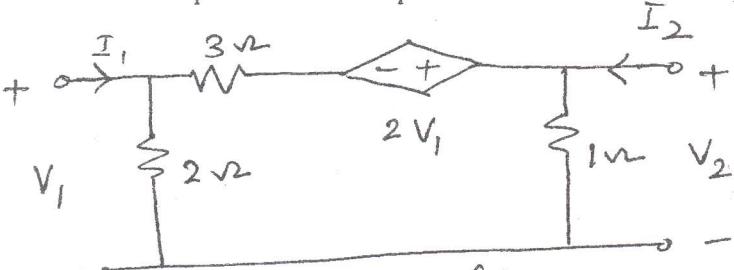
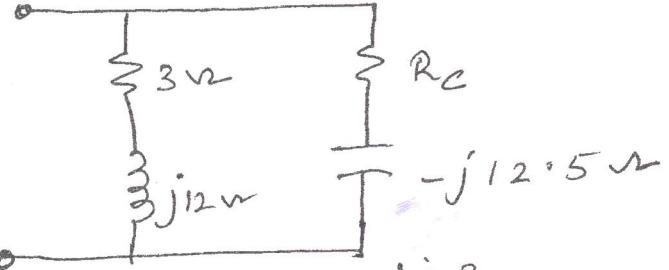


## Internal Assessment Test - III

Sub:	Electric Circuit Analysis				Code:	18EE32
Date:	16/11/2019	Duration:	90 mins	Max Marks:	50	Sem: 3 Branch: EEE(A)

Answer Any FIVE FULL Questions

	Marks	OBE	
		CO	RBT
1. Define [Y] parameter and draw the equivalent circuit of it. Calculate the [Z] parameter of the circuit shown in fig1.	[5+5]	CO4	L1,L3
			
Fig 1.			
2. Define [T] parameter. Calculate the [Y] parameter of the circuit shown in fig2. Then use the parameter relationship to find ABCD parameter.	[4+6]	CO4	L1,L3
			
fig 2.			
3. Prove that for series resonant circuit, the resonant frequency is the geometric mean of two half power frequencies. Determine the value of R_c for which the circuit of the fig3. resonates.	[5+5]	CO4	L1,L3
			
fig 3.			

P.T.O

P.D.F (CC-I)

P.D.F (CC-I)

4. Derive expression for resonant frequency in series RLC circuit.  
 A series RLC circuit has  $R=4\Omega$ ,  $L=1\text{mH}$  and  $C=10\mu\text{F}$ . Calculate Q factor, bandwidth, resonant frequency and half power frequencies.

[4+6] CO4 L3

5. Find the equation of current if the switch is closed at  $t=0$ . Find also the voltage across L and R, the current at  $t=0.1$  sec shown in fig5.

[10] CO4 L4

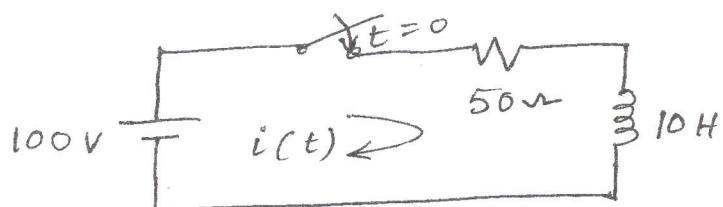


fig 5.

- 6a. Show the behaviour of R, L, C elements at the time of switching at  $t=0$  both at  $t=0+$  and  $t=\infty$ .

[5] CO3 L1

- 6b. Draw the dual network for the given network shown in fig6b.

[5] CO3 L3

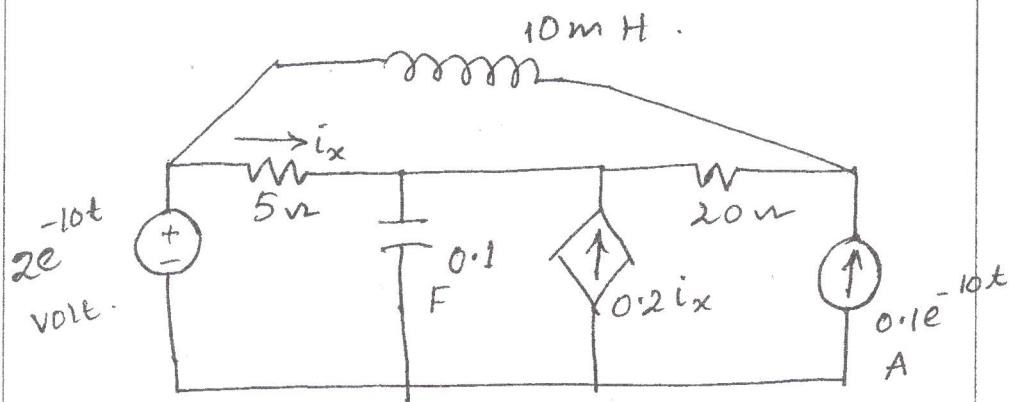



fig 6b

- end -

P.P.Y (CC-I)  
par (CC-I)

1)  $\text{Y}$  parameter model

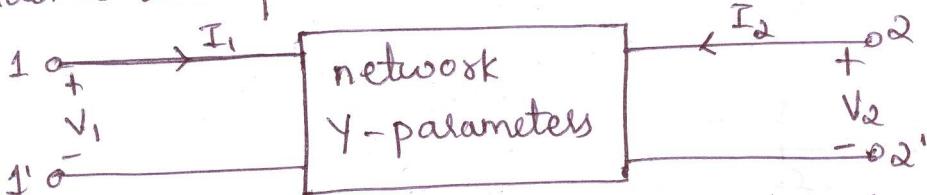a) Consider a two port network as shown below



$$[I] = [Y] [V]$$

Considering  $I_1$  and  $I_2$  to be dependant variables that depend on independant  $V_1$  and  $V_2$  we can write the following equations :

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

Short circuit the input port ie)  $V_1 = 0$ .

- $Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \Rightarrow$  short circuited transfer reverse admittance in S


- $Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} \Rightarrow$  short circuited driving point output admittance in S or  $\omega$ .

Short circuit the output port ie)  $V_2 = 0$ .


- $Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \Rightarrow$  short circuited driving point input admittance in S or  $\omega$

- $Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \Rightarrow$  short circuited transfer forward admittance in S or  $\omega$

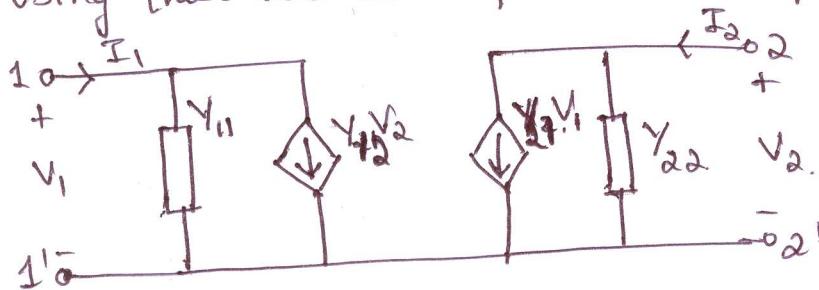These four parameters  $Y_{11}, Y_{12}, Y_{21}, Y_{22}$  are called as admittance ( $\text{y}$ ) parameters / short circuit parameters. Using these we can represent an equivalent circuit as below:-



b)

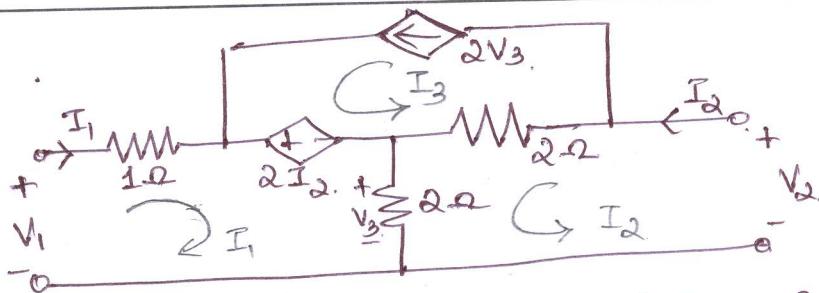

- Applying KVL in mesh I :-  $-1I_1 - 2I_2 - 2(I_1 + I_2) = 0 - V_1$

$$-I_1 - 2I_2 - 2I_1 - 2I_2 = 0 - V_1$$

$$-3I_1 - 4I_2 = 0 - V_1$$

$$3I_1 + 4I_2 = V_1 \quad \text{--- (1)}$$

- Applying KVL in mesh II :-  $-2(I_2 - I_3) - 2(I_1 + I_2) = 0 - V_2$

$$-2I_2 + 2I_3 - 2I_1 - 2I_2 = -V_2$$

$$-2I_1 - 4I_2 + 2I_3 = -V_2$$

$$2I_1 + 4I_2 - 2I_3 = V_2 \quad \text{--- (2)}$$

- In mesh III constraint equation :-  $I_3 = 2V_3$

$$V_3 = 2(I_1 + I_2) = 2I_1 + 2I_2$$

$$\therefore I_3 = 2(2I_1 + 2I_2) = 4I_1 + 4I_2 \quad \text{--- (3)}$$

- Sub (3) in (2)

$$2I_1 + 4I_2 - 2(4I_1 + 4I_2) = V_2$$

$$2I_1 + 4I_2 - 8I_1 - 8I_2 = V_2$$

$$-6I_1 - 4I_2 = V_2 \quad \text{--- (4)}$$

- In (1) put  $I_1 = 0$ .

$$4I_2 = V_1$$

$$\frac{V_1}{I_2} = 4$$

$$Z_{12} = 4\Omega$$

In (4) put  $I_1 = 0$

$$-4I_2 = V_2$$

$$-4 = \frac{V_2}{I_2}$$

$$Z_{22} = -4\Omega$$

In ① put  $I_2 = 0$

$$3I_1 = V_1$$

$$3 = \frac{V_1}{I_1}$$

$$\boxed{Z_{11} = 3 \Omega}$$

In ④ put  $I_2 = 0$

$$-6I_1 = V_2$$


$$-6 = \frac{V_2}{I_1}$$

$$\boxed{Z_{21} = -6 \Omega}$$

$$\therefore [Z] = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 3 & 4 \\ -6 & -4 \end{bmatrix} \Omega.$$

2.) Transmission (T) parameters / ABCD parameters :-

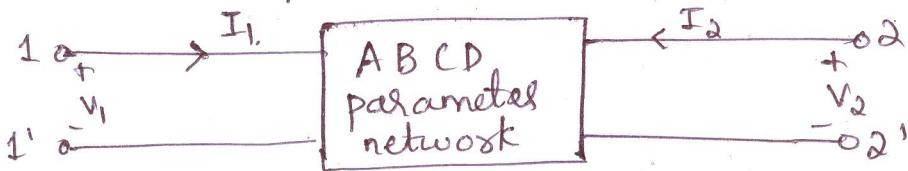a) Consider a two port network as shown below:-



Considering  $I_1$  and  $V_1$  to be dependent on the independent variables  $V_2$  and  $I_2$ , we can write the following equations

$$I_1 = AV_2 + B(-I_2)$$

$$V_1 = CV_2 + D(-I_2)$$

• When  $V_2 = 0$


$$B = \left. \frac{I_1}{-I_2} \right|_{V_2=0} \Rightarrow \text{Short circuit reverse current gain (no unit)}$$

$$D = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \Rightarrow \text{Short circuit input transfer impedance } (-\Omega)$$

• When  $I_2 = 0$

$$A = \left. \frac{I_1}{V_2} \right|_{I_2=0} \Rightarrow \text{Open circuit output transfer admittance } (-\sigma) \text{ or } (s)$$

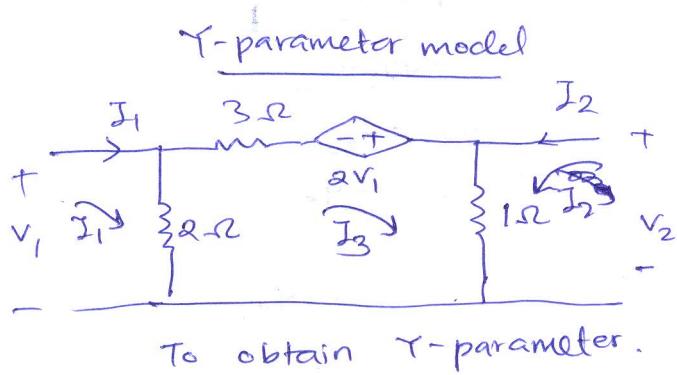2. T-parameter is a representation of 2-port network using the A, B, C, D as its component.



$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

Apply KVL in

$$V_1 - 2(I_1 - I_3) = 0$$

$$V_1 = 2I_1 - 2I_3 \quad \textcircled{1}$$

$$V_2 - i(I_2 + I_3) = 0$$

$$V_2 = I_2 + I_3 \quad \textcircled{3}$$

At  $V_2 = 0$ , to find  $Y_{11}, Y_{21}$

$$V_2 = I_2 + I_3$$

$$\boxed{I_2 = -I_3}$$

$$V_1 = 2I_1 - 2(-I_2)$$

$$V_1 = 2I_1 + 2I_2 \quad \textcircled{1}$$

$$\frac{V_1 - 2I_1}{2} = I_2 \quad \textcircled{1}$$

$$\frac{V_1 - 2I_2}{2} = I_1 \quad \textcircled{1}$$

$$-2V_1 = \frac{2V_1 - 4I_2}{2} + 5I_2$$

$$-4V_1 = 2V_1 - 4I_2 + 10I_2$$

$$-6V_1 = 6I_2$$

$$\boxed{Y_{21} = \frac{I_2}{V_1} = -\frac{6}{6} = -1S}$$

$$-2(I_3 - I_1) - 3I_3 + 2V_1 - 1(I_3 + I_2) = 0$$

$$-2I_3 + 2I_1 - 3I_3 + 2V_1 - I_3 - I_2 = 0$$

$$2V_1 = 2I_1 - I_2 - 6I_3 + 2V_1 = 0$$

$$-2V_1 = 2I_1 - I_2 - 6I_3 \quad \textcircled{2}$$

$$-2V_1 = 2I_1 - I_2 - 6(-I_2)$$

$$-2V_1 = 2I_1 - I_2 + 6I_2$$

$$-2V_1 = 2I_1 + 5I_2$$

$$-2V_1 = 2I_1 + \frac{5V_1 - 10I_1}{2}$$

$$-4V_1 = 4I_1 + 5V_1 - 10I_1$$

$$-9V_1 = -6I_1$$

$$\boxed{Y_{11} = \frac{I_1}{V_1} = \frac{9}{6} = \frac{3}{2} S}$$

To find  $Y_{22}, Y_{12}$ , Take  $V_1 = 0$

$$0 = 2I_1 - 2I_3$$

$I_1 = I_3$

$$V_2 = I_2 + I_1$$

$$V_2 = I_2 + \left(-\frac{1}{4}I_2\right)$$

$$\Rightarrow I_2 = I_2 \left(1 - \frac{1}{4}\right)$$

$$\frac{I_2}{V_2} = \boxed{Y_{22} = \frac{4}{3}s}$$

$$0 = 2I_1 - I_2 - 6I_1$$

$$0 = -4I_1 - I_2$$

$$4I_1 = -I_2$$

$$I_2 = -4I_1$$

$$V_2 = -4I_1 + I_1$$

$$\boxed{Y_{12} = \frac{I_1}{V_2} = -\frac{1}{3}s}$$

To obtain ABCD parameter.

$$A = \cancel{\frac{V_1}{V_2}} \quad B = V_1 = AV_2 - BI_2, \quad I_2 = \frac{A}{B}V_2 - \frac{1}{B}V_1 \quad \text{--- (1)}$$

$$I_1 = CV_2 - DI_2, \quad I_1 = CV_2 - D \left[ \frac{A}{B}V_2 - \frac{1}{B}V_1 \right]$$

Comparing eqn of  $\Upsilon$ -parameter.

$$I_1 = \left(C - \frac{AD}{B}\right)V_2 + \frac{D}{B}V_1$$

$$I_2 = \frac{A}{B}V_2 - \frac{1}{B}V_1$$

$$Y_{11} = \frac{D}{B}, \quad Y_{12} = C - \frac{AD}{B}$$

$$Y_{21} = -\frac{1}{B}, \quad Y_{22} = \frac{A}{B}$$

$$I_1 = \left(C - \frac{AD}{B}\right)V_2 + V_1 \left[\frac{D}{B} + \cancel{\frac{1}{B}}\right]$$

$$I_1 = \left(C - \frac{AD}{B}\right)V_2 + \frac{D}{B}V_1 \quad \text{--- (2)}$$

For  $\Upsilon$

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$B = \frac{-1}{Y_{21}} = \frac{-1}{-\frac{1}{3}} = 1$$

$$Y_{22} = \frac{A}{B}$$

$$Y_{11} = \frac{D}{B}$$

$$\boxed{B = 1\Omega}$$

$$A = \frac{4}{3} \times 1$$

$A = \frac{4}{3}$

$$D = \frac{3}{2}$$

$\cancel{\frac{3}{2}}$



$$Y_{12} = C - \frac{AD}{B}$$

$$C = -\frac{1}{3} + \frac{\frac{4}{3} \times \frac{3}{2}}{1}$$

$$= \frac{5}{3}$$

$\cancel{\frac{5}{3}}$

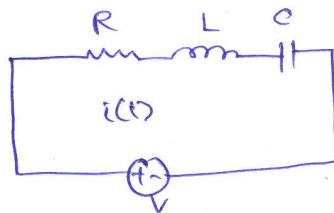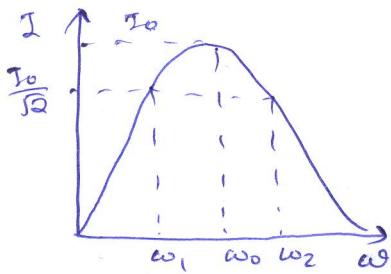3. In series resonant circuit,  $\omega_0 = \sqrt{\omega_1\omega_2}$



For the circuit  $P_{max} = I_0^2 R$

$$\frac{P_{max}}{2} = \left(\frac{I_0}{\sqrt{2}}\right)^2 R$$

At half power of circuit

$$I = \frac{I_0}{\sqrt{2}}$$

$$I = \frac{V}{R\sqrt{2}} - \textcircled{1}$$

$$I = \sqrt{R^2 + (X_L - X_C)^2} - \textcircled{2}$$

equating

$$R\sqrt{2} = \sqrt{R^2 + (X_L - X_C)^2}$$

~~$$R^2 \cancel{2} = R^2 + (X_L - X_C)^2$$~~

$$(X_L - X_C)^2 = R^2$$

$$X_L - X_C = \pm R$$

$$\omega_1 L - \frac{1}{\omega_1 C} = -R - \textcircled{A}$$

$$\omega_2 L - \frac{1}{\omega_2 C} = R - \textcircled{B}$$

Add  $\textcircled{A} + \textcircled{B}$

$$L[\omega_1 + \omega_2] - \frac{1}{C} \left[ \frac{\omega_1 + \omega_2}{\omega_1 \omega_2} \right] = 0$$


$$L[\omega_1 + \omega_2] = \frac{1}{C} \left[ \frac{\omega_1 \omega_2}{\omega_1 + \omega_2} \right]$$

$$\omega_1 \omega_2 = \frac{1}{L C}, \quad \text{where } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0^2 = \omega_1 \omega_2$$

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

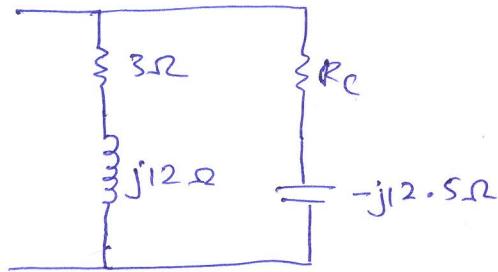Hence geometric mean of 2 half power frequencies is  $\omega_0$ .



$$-jX_C = -j12.5 \Omega \\ = \frac{1}{jX_C} = \omega C$$

~~$jX_L = j12 \Omega$~~

~~$\cancel{jX_L} = X_L$~~ 

$$X_L = 12 \Omega$$

$$\frac{1}{\omega C} = 12 \Omega$$

$$C = \frac{1}{12 \omega} \quad \text{--- (1)}$$

$$\omega L = 12$$

$$L = \frac{12}{\omega} \quad \text{--- (2)}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \cdot \left[ \frac{R_L^2 - \frac{L}{C}}{R_C^2 - \frac{L}{C}} \right]^{\frac{1}{2}}$$

$$\frac{X_L}{R_L^2 + X_L^2} = \frac{X_C}{R_C^2 + X_C^2} \quad / \quad X_C = 12.5 \quad X_L = 12$$


$$X_L(R_C^2 + X_C^2) = X_C(R_L^2 + X_L^2)$$

$$R_C^2 = \frac{X_C[R_L^2 + X_L^2] - X_L X_C^2}{X_L} \\ = \frac{12.5 [3^2 + 12^2] - [12 \times 12.5^2]}{12}$$

$$R_C^2 = 3.125$$

$$\underline{\underline{R_C = 1.7677 \Omega}}$$

4. series RLC circuit

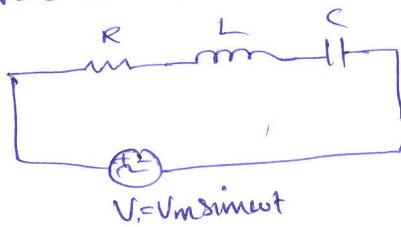

$$V = V_R + V_L + V_C$$

$$V = V_R + \frac{1}{2} \frac{di}{dt} + \frac{1}{C} \int V dt, \quad Z = \sqrt{R^2 + (X_L - X_C)^2}$$

For circuit to resonate

$$X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega_0^2 = \frac{1}{LC}, \quad \omega_0 = \frac{1}{\sqrt{LC}}, \quad \phi_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\omega_0 = 10,000 \text{ rad/s}$$

Given,  $R = 4 \Omega$ ,  $L = 1 \text{ mH}$ ,  $C = 10 \mu\text{F}$

$$\omega_0 = 31622.77 \text{ rad/s}$$

$$\begin{aligned} Q \text{ factor} &= \frac{\omega L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}} \\ &= \frac{31622.77 \times 10^{-3}}{4} \\ &= \underline{\underline{8.5}} \end{aligned}$$

$$BW = \frac{R}{L} = \frac{4}{10^3} = \underline{\underline{4000 \text{ rad/s}}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi \times \sqrt{10^3 \times 10^{-6}}} = \underline{\underline{1591.549 \text{ Hz}}}$$

$$\omega_1 = \omega_0 + \frac{BW}{2} = 10000 + \frac{4000}{2} = \underline{\underline{8000 \text{ rad/s}}}$$


$$\omega_2 = \omega_0 + \frac{BW}{2} = 10000 + \frac{4000}{2} = \underline{\underline{12000 \text{ rad/s}}}$$

5) At  $t=0^-$  switch is closed.

$$t = 0^-$$

$$i(0^-) = 0 = i(0^+)$$

At  $t=0$

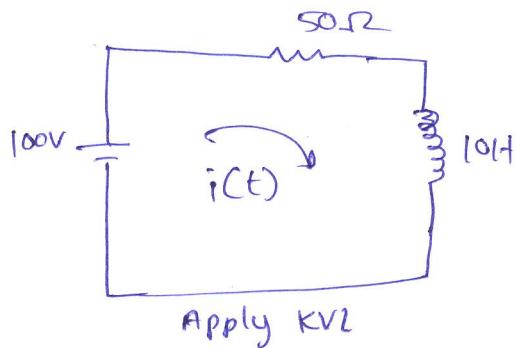

Apply KVZ

$$100 = 50i(t) + 10 \frac{di}{dt}$$

for circuit at any instant of time.

$$I(t) = \frac{V}{R} \left( 1 - e^{-\frac{t}{\tau}} \right)$$

$$\tau = \frac{L}{R} = \frac{10}{50} = 0.2$$

$$\begin{aligned} I(t) &= \frac{100}{50} \left( 1 - e^{-\frac{t}{0.2}} \right) \\ &= 2 \left( 1 - e^{-\frac{t}{0.2}} \right) \end{aligned}$$

At  $t=0.1s$

$$\begin{aligned} I(0.1) &= 2 \left( 1 - e^{-\frac{0.1}{0.2}} \right) \\ &= 0.7869 \text{ A} \end{aligned}$$

$$= 0.7869 \text{ A}$$

$$V_L = 100 e^{-\frac{t}{0.2}}$$

$$V_L(0.1) = 100 e^{-\frac{0.1}{0.2}}$$


$$= 60.65 \text{ V}$$

$$V_L = L \frac{di}{dt}$$

$$V_L = L \cdot \frac{V}{R} \cdot e^{-\frac{t}{\tau}} \cdot -\frac{1}{\tau}$$

$$V_L = V e^{-\frac{t}{\tau}}$$

- 6) a). • A purely resistive circuit :-

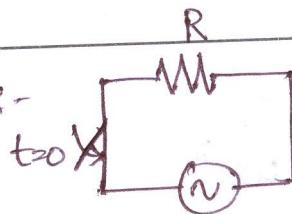


$$\text{At } t=0^- \Rightarrow R = \frac{V}{I}$$

$$\text{At } t=0^+ \Rightarrow R = \frac{V}{I}$$

Since  $R$  is independent of  $t$ , Resistor behaves the same in both steady state ( $t=\infty$ ) and transient state ( $t=0$ )

- Considering a pure inductive circuit

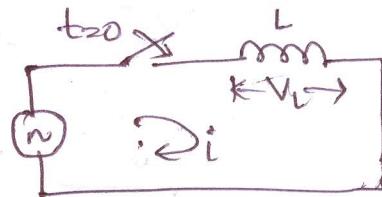

Current through inductor

$$i_L = i = \frac{1}{L} \int i dt$$

$$i_L(0^-) = \frac{1}{L} \left[ \int_{-\infty}^t i dt \right]$$

$$= \frac{1}{L} \left[ \int_{-\infty}^0 i_L dt + \int_0^t i_L dt \right]$$

$$i_L(0^-) = \frac{1}{L} \int_{-\infty}^0 i_L dt + 0$$

$$\boxed{i_L(0^-) = i_L(0^+)} \Rightarrow \text{Inductor current does not change instantaneously.}$$

$\therefore$  At  $t=0$ ,  $L$  acts as open circuit


At  $t=\infty$ ,  $L$  acts as short circuit

- Considering a capacitive circuit

Voltage through capacitor

$$V_C = \frac{1}{C} \int V dt$$
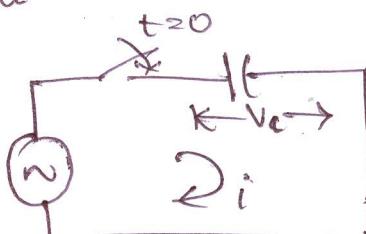
$$V_C(0^-) = \frac{1}{C} \left[ \int_{-\infty}^t V dt \right]$$



$$V_c(0^-) = \frac{1}{C} \int_{-\infty}^0 V_c dt + \frac{1}{C} \int_0^t V_c dt$$


$$= \frac{1}{C} \int_{-\infty}^0 V_c dt + 0$$

$\boxed{V_c(0^-) = V_c(0^+)} \Rightarrow$  Capacitor voltage does not change instantaneously.

$\therefore$  At  $t=0$ , C acts as short circuit

At  $t=\infty$ , C acts as open circuit.

b)

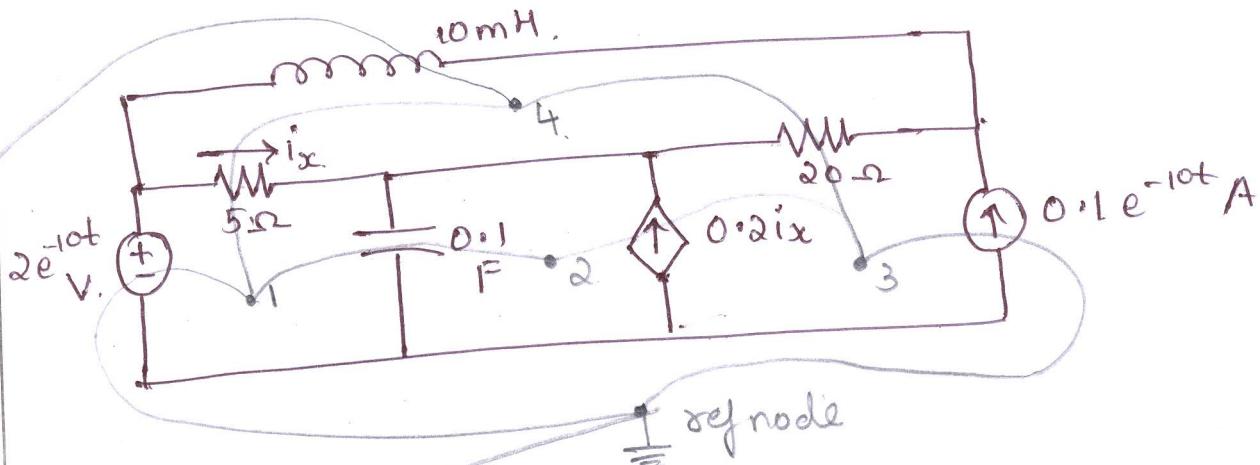

Dual network is represented as :-

