

# Expression for $g_m$

$$g_m = \frac{dI_D}{dV_{GS}} \Big|_{Q\text{-pt.}}$$

$$\text{But } I_D = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_P} \right]^2$$

$$g_m = 2I_{DSS} \left[ 1 - \frac{V_{GS}}{V_P} \right] \left[ -\frac{1}{V_P} \right]$$

$\frac{V_{GS}}{V_P}$  is true for both n-channel & p-

To get the value for  $g_m$ .

$$g_m = \frac{2I_{DSS}}{|V_P|} \left[ 1 - \frac{V_{GS}}{V_P} \right]$$

When  $V_{GS} = 0$

$$g_{m0} = \frac{2I_{DSS}}{|V_P|}$$

$$\left[ 1 - \frac{V_{GS}}{V_P} \right]$$

$200\Omega$ ,  $R_d \geq 10R_D$

$$R_d \parallel R_D = 0.909R_D$$

$$R_d \parallel R_D \leq R_D$$

$$Z_o \leq R_D$$


$$A_v \leq -g_m R_D$$

$$Z_o = r_d \parallel R_D$$

voltage gain :-

$$A_V = \frac{V_o}{V_i}$$

$$V_i = V_{gs}$$

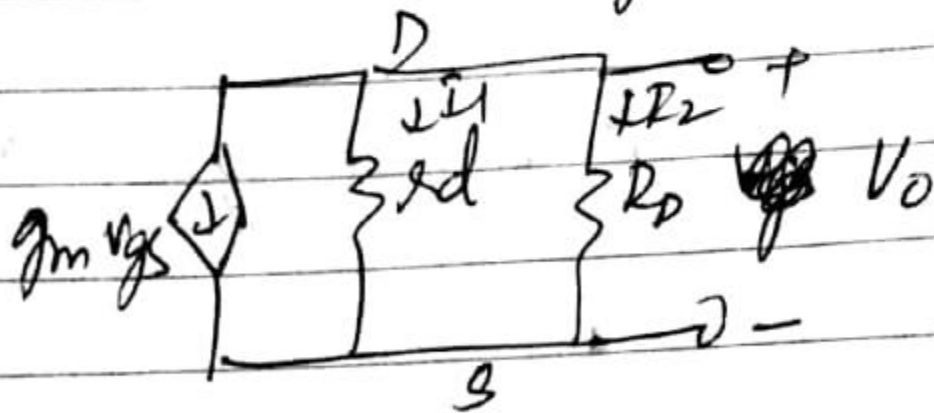


Apply KCL at the node

$$g_m V_{gs} + I_1 + I_2 = 0$$

$$I_1 = \frac{V_o}{r_d}$$

$$I_2 = \frac{V_o}{R_D}$$

AC Eq. Ckt is as shown

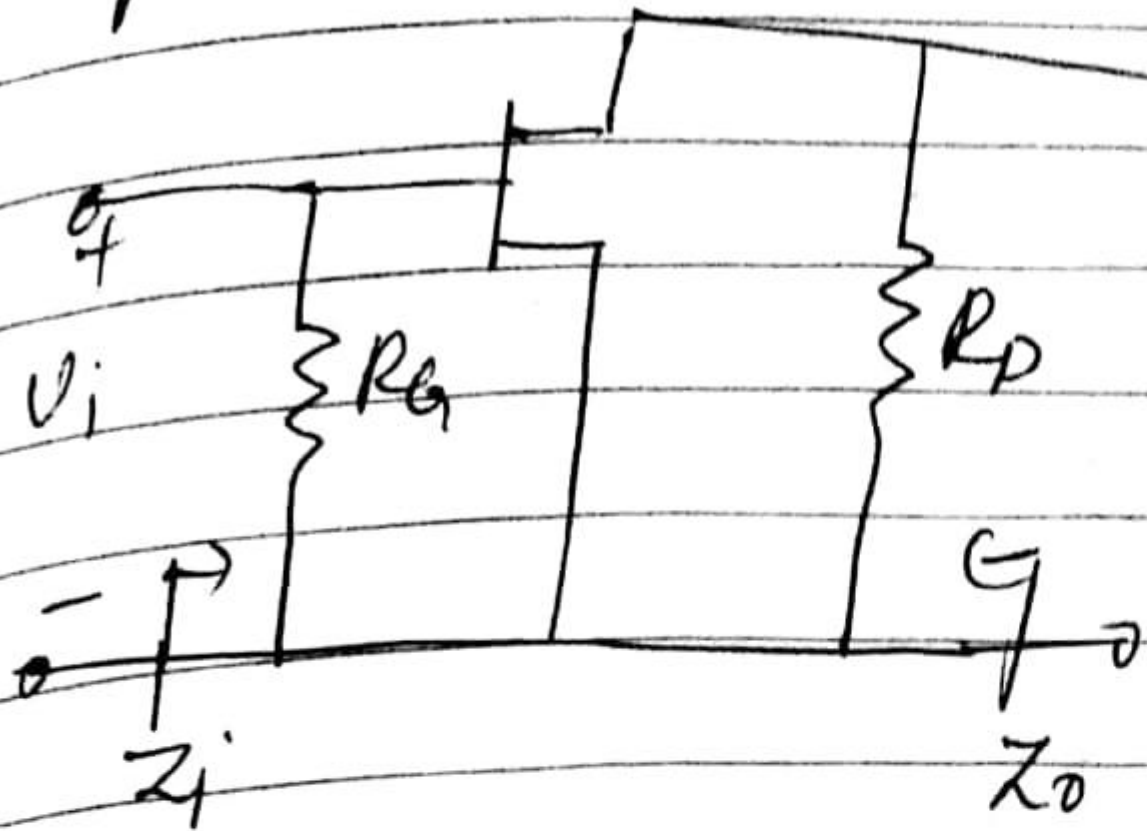

Let replace the JFET by its  
Ckt. The resulting Ckt is sho



$x_f'$  is identically equal to the signal  $x_f$ . If the external source terminal 2 is connected to terminal 1 the amplifier will continue to give

$x_f' = x_f$  means the instantaneous values are exactly equal at all times.  $x_f'$ 's feedback is the

$$\text{loop gain} = -A\beta$$

$$-A\beta = 1 + \dots$$

$$-A\beta = \dots$$

$$\therefore -A\beta = \dots$$

$$|1 - A\beta| = |A\beta| = 1$$

$$0 = 1 - A\beta = \dots$$

Conditions for Barkhausen

An oscillator is a circuit designed to  
 with no i/p signal. It requires an  
 An oscillator is basically an amp  
 feedback.

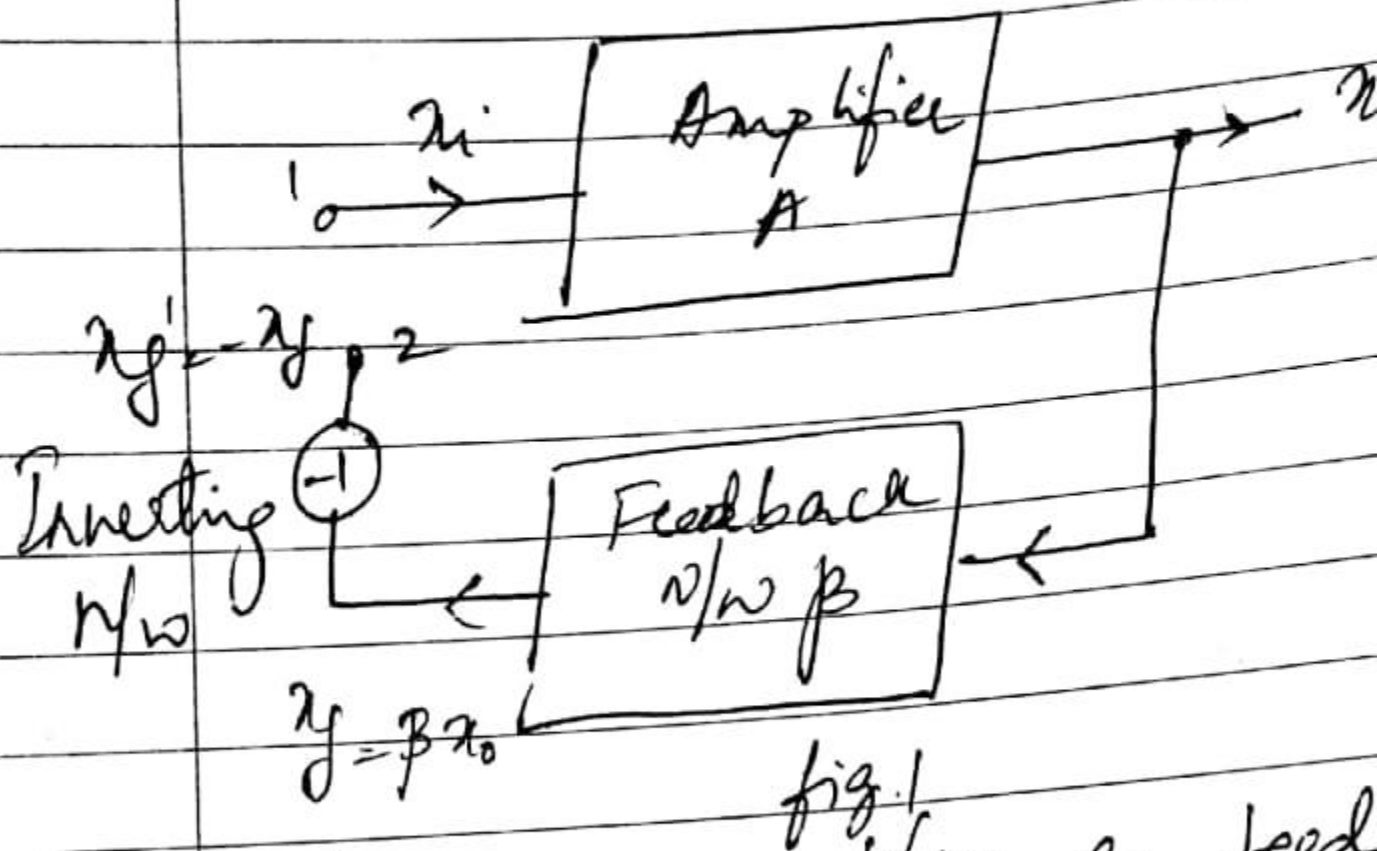


fig.1

fig.1 shows an amplifier a feed  
 inverting ~~amplifier~~  $n/w$  not yet a  
 closed loop.


The amplifier provides an o/p signal  
 signal  $x_i$  applied directly to the

Wien Bridge oscillator  
 is an RC oscillator & is used  
 in the audio frequency range.  
 It consists of an op-amp having  
 the feedback path of a lead-lag  
 path.

Series RC,  $n/w \rightarrow$  lead  $n/w$



parallel RC,  $n/w \rightarrow$  lag  $n/w$

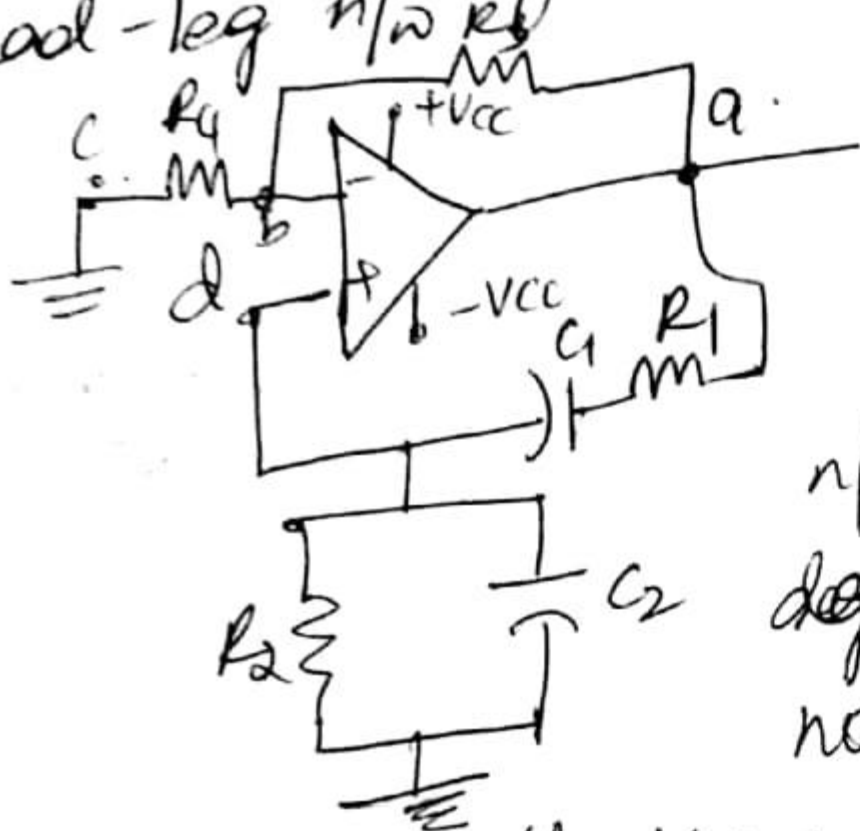The fb resistors  $R_3$  &  $R_4$  of op-  
 amp forms a bridge as



At the oscillation  
 $n/w$  is designed  
 degree phase  
 non-inverting a

Hence the total

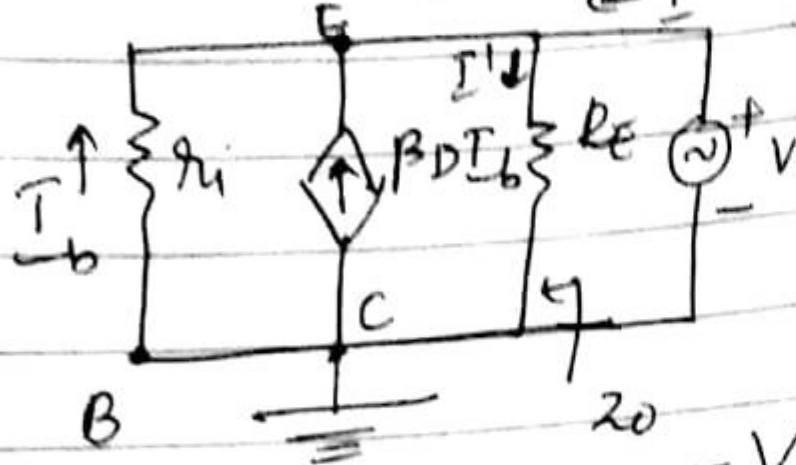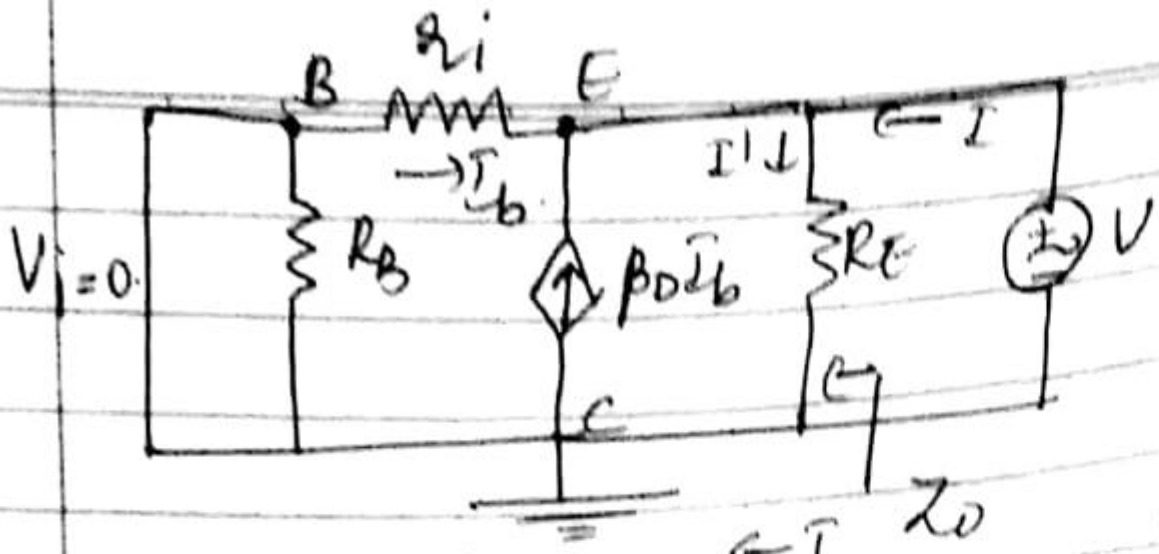

Apply

$$I_b + \beta_D I_b = \frac{V}{R_E + R_L}$$

$$I_b = \frac{-V}{r_i}$$

$$\frac{-V}{r_i} + \beta_D \left( \frac{-V}{r_i} \right)$$

$$V \left[ \frac{1}{r_i} + \frac{\beta_D}{r_i} + \frac{1}{R_E + R_L} \right]$$

$$\frac{V}{I} = \left[ \frac{1}{\frac{1}{r_i} + \frac{\beta_D}{r_i} + \frac{1}{R_E + R_L}} \right]$$

$$\frac{V}{I} = r_i \parallel \beta_D \parallel (R_E + R_L)$$



$$\frac{I_b}{I_i} = \frac{R_B}{R_B + Z_b}$$

$$A_i = \beta_D \frac{R_B}{R_B + Z_b}$$

voltage gain:  $-(A_v)$

$$V_o = I_e R_E \\ = (1 + \beta_D) I_b R_E$$

$$V_i = I_b [Z_i] \\ = I_b [R_i + (1 + \beta_D) R_E]$$

$$\text{Now } A_v = \frac{V_o}{V_i} = \frac{(1 + \beta_D) I_b R_E}{I_b [R_i + (1 + \beta_D) R_E]}$$

Ac i/p impedance ( $Z_i$ )

Applying KVL to the i/p ckt

$$V_i = I_b r_i + I_e R_E$$

w.k.t  $I_e = (1 + \beta_D) I_b$

$$V_i = I_b r_i + (1 + \beta_D) R_E I_b$$

$$Z_b = \frac{V_i}{I_b} = r_i + (1 + \beta_D) R_E$$

$\beta_D$  is very high, Hence


$$Z_i = \frac{V_i}{I_i} = R_B \parallel Z_b$$

Current gain  $i$

$$A_I = \frac{I_o}{I_i} = \frac{I_o}{I_b} \times \frac{I_b}{I_i}$$
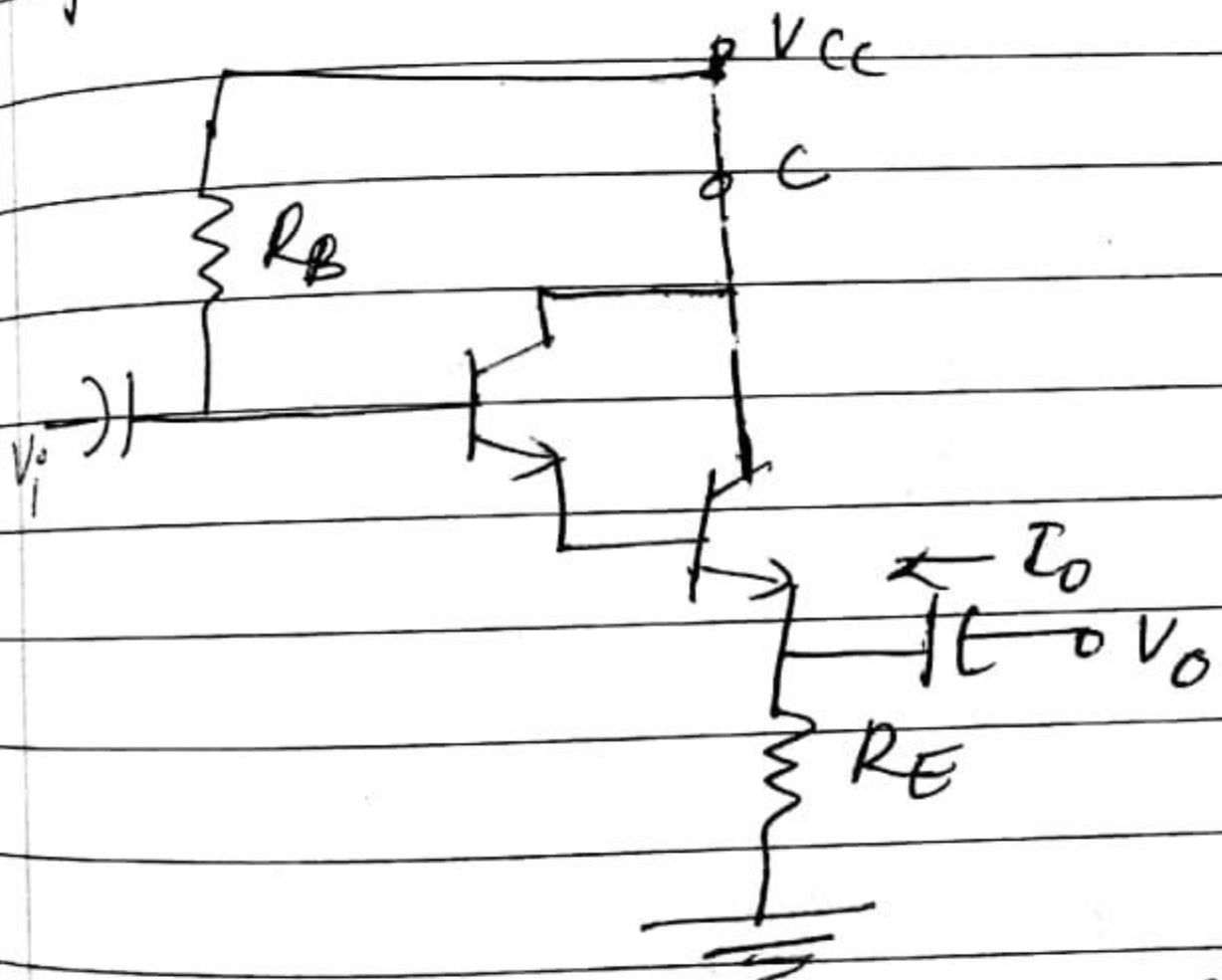
# Darlington emitter follower

The ac input  $v_i$  is coupled to the base of the first transistor of the darlington transistor through the coupling capacitor  $C_1$ . The ac output is taken from the emitter of the second transistor through the capacitor  $C_2$ .



The ac equivalent circuit of the

The o/p impedance will be eq  
impedance of the last stage.

$$Z_i = Z_{i1} \quad \& \quad Z_o = Z_{o3}.$$

Since the o/p of one stage is con  
the other stage.

$$V_{i2} = V_{o1} \quad \& \quad V_{i3} = V_{o2}.$$

The overall vlg gain,

$$A_{VT} = \frac{V_o}{V_i}$$


$$= \frac{V_o}{V_{i3}} \times \frac{V_{i3}}{V_{i2}}$$

$$A_{VT} = A_{V3} \times A_{V2} \times A_{V1}$$

The cascade of CE & CB stages of amplifiers.

Cascaded systems :-

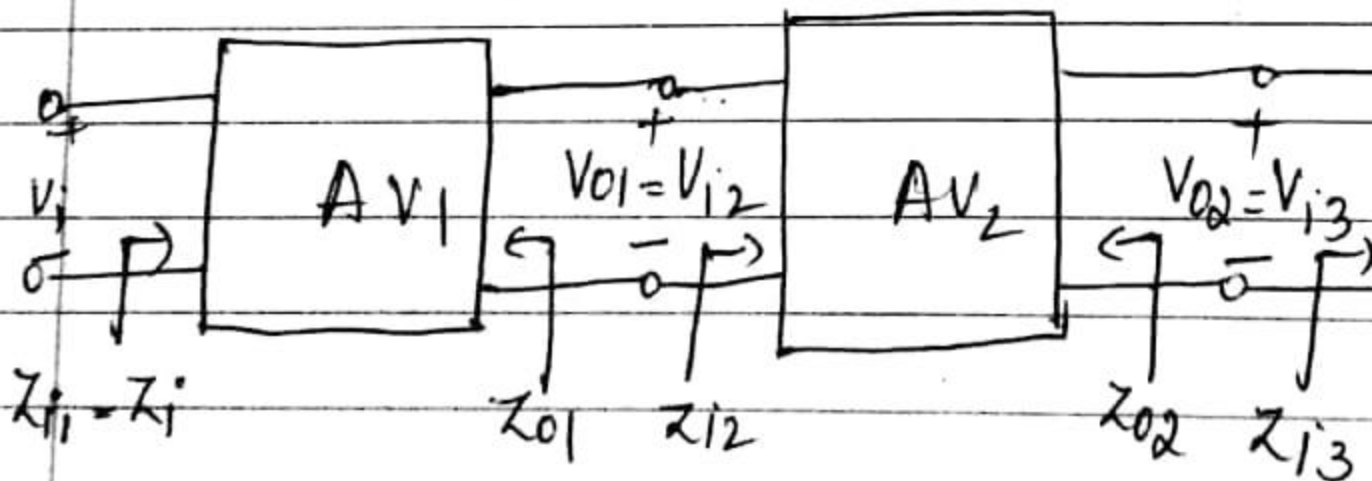When the amplification from a amplifier is not sufficient for a when the input or o/p impedance magnitude for the intended application amplifiers are connected in cascade given stage is connected to the stage. Such an arrangement is known as multistage amplifiers.



Relation B/w  $I_D$  &  $g_m$ .

$$I_D = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_p} \right]^2$$

$$\frac{I_D}{I_{DSS}} = \left[ 1 - \frac{V_{GS}}{V_p} \right]^2$$

$$\left[ \frac{1 - V_{GS}}{V_p} \right]^2 =$$

w.k.T  $g_m = g_{m0}$

$$\frac{g_m}{g_{m0}}$$