

Re-modified
13/11/2020

CBGS SCHEME

USN

--	--	--	--	--	--	--	--

18EE32

Third Semester B.E. Degree Examination, Dec.2019/Jan.2020 Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Setup nodal equations for the circuit of Fig.Q1(a) and then find the power supplied by 5 – V source.

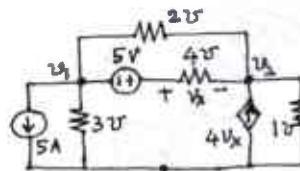


Fig.Q1(a)

(08 Marks)

- b. Making use of source shifting procedure, simplify the circuit of Fig.Q1(b) in such a way that the voltage V_x is determined.

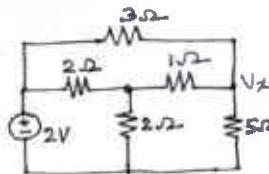


Fig.Q1(b)

(06 Marks)

- c. Use mesh analysis to determine the branch currents in the network indicated in Fig.Q1(c).

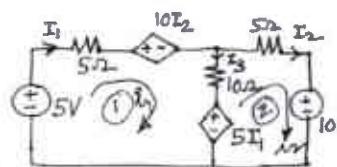


Fig.Q1(c)

(06 Marks)

OR

- 2 a. Find 'Req' for the network shown in Fig.Q2(a) across A and B.

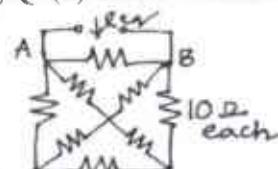


Fig.Q2(a)

(06 Marks)

- b. Draw the exact dual of the network shown in Fig.Q2(b) by writing Kirchhoff's law equations.

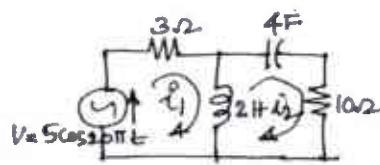


Fig.Q2(b)

(08 Marks)

- c. Reduce the network of Fig.Q2(c) to a form with only one current source across terminals using source transformation (terminals A and B).

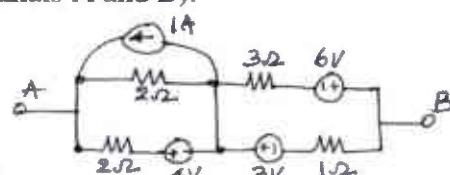


Fig.Q2(c)

Module-2

- 3 a. Find the Thevenin's equivalent circuit at the terminals A and B of the circuit in Fig.Q3(a).

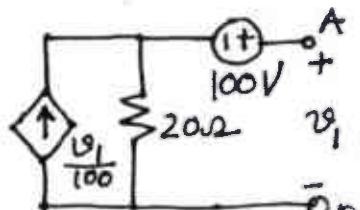


Fig.Q3(a)

(08 Marks)

- b. Find the value of R_L in the network shown in Fig.Q3(b) that will absorb a maximum power and specify the value of that power.

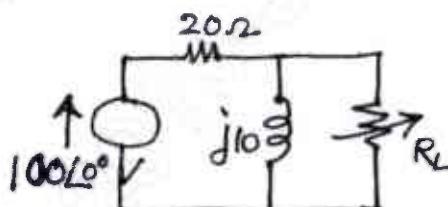


Fig.Q3(b)

(06 Marks)

- c. In the network shown in Fig.Q3(c) the voltage source of 5V causes a current I in the 2Ω resistor. Find 'I'. Verify the reciprocity theorem.

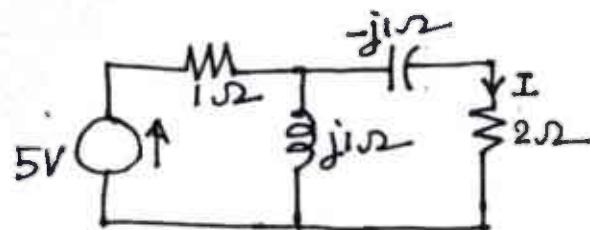


Fig.Q3(c)

(06 Marks)

OR

- 4 a. In the network shown in Fig.Q4(a) determine the nodal voltage V_2 using superposition theorem.

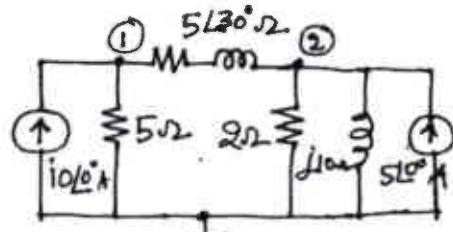


Fig.Q4(a)

(08 Marks)

- b. Use Thevenin's theorem to find current in $R_L = 6\Omega$ in Fig.Q4(b).

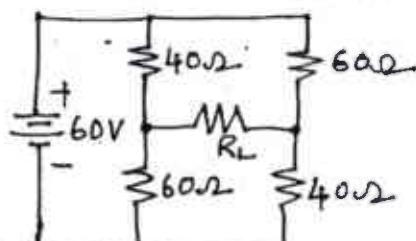


Fig.4(b)

(08 Marks)

- c. State and prove Millman's theorem.

(04 Marks)

Module-3

- 5 a. Derive an expression for resonant frequency ' f_0 ' for the general parallel resonant circuit show in Fig.Q5(a).

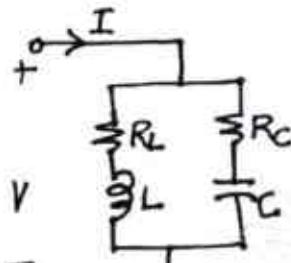


Fig.Q5(a)

(08 Marks)

- b. Fig.Q5(b) shows a network with zero capacitor voltage and zero inductor current when the switch 'K' is open. At $t = 0$ the switch 'K' is closed. Solve for :

- V_1 and V_2 at $t = 0^+$
- $\frac{dv_1}{dt}$ and $\frac{dv_2}{dt}$ and $t = 0^+$
- V_1 and V_2 at $t = \infty$

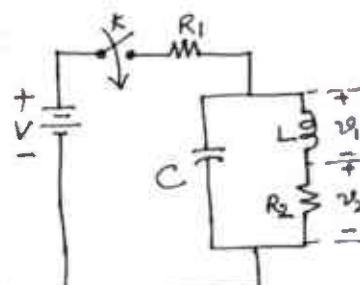


Fig. Q5(b)

(12 Marks)

OR

- 6 a. Fig.Q6(a) shows a RCL parallel circuit excited by a DC current source. At $t = 0$, the switch K is opened. Find $v(t)$.

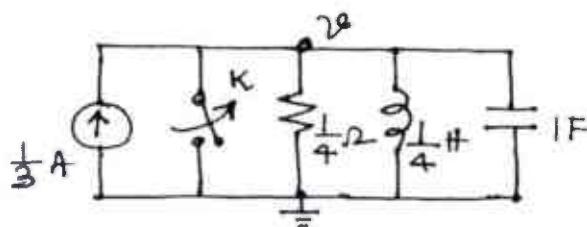


Fig.Q6(a)

(08 Marks)

- b. A 400V, 200Hz AC source is connected in series with a capacitor and a coil whose resistance and inductance are $20\text{m}\Omega$ and 6mH respectively. If the circuit is in resonance at 200Hz, find :
- Value of capacitor
 - V_g A/C the capacitor
 - Maximum energy stored (instantaneous) in the coil
 - The half – power frequencies.

(08 Marks)

What are initial conditions in network? Write the equivalent form of the network elements in terms of the initial conditions.

(04 Marks)

Module-4

- 7 a. Find the Lapalce transform of the square wave shown in Fig.Q7(a).

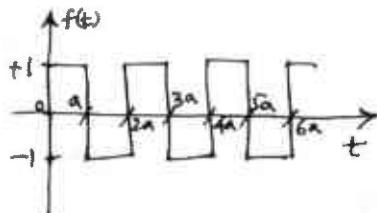


Fig.Q7(a)

(08 Marks)

- b. Fig.Q7(b) shows a series R-L-C circuit excited by a voltage $v(t) = 12 \sin 5t$. The initial current in the circuit is 5A and the initial voltage across capacitor is one volt with polarity shown. Find $i(t)$ using Lapalce transformation method.

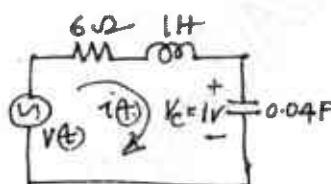


Fig.Q7(b)

(08 Marks)

- c. State and prove the initial-value theorem in the context of Lapalce transformation. (04 Marks)

OR

- 8 a. A rectangular voltage pulse of unit height and duration 'T' is applied to a series R-C combination at $t = 0$. Determine the voltage across the capacitance 'C' as a function of time. Use Laplace transformation method. (10 Marks)
- b. Find the Laplace transforms of the two different functions given below and sketch the waveforms. i) $\sin(wt) u(t - t_0)$ ii) $\sin w(t - t_0) u(t - t_0)$. (10 Marks)

Module-5

- 9 a. A symmetrical 3 - ϕ , 100V, 3-wire supply feeds an unbalanced star-connected load with impedances of the load as $Z_R = 5|0^\circ\Omega$, $Z_Y = 2|90^\circ\Omega$ and $Z_B = 4|-90^\circ\Omega$. Find the line currents, voltage across the impedances and the displacement natural voltage. Also calculate the power consumed by the load. Draw the phasor diagram sequence RYB. Take V_{RY} as ref. (10 Marks)
- b. For the circuit of Fig.9(b) find Z-parameters. Hence calculate transmission (ABCD) parameters. Find whether the network is symmetrical? Reciprocal?

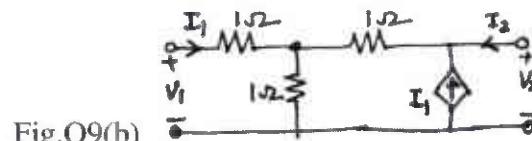


Fig.Q9(b)

(10 Marks)

OR

- 10 a. A 3- ϕ delta connected load has $Z_{RY} = (100 + j50)\Omega$, $Z_{YB} = (20 - j75)\Omega$ and $Z_{BR} = (70.7 + j70.7)\Omega$ and it is connected to balanced 3 - ϕ , 400V supply. Determine the line currents, power consumed by the load. Sketch the phasor diagram. Assume RYB phase sequence and take V_{YB} as the reference phasor. (10 Marks)
- b. For the circuit shown in Fig.Q10(b) find Y-parameters. Is the network symmetrical? Reciprocal?

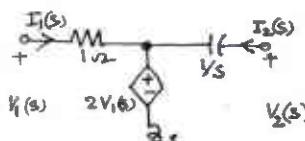


Fig.10(b)

(10 Marks)

Modification in Scheme and solutions in subjects Electrical Circuit Analysis

message

Ir. A.Manjunath <manjuprinci@gmail.com>
o: pmanjunath p <pmanjunathvtu@gmail.com>

Mon, Jan 13, 2020 at 1:12 PM

Good Morning

The modifications in Scheme and solutions of subjects 18EE32 Electrical Circuit Analysis


Q.no.5b. Full marks may be awarded for steps with wrong solution.

Q.no.6a. Full marks may be awarded for steps with wrong solution.

Q.no.7b. Full marks may be awarded for steps with wrong solution.

Dr.A.Manjuanthan
Chairman BOE,EEE

APPROVED

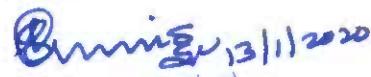

Registrar (Evaluation)

Visvesvaraya Technological University

BELAGAVI - 18



Pinni
Signature of Scrutinizer

Subject Title : Electric circuit Analysis

Subject Code : 18EE32

Question Number

Solution

Marks Allocated

Q1 @

$$\text{KCL at node } 1 : 9V_1 - 6V_2 = -25 \quad (02)$$

$$\text{KCL at node } 2 : -10V_1 + 11V_2 = 40 \quad (02)$$

$$V_1 = -0.8974 \text{ V} ; V_2 = 2.8205 \text{ V} \quad (02)$$

$$\text{Power supplied} = P_{SV} = 5 \times 4 \times 1.282 \quad (02)$$


$$P_{SV} = 25.6 \text{ W} \quad (02)$$

$$P_{SV} = 5 \times (V_x/4) \quad (02)$$


$$\text{Share} \\ V_x = V_1 + 5 - V_2 \\ V_x = 1.282 \text{ V} \quad (02)$$

08

(b)

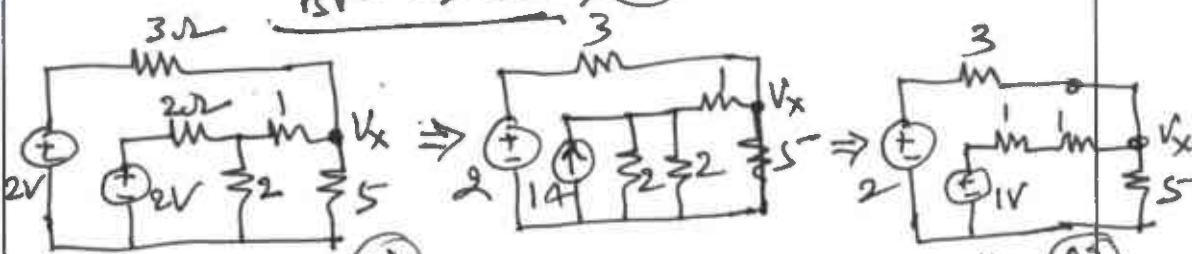

08

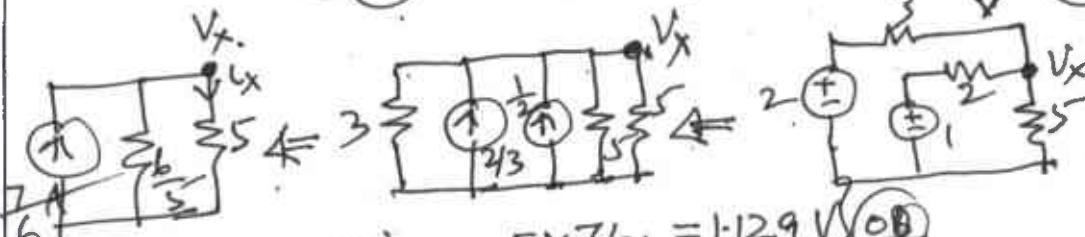

06

(c)

$$\text{Loop } 1 : 5i_1 + 10i_2 + 10(i_1 - i_2) + 5i_4 - 5 = 0. \quad (02)$$

$$5i_1 + 10i_2 + 10i_1 - 10i_2 + 5i_1 = 5 \quad \& \quad i_2 = i_1$$

$$20i_1 = 5 \quad \therefore i_1 = 0.25 \text{ A} \quad (02)$$

$$\text{Loop } 2 : 5i_2 + 10 - 5i_1 + 10(i_2 - i_1) = 0 \quad (02)$$

$$5i_2 + 10 - 5i_1 + 10i_2 - 10i_1 = 0 \quad (02)$$


$$-15i_1 + 15i_2 = -10 \quad \therefore i_2 = -0.4167 \text{ A} \quad (02)$$

$$i_4 = 0.25 \text{ A} \quad (02)$$

$$i_2 = -0.4167 \text{ A} \quad (02)$$

$$i_3 = 0.6667 \text{ A} \quad (02)$$

Q2 @

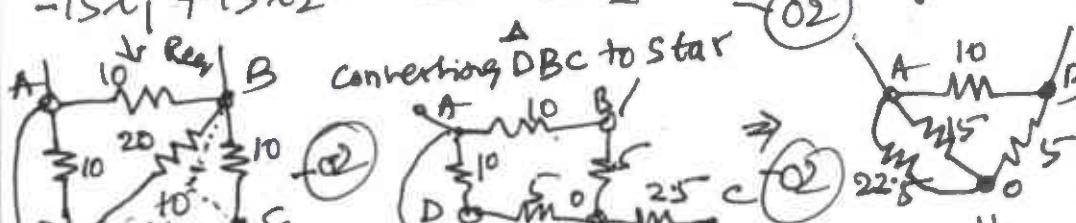

06

APPROVED

Amma



Registrar (Evaluation)




Visvesvaraya Technological University
BELAGAVI - 590018


Question Number	Solution	Marks Allocated
Q2(b)	<p>KVL for Loop 1: $3i_1 + 2 \frac{d(i_1 - i_2)}{dt} = 5 \cos 20\pi t$ (1)</p> <p>KVL for Loop 2: $\frac{1}{4} \int_0^t i_2 dt + 10i_2 + 2 \frac{d(i_2 - i_1)}{dt} = 0 \dots (2)$</p> <p>The exact dual equations of (1) & (2) are</p> <p>$3v_1 + 2 \frac{d(v_1 - v_2)}{dt} = 5 \cos 20\pi t \dots (3)$ (08)</p> <p>$\frac{1}{4} \int_0^t v_2 dt + 10v_2 + 2 \frac{d(v_2 - v_1)}{dt} = 0 \dots (4)$</p>	
Q2(c)		
Q3(a)	<p>To find V_{AB}: open circuit v_2 at terminals AB: Applying KVL eqn.</p> <p>$20\left(\frac{v_1}{100}\right) - v_1 + 100 = 0 \therefore v_1 = V_{AB} = 125V$ (02)</p> <p>To find R_{th}: short circuit terminals AB & find i_{sc}</p> <p>$\therefore i_{sc} = \frac{100}{20} = 5A$ (02)</p> <p>$\therefore R_{th} = \frac{V_{ab}}{i_{sc}} = \frac{125}{5} = 25\Omega$ (02)</p> <p>The eq. ckt:</p>	(08)
3(b)	<p>Thevenin's eq. ckt at the terminals of R_L i.e. Remove the R_L & find the $V_{oc} = V_{RL}$ (01)</p> <p>$\therefore V_{RL} = \frac{100 \angle 0^\circ}{20 + j10} \times j10 = \frac{100 \angle 0^\circ \times 10 \angle 90^\circ}{22.36 \angle 26.56^\circ} = 44.72 \angle 63.44^\circ V$ (02)</p> <p>$Z_{RL} = \frac{20 \times j10}{20 + j10} = 8.94 \angle 63.44^\circ \therefore R_L = Z_{RL} = 8.94 \Omega$ (01)</p> <p>$I_L = \frac{V_{RL}}{2R_L + R_L} = 2.94 \angle 31.72 A$</p> <p>$P_{max} = I_L^2 R_L = 2.94^2 \times 8.94 = 77.27 W$ (01)</p>	(06)

Question Number	Solution	Marks Allocated
3 (c)	$(1+j1)I_1 - j1 I_2 = 5; -jI_1 + 2I_2 = 0$ $I_2 = \frac{j5}{3+j2} = I''(A) \rightarrow 02$ <p>5V source is placed in series with node 2-2</p> $(1+j1)I_1 - j1 I_2 = 0$ $-jI_1 + 2I_2 = -5$ $I_1 = \frac{-5j}{3+j2} = -I'' = \frac{j5}{3+j2} \rightarrow 02$ <p>Hence Theorem.</p>	(06)
Q4 (a)	$\text{KCL at } 1: \left(\frac{1}{5} + \frac{1}{5L30^\circ}\right)V_1' - \frac{1}{5L30^\circ}V_2' = 10L0^\circ \rightarrow 01$ $\text{KCL at } 2: \frac{-1}{5L30^\circ}V_1' + \left[\frac{1}{5L30^\circ} + \frac{1}{2} + \frac{1}{j10}\right]V_2' = 0 \rightarrow 02$ $V_2' = 8 \cdot 5 L-3^\circ V \rightarrow 01 \text{ open } 10 L0^\circ \text{ A source}$ $\text{at node } 1: \left(\frac{1}{5} + \frac{1}{5L30^\circ}\right)V_1'' - \frac{1}{5L30^\circ}V_2'' = 0 \rightarrow 03$ $\text{at node } 2: -\frac{1}{5L30^\circ}V_1'' + \left(\frac{1}{5L30^\circ} + \frac{1}{2} + \frac{1}{j10}\right)V_2'' = 5L0^\circ \rightarrow 04$ $V_2'' = 8 \cdot 14 L12^\circ V \rightarrow 01 \text{ by Superposition}$ $V_2 = V_2' + V_2'' = 16 \cdot 45 L4.35^\circ$	(-1) (02)
Q4 (b)	<p>To find V_{OC} open R_L</p> $I = \frac{60}{100 \times 100} = \frac{6}{5} A : I_1 = \frac{3}{5} A$ $I_2 = \frac{3}{5} A$ $40I_1 + V_{OC} - 60I_2 = 0 \rightarrow 01$ $V_{OC} = (60 - 40)I_1 = 20 \times \frac{3}{5} = 12V \rightarrow 02$ $R_L = 48 \Omega \rightarrow 01$ $V_{OC} = \frac{(60+40) \times (60+40)}{200} = 48V \rightarrow 02$	(02) (01)
(c)	<p>Statement: 02</p> <p>Proof:</p> $E_A = \frac{E_1 Y_1 + E_2 Y_2}{Y_1 + Y_2} \rightarrow 02$	(02)

Question Number	Solution	Marks Allocated
Q5(a)	$Y_{in} = \left(\frac{R_L}{R_L^2 + X_L^2} + \frac{R_C}{R_C^2 + X_C^2} \right) + j \left(\frac{X_C}{R_C^2 + X_C^2} - \frac{X_L}{R_L^2 + X_L^2} \right) - 0.4$ <p>j term is zero at resonance $\omega = \omega_0$</p> $\frac{X_C}{R_C^2 + X_C^2} = \frac{X_L}{R_L^2 + X_L^2} \text{ or } X_C R_L^2 + X_C X_L^2 = X_L R_C^2 + X_L X_C^2$ $\omega_0 = \frac{1}{\sqrt{L C}} \sqrt{\frac{4C - R_L^2}{4C - R_C^2}}$ <p>Eq. ext at $t=0^+$</p>	08
(b)	<p>for $t > 0$ $R_1 i_1 + \frac{1}{C} \int (i_1 - i_2) dt = V$; $L \frac{di_2}{dt} + R_2 i_2 + \frac{1}{C} \int (i_2 - i_1) dt = 0$</p> <p>$i_1(0^+) = \frac{V}{R_1}$; $i_2(0^+) = 0$; $V_1(0^+) = 0$; $V_2(0^+) = 0$</p> <p>$\frac{dV_2}{dt}(0^+) = R_2 \frac{di_2}{dt}(0^+) = 0$; $\frac{dV_1}{dt}(0^+) = \frac{V}{R_1 C}$</p> <p>At $t = \infty$: $V_1(\infty) = 0$; $i_2 = \frac{V}{R_1 + R_2}$; $V_2(\infty) = \frac{VR_2}{R_1 + R_2}$</p> <p>KCL eq. for V: $C \frac{dV}{dt} + G V + \frac{1}{L} \int i_2 dt = I$</p> <p>$\frac{d^2 V}{dt^2} + 4 \frac{dV}{dt} + 4V = 0 \therefore s^2 + 4s + 4 = 0 \therefore s_1 = -2, s_2 = -2$</p> <p>$V(t) = K_1 e^{-2t} + K_2 t e^{-2t}$</p> <p>$K_1 = 0 \text{ and } K_2 = V_3$</p> <p>$\therefore V(t) = \frac{1}{3} t e^{-2t}$</p>	02 02 02 02 12
Q6	<p>(i) $f_0 = \frac{1}{2\pi\sqrt{LC}}$; $C = \frac{1}{4\pi^2 L f_0^2} = 105.54 \mu F$</p> <p>(ii) $I_0 = V/R = 20,000 A$; $V_C = I_0 X_C = 151 kV$</p> <p>(iii) Maximum instantaneous energy = $W = \frac{1}{2} L I_0^2$</p> <p>$W = \frac{1}{2} \times 0.006 \times (20,000 \sqrt{2})^2 = 24 \times 10^6 J$</p> <p>$Q_0 = \frac{w_0 L}{R} = 377$; $\Delta f = \frac{f_0}{Q_0} = 0.53 Hz$</p> <p>$f_1 = f_0 - \frac{1}{2} \Delta f = 199.74 Hz$; $f_2 = f_0 + \frac{1}{2} \Delta f = 200.26 Hz$</p> <p>Definition - 02</p> <p>Eq. ext: </p>	02 02 02 02 08
(c)		04

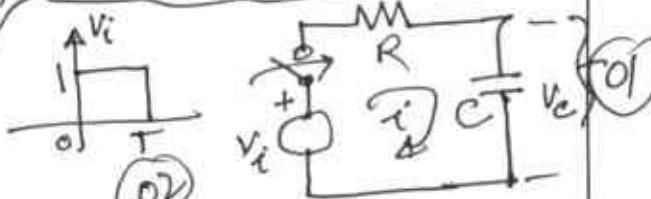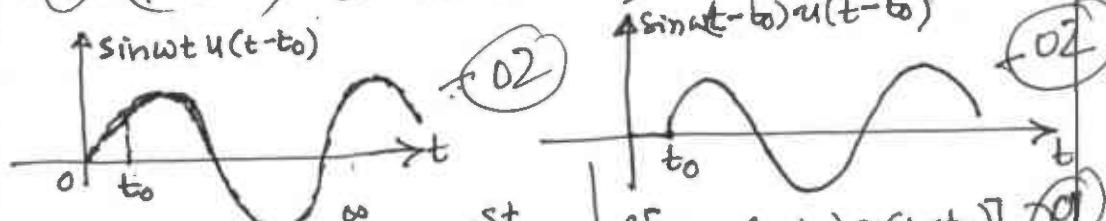Question Number	Solution	Marks Allocated
Q7(a)	$f_1(t) = 2u(t) - 2u(t-a) + 2u(t-2a)$ 02 $F_1(s) = \frac{1}{s}(1 - 2e^{-as} + e^{-2as}) = \frac{1}{s}(1 - e^{-as})^2$ 03 $T = 2a$. LT of sequence $F(s) = \frac{1}{1-e^{Ts}} F_1(s) = \frac{1}{s} \frac{(1-e^{-as})^2}{(1-e^{-2as})}$ 02 $F(s) = \frac{1}{s} \tanh\left(\frac{as}{2}\right)$ 01	08
(b)	<p>KVL eq. for $t > 0$; $6i + \frac{di}{dt} + \frac{1}{0.04} \int idt = 12 \sin 5t$</p> <p>Taking LT. $6I(s) + sI(s) + 25 \frac{dI}{ds} + \frac{1}{s} - 5 = \frac{60}{s^2 + 25}$ 02</p> $I(s) = \frac{60s}{(s^2 + 25)(s^2 + 6s + 25)} + \frac{58-1}{s^2 + 6s + 25}$ 02 $i(t) = 5e^{-3t} \cos 4t - 6.5e^{-3t} \sin 4t + 2 \sin 5t$ 04	08
c	<p>State assert - 02</p> <p>Pruf - 02</p>	
Q8	<p>(a)</p> $RC \frac{dv_c}{dt} + v_c = v_i(t)$ 02  $RC \frac{dv_c}{dt} + v_c = u(t) - u(t-T)$ 02 $RC \frac{dv_c}{dt} + v_c = u(t) - u(t-T)$ 02 $RC[sV_c(s) - v_c(0^+)] + V_c(s) = \frac{1}{s}(1 - e^{-Ts})$ since $v_c(0^+) = 0$ 02 $(RCs + 1)V_c(s) = \frac{1}{s}(1 - e^{-Ts})$; $V_c(s) = \frac{1 - e^{-Ts}}{s(RCs + 1)}$ 01 $v(t) = (1 - e^{-t/RC})u(t) - (1 - e^{-(t-T)/RC})u(t-T)$ 02 <p>(b)</p>  $\mathcal{L}[\sin w t u(t-t_0)] = \int_{t_0}^{\infty} \sin w t e^{-st} dt$ 01 $= \frac{1}{2j} \int_{t_0}^{\infty} (s+jw)t - (s-jw)t dt$ $= e^{t_0 s} \left[\frac{w \cos w t_0 + s \sin w t_0}{s^2 + w^2} \right]$ 02 $\mathcal{L}[\sin w(t-t_0) u(t-t_0)] = \bar{e}^{t_0 s} \mathcal{L}[\sin w t]$ 02 $= \bar{e}^{t_0 s} \left(\frac{w}{s^2 + w^2} \right)$ 02	10

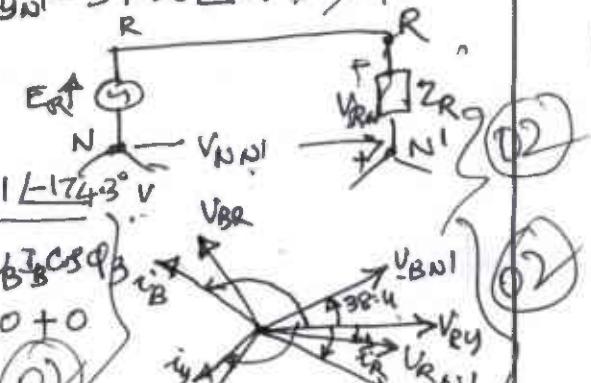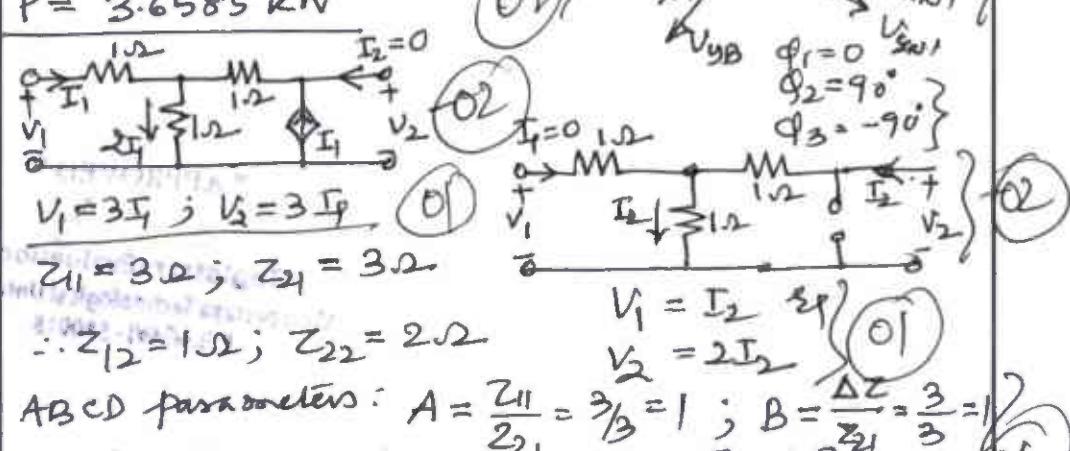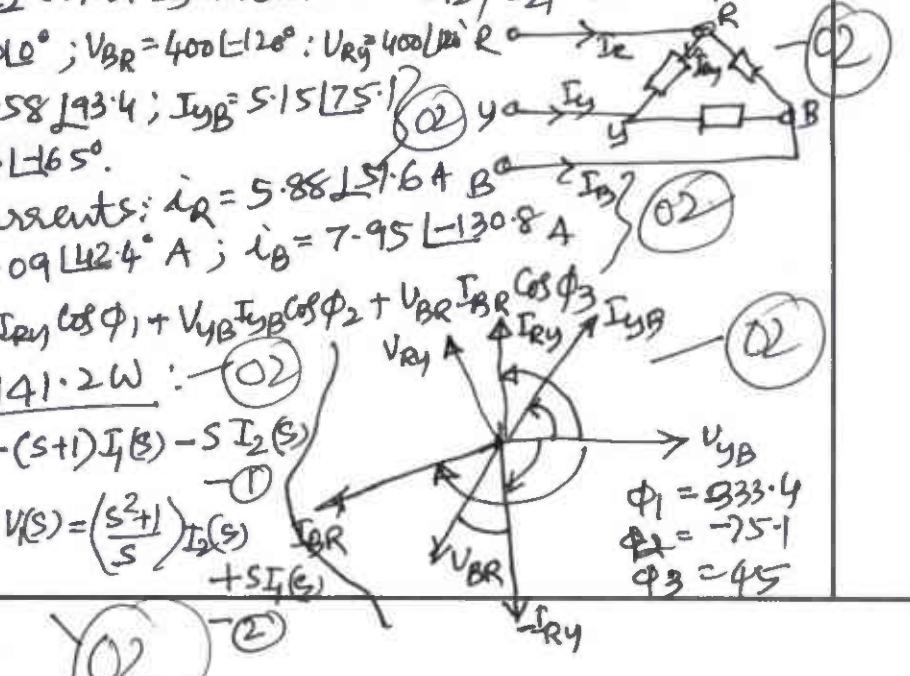Question Number	Solution	Marks Allocated
Q 9(a)	<p>$V_{RY} = 100 \angle 0^\circ$ ref. $V_{yB} = 100 \angle 120^\circ$; $V_{BR} = 100 \angle -240^\circ = 100 \angle 120^\circ$ V.</p> <p>Line currents: $i_R = 27.05 \angle -8.7^\circ$ A; $i_y = 19.7 \angle -121.1^\circ$ A $i_B = 26.69 \angle 128.4^\circ$ A.</p> <p>Voltage across the impedances (i.e. phase voltages) } 02</p> $V_{RN1} = 135.25 \angle -8.7^\circ$ V; $V_{yN1} = 39.38 \angle -37.1^\circ$ V } 02 $V_{BN1} = 106.75 \angle 38.4^\circ$ V <p>$V_{NND1} + V_{RN1} = V_{RN} = E_R$</p> $\therefore V_{NND1} = E_R - V_{RN1} = 84.11 \angle 174.3^\circ$ V <p>$P = V_R I_R \cos \phi_1 + V_y I_y \cos \phi_2 + V_B I_B \cos \phi_3$</p> $= 135.25 \times 27.05 \times \cos 0^\circ + 0 + 0$ $P = 3.6585$ kW 	10
b	<p>$I_1 = 3\angle 0^\circ$ A; $I_2 = 3\angle 90^\circ$ A } 02</p> $Z_{11} = 3\Omega$; $Z_{21} = 3\Omega$ } 02 $\therefore Z_{12} = 1\Omega$; $Z_{22} = 2\Omega$ } 02 <p>ABCD parameters: $A = \frac{Z_{11}}{Z_{21}} = \frac{3}{3} = 1$; $B = \frac{\Delta Z}{Z_{21}} = \frac{3}{3} = 1$ } 02</p> $C = \frac{1}{Z_{21}} = \frac{1}{3}$; $D = \frac{\Delta Z}{Z_{21}} = \frac{3}{3} = 1$; $T = \begin{bmatrix} 1 & 1 \\ 0 & 2/3 \end{bmatrix}$ } 04 <p>$V_1 = I_2 \angle 90^\circ$ } 01</p> $V_2 = 2I_2$ } 01 <p>$Z_{11} \neq Z_{22} \therefore$ Not Symmetrical: $Z_{12} \neq Z_{21}$ not Reciprocal. } 02</p> <p>$V_{yB} = 400 \angle 0^\circ$; $V_{BR} = 400 \angle 120^\circ$; $V_{RY} = 400 \angle 120^\circ$</p> <p>$I_{RY} = 3.58 \angle 93.4^\circ$; $I_{yB} = 5.15 \angle 75.1^\circ$ } 02</p> <p>$I_{BR} = 4 \angle -65^\circ$.</p> <p>Line currents: $i_R = 5.88 \angle 51.6^\circ$ A; $i_y = 7.95 \angle -130.8^\circ$ A } 02</p> <p>$i_B = 2.09 \angle 42.4^\circ$ A } 02</p> <p>$P = V_{RY} I_{RY} \cos \phi_1 + V_{yB} I_{yB} \cos \phi_2 + V_{BR} I_{BR} \cos \phi_3$</p> <p>$P = 2941.2$ W } 02</p> 	10
10(b)	<p>$V_1(s) = -(s+1)I_1(s) - sI_2(s)$ } 01</p> <p>$V_2(s) = 2V_1(s) = \left(\frac{s^2+1}{s}\right)I_1(s) + sI_2(s)$</p> <p>$\Phi_1 = 533.4^\circ$ $\Phi_2 = -75.1^\circ$ $\Phi_3 = 45^\circ$</p> 	10

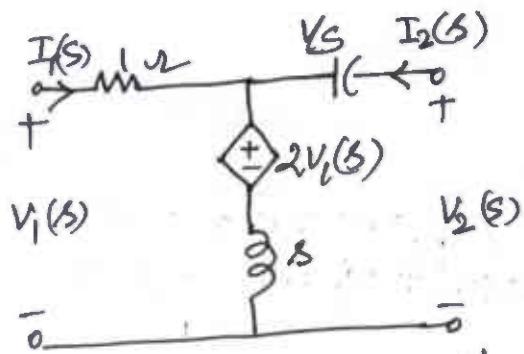

To find y-parameters. $V_2(S) = 0$.

using m/s(1) & (2)

$$I_1(S) = \frac{-1}{S^2 + S + 1} V_1(S) \text{ & } I_2(S) = \frac{-S}{S^2 + S + 1} V_1(S)$$

$$y_{11} = \left. \frac{I_1(S)}{V_1(S)} \right|_{V_2=0} = \frac{-1}{S^2 + S + 1}; \quad y_{21} = \left. \frac{I_2(S)}{V_1(S)} \right|_{V_2=0} = \frac{-S}{S^2 + S + 1} \quad \{04\}$$

Now counting input port: $V_1(S) = 0$:

$$I_1(S) = \frac{-S^2}{S^2 + S + 1} V_2(S); \quad \frac{I_2(S)}{V_2(S)} = \frac{S(S+1)}{S^2 + S + 1} V_2(S)$$

$$\left. \frac{I_1(S)}{V_2(S)} \right|_{V_1=0} = y_{12} = \frac{-S^2}{S^2 + S + 1}; \quad \left. \frac{I_2(S)}{V_2(S)} \right|_{V_1=0} = y_{22} = \frac{S(S+1)}{S^2 + S + 1}$$

— o —

(10) T

"APPROVED"

Ramya
Registrar (Evaluation)
Visvesvaraya Technological University
BELAGAVI - 590018