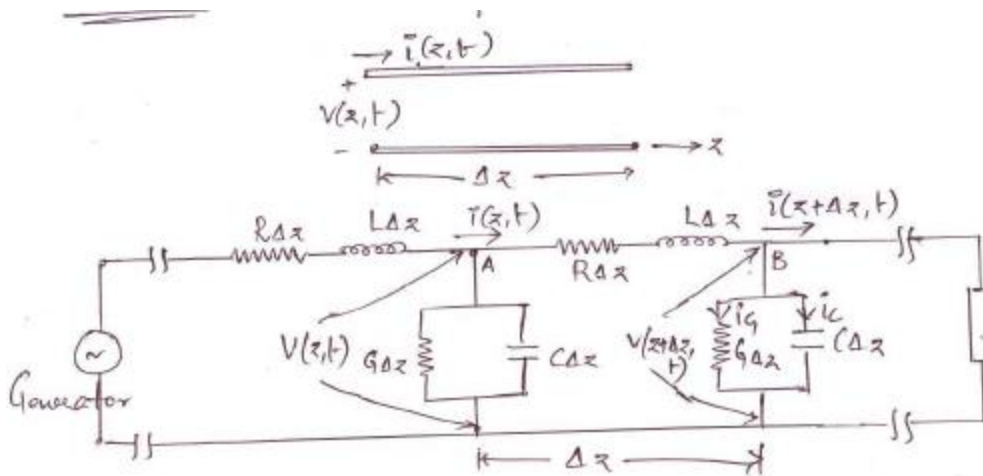


Internal Assessment Test - I

Sub:	Microwave and Antennas	Code:	15EC71
Date:	11/09/2019	Duration:	90 mins
		Max Marks:	50
		Sem:	7th
		Branch:	ECE
Answer Any FIVE FULL Questions			

1. Derive the expression for the voltage and current at any point along a uniform transmission line. [10]



2m

Fig: Equivalent circuit of a two wire transmission line.

- Transmission line constants called distributed constants are spread along the entire length of the transmission line and can't be distinguished separately.
- The amount of inductance, capacitance, resistance depend on the lengths of line, size of conducting wires, spacing between wires and the dielectric between the wires.
- We can analyze a transmission line in terms of voltage, current, impedance and power along the line i.e., using distributed circuit method.

Marks	OBE	
	CO	RBT
CO1	L2	

Applying Kirchhoff's voltage law to loop (1):

$$v(z,t) - R \Delta z \cdot i(z,t) - L \Delta z \frac{\partial i(z,t)}{\partial t} - v(z+\Delta z,t) = 0 \quad \rightarrow (1.a)$$

$$\Rightarrow \lim_{\Delta z \rightarrow 0} \frac{v(z+\Delta z,t) - v(z,t)}{\Delta z} = \lim_{\Delta z \rightarrow 0} \left[ -R i(z,t) - L \frac{\partial i(z,t)}{\partial t} \right]$$

↓ L'Hospital's rule

$$\Rightarrow \boxed{\frac{\partial v(z,t)}{\partial z} = -R i(z,t) - L \frac{\partial i(z,t)}{\partial t}} \quad \rightarrow (2.a)$$

Applying Kirchhoff's current law to node A:

$$i(z,t) - G \Delta z v(z+\Delta z,t) - C \Delta z \frac{\partial v(z+\Delta z,t)}{\partial t} - i(z+\Delta z,t) = 0 \quad \rightarrow (1.b)$$

$$\Rightarrow \lim_{\Delta z \rightarrow 0} \frac{i(z,t) - i(z+\Delta z,t)}{\Delta z} = \lim_{\Delta z \rightarrow 0} \left[ G v(z,t) - C \frac{\partial v(z,t)}{\partial t} \right]$$

$$\Rightarrow \boxed{\frac{\partial i(z,t)}{\partial z} = -G v(z,t) - C \frac{\partial v(z,t)}{\partial t}} \quad \rightarrow (2.b)$$

Equations (2.a) & (2.b) are time domain form of transmission line equations.

For sinusoidal steady state condition, we can substitute  $\frac{\partial}{\partial t}$  with  $j\omega$ . Thus, equations (1.a) and (1.b) can be written as:

$$(1.a) \Rightarrow v(z) - (R + j\omega L) I(z) \Delta z - v(z+\Delta z) = 0$$

$$\Rightarrow \boxed{\frac{dv(z)}{dz} = -(R + j\omega L) I(z)} \quad \rightarrow (3.a)$$

and

$$(1.b) \Rightarrow I(z) - (G + j\omega C) \Delta z v(z+\Delta z) - I(z+\Delta z) = 0$$

$$\Rightarrow \boxed{\frac{dI(z)}{dz} = -(G + j\omega C) v(z)} \quad \rightarrow (3.b)$$

2m

2m

Differentiating (2.a) w.r.t  $z$  and (2.b) w.r.t  $t$  and combining the results will give transmission line equation in voltage form. This is found as:

$$(2.a) \Rightarrow \text{differentiating w.r.t } z : \frac{\partial^2 V}{\partial z^2} = -R \frac{\partial i}{\partial z} - L \frac{\partial^2 i}{\partial z \partial t} \rightarrow (4.a)$$

$$(2.b) \Rightarrow \text{diff. w.r.t } t : \frac{\partial^2 i}{\partial z \partial t} = -G \frac{\partial V}{\partial t} - C \frac{\partial^2 V}{\partial t^2} \rightarrow (4.b)$$

Substituting (2.b) & (4.b) in (4.a) gives:

$$\frac{\partial^2 V}{\partial z^2} = -R \left[ -G V - C \frac{\partial V}{\partial t} \right] - L \left[ -G \frac{\partial V}{\partial t} - C \frac{\partial^2 V}{\partial t^2} \right]$$

$$\Rightarrow \left[ \frac{\partial^2 V}{\partial z^2} = R G V + (R C + L G) \frac{\partial V}{\partial t} + L C \frac{\partial^2 V}{\partial t^2} \right] \rightarrow (5.a)$$

Similarly, differentiating (2.a) w.r.t  $t$  and (2.b) w.r.t  $z$  and combining the results, we get:

$$\left[ \frac{\partial^2 i}{\partial z^2} = R G i + (R C + L G) \frac{\partial i}{\partial t} + L C \frac{\partial^2 i}{\partial t^2} \right] \rightarrow (5.b)$$

Equations (5.a) and (5.b) are the final transmission line equations in voltage and current form.

Now, from equations (3.a) and (3.b), we can get the wave equations for  $V(z)$  and  $I(z)$ . This is done by spatially differentiating both sides of (3.a) and substituting (3.b) for space derivative of current.

$$\text{i.e., (3.a) } \xrightarrow[\text{w.r.t } z]{\text{differentiating}} \frac{d^2 V(z)}{dz^2} = -(R + j\omega L) \frac{dI(z)}{dz}$$



Substituting (3.b) gives:

$$\frac{d^2 V(z)}{dz^2} = (R + j\omega L)(G + j\omega C) V(z)$$

$$\Rightarrow \frac{d^2 V(z)}{dz^2} = \gamma^2 V(z)$$

Similarly,  $\left[ \frac{d^2 I(z)}{dz^2} = \gamma^2 I(z) \right]$

Let  $\gamma^2 = \gamma_s \gamma_p = \text{propagation constant}$

$$\Rightarrow \gamma = \sqrt{\gamma_s \gamma_p} = \sqrt{(R + j\omega L)(G + j\omega C)} = \alpha + j\beta$$

Thus, the eqns become:

$$\frac{d^2 V(z)}{dz^2} - \gamma^2 V(z) = 0 \quad \rightarrow (6.a)$$

$$\& \frac{d^2 I(z)}{dz^2} - \gamma^2 I(z) = 0 \quad \rightarrow (6.b)$$

(6.a, 6.b)  $\Rightarrow$  TL eqns in the form of wave eqns

The possible solution to equation (6.a) is:

$$V = V_+ e^{-\gamma z} + V_- e^{+\gamma z} = V_+ e^{-\alpha z} e^{-j\beta z} + V_- e^{+\alpha z} e^{+j\beta z} \quad (9.a)$$

The quantity  $\beta z$ : electrical length of the line (in radians)

$V_+$  and  $V_-$  are complex quantities.

Term involving  $e^{-j\beta z}$  shows the wave traveling in  $+z$  direction and the term with factor  $e^{+j\beta z}$  is a wave going in  $-z$  direction

Similarly, one solution to equation (6.b) is:

$$I = I_+ e^{-\gamma z} + I_- e^{+\gamma z} = \frac{V_+}{Z_0} e^{-\gamma z} - \frac{V_-}{Z_0} e^{+\gamma z}$$

$$\Rightarrow I = Y_0 (V_+ e^{-\alpha z} e^{-j\beta z} - V_- e^{+\alpha z} e^{+j\beta z})$$

2m

2. (a) Define reflection coefficient. Derive the equation for reflection coefficient at the load end. [07]

CO1 L3

The reflection coefficient, which is designated by  $\Gamma$  is defined as

$$\begin{aligned} \text{Reflection Coefficient} &\equiv \frac{\text{Reflected voltage or current}}{\text{Incident voltage or current}} \\ &= \frac{V_{ref}}{V_{inc}} = -\frac{I_{ref}}{I_{inc}} \quad \checkmark \end{aligned}$$

2m

The voltage to current relationship at the load point is fixed by the load impedance. The incident voltage and the current waves travelling along transmission line are given by,

$$V = V_+ e^{-\gamma z} + V_- e^{+\gamma z} \quad \text{--- (1.1)}$$

$$I = I_+ e^{-\gamma z} + I_- e^{+\gamma z} \quad \text{--- (1.2)}$$

in which the current wave can be expressed in terms of the voltage by,

$$I = \frac{V_+}{Z_0} e^{-\gamma z} - \frac{V_-}{Z_0} e^{+\gamma z} \quad \text{--- (1.3)}$$

If the line has a length of  $L$ , the voltage and current at the receiving end becomes,


$$V_L = V_+ e^{-\gamma L} + V_- e^{+\gamma L} \quad \text{--- (1.4)}$$

$$I_L = \frac{1}{Z_0} (V_+ e^{-\gamma L} - V_- e^{+\gamma L}) \quad \text{--- (1.5)}$$

The ratio of the voltage to the current at the receiving end is the load impedance.

$$Z_L = \frac{V_L}{I_L} = Z_0 \frac{V_+ e^{-\gamma L} + V_- e^{+\gamma L}}{V_+ e^{-\gamma L} - V_- e^{+\gamma L}} \quad \text{--- (1.6)}$$

P.4.1

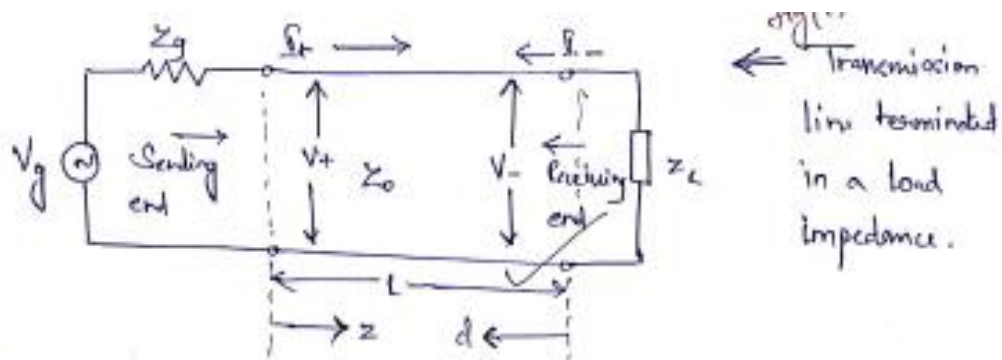

Reflection coefficient,  $\Gamma \equiv \frac{V_{ref}}{V_{inc}} = -\frac{E_{ref}}{E_{inc}}$  (1.7)

3m

Reflection coefficient at the receiving end:

$$\Gamma_L = \frac{V_{-e}^{V_L}}{V_{+e}^{V_L}} = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (1.8)$$

If load impedance and/or the characteristic impedance are complex quantities, the reflection coefficient is generally a complex quantity that can be expressed as

1m

$$\Gamma_L = |\Gamma_L| e^{-j\theta_L} \quad (1.9)$$

where  $|\Gamma_L| \leq 1$ ,  $\theta_L$  is the phase angle between the incident and reflected voltages at the receiving end. It is usually called the phase angle of the reflection coefficient.

The general solution of the reflection coefficient at any point on the line, then corresponds to the incident and reflected waves at that point, each attenuated in the direction of its progress along the line.

1m

The generalized reflection coefficient is defined as,

$$\Gamma \equiv \frac{V_{-e}^{V_z}}{V_{+e}^{V_z}} \quad (1.10)$$



Let  $z = l - d$ . Then the reflection coefficient at some point located at a distance  $d$  from the receiving end is

$$\Gamma_d = \frac{V_{-e}^{\nu(l-d)}}{V_{+e}^{\nu(l-d)}} = \frac{V_{-e}^{\nu d}}{V_{+e}^{\nu d}} e^{-2\nu d} = \Gamma_L e^{-2\nu d} \quad (1.11)$$

Reflection coefficient at that point can be expressed in terms of reflection coefficient at the receiving end as

$$\Gamma_d = \Gamma_L e^{-2\alpha d} e^{-j2\beta d} = |\Gamma_L| e^{-2\alpha d} e^{j(2\beta d - \phi)} \quad (1.12)$$

2. (b) A twin wire transmission line in air has adjacent voltage maxima at 12.5 cm and 27.5 cm. What is the operating frequency of the line?

Distance between 2 maxima =  $\frac{\lambda}{2}$

$$\Rightarrow 27.5 - 12.5 = \frac{\lambda}{2}$$

$$(15 \times 2) \text{ cm} = \lambda$$

$$f = \frac{c}{\lambda} = \frac{3 \times 10^8 \text{ m/s}}{30 \text{ cm}} = 1 \text{ GHz} \quad (1 \times 10^9)$$

2m

1m

3. (a) What are standing waves? Draw the standing wave pattern for:

- (i) Open circuit termination (ii) Short Circuit termination  
(ii) Matched termination

[8]

CO1

L2

In a mismatched terminated line, incident and reflected signals interfere to produce a standing wave pattern along the line.

Equations (9a) & (9b) are the general solutions of transmission line equation and consist of two waves traveling in opposite directions with unequal amplitude:

1m

$$\begin{aligned} \text{equ (9.a)} \Rightarrow V &= V_+ e^{-\alpha z} e^{-j\beta z} + V_- e^{\alpha z} e^{j\beta z} \\ &= V_+ e^{-\alpha z} [\cos(\beta z) - j \sin(\beta z)] \\ &\quad + V_- e^{\alpha z} [\cos(\beta z) + j \sin(\beta z)] \\ \Rightarrow V &= \underbrace{(V_+ e^{-\alpha z} + V_- e^{\alpha z}) \cos(\beta z)}_{(13a)} - j \underbrace{(V_+ e^{-\alpha z} - V_- e^{\alpha z}) \sin(\beta z)}_{(13b)} \end{aligned}$$

With no loss, it is assumed that  $V_+ e^{-\alpha z}$  and  $V_- e^{\alpha z}$  are real.

Open-circuit case: When input approaches load end, the mag. field collapses since current is zero there. This collapsing mag. field produces an electric field (from Maxwell's eqn) which is added to the existing field  $\therefore$  voltage at open circuit end is increased. This additional voltage gives rise to a wave which travels back to the sending end.  
 $\therefore$  at load end:  $V_{inc} + V_{irc} \rightarrow$  doubled  
 $\hookrightarrow$  voltage doubling action


2m

$Z_R = \text{load impedance}$ $(-1 \leq \Gamma \leq 1)$		
$Z_R = Z_0$ (matched line)	$Z_R = 0$ (Short circuit line)	$Z_R = \infty$ (Open circuit line)
$\Gamma = 0$ (no reflection)	$\Gamma = \frac{Z_R - Z_0}{Z_R + Z_0}$ $\Rightarrow \Gamma = -1$	$\Gamma = \frac{Z_R - Z_0}{Z_R + Z_0}$ $\Rightarrow \Gamma = \frac{1 - Z_0/Z_R}{1 + Z_0/Z_R} = \frac{1-0}{1+0}$
! Max power transferred from source to load.	$\Rightarrow V_{ref} = -V_{inc}$ $\Rightarrow$ entire voltage is reflected with magnitude inverse	$\Rightarrow \Gamma = 1$ $\Rightarrow V_{ref} = V_{inc} \Rightarrow$ entire voltage reflects

1m



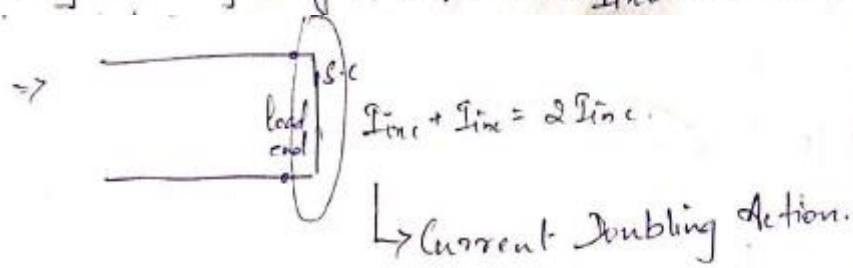Short-circuit case: Electric field collapses which generates a magnetic field which is added to already existing magnetic field.  $\Gamma_{ref} = -1 \Rightarrow I_{ref} = I_{inc}$



2m




Short-circuit:  $Z_R = 0$ ;  $\Gamma = -1 \Rightarrow \rho = \frac{1+1}{1-1} = \infty$

Open-circuit:  $Z_R = \infty$ ;  $\Gamma = 1 \Rightarrow \rho = \infty$

Matched line:  $Z_R = Z_0$ ;  $\Gamma = 0 \Rightarrow \rho = 1$

$$\Rightarrow 1 \leq \rho \leq \infty$$

2m

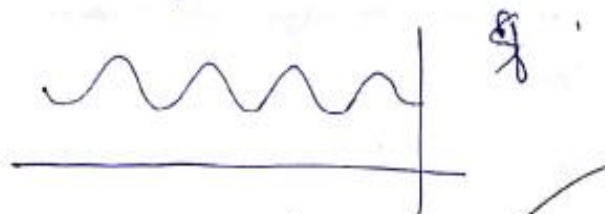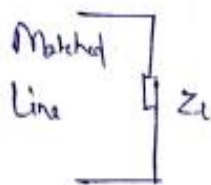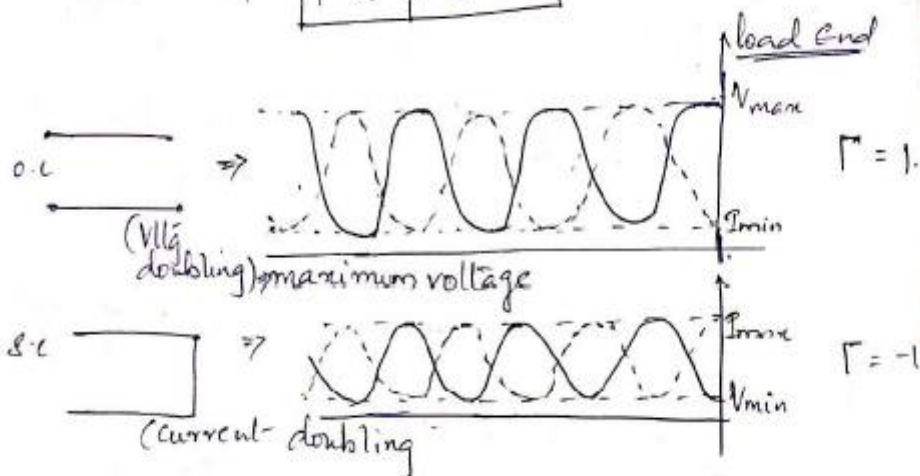

By  $\Gamma = +ve \rightarrow V_{max}$  near load  
 $\Gamma = -ve \rightarrow V_{min}$  near load

3. (b) Derive the relation between SWR and reflection coefficient.

The ratio of the maximum of the standing wave pattern to the minimum is defined as the standing-wave ratio, designated by  $\rho$ .

$$\text{SWR } (\rho) = \left| \frac{V_{\max}}{V_{\min}} \right| = \left| \frac{I_{\max}}{I_{\min}} \right| \quad (14)$$

Two traveling wave components add in phase at some points and subtract at other points

Then, maximum amplitude is:

$$\Rightarrow V_{\max} = V_+ e^{-\alpha z} + V_- e^{+\alpha z} = V_+ e^{-\alpha z} (1 + |\Gamma|) \quad (13.e)$$

which occurs at  $\beta z = n\pi$ ;  $n=0, 1, 2, \dots$   
and minimum amplitude is:

$$\Rightarrow V_{\min} = V_+ e^{-\alpha z} - V_- e^{+\alpha z} = V_+ e^{-\alpha z} (1 - |\Gamma|) \quad (13.f)$$

$$\rho = \frac{V_+ e^{-\alpha z} (1 + |\Gamma|)}{V_+ e^{-\alpha z} (1 - |\Gamma|)} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

From the eqns of  $V_{\max}$  and  $V_{\min}$  [(13.e) & (13.f)]

we get:

$$\rho = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|} \quad (15)$$

1m

1m

4. A transmission line has the following primary constants per km of the line: [10]  
 $R=8\Omega/\text{m}$ ,  $G=0.1\mu\text{S}/\text{m}$ ,  $L=3.5\text{mH}/\text{m}$ ,  $C=9\text{nF}/\text{m}$ . Calculate  $Z_0$ ,  $\alpha$ ,  $\beta$ ,  $v_p$  and  $\gamma$  at  $\omega=50 \times 10^6 \text{ rad/sec}$ .

CO1 L3

$$Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \sqrt{\frac{8+j(5000 \times 3.2 \times 10^{-3})}{(0.1 \times 10^{-6}) + j(5000 \times 9 \times 10^{-9})}}$$

$$= \sqrt{\frac{19.241 \angle 65.43}{4.5 \times 10^{-5} \angle 89.87}} = 653.87 \angle -12.22$$

$$= 639.05 - j138.40 \Omega$$

3m

$$\alpha = \frac{1}{2} \left[ R \sqrt{\frac{C}{L}} + G \sqrt{\frac{L}{C}} \right] = 6.445 \times 10^{-3} \text{ Np/km}$$

3m

$$\beta = \omega \sqrt{LC} = 0.02606 \text{ rad/km}$$

1m

$$v_p = \frac{\omega}{\beta} = 178.174 \text{ km/s}$$

$$\gamma = \alpha + j\beta = (6.445 \times 10^{-3}) + j(0.02606)$$

3m

5. Define transmission coefficients. Derive an expression for transmission coefficient in the transmission line. Also, derive the relationship between  $\Gamma$  and  $T$ .

[10]

CO1

L3

- A transmission line terminated in its characteristic impedance  $Z_0$  is called a properly terminated line. Otherwise, it is called improperly terminated.
- According to principle of conservation of energy the incident power minus the reflected power must be equal to the power transmitted to the load.


$$1 - \Gamma_l^2 = \frac{Z_0}{Z_L} \Gamma^2$$

2m

Transmission coefficient,  $T$ , is defined as:

$$T = \frac{\text{transmitted voltage or current}}{\text{incident voltage or current}}$$
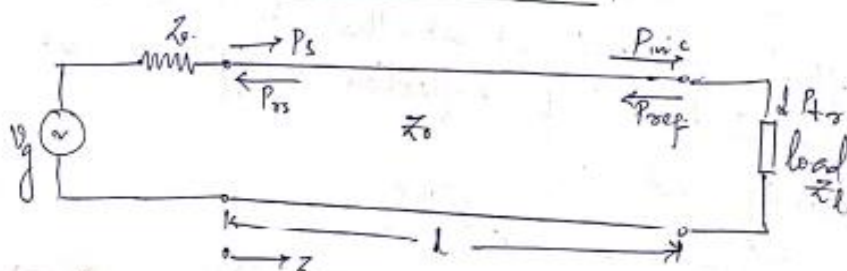
$$\Rightarrow \boxed{T \equiv \frac{V_{tr}}{V_{inc}} = \frac{I_{tr}}{I_{inc}}} \quad (12.2)$$





Let the traveling wave at the receiving end

be:

$$\text{from (a) \& (b) } \begin{cases} V_+ e^{-\gamma l} + V_- e^{\gamma l} = V_{t_2} e^{-\gamma l} & \text{--- (12.a)} \\ \frac{V_+}{Z_0} e^{-\gamma l} - \frac{V_-}{Z_0} e^{\gamma l} = \frac{V_{t_2}}{Z_L} e^{-\gamma l} & \text{--- (12.b)} \end{cases}$$

Join (12.a) & (12.b):

→ (12.b) by  $V_+ e^{-\gamma l}$ , we get:

$$\frac{V_{t_2} e^{-\gamma l}}{V_+ e^{-\gamma l}} = 1 + \frac{V_- e^{\gamma l}}{V_+ e^{-\gamma l}}$$

$$\Rightarrow T = 1 + \Gamma = 1 + \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{2Z_L}{Z_L + Z_0} \quad \text{--- (12.b)}$$

The power carried by the two in the side of the incident & reflected waves is:

$$P_{inc} = P_{inc} - P_{ref} = \frac{(V_+ e^{-\gamma l})^2}{2Z_0} - \frac{(V_- e^{\gamma l})^2}{2Z_0} \quad \text{--- (12.c)}$$

$$P_{avg} = \frac{1}{2} V I^* = \frac{|V|^2}{2Z_0}$$

∴ here  $P_{inc} = \frac{|V_+ e^{-\gamma l}|^2}{2Z_0} = \frac{(V_+ e^{-\gamma l})^2}{2Z_0}$

The Power carried to the load by the transmitted wave is:

$$P_{t_2} = \frac{(V_{t_2} e^{-\gamma l})^2}{2Z_L}$$

By setting  $P_{inc} = P_{t_2}$ , we have from (12.c)

$$\frac{(V_{t_2} e^{-\gamma l})^2}{2Z_L} = \frac{(V_+ e^{-\gamma l})^2}{2Z_0} - \frac{(V_- e^{\gamma l})^2}{2Z_0}$$

$$\Rightarrow \left( \frac{V_{t_2} e^{-\gamma l}}{V_+ e^{-\gamma l}} \right)^2 = \frac{Z_L}{Z_0} \left[ 1 - \left( \frac{V_- e^{\gamma l}}{V_+ e^{-\gamma l}} \right)^2 \right]$$

$$\Rightarrow T^2 = \frac{Z_L}{Z_0} (1 - \Gamma^2) \quad \text{--- (12.d)}$$

2m

2m

2m

- 6 (a). A transmission line has characteristic impedance of  $50+j0.01 \Omega$  and is terminated in a load impedance of  $73-j42.5\Omega$ . Calculate (i) Reflection coefficient (ii) SWR. [07]

CO1 L2

i) Reflection Coefficient

$$\Gamma_F = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(73 - j42.5) - (50 + j0.01)}{(73 - j42.5) + (50 + j0.01)}$$

$$\Gamma_L = 0.12729 - j0.2517 = 0.271 \angle -42.58^\circ$$

ii) SWR

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = 2.18$$

3.5m

3.5m

- 6 (b) In air, a lossless transmission line of length (l) 50cm with  $L=10\mu\text{H}/\text{m}$ ,  $C=40\text{pF}/\text{m}$  is operated at a 25 MHz frequency. What is the electrical length ( $\beta l$ ) of the line? [03]

CO2 L2

$$\beta = \omega \sqrt{LC} = 2\pi \cdot 25 \times 10^6 \sqrt{40 \times 10^{-12} \times 10 \times 10^{-6}} = \pi$$

$$f = 25 \text{ MHz} \Rightarrow \lambda = \frac{v_p}{f} \quad v_p = \frac{1}{\sqrt{LC}} \quad \beta = \frac{2\pi}{\lambda} = \frac{2\pi}{v_p/f} = \frac{2\pi f}{v_p} = \frac{2\pi f}{1/\sqrt{LC}} = 2\pi f \sqrt{LC}$$

$$\text{elec. length} = \beta l = \pi \times 50 \times 10^{-2} = \underline{\underline{2 \text{ rad}}}$$

1m

2m

7. A 30 m long lossless line with  $Z_0=50\Omega$  operating at 2MHz is terminated with load  $Z_L = (60+j40) \Omega$ . Find  $\Gamma$  and  $\rho$ . [10]

CO2 2

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{60 + j40 - 50}{60 + j40 + 50} = \frac{10 + j40}{110 + j40} = 0.35 \angle 58^\circ$$

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.35}{1 - 0.35} = \frac{1.35}{0.65} = \underline{\underline{2.07}}$$

5m

5m