

Internal Assessment Test - III

Sub:	Basic Electronics	Code: 18ELN14

Marks

1.a Explain the working of transistor as Voltage amplifier

[6]

BJT as an Amplifier: (Voltage Amplifier)


→ Amplification is the process of linearly increasing the amplitude of an electrical signal and is one of the major properties of Transistor.

→ BJT is biased in Active region (linear region), the EB Junction has low resistance due to forward bias (F.B) and CB Junction has a high resistance due to R.B.

→ Transistor amplifies Current because the Collector Current is equal to the base Current multiplied by Current gain ' $\beta$ '.  
i.e.  $I_c = \beta \cdot I_b$

→ The Base Current is small compared to the Collector Current & Emitter Current, Because of this Collector Current approximately equal to the Emitter Current.

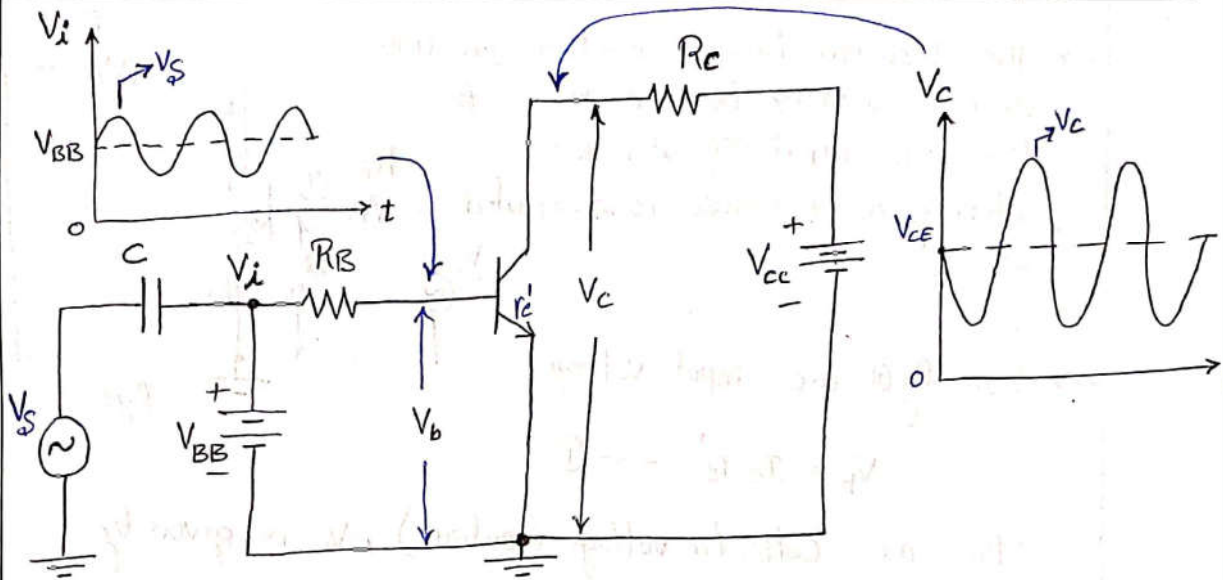→ An A.C Voltage  $V_s$ , Super imposed on the dc bias  $V_{EB}$  by Capacitive Coupling as shown in figure.



### Basic To Amplifier Circuit

$r_e'$  - internal ac emitter resistance


→ An A.C voltage  $V_s$  to be amplified is super imposed on the d.c bias voltage  $V_{BB}$  by Capacitive Coupling shown above. The d.c bias voltage  $V_{CC}$  is Connected to the Collector through Collector resistor  $R_C$ .

→ The a.c input voltage  $V_s$  produces an a.c base current which results in much larger a.c voltage across  $R_C$ , which is amplified and inverted version of ac input voltage as shown in above waveform.

→ A.c equivalent circuit is written to analyze the voltage gain of amplifier.

→ Equivalent circuit can be obtained by making all D.C bias voltage equal to zero i.e.  $V_{BB} = 0$  and  $V_{CC} = 0$ .

 → The forward biased emitter junction exhibits a very low resistance to the a.c input signal, this internal a.c resistance is designated as  $r_e'$



→ From fig 1 a.c input voltage

$$V_b = I_e \cdot r_e' \quad \text{--- (1)}$$

The a.c Collector voltage (output),  $V_c$  is given by

$$V_c = I_c \cdot R_c$$

Since  $I_c \approx I_e$ , the Collector v<sub>t</sub>g is

$$V_c \approx I_e \cdot R_c \quad \text{--- (2)}$$

and also we can write  $V_b = V_s - I_b \cdot R_B$

→  $V_b$  can be considered as to a.c input v<sub>t</sub>g and  
 $V_c$  can be " as transistor output voltage

→ Since the v<sub>t</sub>g gain is the ratio of the output voltage to the input voltage, the ratio of  $V_c$  to  $V_b$  is the v<sub>t</sub>g gain,  $A_v$   
 from eq 1 & 2


$$A_v = \frac{V_c}{V_b} = \frac{I_e \cdot R_c}{I_e \cdot r_e'}$$

So  $A_v \approx \frac{R_c}{r_e'}$

Since  $R_c \gg r_e'$ , the output is always greater than input voltage i.e the output voltage  $V_c$  is amplified version of  $V_b$ .

1 (b) The transistor in CE Configuration is shown in figure. With  $R_C = 10\text{ K}\Omega$ ,  $\beta_{DC} = 200$ ,  $V_{CC} = 10\text{ V}$ ,  $V_{CE(sat)}$  is neglected. Determine when  $V_{in} = 5\text{ V}$  (i)  $I_{B\text{ min}}$  (ii)  $R_{B\text{ max}}$

[4] CO1

 

(a) When  $V_{IN} = 0\text{ V}$ , the transistor is in cutoff (acts like an open switch) Therefore,  $V_{CE} = V_{CC} = 10\text{ V}$

(b) Since  $V_{CE(sat)}$  is neglected, assume  $V_{CE(sat)} = 0\text{ V}$

$$I_{C(sat)} = \frac{V_{CC}}{R_C} = \frac{10\text{ V}}{1.0\text{ k}\Omega} = 10\text{ mA}$$

$$I_{B(min)} = \frac{I_{C(sat)}}{\beta} = \frac{10\text{ mA}}{200} = 50\text{ }\mu\text{A}$$

This is the value of  $I_B$  necessary to drive the transistor to the point of saturation. Any further increase in  $I_B$  will ensure the transistor remains the saturation but there cannot be any further increase in  $I_C$

(c) When the transistor is on,  $V_{BE} \approx 0.7\text{ V}$ . The voltage across  $R_B$  is

$$V_{R_B} = V_{IN} - V_{BE} \approx 5\text{ V} - 0.7\text{ V} = 4.3\text{ V}$$

Calculate the maximum value of  $R_B$  needed to allow a minimum  $I_B$  of  $50\text{ }\mu\text{A}$  using Ohm's law as follows:

$$R_{B(max)} = \frac{V_{R_B}}{I_{B(min)}} = \frac{4.3\text{ V}}{50\text{ }\mu\text{A}} = 86\text{ k}\Omega \quad 860\text{ k}\Omega$$



- 2 List the types of feedback system. Derive the gain with feedback expression for Voltage series feedback amplifier. [10]

### Types of Feedback :-

There are four basic types :-

- ① Voltage Series feedback
- ② Voltage-Shunt feedback
- ③ Current-Series feedback.
- ④ Current-Shunt feedback.

→ Here, voltage refers to connecting the output voltage as input to the feedback network,  
→ Current refers to tapping off some output current through the feedback network.  
→ Series refers to connecting the feedback signal in series with the input signal voltage.  
→ Shunt (parallel) refers to connecting the feedback signal in shunt (parallel) with an input current source.

NOTE :- ① Series feedback connection increases the input Res  
while shunt feedback connections decreases the input Res

② Voltage Feedback ③ decreases the output impedan  
while current feedback increases the output impedan  
→ Typically higher input and lower output impedan  
are desired. Both of these are provided us  
voltage-Series feedback connection.

I°

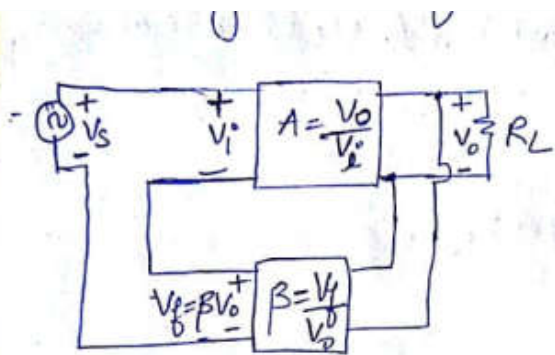


Fig 2(a)  
Voltage-Series Feedback Amplifier ( $A_f = \frac{V_o}{V_s}$ )

 


Fig 2(b)  
Voltage-Shunt Feedback Amplifier ( $A_f = \frac{V_o}{I_s}$ )

 


Fig 2(c)  
Current-Series Feedback Amplifier ( $A_f = \frac{I_o}{V_s}$ )

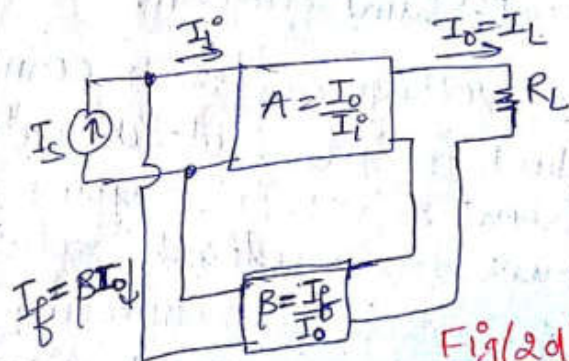


Fig 2(d)  
Current-Shunt Feedback Amplifier ( $A_f = \frac{I_o}{I_s}$ )

Fig(2) :- Different Types of feedback Amplifier/Com

Voltage Series feedback :- (4)

As shown in Fig(a) i.e. Voltage Series feedback circuit

If  $V_f = 0$ , the voltage gain of Amplifier stage is

$$A = \frac{V_o}{V_s} = \frac{V_o}{V_i} \quad \text{--- (1)}$$

connected with



$V_s$   $V_i$   
If feedback signal  $V_f$  is connected in series with input, then,

$$V_i = V_s - V_f \quad \text{--- (2)}$$

$$\Rightarrow \boxed{V_o = AV_i} = A(V_s - V_f)$$

eqn ①

$$V_o = AV_s - AV_f \Rightarrow V_o = AV_s - A(\beta V_o)$$

Since  $\beta = \frac{V_f}{V_o}$

$$\Rightarrow V_o(1 + A\beta) = AV_s$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{A}{1 + A\beta}$$

$$\Rightarrow \boxed{A_f = \frac{V_o}{V_s} = \frac{A}{1 + A\beta}} \quad \text{--- (3)}$$

$A_f$  is the overall gain with feedback.


→ eqn ③ shows that gain with feedback is the amplifier gain reduced by factor  $(1 + A\beta)$ .

$A_f$  is voltage gain with feedback.

Explain Barkhausen's criteria. Explain the working of Wien Bridge oscillator with the help of circuit and derive the frequency of oscillation.


Barkhausen Criterion for Oscillation

 Consider a basic inverting Amplifier with an open loop gain  $A$ . The feedback network attenuation factor  $\beta$  is less than unity. As basic amplifier is inverting, it produces a phase shift of  $180^\circ$  between input and output, as shown in fig(a).



Fig(a) :- Inverting Amplifier

 → But the feedback must be +ve i.e. voltage derived from output using feedback network must be in phase with  $V_i$ . Thus, feedback network must introduce a phase shift of  $180^\circ$ . This ensures positive feedback.



Fig(b) :- Basic Block diagram of oscillator circuit.



Consider a fictitious voltage  $V_i$  applied at input of amplifier so,

$$V_o = A V_i \quad \text{--- (1)}$$

now  $V_f = \beta V_o$  --- (2)

so put  $V_f$  from eq<sup>n</sup> (2) into eq<sup>n</sup> (1)

$$\boxed{V_f = \beta A V_i}$$

For oscillator, we want that feedback should drive the amplifier hence  $V_f$  acts as  $V_i$   
→  $V_f$  is sufficient to act as  $V_i$  when  
 $|AB| = 1$

The two conditions are required to work the circuit as an oscillator, are called Barkhausen Criterion for Oscillation.

Barkhausen Criterion states that :-

① The total phase shift around a loop, as signal proceeds from input through amplifier, feedback network back to input again, completely a loop is precisely  $0^\circ$  or  $360^\circ$ .

② The magnitude of the product of the open loop gain of amplifier ( $A$ ) and magnitude of the feedback factor  $\beta$  is unity  $|AB| = 1$


Satisfying above conditions, circuit works as an oscillator producing sustained oscillations of

constant frequency and amplitude.

①  $|AB| > 1 \rightarrow$  when total phase shift around a loop is  $0^\circ$  or  $360^\circ$  and  $|AB| > 1$ , then output oscillates but the oscillations are of growing type.




②  $|AB| = 1 \rightarrow$  when total phase shift around the loop is  $0^\circ$  or  $360^\circ$  and  $|AB| = 1$ , then oscillations are with constant frequency and amplitude called as sustained oscillations.

 

③  $|AB| < 1 \rightarrow$  when total phase shift is  $0^\circ$  or  $360^\circ$  but  $|AB| < 1$  then oscillations are of decaying type.



 4 Explain the construction and working of JFET with drain characteristics and transfer characteristics. [10]






**FABRICATION OF N-CHANNEL JFET: (Construction)**

1. A narrow bar of N-type semiconductor material is taken. At its middle part, two heavily doped p-type regions are formed by diffusion.
2. The junction form two P-N diodes or gates. The area between the gates is called a channel.
3. One end of the N-type bar is called as source terminal 'S'.
4. The other end of the N-type bar is called as drain terminal 'D'.
5. The souce and drain terminal may be interchanged.
6. When a potential difference is established between source and drain, a current flows from one end to the other end in N-type material.
7. This current consists of majority carriers i.e. electrons.
8. Following notations for FET should be remembered.
  - a) SOURCE: The source 'S' is the terminal through which majority carrier enter the bar.
  - b) DRAIN: The drain 'D' is the terminal through which the majority carrier leave the bar.
  - c) GATE: These are heavily doped regions which forms two P-N junctions.
  - d) CHANNEL: The space between two gates through which majority carriers pass.


**OPERATION OF N-CHANNEL FET:**

 

**N-Channel JFET**


1. When no volatges are applied, the depletion regions were uniformly distributed.
2. As a positive voltage is applied across the channel and the gate is connected directly to the source to establish the condition  $V_{GS} = 0V$ . Then the width of the depletion region starts increasing.
3. As  $V_{DD}$  is applied , the electrons are drawn to the drain terminal, hence a current will flow in a defined direction.

 4. The path of charge flow clearly define that  $I_D = I_S$
5. The depletion region is wider near the top of both the P-type material.






 
6. Assume a uniform resistance in the N-channel, we can break down the resistance into some division.
7. The upper region of the P-type material will be reverse biased by 1.5V comparison with the lower region.
8. We know from the diode operation, the greater the applied reverse bias, the wider is the depletion region. Hence the depletion region is shown like this.
9. As  $V_{DS}$  increases and approaches a level referred as  $V_p$ , the depletion region will widen, causing a reduction in channel width. The reduced path of conduction causes the resistance to increase.
10. When two depletion region touch the condition is referred to as pinch-off.
11. The level of  $V_{DS}$  that establishes this condition is known as pinch-off voltage and denoted as  $V_p$
12. In actuality pinch-off suggests, the current  $I_D$  is pinched off and drop to 0V, but in reality a very small channel still exists, with a very high current density. Hence the  $I_D$  doesn't drop at pinch-off but maintains the saturation level.



13.  $I_{DSS}$  is the maximum drain current for a JFET and is defined by the condition  $V_{GS} = 0V$  and  $V_{DS} \geq |V_p|$
14. The voltage from gate to source  $V_{GS}$  is the controlling voltage of JFET. The reason to apply  $-ve$  bias  $V_{GS}$  is to establish depletion region similar to those obtained with  $V_{GS} = 0V$  but at lower level of  $V_{DS}$ . Hence saturation level can be achieved at lower  $V_{DS}$ .

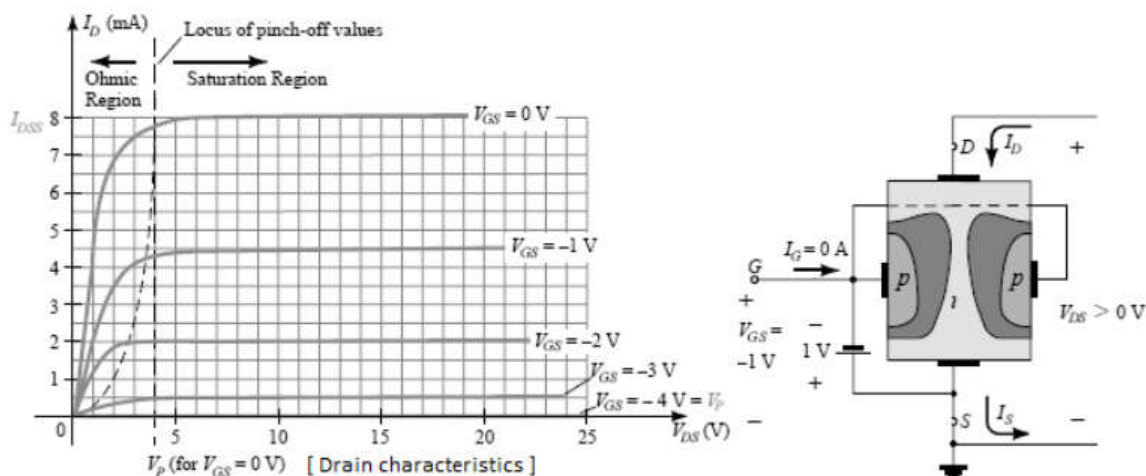

**TRANSFER CHARACTERISTICS:**

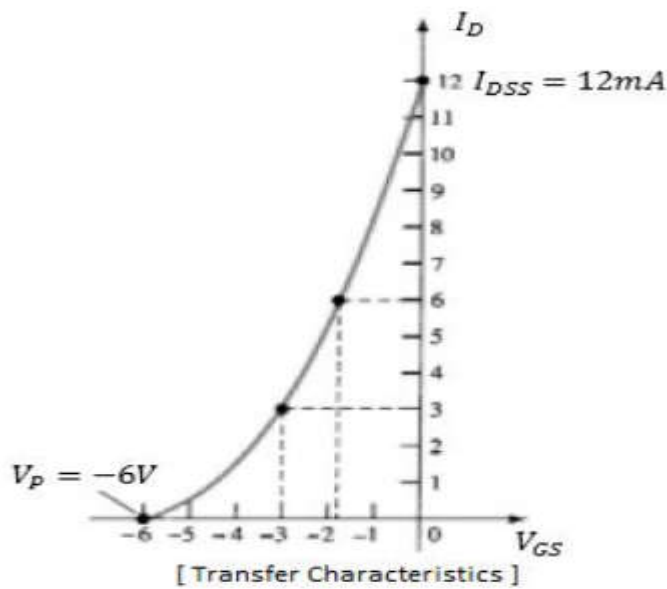

5 (a) Explain the working of CMOS Inverter with relevant circuit.

[5]

→ CMOS is a **Complementary Metal Oxide Semiconductor** which is a technology used for constructing integrated circuits.


→ CMOS circuitry has ~~two~~ advantages :-

(i) Low static power consumption.

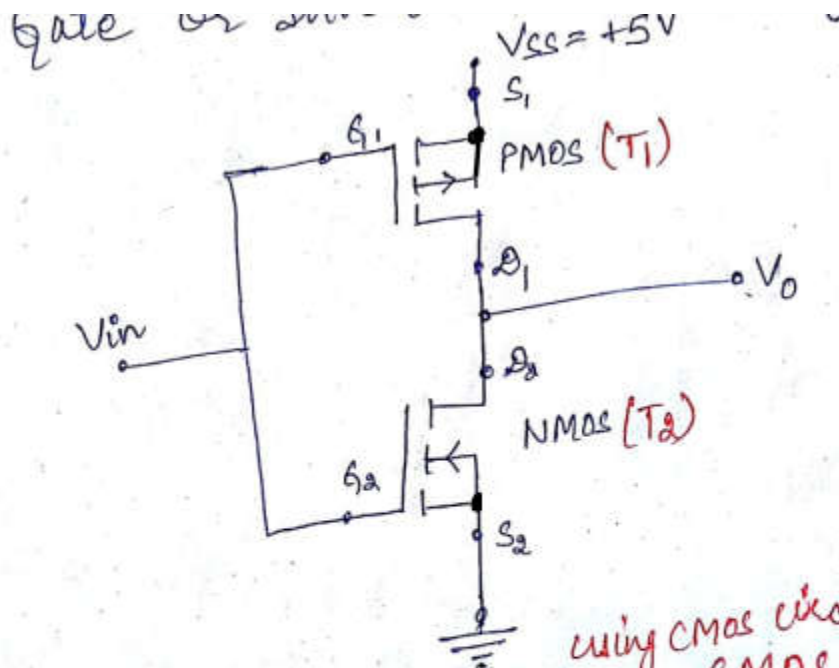(ii) High Noise Immunity.

→ CMOS circuits use a combination of P-type and N-Type MOSFET'S to implement logic gates and other digital circuits.

CMOS circuit ~~is~~ can be used to implement NOT Gate or Inverter as shown in figure below.  
 $V_{SS} = +5V$



Fig(a) :- NOT Gate <sup>using CMOS circuit</sup> or CMOS Inverter

→ Fig(a) shows CMOS Inverter which uses an enhancement Type NMOS and an enhancement type PMOS.

→ The source of PMOS ( $T_1$ ) is connected to  $V_{SS} = +5V$ , while the source of NMOS ( $T_2$ ) is grounded.

→ The gates  $G_1$  and  $G_2$  are shorted together and input is provided at the gate.


→ The drains  $D_1$  and  $D_2$  are shorted and output is obtained at drain as  $V_o$ .



Operation :-



Case-1 When  $V_{in} = 0V$  (logic low),

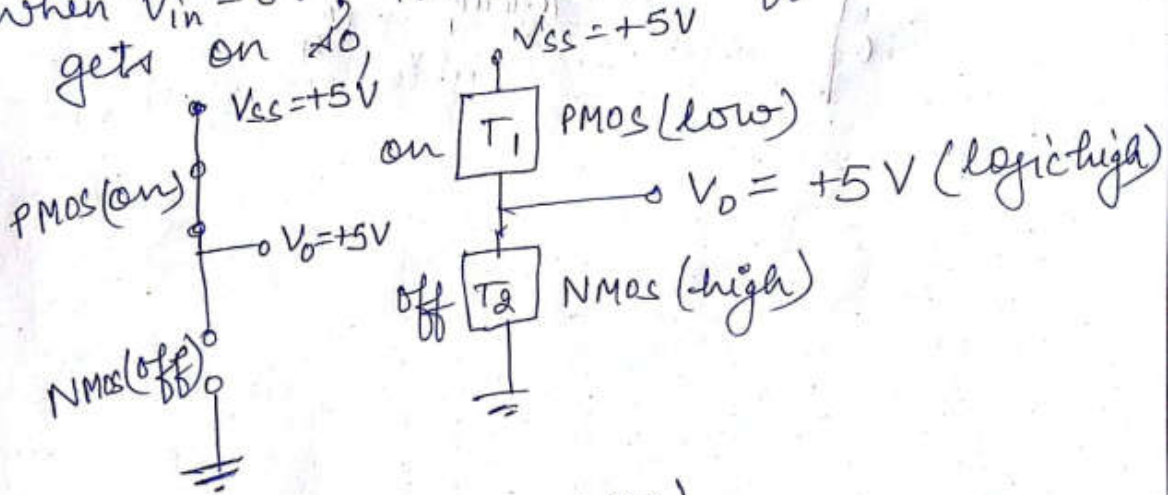→ When  $V_{in} = 0V$ , NMOS will be off and PMOS gets on so,




so,  $V_o = +5V$  (logic high)

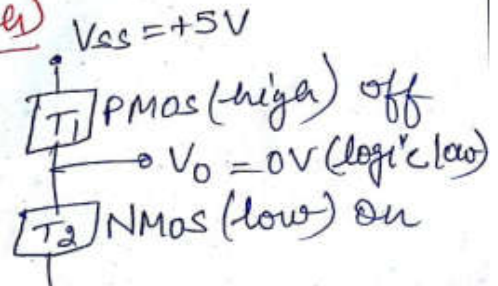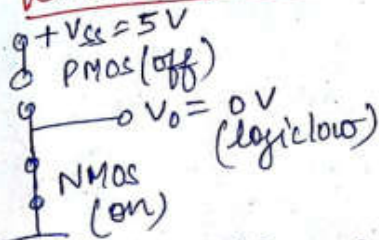Case-2 When  $V_{in} = +5V$  (logic high)




so, when  $V_{in} = 0V \Rightarrow V_o = +5V$  (logic high)  
 $V_{in} = +5V \Rightarrow V_o = 0V$  (logic low).

Voltage Transfer characteristics

 



Ideal characteristics

 

5 (b) Explain SCR as two transistor model.

Silicon Controlled Rectifier (SCR) :- Sept 21

  SCR is a rectifier constructed of Silicon material with three terminals namely gate, Anode and Cathode. Silicon is chosen because of high temperature and power capabilities.





Fig(a) :- Symbol

Fig(b) :- Basic Construction

SCR is basically a four layer P n P n structure as shown in fig(b).

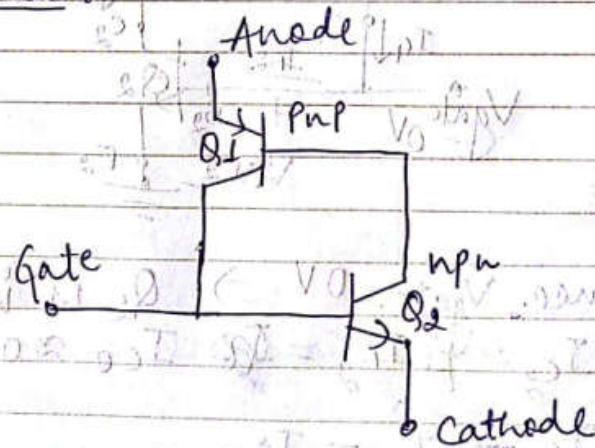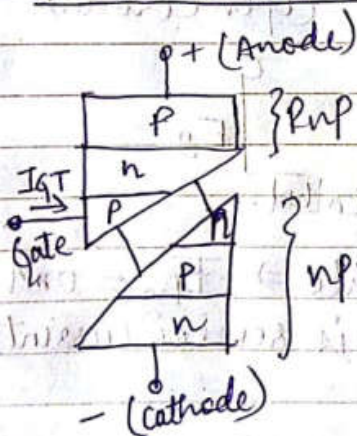The operation of SCR can be explained using two transistor model.



Fig(c) SCR two transistor model

SCR is splitted into two three layer transistor



structures as shown in fig (c). One transistor is npn device while the other is pnp device.

A signal as shown in fig (d) is applied at the gate of SCR.


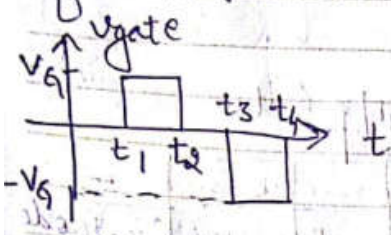


fig (d) :- Signal applied at the gate of SCR.

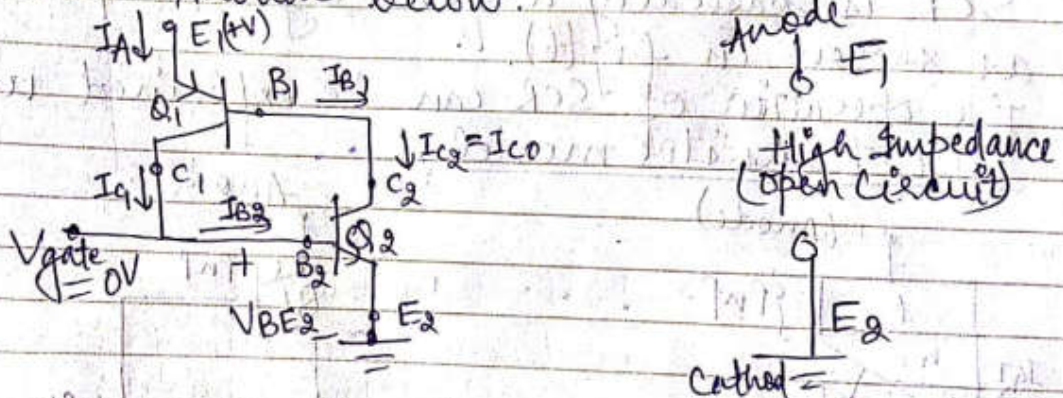During the interval  $0 \rightarrow t_1$ ,  $V_{gate} = 0V$ , the circuit appears as shown below.



Since  $V_{gate} = 0V \Rightarrow Q_2$  is in off state  $\Rightarrow I_{B2} = 0mA$   
 $\Rightarrow I_{C2} = \beta I_{B2} = I_{C0} \approx 0$  ( $I_{C0}$  is reverse current)

$\Rightarrow I_{B1} \approx I_{C2} = I_{C0}$


$\Rightarrow I_{C1} = \beta I_{B1} \approx 0$

So,  $I_A \approx 0$  (so, transistors are in off state and thus replaced by open circuit or high impedance between collector and emitter)



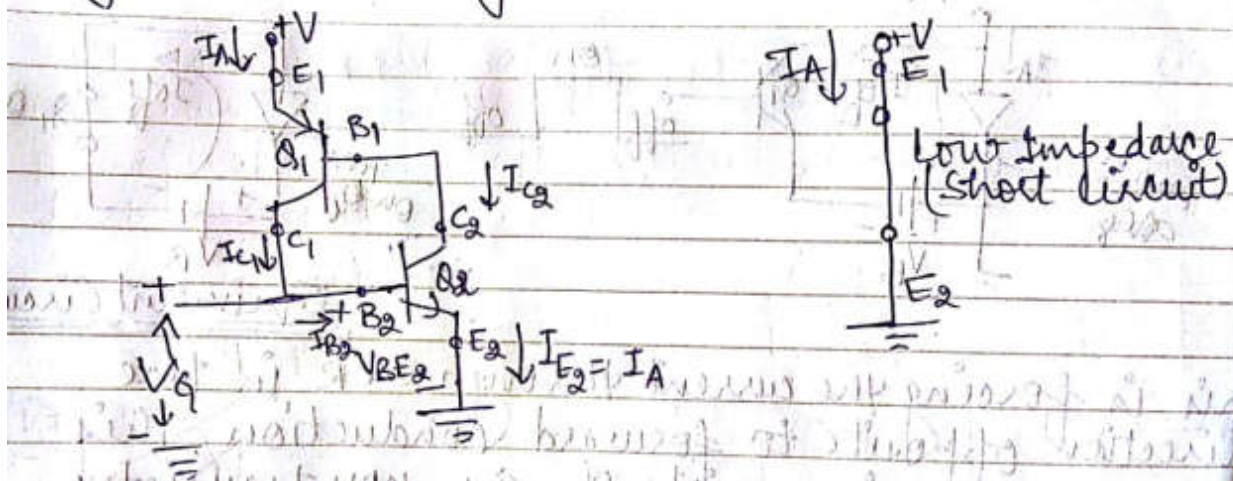(2) At  $t = t_1$ , a pulse of  $V_G$  volts is applied at the gate of SCR.  $V_G$  is large so  $Q_2$  turns on and thus there is  $I_{B2}$  and  $I_{C2} = \beta I_{B2}$  in the circuit.

$I_{B1} = I_{C2}$  so, the transistor  $Q_1$  turns on and thus a current  $I_{C1}$  flows through it. This increase or flow of  $I_{C1}$  corresponding increases  $I_{B2}$ . The increase in  $I_{B2}$  further increases  $I_{C2}$ . The net result is regenerative increase in collector current of ~~transistors~~ each transistor. Thus anode to cathode resistance ( $R_{SCR} = \frac{V}{I_A}$ ), since  $I_A$  is large  $R_{SCR}$  is very small.



→ SCR cannot be turned off by simply removing the gate signal, thus negative pulse is needed to applied at the gate of SCR. i.e. at  $t = t_3$ .

Methods to turn-off SCR :-


There are two Methods :-

- ① Natural commutation or Anode Current Interruption Technique.
- ② Forced-Commutation Technique.

6 Explain the construction and working of n channel enhancement type MOSFET with relevant drain characteristics and transfer characteristics. [10]

 
**Construction of N-channel Enhancement type MOSFET:**

The construction of n-channel enhancement type MOSFET is similar to the construction of depletion type MOSFET. Here the channel between the two n-doped regions is absent. This is the primary difference between the construction of depletion type and enhancement type MOSFET.



**N- Channel Enhancement Type MOSFET**


**OPERATION:**

 

1. Although some positive  $V_{DS}$  is applied, as the  $V_{GS} = 0V$ , no channel exists hence the current through the device is 0A i.e.  $I_D = I_S = 0A$
2. As some positive voltage  $V_{GS}$  is applied to the gate terminal, the positive potential at the gate will pressure the holes in the p-substrate. Electron in the p substrate will be attracted to the positive gate and accumulated in the region near to the surface of  $SiO_2$  layer.
3. As  $V_{GS}$  increases in magnitude, the concentration of electron near  $SiO_2$  surface increases.
4.  $V_{GS}$  has to be increased until the induced N-type region can support the flow of current.

 5. The level of  $V_{GS}$  that results in the significant increase in drain current is called the threshold voltage and represented as  $V_T$  or  $V_{GS(th)}$






Applying KVL to the terminal

$$V_{DG} = V_{DS} - V_{GS}$$

Let  $V_{GS} = 8V$  and  $V_{DS} = 2$  to  $5V$  (i.e. increasing from 2 to 5V)

$V_{DG}$  drops from  $-6V$  to  $-3V$

 - This reduction in gate to drain voltage will reduce the attractive force for free carriers, causes reduction in channel width.



- The channel will be reduced to the point of pinch off and saturation condition will be established.
- But any further increase in  $V_{DS}$  at the fixed value of  $V_{GS}$  will not affect the saturation level of  $I_D$  until breakdown condition occurs.

$$V_{DS(sat)} = V_{GS} - V_T$$

- For fixed  $V_T$ , higher the level of  $V_{GS}$  the greater will be the saturation level of  $V_{DS}$
- For  $V_{GS}$  less than the threshold voltage, the drain current of an enhancement type MOSFET is 0mA.
- As  $V_{GS}$  increases from  $V_T$ , the resulting saturation level for  $I_D$  also increases.


- For  $V_{GS} > V_T$ , the drain current is related to the applied gate to source voltage by the following relationship.

$$I_D = k(V_{GS} - V_T)^2$$

Where  $k$  = constant and it is a function of the construction of the device


 
$$k = \frac{I_{D(on)}}{(V_{GS(on)} - V_T)^2}$$



7(a) For a N-channel JFET if  $I_{DSS} = 8\text{mA}$  &  $V_P = V_{GS(off)} = -5\text{V}$ , calculate  $I_D$  at  $V_{GS} = -3\text{V}$  and  $V_{GS}$  at  $I_D = 3\text{mA}$ . [5]


⑦ a) 
$$I_D = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_P} \right]^2$$


$$I_D \Big|_{V_{GS} = -3\text{V}} = 1.28\text{mA}$$

$$V_{GS} = V_P \left( 1 - \sqrt{\frac{I_D}{I_{DSS}}} \right) = -1.938\text{V}$$

7(b) Explain the working of 555 Timer as astable oscillator with necessary equations. [5]

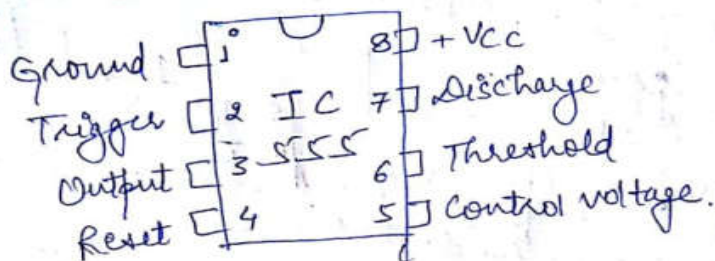IC 555 Timer :- It is a versatile analog-digital integrated circuit. Entire circuit is housed in an 8-pin package.  
Pin diagram of IC 555 :- It has 8 pins.



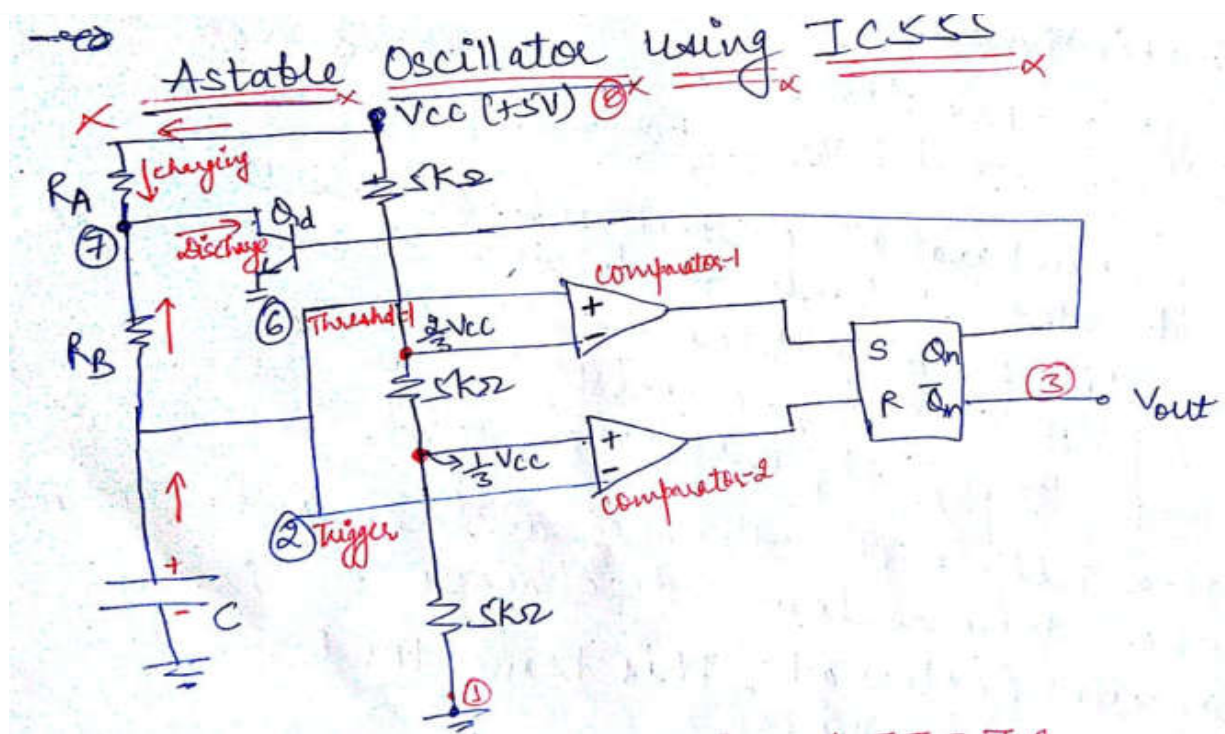

Fig(a) shows IC 555 connected as Astable oscillator Multivibrator. The threshold input is connected to trigger input. The two external resistances  $R_A$ ,  $R_B$  and a capacitor  $C$  is used in the circuit.

→ The circuit has no stable state. The circuit changes its state alternately. Hence the operation is also called free running non-sinusoidal oscillator.

### Operation:

- When flip flop is set,  $Q_n$ 's high which drives transistor  $Q_d$  in saturation and capacitor gets discharged.
- Now the capacitor voltage is just the trigger voltage. So while discharging, when it becomes less than  $\frac{1}{3}V_{cc}$ , then comparator 2 output goes high.
- This resets the flip flop hence  $Q_n = 1$  or high.
- Since  $Q_n = 1 \Rightarrow Q_n = 0 \Rightarrow Q_d$  transistor will be in cutoff and thus capacitor starts charging through the resistances  $R_A$ ,  $R_B$  and  $V_{cc}$ .
- charging Time constant is  $(R_A + R_B)C$ .



### Charging Time constant

Now the capacitor voltage is also a threshold voltage. While charging, capacitor voltage increases and thus threshold voltage increases. When it exceeds  $\frac{2}{3}V_{cc}$ , then Comparator-1 output goes high which sets the flip-flop and thus  $Q_n$  is high and  $\bar{Q}_n$  becomes low.

Discharging Time constant is  $R_B C$ .

When ~~comparator-2~~ capacitor voltage becomes less than  $\frac{1}{3}V_{cc}$ , Comparator-2 output goes high, resetting the flip-flop. This cycle repeats.

When capacitor charges, output is high while when it is discharging the output is low.


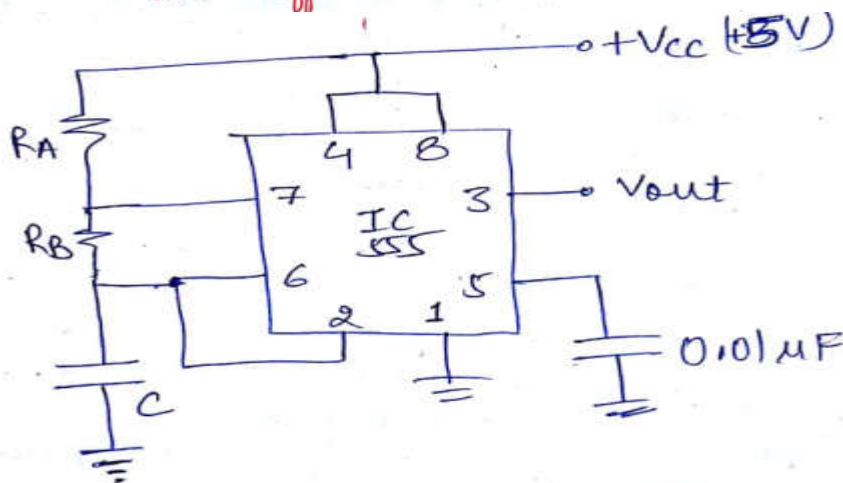


Fig (c): Schematic diagram of Astable Oscillator using IC 555.

 

### Duty Cycle :-

It is defined as the ratio of high output ~~period~~ (i.e. on time) to the total time of one cycle.

$$D = \frac{T_{on}}{T_{on} + T_{off}} \times 100\% \quad \text{or} \quad \frac{T_c}{T_c + T_d} \times 100\%$$

Charging Time for the Capacitor ( $T_c$ ) =  $0.693(R_A + R_B)C$   
 Discharging " " " " ( $T_d$ ) =  $0.693(R_B)C$


$$T = T_c + T_d = 0.693(R_A + 2R_B)C$$

$$\Rightarrow D\% = \frac{0.693(R_A + R_B)C}{0.693(R_A + 2R_B)C} \times 100$$

$$D\% = \frac{R_A + R_B}{R_A + 2R_B} \times 100$$

8(a) Explain the working of Integrator using op-amp and derive the output expression.

[5]

 

By virtual ground concept,

$$V_A = V_B = 0$$

As input current of op-amp is zero, the entire current  $I$  flowing through  $R_1$ , also flows through  $C$ .

From fig.

$$I = \frac{V_{in} - V_A}{R_1} = \frac{V_{in}}{R_1} \quad \text{--- (1)}$$

From o/p side,

$$I = C \frac{d(V_A - V_o)}{dt}$$

$$I = -C \frac{dV_o}{dt} \quad \text{--- (2)}$$

Eq (1) & (2)

$$\frac{V_{in}}{R_1} = -C \frac{dV_o}{dt}$$

Integrating both sides

$$\int_0^t \frac{V_{in}}{R_1} dt = - \int_0^t C \frac{dV_o}{dt}$$

$$V_o = -\frac{1}{R_1 C} \int_0^t V_{in} dt$$

This o/p is integration of input. hence called integrator  
where RC is called time constant of integrator

- integration of Step waveform is Ramp waveform
- " " " Square " " " Triangular "
- " " " Sine " " " neg Cosine

Also Draw wave forms



8.b) Design the circuit using opamp's for  $V_o = -(2V_1 + 3V_2 + 6V_3)$  for  $R_f = 10K\Omega$ .

[5]

(8b)  $V_o = -(2 \cdot V_1 + 3 \cdot V_2 + 6 \cdot V_3)$

$$V_o = -\left[ \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

$$\frac{R_f}{R_1} = 2 \quad \frac{R_f}{R_2} = 3 \quad \frac{R_f}{R_3} = 6$$

assuming  $R_f = 10k\Omega$

$$R_1 = 5k\Omega \quad R_2 = 3.3k\Omega \quad R_3 = 1.66k\Omega$$



Scanned with  
CamScanner

