

Modified

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EC32

## Third Semester B.E. Degree Examination, Dec.2019/Jan.2020 Network Theory

Time: 3 hrs.


Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1


- 1 a. Using source transformation technique find the current through  $5\Omega$  resistor for the circuit shown in Fig.Q.1(a) (06 Marks)

Fig.Q.1(a)

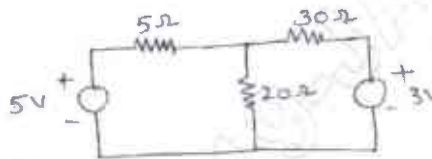


- b. Use Mesh Analysis to determine the Mesh currents  $i_1$ ,  $i_2$  and  $i_3$  for the network shown in Fig.Q.1(b). (06 Marks)

Fig.Q.1(b)

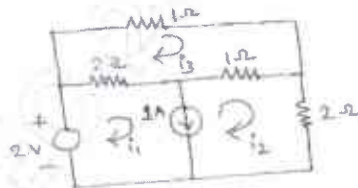

- c. Find the power delivered by 1A current source using nodal analysis for the circuit shown in Fig.Q.1(c). (08 Marks)


Fig.Q.1(c)

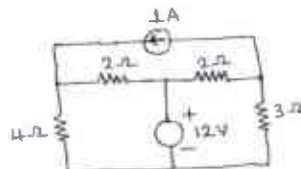

OR


- 2 a. Three Impedances are connected in delta, obtain the star equivalent of the network. (06 Marks)
- b. Use Mesh Analysis to find the power delivered by the dependent voltage source in the circuit shown in Fig.Q.2(b). (06 Marks)

Fig.Q.2(b)

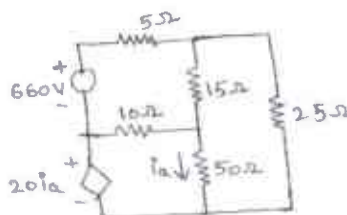

- c. Determine all the node voltages for the circuit shown in Fig.Q.2(c) using nodal analysis. (08 Marks)

Fig.Q.2(c)

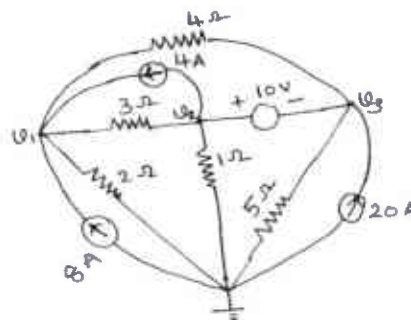

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

**Module-2**

- 3 a. State and explain superposition theorem (06 Marks)  
 b. Use Millman's Theorem to find the current flowing through  $(2 + j3)\Omega$  impedance for the circuit shown in Fig.Q.3(b). (08 Marks)

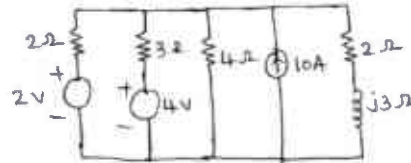


Fig.Q.3(b)

- c. State and prove Norton's theorem. (06 Marks)

**OR**

- 4 a. Find the Thevenin's equivalent for the circuit shown in Fig.Q.4(a) with respect to terminals X-Y. (08 Marks)

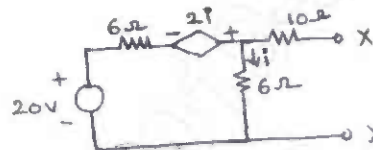


Fig.Q.4(a)

- b. Find the condition for maximum power transfer in the AC circuit, where both  $R_L$  and  $X_L$  are varying. (06 Marks)  
 c. Determine the current through the load resistance using Norton's Theorem for the circuit shown in Fig.Q.4(c). (06 Marks)

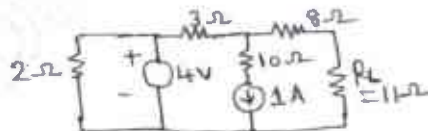


Fig.Q.4(c)

**Module-3**

- 5 a. Explain the behavior of R, L, C elements at the time of switching at  $t = 0$ , at  $t = 0^+$  and  $t = \infty$ . (07 Marks)  
 b. In the network shown in Fig.Q.5(b). Find  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ . Assume that the capacitor is initially uncharged. (07 Marks)

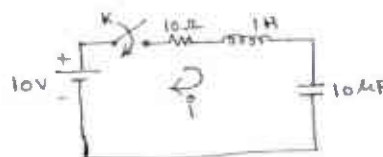


Fig.Q.5(b)

- c. In the network shown in Fig.Q.5(c) find,  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ . The switch k is closed at  $t = 0$  with zero current in the inductor. (06 Marks)

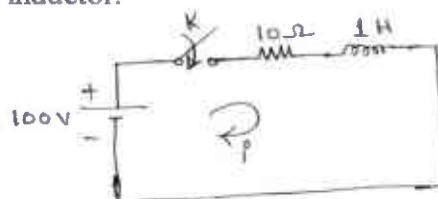


Fig.Q.5(c)

OR

- 6 a. In the network shown in Fig.Q.6(a). The switch k is changed from position a to b at  $t = 0$ , the steady state is reached at position a. Find  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ . Assume that the capacitor is initially uncharged. (10 Marks)

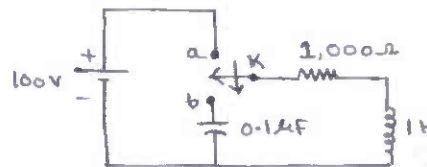


Fig.Q.6(a)

- b. For the network shown in Fig.Q.6(b). The network is in steady state with switch k is closed. At  $t = 0$ , the switch is opened. Determine the voltage across the switch  $V_k$  and  $\frac{d}{dt}V_k$  at  $t = 0^+$ . (10 Marks)

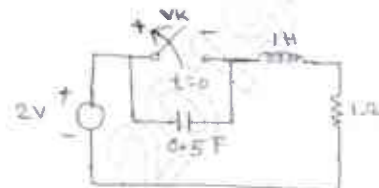


Fig.Q.6(b)

**Module-4**

- 7 a. Obtain Laplace transform of  
 i) Step function  
 ii) Ramp function  
 iii) Impulse function. (09 Marks)
- b. Find the Laplace transform of the periodic signal  $x(t)$  as shown in Fig.Q.7(b). (11 Marks)

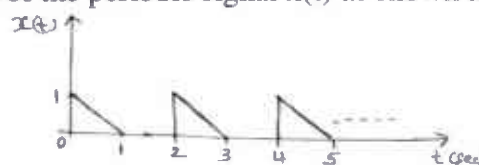


Fig.Q.7(b)

OR

- 8 a. In the series RL circuit shown in Fig.Q.8(a), the source voltage is  $v(t) = 50 \sin 250tV$ . Using Laplace transform determine, the current when switch K is closed at  $t = 0$ . (10 Marks)

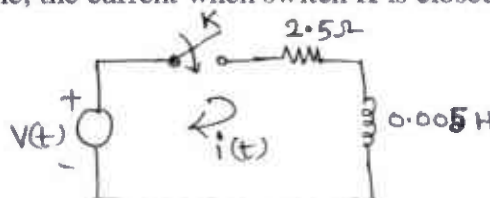


Fig.Q.8(a)

- b. Find the Laplace transform of the non-sinusoidal periodic waveform shown in Fig.Q.8(b)

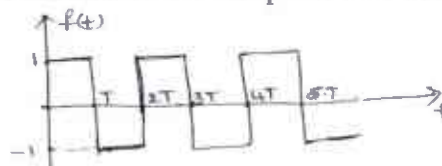


Fig.Q.8(b)

(10 Marks)

**Module-5**

- 9 a. Define Z parameters. Determine Z parameters in terms of Y parameters. (06 Marks)
- b. Determine h parameters of the circuit shown in Fig.Q.9(b) (07 Marks)

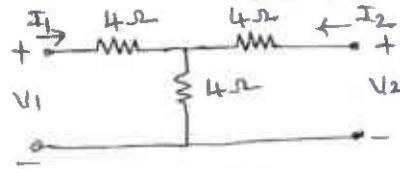


Fig.Q.9(b)

- c. For the network shown in Fig.Q.9(c). Find the transmission parameters. (07 Marks)

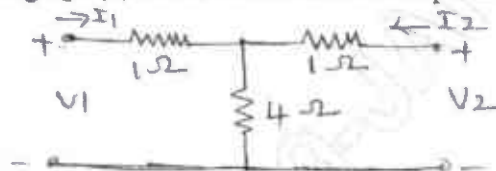


Fig.Q.9(c)

**OR**

- 10 a. Define Q-factor, selectivity and Band width. (03 Marks)
- b. A series RLC circuit has a resistance of  $10\Omega$ , an inductance of  $0.3\text{H}$  and a capacitance of  $100\mu\text{F}$ . The applied voltage is  $230\text{V}$ . Find: i) The resonant frequency ii) lower and upper cut off frequencies iii) current at resonance iv) currents at  $f_1$  and  $f_2$  v) Voltage across the inductance at resonance. (07 Marks)
- c. Derive the expression for the resonant frequency of the circuit shown in Fig.Q.10(c). Also show that the circuit will resonate at all frequency if  $R_L = R_C = \sqrt{\frac{L}{C}}$ . (10 Marks)

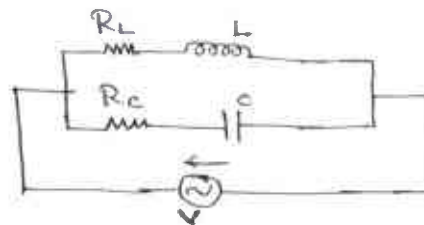


Fig.Q.10(c)

\*\*\*\*\*



APV  
Signature

Scheme & Solution

Signature of Scrutinizer

Subject Title: Network Theory

Subject Code: 18EC32

Question Number	Solution	Marks Allocated
1 a.	<p>Module-1</p> <p><math>5V</math> source, <math>5\Omega</math> resistor, <math>20\Omega</math> and <math>30\Omega</math> resistors in parallel. <math>3/30 = 0.1A</math></p> <p><math>1.5 \times 4 = 06 \text{ Marks}</math></p> <p><math>20 \parallel 30 = 12\Omega</math></p> <p><math>5V</math> source, <math>5\Omega</math> resistor, <math>12\Omega</math> resistor, <math>0.1A</math> current source</p> <p><math>12 \times 0.1 = 1.2V</math></p> <p><math>5V</math> source, <math>5\Omega</math> resistor, <math>12V</math> source, <math>12\Omega</math> resistor</p> <p><math>i = \frac{12/5}{17} = \frac{5-1.2}{17} = 0.2235A</math></p>	<p>1.5 marks</p> <p>1.5 marks</p> <p>1.5 marks</p> <p>1.5 marks</p>
b.	<p><math>i_1 - i_2 = 1A</math> constraint equation <math>\rightarrow</math></p> <p>Supermesh equation</p> <p><math>2(i_1 - i_3) + (i_2 - i_3) + 2i_2 - 2 = 0</math></p> <p><math>2i_1 + 3i_2 - 3i_3 = 2 \rightarrow 2</math></p> <p>KVL for mesh 3</p> <p><math>2(i_3 - i_1) + i_3 + (i_3 - i_2) = 0</math></p> <p><math>-2i_1 + i_2 + 4i_3 = 0 \rightarrow 3</math></p> <p>Solving 2 &amp; 3</p> <p><math>i_1 = 1.545A</math> <math>i_2 = 0.545A</math> <math>i_3 = 0.909A</math></p> <p>Solving <math>i_1, i_2, i_3</math> } 3 marks</p>	<p>0.1 marks</p> <p>0.2 marks</p> <p>0.1 marks</p> <p>0.3 marks</p>
c.	<p><math>V_1</math>, <math>V_2</math>, <math>V_3</math> nodes</p> <p><math>V_2 = 12V \rightarrow</math></p> <p><math>V_a = V_1 - V_3 \rightarrow</math></p>	<p>1 marks</p> <p>1 marks</p>

"APPROVED"

Registrar

Registrar (Evaluation)

Visvesvaraya Technological University  
BELAGAVI - 590018



Question Number	Solution	Marks Allocated
-----------------	----------	-----------------

At Node 1:  $\frac{V_1 - V_2}{2} + \frac{V_1}{6} - 1 = 0$

$\frac{V_1 - 12}{2} + \frac{V_1}{6} - 1 = 0 \implies V_1 = 9.33V \rightarrow$

02 Marks

At Node 3:  $\frac{V_3 - V_2}{2} + \frac{V_3}{3} + 1 = 0 \implies V_3 =$

$V_2 = 12V \implies V_3 = 6V \rightarrow$

02 Marks



$V_a = V_1 - V_3 = 3.33V \rightarrow$

01 Mark

Power delivered by 1A current source  
 $= 1 \times V_a = 3.33W \rightarrow$

01 Mark

2(c)

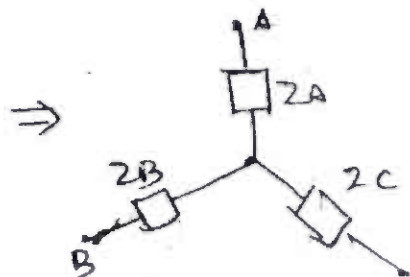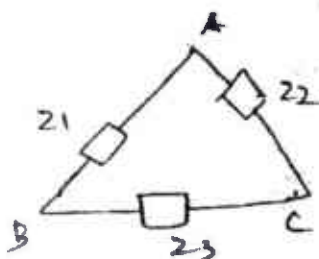

Circuit  $\rightarrow$  1 Mark

$Z_{AB} = Z_1 \parallel (Z_2 + Z_3)$   
 $Z_{BC} = Z_3 \parallel (Z_1 + Z_2)$   
 $Z_{AC} = Z_2 \parallel (Z_1 + Z_3)$


$Z_{AB} = Z_A + Z_B$   
 $Z_{BC} = Z_B + Z_C$   
 $Z_{AC} = Z_A + Z_C$

02 Marks

$Z_A = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3} \implies$  1 Mark  
 $Z_B = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3} \implies$  1 Mark  
 $Z_C = \frac{Z_2 Z_3}{Z_1 + Z_2 + Z_3} \implies$  1 Mark

$Z_A \rightarrow$  1 Mark  $Z_B \rightarrow$  1 Mark  $Z_C \rightarrow$  1 Mark

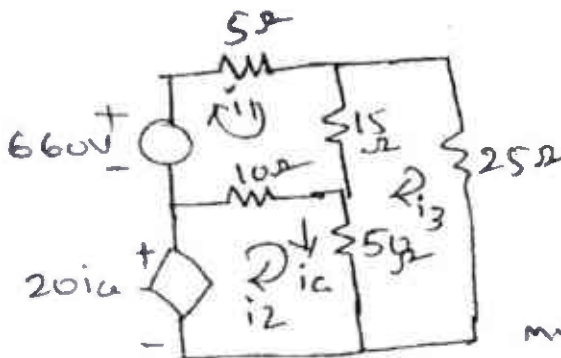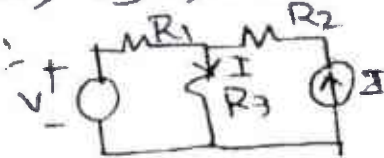

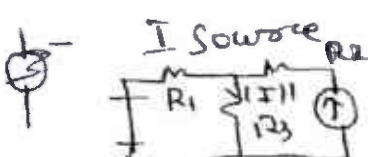
b.



$i_a = i_2 - i_3$

Mesh 1:  $30i_1 - 10i_2 - 15i_3 = 660 \rightarrow$  01 Mark


Mesh 2:  $-10i_1 + 60i_2 - 50i_3 = 20i_a \rightarrow$  01 Mark

Question Number	Solution	Marks Allocated
	<p>mesh 3 <math>-15i_1 - 50i_2 + 90i_3 = 0</math> <math>\rightarrow</math> (3)</p> <p>Solving eq 1, 2 &amp; 3</p> <p><math>i_1 = 42A</math> <math>i_2 = 27A</math> <math>i_3 = 22A</math></p> <p><math>i_a = 5A</math></p> <p>Power delivered by the dependent voltage source <math>= 20i_6 \cdot i_2</math>  <math>= 100 \cdot 27 = 2700W</math> <math>\rightarrow</math> (delivered)</p> <p>2 c <math>V_2 - V_3 = 10V \rightarrow</math> (1)</p> <p>Node 1 <math>\frac{V_1 - V_3}{4} + \frac{V_1 - V_2}{3} + \frac{V_1}{2} + 8 - 4 = 0</math></p> <p><math>1.083V_1 - 0.333V_2 - 0.25V_3 = 12 \rightarrow</math> (2)</p> <p>Super node <math>\frac{V_2 - V_1 + V_2 + 4 - 20}{3} + \frac{V_3 - V_1 + V_3/5}{4} = 0</math></p> <p><math>-0.583V_1 + 1.333V_2 + 0.45V_3 = 16 \rightarrow</math> (3)</p> <p>Solving eq 1, 2 &amp; 3</p> <p><math>V_1 = 18.15V</math> <math>V_2 = 17.43V</math> <math>V_3 = 7.43V</math></p>	<p>0 marks</p> <p>02 marks</p> <p>0 marks</p> <p>0 marks</p> <p>6</p> <p>01 marks</p> <p>01 marks</p> <p>02 marks</p> <p>02 marks</p> <p>03 marks</p> <p>1 marks</p> <p>1 marks</p> <p>1 marks</p> <p>8</p>
3 a.	<p>module - 2</p> <p>Statement <math>\rightarrow</math> 03 marks</p> <p>Explanation: <math>\rightarrow</math> 03 marks</p>  <p>Considering V source</p>   <p><math>I = I' + I''</math></p>	<p>03 marks</p> <p>03 marks</p> <p>6</p>

Question Number	Solution	Marks Allocated
-----------------	----------	-----------------


Exp calculations can also be done by considering both the voltage sources.

b. Converting I-V source

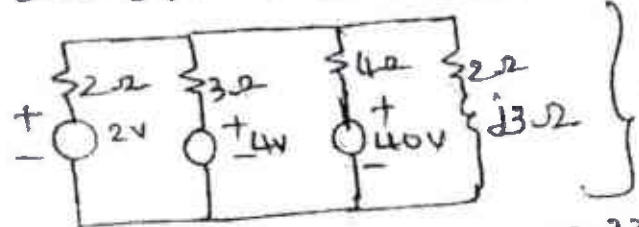

$$E = \frac{2/2 + 4/3 + 40/4}{1/2 + 1/3 + 1/4} = \frac{12.333}{1.083} = 11.38V \rightarrow 02 \text{ marks}$$
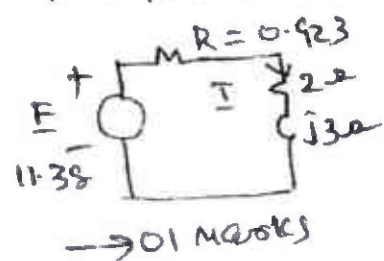
$$R = 1/1.083 = 0.923 \Omega \rightarrow 01 \text{ mark}$$




$$I = \frac{11.38}{0.923 + 2 + j3} = \frac{11.38}{2.923 + j3}$$

$$= \frac{11.38}{4.18 \angle 45.744^\circ} = 2.717 \angle -45.744^\circ \text{ A} \rightarrow 02 \text{ marks}$$

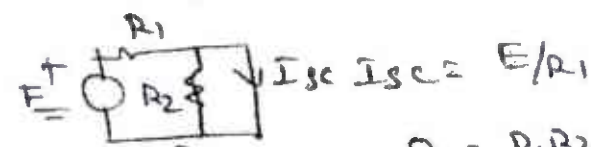c. Statement with circuit  $\rightarrow 03 \text{ marks}$





$$I_L = \frac{E R_2}{R_1 R_2 + R_2 R_L + R_1 R_L} \rightarrow \text{C}$$



$$I_{sc} = E/R_1$$




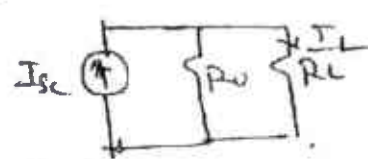
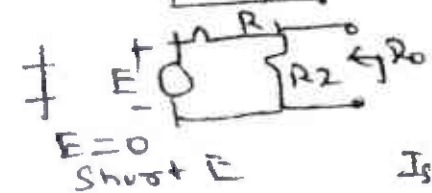
$$R_0 = \frac{R_1 R_2}{R_1 + R_2} \text{ Proof} \rightarrow 03 \text{ marks}$$



$$I_L = \frac{I_{sc} \cdot R_0}{R_0 + R_L} = \frac{E R_2}{R_1 R_2 + R_2 R_L + R_1 R_L} \rightarrow \text{D}$$

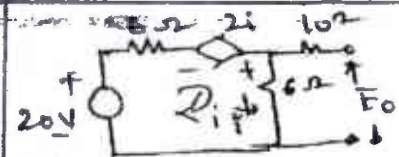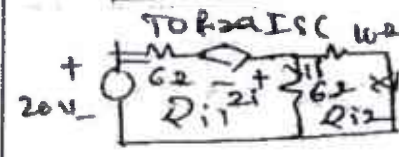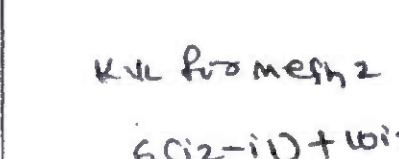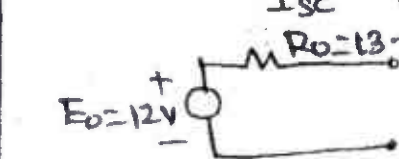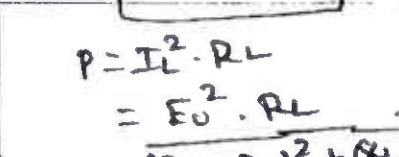Q & D of 2 are same. Hence the theory is proved.



Question Number	Solution	Marks Allocated
<p>a.</p>  	<p>Apply KVL</p> $6i - 2i + 6i - 20 = 0$ $i = 2A \quad E_0 = 2 \times 6 = 12V \rightarrow 0.2 \text{ marks}$ <p>TO find Isc</p>  <p>KVL for mesh 1</p> $-20 + 6i_1 - 2(i_1 - i_2) + 6(i_1 - i_2) = 0$ <p>KVL for mesh 2</p> $10i_1 - 4i_2 = 20 \rightarrow (1)$ $6(2 - i_1) + 10i_2 = 0$ $-6i_1 + 16i_2 = 0 \rightarrow (2)$ <p>Solving (1) &amp; (2)</p> $i_2 = I_{sc} = 0.8823A \rightarrow 0.1 \text{ marks}$ $R_0 = \frac{E_0}{I_{sc}} = \frac{12}{0.8823} = 13.6\Omega \rightarrow 0.1 \text{ marks}$ 	<p>0.2 marks</p> <p>0.1 marks</p> <p>0.1 marks</p> <p>0.1 marks</p> <p>0.1 marks</p>
<p>b.</p> 	$I_L = \frac{E_0}{R_L + R_0 + j(X_L + X_0)}$ $I_L = \frac{E_0}{\sqrt{(R_L + R_0)^2 + (X_L + X_0)^2}}$ $P = I_L^2 \cdot R_L = \frac{E_0^2 \cdot R_L}{(R_L + R_0)^2 + (X_L + X_0)^2} \rightarrow (1)$ <p><math>\frac{dP}{dX_L} = 0</math> differentiate w.r.t <math>X_0</math></p> $X_L = -X_0$ <p>Substituting this condition in (1)</p> $P = \frac{E_0^2 \cdot R_L}{(R_L + R_0)^2} \quad \frac{dP}{dR_L} = 0 \quad R_L = R_0 \rightarrow 0.2 \text{ marks}$ <p><math>Z_L = Z_0^* \rightarrow</math> <u>2 marks</u></p> <p>Load impedance is the complex conjugate of the source impedance</p>	<p>0.2 marks</p> <p>0.2 marks</p>

Question Number	Solution	Marks Allocated																								
4 c.	<p>2Ω resistor can be ignored. 10Ω resistance is series with 1A current source.</p> <p>Node equations</p> $\frac{V_1}{8} + \frac{V_1 - 4}{3} + 1 = 0$ $\frac{V_1}{8} + \frac{V_1}{3} = \frac{4}{3} - 1 = \frac{1}{3}$ $0.4583V_1 = \frac{1}{3} \quad V_1 = 0.727V$ <p><math>I_{sc} = \frac{V_1}{8} = \frac{0.727}{8} = 0.0908A</math> → 0.3 marks</p> <p><math>R_o = \text{open circuit resistance} = 8 + 3 = 11\Omega</math> → 0.1 marks</p> <p>Current through load resistance = <math>\frac{0.0908}{2} = 0.0454A</math> → 0.1 marks</p> <p>→ 0.1 marks</p>																									
<u>Module-3</u>																										
5 a.	<table border="0"> <thead> <tr> <th>Element</th> <th>behaviour at <math>t=0^+</math></th> <th>behaviour at <math>t=\infty</math></th> <th></th> </tr> </thead> <tbody> <tr> <td>R</td> <td>R</td> <td>R</td> <td>→ 0.1 marks</td> </tr> <tr> <td>L</td> <td>OC</td> <td>SC</td> <td>→ 1/2 marks</td> </tr> <tr> <td>C</td> <td>SC</td> <td>OC</td> <td>→ 1/2 marks</td> </tr> <tr> <td>Capacitor with <math>V_0</math></td> <td>OC</td> <td>OC</td> <td>→ 1/2 marks</td> </tr> <tr> <td>Inductor with <math>I_0</math></td> <td>SC</td> <td>SC</td> <td>→ 1/2 marks</td> </tr> </tbody> </table>	Element	behaviour at $t=0^+$	behaviour at $t=\infty$		R	R	R	→ 0.1 marks	L	OC	SC	→ 1/2 marks	C	SC	OC	→ 1/2 marks	Capacitor with $V_0$	OC	OC	→ 1/2 marks	Inductor with $I_0$	SC	SC	→ 1/2 marks	
Element	behaviour at $t=0^+$	behaviour at $t=\infty$																								
R	R	R	→ 0.1 marks																							
L	OC	SC	→ 1/2 marks																							
C	SC	OC	→ 1/2 marks																							
Capacitor with $V_0$	OC	OC	→ 1/2 marks																							
Inductor with $I_0$	SC	SC	→ 1/2 marks																							
b.	<p><math>i(0^+) = 0</math> → 1 mark</p> <p>Switch <math>v = Ri + L \frac{di}{dt} + v_C</math></p> <p>at <math>t=0^+</math></p> <p><math>v = R i(0^+) + L \frac{di}{dt}(0^+) + 0</math></p> <p><math>\frac{di}{dt}(0^+) = \frac{v}{L} = 10A/sec</math> → 3 marks</p> <p>Differential eqn <math>0 = R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{i}{C}</math></p>																									

Question Number	Solution -	Marks Allocated
-----------------	------------	-----------------

$$R \frac{di(t)}{dt} + L \frac{d^2 i(t)}{dt^2} + i/c = 0$$

$$10 \cdot 10 + L \frac{d^2 i(t)}{dt^2} + 0 = 0 \quad \frac{di(t)}{dt} = \frac{-100}{L} = -100 \text{ A/sec} \rightarrow 3 \text{ marks}$$

$$\frac{d^2 i(t)}{dt^2} = -100 \text{ A/sec}^2$$

C. KVL immediately after switch

$$i(t) = 0 \rightarrow 0 \text{ marks}$$


$$V = Ri + L \frac{di}{dt}$$

$$\frac{di}{dt}(t) = \frac{V - Ri(t)}{L} = \frac{V}{L} = 100 \text{ A/sec} \rightarrow 2 \frac{1}{2} \text{ marks}$$

differentiating eq 1

$$\frac{d^2 i(t)}{dt^2} = -R/L \frac{di(t)}{dt} = -\frac{10}{1} \cdot 100$$

$$= -1000 \text{ A/sec}^2 \rightarrow 2 \frac{1}{2} \text{ marks}$$

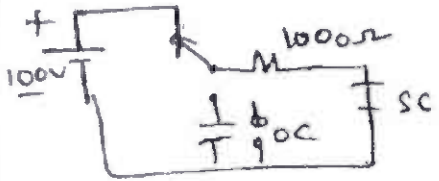6a.  switch like position a

$$i(t) = V/R = 0.1 \text{ A}$$

$$i(t) = i(t) = 0.1 \text{ A} \rightarrow 0.2 \text{ marks}$$

Switch removed from a to b

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0 \rightarrow V_c(t) = 0V \rightarrow 0 \text{ marks}$$

$$\text{at } t=0^+ \quad Ri(t) + L \frac{di(t)}{dt} + 0 = 0$$

$$\frac{di}{dt}(t) = -\frac{R \cdot i(t)}{L} = \frac{-1000 \times 0.1}{1} = -100 \text{ A/sec} \rightarrow 0.3 \text{ marks}$$


differentiating eq 1

$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + i/c = 0$$

$$\text{at } t=0^+ \quad R \frac{di(t)}{dt} + L \frac{d^2 i(t)}{dt^2} + \frac{i(t)}{C} = 0$$

$$\frac{d^2 i(t)}{dt^2} = -9 \times 10^5 \text{ A/sec}^2 = -9 \times 10^5 \text{ A/sec}^2 \rightarrow 0.4 \text{ marks}$$

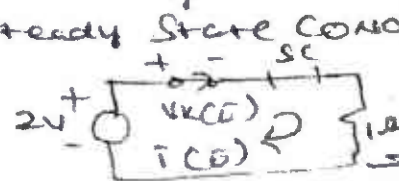b. Under Steady State condition circuit is shown




inductor circuit operation

$$V_L(t) = V_L(t) = 0V \rightarrow 0.2 \text{ marks}$$

$$i(t) = i(t) = 2 \text{ A} \rightarrow 0.2 \text{ marks}$$

Question Number	Solution	Marks Allocated
-----------------	----------	-----------------

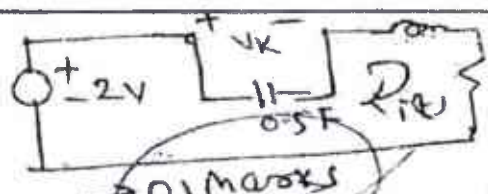

→ 01 marks

$$i(t) = C \frac{dV}{dt}$$

$$\text{at } t=0^+$$

$$i(0^+) = C \frac{dV(0^+)}{dt} \rightarrow$$

$$\frac{dV(0^+)}{dt} = \frac{i(0^+)}{C} = \frac{2}{0.5} = 4 \text{ V/sec}$$

01 marks

01 marks


02 marks

10

Module - 4

7a.

(i) Step Function

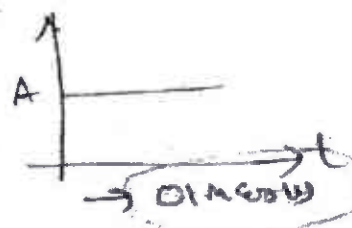

→ 01 marks


$$f(t) = A$$

$$F(s) = A/s$$

$$L[A u(t)] = A/s \rightarrow$$

02 marks

(ii) Ramp Function

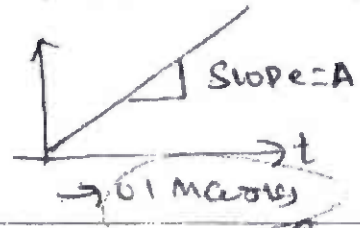

→ 01 marks

$$f(t) = A t u(t)$$

$$L[A t u(t)] = \frac{A}{s^2} \rightarrow$$

02 marks

(iii) Impulse Function




→ 01 marks

$$f(t) = k \delta(t)$$

$$L[k \delta(t)] = k \rightarrow$$

02 marks

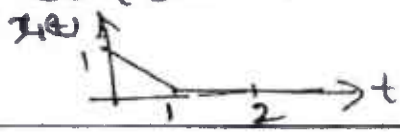b. The signal  $x(t)$  considered over one period is denoted as  $x_1(t)$  as shown





The signal  $x_1(t)$  may be viewed as  $x_1(t)$  and  $g(t)$


01 marks

9

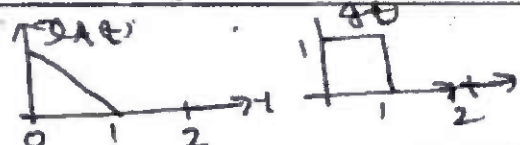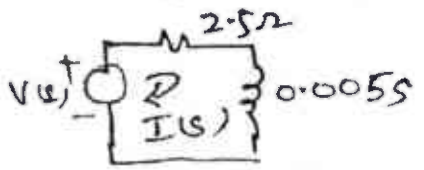

Question Number	Solution	Marks Allocated
	 <p>The signal <math>i(t)</math> may be viewed as multiplication of <math>f(t)</math> and <math>g(t)</math> i.e. <math>i(t) = f(t) \cdot g(t)</math></p> $= [-t+1][u(t)-u(t-1)]$ $f(s) = -tu(t) + tu(t-1) + u(t) - u(t-1)$ $= -t u(t) + (t-1+1)u(t-1) + u(t) - u(t-1)$ $= u(t) - \sigma(t) + \sigma(t-1)$ <p>Taking Laplace Transforming</p> $X_1(s) = \frac{1}{s} - \frac{1}{s^2} + \frac{1}{s^2} e^{-s}$ $= \frac{s-1+e^{-s}}{s^2} \quad T=2 \text{ sec}$	<p>02 marks</p> <p>01 marks</p> <p>03 marks</p>
8a	<p>The switch is closed at <math>t=0</math> and before it was open. Hence initial inductor current is zero <math>i(0) = 0A</math></p> $V(t) = 50s \Rightarrow 250t$	<p>04 marks</p>
	$V(s) = \frac{50 \cdot 250}{s^2 + 250^2}$ <p>The s-domain network is shown</p>  $V(s) = 2.5 I(s) + 0.005 s I(s)$ $I(s) = \frac{V(s)}{2.5 + 0.005 s}$ <p>Substituting <math>V(s)</math> &amp; simplifying</p> $I(s) = \frac{2.5 \times 10^6}{(s+500) [s^2 + (250)^2]}$ <p>Taking inverse Laplace Transforming</p> $I(s) = \frac{8}{s+500} - \frac{8 \cdot s}{s^2 + (250)^2} + \frac{4000 \times 250}{250 [s^2 + (250)^2]}$ <p>Taking inverse Laplace Transforming</p>	<p>01 marks</p> <p>01 marks</p> <p>04 marks</p>

11

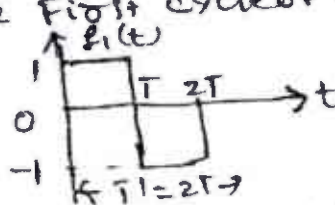Question Number	Solution	Marks Allocated
8 b	<p> <math display="block">i(t) = 8 \cdot e^{-500t} - 8 \cos(250t) + 16 \sin(250t)</math> <math display="block">= [8 \cdot e^{-500t} - 8 \cos(250t) + 16 \sin(250t)] A</math> </p> <p>                     considers the first cycle of the function <math>f(t)</math> as shown                 </p>  <p>                     Let <math>T</math> be the time period of <math>f(t)</math> which is <math>2T</math> </p> <p> <math>f_1(t) = 1</math> at <math>t=0</math> <math>f_2(t) = u(t)</math> </p> <p>                     at <math>t=T</math> instantaneous change from 1 to -1  <math>\therefore -2</math> at <math>t=2T</math> <math>f_3(t) = -2(u(t-T))</math> </p> <p>                     at <math>t=2T</math> <math>f_1(t)</math> changes from -1 to 0                      step of +1 at <math>t=2T</math> </p> <p> <math>f_4(t) = u(t-2T)</math> </p> <p> <math>f_5(t) = f_1(t) + f_2(t) + f_3(t) + f_4(t) = u(t) - 2u(t-T) + u(t-2T)</math> </p> <p> <math display="block">F(s) = \frac{1}{s} - \frac{2}{s} e^{-Ts} + \frac{1}{s} e^{-2Ts}</math> </p> <p> <math display="block">F(s) = \frac{F_1(s)}{1 - e^{-Ts}} = \frac{1}{s} \cdot \frac{1 - e^{-Ts}}{1 + e^{-Ts}} = \frac{1}{s} \tanh\left(\frac{Ts}{2}\right)</math> </p> <p style="text-align: center;"><u>Module -5</u></p>	<p>03 marks</p> <p>10</p> <p>02 marks</p> <p>02 marks</p> <p>02 marks</p> <p>02 marks</p> <p>02 marks</p> <p>10</p>
9 a.	<p> <math display="block">\begin{cases} V_1 = Z_{11}I_1 + Z_{12}I_2 \\ V_2 = Z_{21}I_1 + Z_{22}I_2 \end{cases}</math> </p> <p> <math display="block">Z_{11} = \frac{y_{22}}{\Delta y} \quad \Delta y = y_{11}y_{22} - y_{12}y_{21}</math> </p> <p> <math display="block">Z_{12} = \frac{-y_{12}}{\Delta y} \quad Z_{21} = \frac{-y_{21}}{\Delta y}</math> </p> <p> <math display="block">Z_{22} = \frac{y_{11}}{\Delta y}</math> </p>	<p>02 marks</p> <p>01 marks</p> <p>01 marks</p> <p>01 marks</p>

Question Number	Solution	Marks Allocated
9 b.	$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned} \quad \left. \begin{array}{l} \\ \\ \\ \\ \end{array} \right\} \longrightarrow$ $h_{11} = \frac{V_1}{I_1} \Big _{V_2=0} \quad V_1 = I_1 [4 + 4h_{11}]$ $h_{11} = \frac{V_1}{I_1} = 6 \Omega \longrightarrow$ $h_{21} = \frac{I_2}{I_1} \Big _{V_2=0} \quad -I_2 = \frac{I_1 \cdot 4}{4+4} = h_{21} = -1/2 \longrightarrow$ $h_{12} = \frac{V_1}{V_2} \Big _{I_1=0} \quad V_1 = \frac{V_2 \cdot 4}{4+4} = h_{12} = 1/2 \longrightarrow$ $h_{22} = \frac{I_2}{V_2} \Big _{I_1=0} \quad V_2 = (4+4) I_2 \quad h_{22} = \frac{1}{8} S \longrightarrow$	<p>01 marks</p> <p>1/2 marks</p> <p>1/2 marks</p> <p>1/2 marks</p> <p>1/2 marks</p>
c.	$V_1 = A V_2 - B I_2 \quad I_1 = C V_2 - D I_2 \longrightarrow$ $A = \frac{V_1}{V_2} \Big _{I_2=0} = 5/4 \longrightarrow$ $D = -\frac{I_1}{I_2} \Big _{V_2=0} = 5/4 \longrightarrow$ $C = \frac{I_1}{V_2} \Big _{I_2=0} = \frac{1}{4} S \longrightarrow$ $B = \frac{V_1}{-I_2} \Big _{V_2=0} = \frac{9}{4} \Omega \longrightarrow$	<p>01 marks</p> <p>1/2 marks</p> <p>1/2 marks</p> <p>1/2 marks</p> <p>1/2 marks</p>
10 a.	<p>Q factor = <math>\frac{XL}{R}</math> or <math>\frac{XC}{R} \longrightarrow</math> 01 marks</p> <p>Selectivity = <math>\frac{f_s}{f_2 - f_1} \longrightarrow</math> 01 marks</p> <p>Band width = <math>f_2 - f_1 \longrightarrow</math> 01 marks</p> <p>b. (i) <math>f_0 = \frac{1}{2\pi\sqrt{LC}} = 29.07 \text{ Hz} \longrightarrow</math> 01 marks</p> <p>(ii) <math>f_1 = \frac{1}{2\pi} \left[ \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right] = 26.53 \text{ Hz} \longrightarrow</math> 1/2 marks</p>	<p>3</p>



Question Number	Solution	Marks Allocated
100	<p><math>f_0 = \sqrt{f_1 f_2}</math></p> <p><math>f_2 = 31.8242</math> →</p> <p>(iii) current at resonance = <math>230/10 = 23A</math> →</p> <p>(iv) current at <math>f_1</math> &amp; <math>f_2 = I_m/\sqrt{2} = 23/\sqrt{2} = 16.26A</math> →</p> <p>(v) Voltage across inductor = <math>V_L = I \cdot X_L = 1259.44V</math> →</p> <p>Admittance of R-L circuit = <math>Y_L = \frac{1}{R_L + j\omega L} = \frac{R_L - j\omega L}{R_L^2 + \omega^2 L^2}</math></p> <p>Admittance of R-C circuit = <math>Y_C = \frac{1}{R_C - j\omega C} = \frac{R_C + j\omega C}{R_C^2 + \omega^2 C^2}</math></p> <p><math>Y = Y_L + Y_C</math></p> $= \frac{R_L}{R_L^2 + \omega^2 L^2} + \frac{R_C}{R_C^2 + \omega^2 C^2} + j \left( \frac{\omega C}{R_C^2 + \omega^2 C^2} - \frac{\omega L}{R_L^2 + \omega^2 L^2} \right)$ <p>equating j part to zero</p> <p>resonance frequency = <math>\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{R_L^2 - L/C}{R_C^2 - L/C}}</math> rad/sec</p> <p>To prove that circuit will resonate at all frequency</p> $\frac{1/\omega C}{R_C^2 + \omega^2 C^2} - \frac{\omega L}{R_L^2 + \omega^2 L^2}$ <p>Substituting <math>R_L = R_C = \sqrt{L/C}</math> in above equation</p> $\frac{1/\omega C}{L/C + \omega^2 C^2} - \frac{\omega L}{L/C + \omega^2 L^2}$ $\frac{1}{\omega L + \omega C} - \frac{1}{\omega L + \omega C} = 0$ <p>∴ circuit resonates at all frequency when <math>R_L = R_C = \sqrt{L/C}</math> →</p>	<p>1/2 marks</p> <p>0.1 marks</p> <p>0.1 marks</p> <p>0.1 marks</p> <p>7</p> <p>0.4 marks</p>
		<p>10</p> <p>0.4 marks</p>

"APPROVED"

*Binnig*

Registrar (Evaluation)

Visvesvaraya Technological University

BELAGANUR - 590018