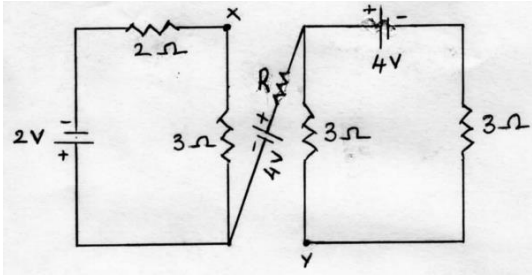
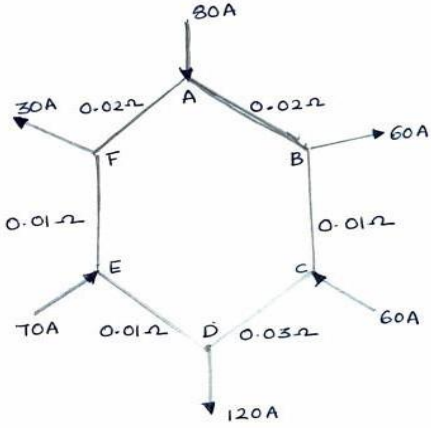
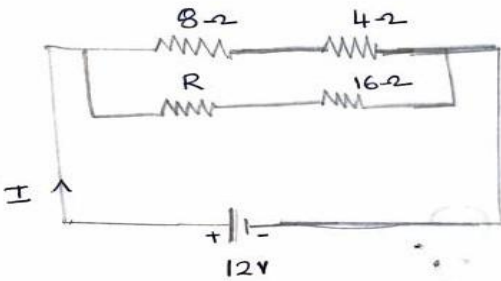



Internal Assessment Test I

Sub:	BASIC ELECTRICAL ENGINEERING					Code:	18ELE13
Date:	27/01/2021	Duration:	90 mins	Max Marks:	50	Sem:	1
						Section:	A,B,C,D,E,F,G


Note: Answer any **FIVE FULL** Questions
Sketch neat figures wherever necessary. Answer to the point. **Good luck!**

Marks OBE
CO RBT

1 (a)	State and explain Ohm's law with an illustration. Also list its limitations	[5]	CO1	L2
(b)	For the circuit shown in figure ,Obtain the voltage between points X and Y 	[5]	CO1	L4
2 (a)	Find the current in various branches of the given network 	[4]	CO1	L3
(b)	A circuit consist of two parallel resistors having resistances of 20 Ω and 30 Ω respectively connected in series with a 15 Ω resistor. If current through 15 Ω resistor is 3 A, find (i) current through the branches; (ii) voltage across whole circuit; and (iii) power consumed by 20 Ω and 15 Ω resistors	[6]	CO1	L3
3 (a)	If the total power dissipated in the circuit is 18 W, find the value of R and its current 	[5]	CO1	L3
(b)	Find the current supplied by each battery & power dissipated across 100Ω resistor	[5]	CO1	L3

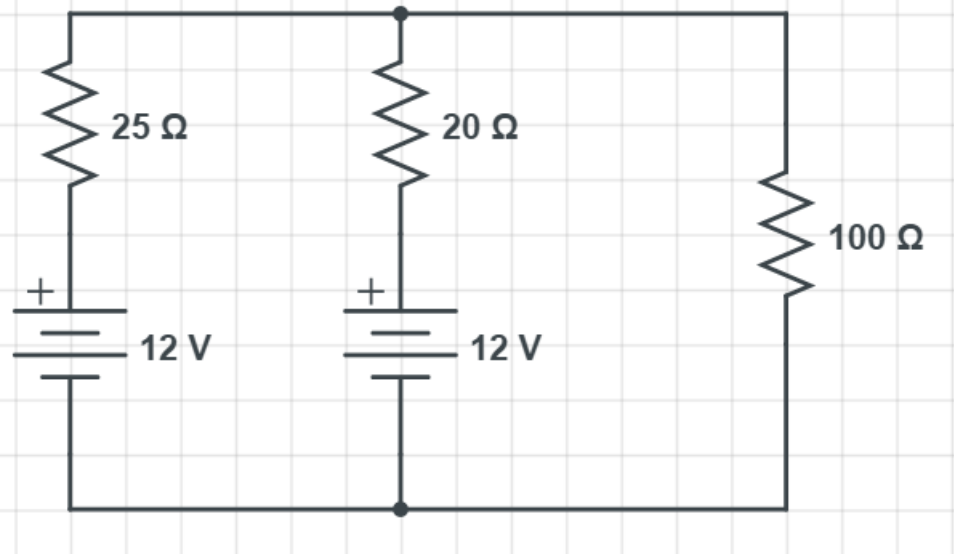


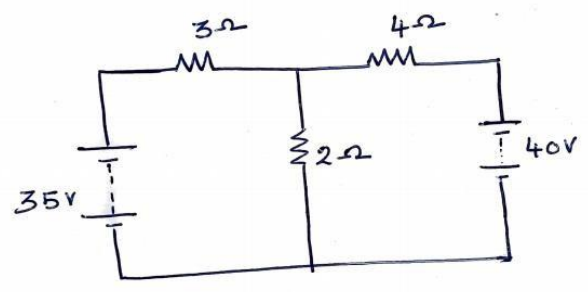4 (a) Calculate the current through the 2 Ω resistor in the given circuit



[5] CO1 L3

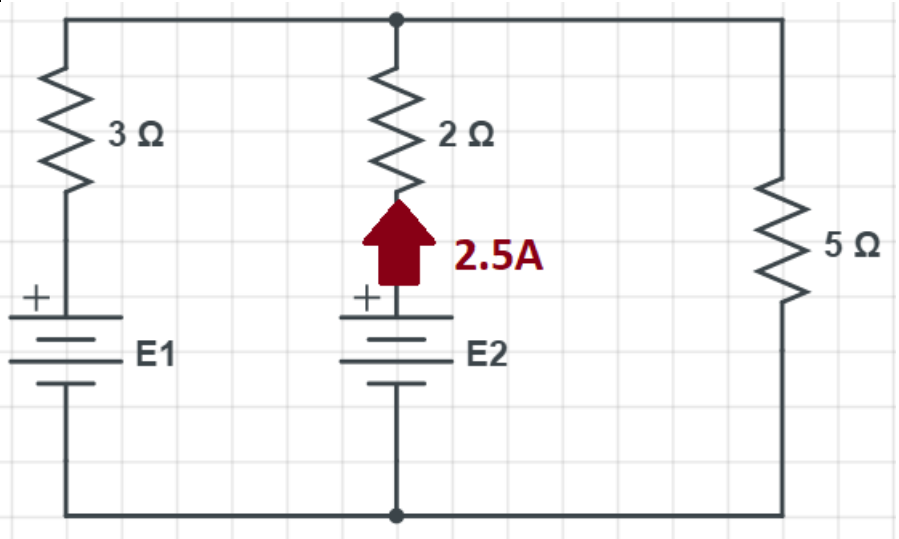(b) Find E_1 , E_2 & I when power dissipated in 5 Ω resistance is 125W.



[5] CO1 L2

5 (a) State and explain KVL and KCL with examples.

[6] CO1 L2

(b) A current of 30A flows through two ammeters A and B in series. The potential difference across A is 0.3V and across B is 0.6V. Find how the same current will divide between A and B when they are in parallel.

[4] CO1 L3

6 Define average value and rms value of a sinusoid. Derive the expressions and obtain the form factor and the peak factor of the sinusoid.

[10] CO2 L3


7 The equation of an AC voltage & current are given as $v(t) = 100 \sin(314t + 60^\circ)$ V , $i(t) = 10 \sin(314t)$ A, determine (i) peak current; (ii) average voltage; (iii) frequency; (iv) time period; (v) RMS value of current; (vi) instantaneous value of voltage at $t = 3$ ms; (vii) form factor; and (viii) phase difference between voltage and current & state which one is leading

[10] CO2 L3

8(a) Explain the terms (i) Time period (ii) Frequency (iii) Instantaneous value (iv) Amplitude (v) Angular Frequency of a sinusoidal alternating voltage.

[5] CO2 L2

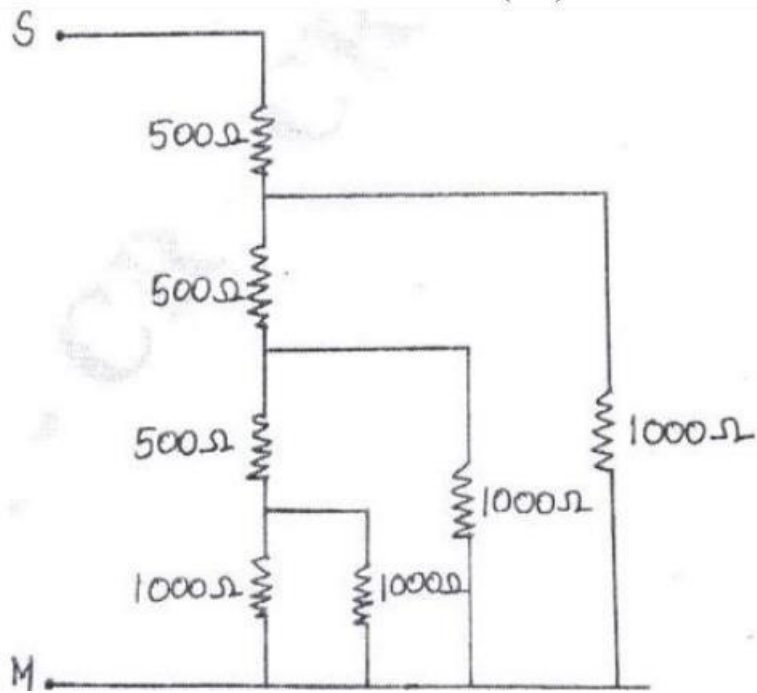(b) Find the equivalent resistance across S and M in the given figure



[5]

CO1

L3



BEE - Scheme of Evaluation for IAT-1.

- 1) a) Ohms law - Statement and formula }
- 2.5m. } 5m.
Limitations of Ohms law - 2.5m }

1) b)

$$I_1 = 2/5 \text{ A}, \quad I_2 = 2/3 \text{ A.} \quad \longrightarrow 3 \text{ m.}$$

$$V_{xy} = -3.2 \text{ A} \quad \longrightarrow 2 \text{ m.}$$

2) a)

$$I = 39 \text{ A} \quad \longrightarrow 4 \text{ m.}$$

2) b)

i),

$$\begin{aligned} I_{20\Omega} &= 1.8 \text{ A} \\ I_{30\Omega} &= 1.2 \text{ A} \end{aligned} \quad \left. \vphantom{\begin{aligned} I_{20\Omega} \\ I_{30\Omega} \end{aligned}} \right\} 2 \text{ m.}$$

ii),

$$\begin{aligned} R_{eq} &= 27\Omega \\ V_{ab} &= 8 \text{ V} \end{aligned} \quad \left. \vphantom{\begin{aligned} R_{eq} \\ V_{ab} \end{aligned}} \right\} 2 \text{ m.}$$

$$\begin{aligned} \text{(iii)} \quad P_{20\Omega} &= 64.8 \text{ W} \\ P_{15\Omega} &= 135 \text{ W} \end{aligned} \left. \vphantom{\begin{aligned} P_{20\Omega} \\ P_{15\Omega} \end{aligned}} \right\} 2 \text{ m.}$$

3) a)

$$\begin{aligned} R &= 8 \Omega \\ I_R &= 0.5 \text{ A} \end{aligned} \left. \vphantom{\begin{aligned} R \\ I_R \end{aligned}} \right\} 5 \text{ m.}$$

3) b)

$$I_1 = 0.048 \text{ A}, \quad I_2 = 0.108 \text{ A} \quad \longrightarrow 3 \text{ m.}$$

$$P_{DC(100\Omega)} = 1.1664 \text{ W} \quad \longrightarrow 2 \text{ m.}$$

4) a)

$$I_1 = 11.154 \text{ A}, \quad I_2 = 10.385 \text{ A.} \quad \longrightarrow 3 \text{ m.}$$

$$I_{2\Omega} = 21.538 \text{ A} \quad \longrightarrow 2 \text{ m.}$$

4) b)

Procedure — 2 m

$$E_1 = 32.5 \text{ V} \quad \longrightarrow 1 \text{ m}$$

$$E_2 = 30 \text{ V} \quad \longrightarrow 1 \text{ m}$$

$$I = 2.5 \text{ A} \quad \longrightarrow 1 \text{ m}$$

5) a) $KCL + \text{Example} \rightarrow 3m.$ } $6m.$
 $KVL + \text{Example} \rightarrow 3m.$

5) b) ~~$I_{20A} =$~~ $\Sigma A = 20A$ } $4m.$
 $I_B = 10A$

6) Average value derivation $\rightarrow 3m$
 rms " " $\rightarrow 3m$
 form factor " $\rightarrow 2m.$
 peak factor " $\rightarrow 2m$ } $10m.$

7) (i) $I_{peak} = 10A \rightarrow 1m$

(ii) $V_{avg} = 63.694V \rightarrow 1m$

(iii) $f = 50Hz \rightarrow 1m$

iv, $T = 0.02 \text{ s} \rightarrow 1 \text{ m}$

v, $I_{\text{rms}} = 7.071 \text{ A} \rightarrow 1 \text{ m}$

vi, $v(t) = 91.354 \text{ V} \rightarrow 3 \text{ m}$.

vii, Form factor = 1.11 $\rightarrow 1 \text{ m}$

viii, $\phi = 60^\circ$, Voltage is leading $\rightarrow 1 \text{ m}$.

8) a)

i, Time period $\rightarrow 1 \text{ m}$

ii, Frequency $\rightarrow 1 \text{ m}$.

iii, Instantaneous value $\rightarrow 1 \text{ m}$

iv, Amplitude $\rightarrow 1 \text{ m}$

v, Angular frequency $\rightarrow 1 \text{ m}$

} 5m.

8) b)

$R_{\text{eq}} = 1000 \Omega \rightarrow 3 \text{ m}$.

procedure $\rightarrow 2 \text{ m}$

} 5m.