

Internal Assessment Test II										
Sub:	BASIC ELECTRICAL ENGINEERING						Code:	18ELE13		
Date:	02/03/2021	Duration:	90 mins	Max Marks:	50	Sem:	1	Section:	A,B,C,D,E,F,G	
Note: Answer any FIVE FULL Questions Sketch neat figures wherever necessary. Answer to the point. Good luck!										
								Marks	OBE	
									CO	RBT
1a	Show that in a pure inductor the current lags behind the voltage by 90° . Also draw the voltage and current waveforms.						[5]	CO2	L2	
1b	A coil of power factor 0.6 is in series with $100\mu\text{F}$ capacitor. When connected to a 50Hz supply, the potential difference across the coil is equal to potential difference across the capacitor. Find the resistance and inductance of the coil.						[5]	CO2	L3	
2	With a neat diagram, explain how the 3-phase active power can be measured by two wattmeter method. Hence, obtain the expression for power factor. Draw the phasor diagram.						[10]	CO3	L3	
3a	Three similar coils each having resistance of $10\ \Omega$ and reactance of $8\ \Omega$ are connected in star across a 400 V, 3-phase supply. Determine (i) Line current; (ii) Total power; and (iii) reading of each of the two wattmeters connected to measure the active power.						[6]	CO3	L4	
3b	What is meant by power factor in an ac circuit? What is its significance?						[4]	CO2	L1	
4a	Three coils each of impedances $20\angle 60^\circ\ \Omega$ are connected in star to a 3-phase 400 V, 50 Hz supply. Find the reading on each of the two wattmeters connected to measure the power input.						[4]	CO3	L4	
4b	Deduce the relationship between the phase and line currents of a 3-phase delta connected system.						[6]	CO3	L3	
5a	A resistance of $7\ \Omega$ is connected in series with a pure inductance of 31.8 mH and the circuit is connected to a single phase 100 V, 50 Hz, sinusoidal supply. Calculate (i) Circuit current; (ii) Phase angle; (iii) Power factor; and (iv) Power.						[5]	CO2	L3	
5b	Show that voltage and current in a pure resistive circuit are in phase and power consumed in the circuit is equal to product of rms value of voltage and current.						[5]	CO2	L2	
6a	Derive the expression for power in AC circuit in terms of voltage, current and power factor of the circuit.						[5]	CO2	L2	
6b	Two impedances $Z_1 = (0.167 - j0.167)\ \Omega$ and $Z_2 = (0.1 + j0.05)\ \Omega$ are connected in parallel across a 100 V, 50 Hz ac supply. Calculate the current in each branch and total current. Also, find the power factor of the circuit.						[5]	CO2	L3	
7a	With a neat connection diagram explain three-way control of lamp. Also develop the truth table indicating the state of lamp for different positions of switches.						[6]	CO5	L2	
7b	Write short note on (i) MCB; and (ii) Precautions against electric shock.						[4]	CO5	L2	
8a	What is earthing? Why is earthing required? With a neat sketch explain plate earthing.						[6]	CO5	L2	
8b	Given $v(t) = 200 \sin(377t)$ V and $i(t) = 8 \sin(377t - 30^\circ)$ A for an AC circuit. Determine: (i) Reactive Power; (ii) True power; and (iii) Apparent power.						[4]	CO5	L2	

Scheme of Evaluation - IAT 2.

1) a) Derivation for pure Inductor — 4 M.

Voltage & Current wavefams — 1 M

5 m

1) b)

$$R = 19.09 \Omega \quad \text{— 2 M}$$

$$L = 0.0811 \text{ H} \quad \text{— 2 m.}$$

steps — 1 m.

5 m

2) a)

3-d Active power derivation — 4 M.

Power factor measurement — 6 M.

(Phasor diagram — 2 m)

10 m

3) a)

$$i_1 = 18.0337 \text{ A} \rightarrow 2 \text{ m.}$$

$$ii', p = 9.7562 \text{ kW} \rightarrow 2 \text{ m}$$

$$ii'', w_1 = 2.6249 \text{ kW} \rightarrow 1 \text{ m}$$

$$w_2 = 7.13124 \text{ kW} \rightarrow 1 \text{ m}$$

6 m

3) b) definition of P.f $\rightarrow 2m$.

Significance $\rightarrow 2m$
4m

4) a) $W_1 = 0 \rightarrow 2m$

$W_2 = 2309.398W \rightarrow 2m$
4m

4) b) $I_L = \sqrt{3} I_{ph}$ derivation $\rightarrow 3m$.

$V_L = V_{ph} \rightarrow 1m$.

phasor diagram $\rightarrow 2m$
6m

5) a) (i) $I_L = 8.1978 A \rightarrow 1m$

(ii) $\phi = -54.98^\circ \rightarrow 1m$

(iii) $\cos\phi = 0.5739 \rightarrow 1m$

(iv) $P = 470.44W \rightarrow 1m$

Steps $\rightarrow 1m$
5m

5) b)

Pure resistive circuit derivation \rightarrow 2 m.

Instantaneous power \rightarrow 2 m

phasor diagram \rightarrow $\frac{1 \text{ m}}{5 \text{ m}}$

6) a)

Derivation of voltage
Current
P-f $\left. \vphantom{\begin{matrix} \text{Derivation of voltage} \\ \text{Current} \\ \text{P-f} \end{matrix}} \right\} 5 \text{ m.}$

6) b) $I = (1099.15 - j100.67) \text{ A} \rightarrow 2 \text{ m.}$

$I_1 = (299.34 + j299.34) \text{ A} \rightarrow 1 \text{ m.}$

$I_2 = (799.81 - j400.01) \text{ A} \rightarrow 1 \text{ m}$

$\cos \phi = 0.9958 \rightarrow \frac{1 \text{ m}}{5 \text{ m}}$

7) a) Circuit diagram $\rightarrow 2m$.

Explanation $\rightarrow 2m$

Truth table $\rightarrow 2m$

6m

7) b) MCB $\rightarrow 2m$.

Electric shock $\rightarrow 2m$

4m

8) a) What is Earthing $\rightarrow 1m$

Why Earthing required $\rightarrow 1m$.

plate Earthing diagram $\rightarrow 2m$.

Explanation $\rightarrow 2m$

6m

8) b) (i), $Q = 400 \text{ VAR} \rightarrow 1m$

(ii), $P = 692.811 \text{ W} \rightarrow 1m$.

(iii), $S = 800.015 \text{ VA} \rightarrow 1m$

Steps $\rightarrow 1m$

4m