

USN

--	--	--	--	--	--	--	--	--	--

10ELE15/25

First/Second Semester B.E. Degree Examination, June/July 2017
Basic Electrical Engineering

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting
atleast TWO questions from each Part.**

PART – A

- 1 a. Choose the correct answers for the following : (04 Marks)
- i) As per ohms law
 A) $V \propto I$ B) $V \propto R$ C) $I \propto R$ D) $V = IR$
- ii) Which of the following is true both for a series and parallel circuit
 A) Resistances are additive B) Currents are additives
 C) Voltage drops are additive D) Powers are additives
- iii) Inductance opposes _____ in current in a circuit
 A) Only increases B) Only decreases
 C) Change D) None of these
- iv) A wire of resistance R is stretched to doubled its length the new resistance of the wire is
 A) R/2 B) 2R C) 4R D) R/4.
- b. State and explain Kirchoff's laws. (06 Marks)
- c. Define co-efficient of coupling and obtain the relation between self inductances, mutual inductance and co-efficient of coupling. (04 Marks)
- d. Two identical coils of 1200 turns each, are placed side by side such that, 60% of flux produced by one coil links the other. A current of 10A in the first coil, sets up a flux of 0.12 mwb. If the current in the first coil changes from +10A to - 10A in 20m sec.
 Find : i) The self inductance of coils
 ii) The EMF's induced in both coils. (06 Marks)
- 2 a. Choose the correct answers for the following : (04 Marks)
- i) An AC voltage is given by $100 \sin 314 t$. The frequency is
 A) 50 Hz B) 75 Hz C) 25 Hz D) 100 Hz
- ii) An alternating current is given by $i = 20 \sin 314 t$ and the time taken to complete 10 cycles is _____
 A) 0.02S B) 0.2S C) 2S D) 0.1S
- iii) The phase difference between V and I for the series R-L circuit _____ as X_L increases
 A) Decreases B) Remains constant
 C) Increases D) None of these
- iv) The voltage and current in AC circuit are given by $V = 50 \cos \omega t$ and $i = 5 \sin \omega t$.
 The power consumed by the circuits.
 A) 0 Watts B) 250 Watts C) 100 Watts D) 50 Watts.
- b. Define average and RMS value of all alternating current and find their relation with maximum value, if the alternating quality is sinusoidal. (08 Marks)
- c. A circuit consists of a resistance of 10Ω , an inductance of 16mH and a capacitance of $150\mu F$ connected in series. A supply of 100V at 50Hz is given to the circuit. Find the current, power factor and power consumed by the circuit. Draw the vector diagram. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.

- 3 a. Choose the correct answers for the following : (04 Marks)
- In a 3-phase system, the emf's are _____
A) 30° apart B) 60° apart C) 90° apart D) 120° apart
 - When the two watt meters used to measure a 3-phase power, give equal readings then the power factor of the circuit is
A) 0.5 B) 0 C) 0.866 D) 1
 - Active power drawn by a 3-phase balanced load is given by
A) $P = V_L I_L \cos \phi$ B) $P = \sqrt{3} V_L I_L$
C) $P = \sqrt{3} V_L I_L \cos \phi$ D) $P = \sqrt{3} V_{Ph} I_{Ph} \cos \phi$
 - The resistance between any two terminals of a balanced delta connected load is 20Ω. A resistance of each phase is _____
A) 20Ω B) 30Ω C) 10Ω D) 60Ω
- b. With the aid of a phasor diagram obtain the relationship between the line and phase values of voltages in a three-phase, star connected. (06 Marks)
- c. Show that two Watt meters are sufficient to measure 3φ power for balanced 3φ power system. (06 Marks)
- d. Three coils each having a resistance of 10Ω and an inductance of 0.02H are connected in star across 440V, 50Hz, 3-phase supply. Calculate the line current and total power consumed. (04 Marks)
- 4 a. Choose the correct answers for the following : (04 Marks)
- The dynamometer type Watt meters is used to measure _____
A) Only DC power B) Only AC power
C) Both DC and AC power D) None of these
 - The unit of electrical is equivalent
A) 3600 w – s B) 3.6 kw-s C) 1 KWH D) 100 WH
 - The rotating disc of the energy meter is made of _____
A) Copper B) Aluminium C) Platinum D) Silver
 - In an induction type energy meter, the braking torque is directly proportional to _____
A) Deflecting torque B) Controlling torque C) Speed of the disc D) Damping torque.
- b. With the help of a neat diagram, describe the constructional features and working of a dynamometer type Watt meter. (06 Marks)
- c. Name different types of domestic wiring and explain any one type of wiring. (04 Marks)
- d. What is the necessity of earthing? With a neat diagram, explain the pipe earthing. (06 Marks)

PART – B

- 5 a. Choose the correct answers for the following : (04 Marks)
- In a wave – winding, the number of parallel paths is equal to _____
A) P/2 B) 2 C) P D) 2P
 - A 4-pole wave connected generator has a useful flux of 0.02. Weber and generates a voltage of 288 V at 1200 rpm the number of conductors in the armature are
A) 180 B) 360 C) 720 D) 90
 - High voltage Dc generators uses _____ winding
A) Lap B) Wave C) Either A or B D) None of these
 - A commutator is made up of _____
A) Iron B) Copper segments C) Both A and B D) None of these.
- b. Derive an expression for armature torque in a DC motor. (05 Marks)
- c. The field current in a DC shunt machine is 2A and the line current is 20A at 200V. Calculate: i) The generated EMF. When working as generator ii) Torque in N-m when running at 1500 rpm as motor. Take the armature resistance as 0.5Ω. (06 Marks)
- d. What is back emf in a Dc motor? What is its significance? (05 Marks)

- 6 a. Choose the correct answers for the following : (04 Marks)
- When the supply frequency of a transformer is doubled then the hysteresis losses
 - Remains same
 - Doubled
 - Reduced by 50%
 - Hysteresis is equal to Eddy current loss
 - The losses which do not occur in transformer are _____
 - copper losses
 - magnetic losses
 - Friction losses
 - none of these
 - A transformer transfers electrical energy from primary to secondary usually with a change in
 - Frequency
 - Power
 - Voltage
 - Time period
 - The core of the transformer is laminated to reduce
 - Eddy current loss
 - Hysteresis loss
 - Copper loss
 - Friction loss.
- b. Derive an Emf equation of transformer. (05 Marks)
- c. A 600 KVA transformer has a efficiency of 92% at full load, unity power factor and at half load, 0.9 power factor. Determine its efficiency at 75% of full load and 0.9 power factor. (06 Marks)
- d. What are the various types of losses and how to overcome these losses in a transformer? (05 Marks)
- 7 a. Choose the correct answers for the following : (04 Marks)
- The disadvantages of a short pitched coils in an alternator is that
 - Harmonics are introduced
 - Waveform become non-sinusoidal
 - Voltage round the coil is reduced
 - None of the above
 - An 8-pole alternator runs at 600 rpm. The frequency of the induced Emf is _____
 - 40Hz
 - 50Hz
 - 60Hz
 - 75Hz
 - In an alternator, the number of slots per pole per phase is 4 and the slot angle is 15° . The distribution factor is _____
 - 0.945
 - 0.966
 - 0.956
 - 0.987
 - An alternator generates a no load line voltage of 11 KV. The full load terminal voltage is 10.6KV. The voltage regulation is.
 - 5%
 - 6%
 - 4%
 - 3.77%.
- b. Derive an expression for Emf equation of an alternator. What is the necessity of considering pitch factor and distribution factor for Emf equation? (08 Marks)
- c. A 12 pole, 500rpm, star connected alternator has 60 slots, with 20 conductors per slot. The flux per pole is 0.02 wb and is distributed sinusoidally. The winding factor is 0.97. Calculate: i) frequency ii) phase Emf iii) Line Emf. (08 Marks)
- 8 a. Choose the correct answers for the following : (04 Marks)
- When the rotor of 3 ϕ induction motor is blocked, the slip is _____
 - 0
 - 0.5
 - 0.1
 - 1
 - The direction of rotation of 3 ϕ induction motor depends on _____
 - supply voltage
 - Number of poles
 - The supply frequency
 - The phase sequence of the supply
 - A 4 pole, 50Hz induction motor has a slip of 4%. The frequency of the rotor current is _
 - 2.5Hz
 - 2Hz
 - 3Hz
 - 4Hz
 - Three phase wound rotor induction motors are also called as _____ motors
 - synchronous
 - Series
 - Commutator
 - Slip ring.
- b. Mention the advantages and disadvantages of squirrel cage and slip ring induction motors. (03 Marks)
- c. Explain why a starter is required for a 3- ϕ induction motor. With a circuit diagram explain the working of a star-delta starter for a 3- ϕ induction motor. (08 Marks)
- d. A 3- ϕ induction motor has 6 poles and runs at 940 rpm on full load. It is supplied from an alternator having 4 poles and running at 1500 rpm, Calculate the full load slip and the frequency of the rotor currents of the induction motor. (05 Marks)

CMRIT Library