

USN

--	--	--	--	--	--	--	--	--	--

10ELN/15/25

First/Second Semester B.E. Degree Examination, June/July 2017

Basic Electronics

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, choosing at least two from each part.

PART – A

- 1 a. Choose the correct answers for the following :
- The cut in voltage of a silicon diode is about _____
 A) 0.6V B) 0.6mV C) 1.2V D) 1.2mV
 - The ripple factor for a full wave rectifier is
 A) 0.482 B) 0.5 C) 1.21 D) -1.21
 - PIV rating of a diode in a bridge rectifier is _____
 A) V_m B) $2V_m$ C) $\frac{V_m}{2}$ D) $\frac{V_m}{\sqrt{2}}$
 - The zener resistance of a zener diode, which exhibits 50mV change in V_z for a 2.5mA change in I_z is _____
 A) 10Ω B) 40Ω C) 20Ω D) 60Ω (04 Marks)
- b. Draw and explain the V-I characteristics of silicon diode (04 Marks)
- c. Deduce the following for Fullwave rectifier i) I_{dc} ii) I_{rms} iii) Ripple factor (08 Marks)
- iv) Efficiency of rectification. (08 Marks)
- d. A full wave rectifier (bridge) supplies a load of 400Ω in parallel with a capacitor of $500\mu F$. If the ac-supply voltage is $230 \sin 314t$, V find the i) Ripple factor ii) Dc load current. (04 Marks)
- 2 a. Choose the correct answers for the following :
- The transistor acts as an amplifier in the _____ region.
 A) cut off B) active C) saturation D) inverse.
 - In a transistor the current conduction is due to _____ carriers.
 A) Majority B) Minority C) Both D) None of these.
 - The input resistance is highest for _____
 A) CB amplifier B) CC amplifier C) CE amplifier D) None of these.
 - The position of Q-point on the dc load line should be _____
 A) stable B) unstable C) bistable D) all the above. (04 Marks)
- b. Draw input and output characteristics of a transistors in common emitter configuration and explain in detail. (04 Marks)
- c. Obtain the relationship between α_{dc} and β_{dc} . (08 Marks)
- d. Calculate the values of I_c , I_E and β_{dc} for a transistor with $\alpha_{dc} = 0.98$ and $I_B = 120\mu A$. (04 Marks)
- 3 a. Choose the correct answers for the following :
- The reverse saturation current doubles for every _____ $^{\circ}C$ rise in temperature.
 A) 40 B) 45 C) 10 D) 50.
 - The stability factor "S" as the rate of change of collector current with _____
 A) Base current B) Reverse saturation current
 C) Emitter current D) V_{cc} .
 - For an emitter follower, the voltage gain is _____
 A) unity B) greater than unity C) less than unity D) zero.

- iv) In the fixed bias circuit, the stabilization of the Q-point is _____.
 A) very poor B) very high C) better D) very good. (04 Marks)
- b. Explain the circuit operation and analysis of voltage divider bias. (08 Marks)
- c. In the circuit shown in Fig. Q3(c), a NPN transistor with $\beta = 100$ is used. Find I_B , I_C and V_{CE} . Draw the dc load line and indicate the Q-point. Take $V_{BE} = 0.7$ volts. (08 Marks)

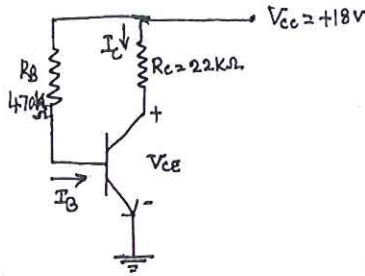


Fig. Q3(c)

- 4 a. Choose the correct answers for the following :
- An SCR has _____ number of p-n junctions
 A) One B) Two C) Three D) Four
 - FET is a _____ controlled device.
 A) Voltage B) Current C) Power D) None of these.
 - The holding current in an SCR is _____ the latching current.
 A) More than B) Less than C) Equal to D) none of these
 - A relaxation uses
 A) MOSFET B) SCR C) UJT D) BJT. (04 Marks)
- b. Draw and explain the V-I characteristic of SCR. (08 Marks)
- c. Explain the basic construction and equivalent circuit of UJT. (08 Marks)

PART - B

- 5 a. Choose the correct answers for the following :
- Bandwidth of an amplifier is given by _____
 A) $BW = f_L - f_H$ B) $BW = f_H - f_L$ C) $BW = f_L + f_H$ D) $BW = 2f_L - f_H$
 - An amplifier is RC phase shift oscillator contributes _____ phase shift.
 A) 180° B) 0° C) 90° D) 60° .
 - The crystal oscillator finds use, when the _____ stability is required.
 A) Amplitude B) Frequency C) Phase D) None of these.
 - In an oscillator, we use _____ feedback.
 A) Positive B) Negative C) Unity gain D) None of these. (04 Marks)
- b. Draw a neat circuit diagram of Hartley's oscillator and explain its working. What is the frequency of oscillations? (08 Marks)
- c. With a neat circuit diagram and frequency response, explain the operation of single stage RC coupled amplifier. (08 Marks)
- 6 a. Choose the correct answers for the following :
- An audio amplifier works over the frequency range _____.
 A) 20Hz to 20KHz B) 20Hz to 1MHz C) 1KHz to 4KHz D) None of these.
 - Op-amp is basically a _____ amplifier.
 A) Power B) Differential C) Optical D) Current.
 - In inverting amplifier there is _____ phase shift between input and output.
 A) 0° B) 90° C) 180° D) 360°
 - The maximum rate at which amplifier output can change in volts per microseconds ($V/\mu s$) is called _____.
 A) over rate B) slew rate C) under rate D) None of these. (04 Marks)

- b. List the characteristics of an ideal op.amp. (06 Marks)
- c. Show with a circuit diagram, how the op-amp can be used as an integrator. (05 Marks)
- d. Find the O/pP voltage of the 3 i/p adder circuit shown below Fig. Q6(d). (05 Marks)

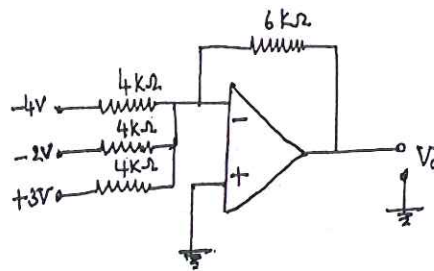


Fig. Q6(d)

- 7 a. Choose the correct answers for the following :
- The radio communication uses _____ as communication medium.
A) Optical fibre B) Free space C) conducting wire D) None of these.
 - The circuit that recovers the original modulating information from an AM signal is known as
A) Modulator B) Mixer C) Demodulator D) Oscillator.
 - 2's complement of binary number 10110 as
A) 00011 B) 01010 C) 11100 D) 11111.
 - $(28)_{10} = (\quad)_2$
A) 11100 B) 01110 C) 11000 D) 00011. (04 Marks)
- b. Explain the need for modulation. (04 Marks)
- c. Draw the block diagram of a super heterodyne receiver and explain the function of each block. (06 Marks)
- d. Perform the following :
- Convert $(725.25)_8 = (\quad)_{10} = (\quad)_2$
 - Subtract using 2's complement $(4 - 9)_{10}$
 - $(11010.101)_2 = (\quad)_8 = (\quad)_{16}$. (06 Marks)
- 8 a. Choose the correct answers for the following :
- Universal gates are _____ and _____.
A) NOT and NOR B) AND or OR C) NAND and NOR D) EX-OR and EX-NOR.
 - $(A+B)(B+C) =$ _____
A) $B + \overline{AC}$ B) $B + \overline{BC}$ C) $B + AC$ D) AB.
 - The output is high, when all the inputs are low, such a gate is called _____.
A) NAND B) AND C) OR D) EX-OR
 - Full adder has _____ inputs.
A) 1 B) 2 C) 3 D) 4. (04 Marks)
- b. State and prove De Morgan's theorem. (04 Marks)
- c. Simplify
- $\overline{A} \overline{B} \overline{C} + \overline{A} B \overline{C} + A \overline{B} \overline{C} + A B \overline{C}$, realize using basic gates.
 - $(A + \overline{B} + C)(\overline{A} + B + C)$, realize using two input NAND gates. (08 Marks)
- d. Realize a full adder using 2 Half adder and OR gate. (04 Marks)

* * * * *

CMRIT Library