

--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, June/July 2017

Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Transform the network given in Fig Q1(a) in to a single voltage source using source transformation technique. (05 Marks)
- b. Find the currents i_1 , i_2 and i_3 in the network given Fig Q1(b) using mesh analysis. (06 Marks)
- c. Find current through 0.5Ω resistance in the Fig Q1(c) using node analysis. (05 Marks)

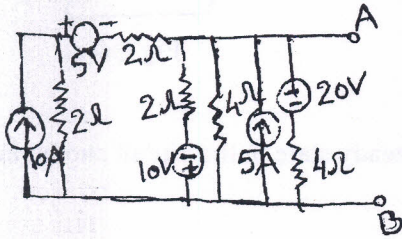


Fig Q1(a)

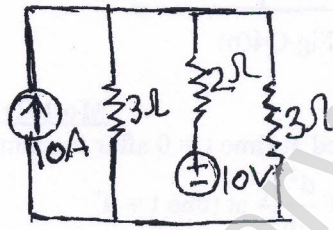


Fig Q1(b)

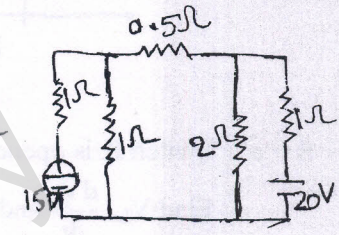


Fig Q1(c)

OR

- 2 a. Determine the equivalent resistance between the terminals A and B in the network in the Fig Q2 (a) using star Delta, transformation. (06 Marks)

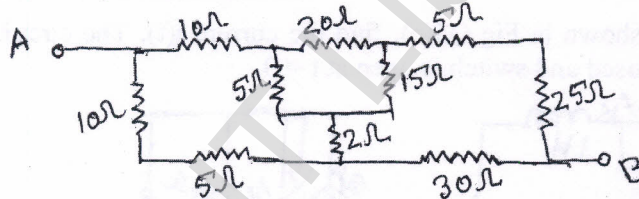


Fig Q2(a)

- b. Derive expression for resonant frequency in series RLC circuit. (05 Marks)
- c. Give the comparison between series and parallel resonance. (05 Marks)

Module-2

- 3 a. State and explain superposition theorem. (05 Marks)
- b. Obtain the current I_x in the circuit shown in Fig Q3(b) using Thevenin's theorem. (05 Marks)
- c. Find the Norton's equivalent circuit at the terminals A and B in the network given in Fig Q3(c). (06 Marks)

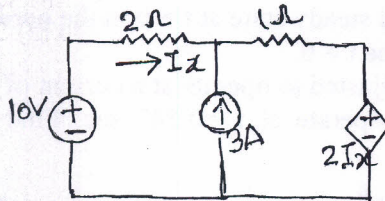


Fig Q3(b)

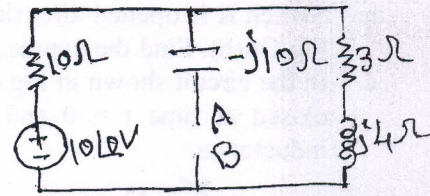


Fig Q3(c)

OR

- 4 a. State and explain Millman's theorem. (05 Marks)
- b. Verify Reciprocity theorem for the network given in Fig Q4(b). (05 Marks)

- c. Find the value of load resistance R_L for maximum power to be transferred to the load and also find maximum power for the network shown in Fig Q4(c) (06 Marks)

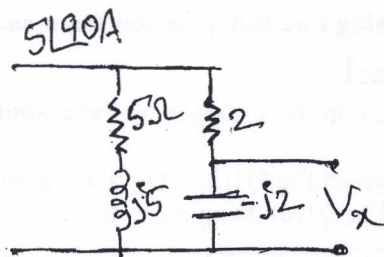


Fig Q4(b)

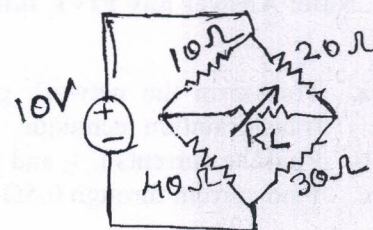


Fig Q4(c)

Module-3

- 5 a. Switch K is opened at time $t = 0$ after reaching steady state in the circuit shown in Fig Q5(a). Find V_k , $\frac{dV_k}{dt}$ and $\frac{d^2V_k}{dt^2}$ at time $t = 0^+$ (05 Marks)
- b. In the circuit shown in Q5 (b) switch is opened at time $t = 0$. Find the values of V , $\frac{dV}{dt}$ and $\frac{d^2V}{dt^2}$ at $t = 0^+$ (05 Marks)
- c. In the circuit shown in Fig Q5(c), find the current $i(t)$. The circuit has reached steady state with switch closed and switch is open at $t = 0$. (06 Marks)

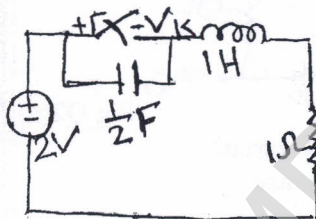


Fig Q5(a)

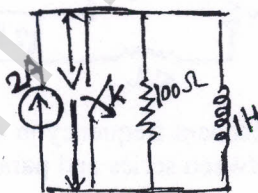


Fig Q5(b)

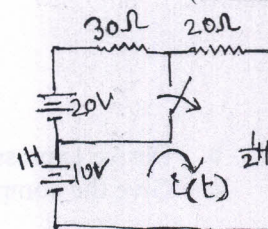


Fig Q5(c)

OR

- 6 a. Switch is closed at time $t = 0$ in the circuit shown in Fig.Q6(a). Find the values of i_1 , i_2 , $\frac{di_1}{dt}$, $\frac{di_2}{dt}$ at time $t = 0^+$. (05 Marks)
- b. Switch K is opened after the circuit has reached steady state at $t = 0$ in the network shown in Fig.Q6(b). Find the expression for $V_2(t)$ for time $t > 0$. (05 Marks)
- c. In the circuit shown in Fig.Q6(c) the relay is adjusted to operate at a current of 5A. Switch is closed at time $t = 0$ and relay is found to operate at $t = 0.347$ sec. Find the value of inductance. (06 Marks)

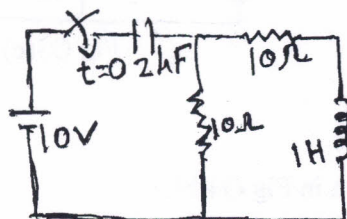


Fig.Q6(a)

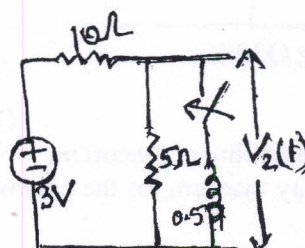


Fig.Q6(b)

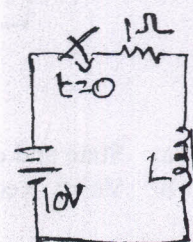


Fig.Q6(c)

Module-4

- 7 a. Find Laplace transform of the following functions i) $\sin \omega t$ ii) $\cos \omega t$ iii) te^{-at} . (05 Marks)
 b. State and prove initial value theorem. (05 Marks)
 c. In the circuit shown in Fig Q7(c) find the expression for current if switch is closed at $t=0$. Assume initial charge on capacitance is zero. (06 Marks)

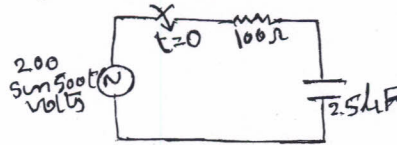


Fig Q7(c)

OR

- 8 a. Find inverse Laplace transform of the following functions.
 i) $\frac{S^2 + 5}{S(S^2 + 4S + 4)}$ ii) $\frac{2S + 6}{S^2 + 6S + 25}$ (05 Marks)
 b. Using initial and final value theorems, where they apply, find $f(0)$ and $f(\infty)$ for the following functions.
 i) $\frac{S^3 + 7S^2 + 5}{S(S^3 + 3S^2 + 4S + 2)}$ ii) $\frac{S(S+4)(S+8)}{(S+1)(S+6)}$ (05 Marks)
 c. Find $i(t)$ using Laplace transforms switch is closed at time $t=0$ with zero initial conditions. (06 Marks)

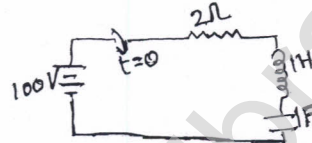


Fig Q8(c)

Module-5

- 9 a. Explain the method of analyzing a 3-ph star connected load by using Millman's theorem. (05 Marks)
 b. A delta connected three phase load with impedance is connected across a 3-ph 230V, 50Hz symmetrical RYB supply. The impedances are $(28 + j0)\Omega$, $(25 + j45)\Omega$ and $(0 - j65)\Omega$. Find line and phase currents. (06 Marks)
 c. Find z parameters of the circuit shown in Fig.Q9(c). (05 Marks)

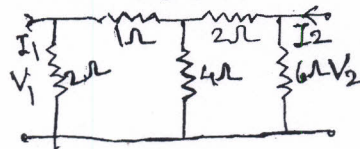


Fig Q9(c)

OR

- 10 a. A star connected load with $(3+j0)\Omega$, $(2+j3)\Omega$ and $(2-j1)\Omega$ connected in 3-ph, 4 wires, Y connected system with phase sequence ACB. Find line currents and neutral current. (06 Marks)
 b. Explain the concept of unbalanced load. State various types of unbalanced loads. (05 Marks)
 c. Find 'T' parameters of the circuit in Fig.Q10(c). (05 Marks)

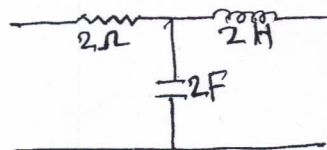


Fig Q10(c)
