

--	--	--	--	--	--	--	--	--	--

Fifth Semester B.E. Degree Examination, June/July 2017
Linear IC's and Applications

Time: 3 hrs.

Max. Marks:100

- Note:** 1. Answer any FIVE full questions, selecting at least TWO questions from each part.
 2. Use of Resistor and Capacitor standard values tables are permitted.

PART – A

- 1 a. With neat circuit diagram explain design and the operation of high input impedance non-inverting amplifier. (10 Marks)
- b. A capacitor coupled inverting amplifier has the following components:
 $R_1 = 2.7 \text{ k}\Omega$; $R_2 = 100 \text{ k}\Omega$; $R_L = 1.5 \text{ k}\Omega$; $C_1 = 3.9 \text{ }\mu\text{F}$; $C_2 = 0.68 \text{ }\mu\text{F}$. Determine the circuit voltage gain, input impedance, lower cutoff frequency and impedance of C_1 at f_1 . (10 Marks)
- 2 a. What is frequency compensation? Explain phase lag compensation method. (08 Marks)
- b. Calculate the slew rate limited cutoff frequency, maximum peak value of the sinusoidal output voltage and cutoff frequency rise time, slew rate limit rise time for 741 op-amp. Given : Peak of sine wave output is to be 6V, $S = 0.5 \text{ V}/\mu\text{S}$ and circuit to operate at 800kHz. (06 Marks)
- c. Briefly explain :
 (i) Loop gain (ii) Phase margin (iii) Unity gain bandwidth (06 Marks)
- 3 a. With a neat circuit diagram explain design and operation of precision fullwave circuit. (10 Marks)
- b. With a neat circuit diagram and waveform explain the working of sample and hold circuit. (10 Marks)
- 4 a. Sketch the circuit of an op-amp astable multivibrator, show the waveforms at various points in the circuit and explain its operation. (08 Marks)
- b. Using a 741 op-amp with a $\pm 18\text{V}$ supply, design an inverting Schmitt trigger circuit to have $UTP = 1.5 \text{ V}$ and $LTP = -3\text{V}$. (07 Marks)
- c. With a circuit diagram, explain the working of a capacitor coupled zero crossing detector and give the design steps. (05 Marks)

PART – B

- 5 a. With neat circuit diagram and waveforms, explain the operation of triangular/rectangular generator. (08 Marks)
- b. Draw the circuit diagram of phase shift oscillator and explain its operation. (06 Marks)
- c. Using a BIFET op-amp with a supply of $\pm 12\text{V}$, design a wein bridge oscillator to have an o/p frequency of 20 kHz. (06 Marks)
- 6 a. Sketch the circuit of a second order active highpass filter. Explain its operation and design procedure with frequency response curve. (12 Marks)
- b. Design a first order active high-pass filter for cut-off frequencies of 4.5 kHz use 741 op-amp. (08 Marks)

- 7 a. Explain the operation of a switched capacitor filter. List out the advantages of switched capacitor filter. (10 Marks)
- b. With a block diagram, explain the operation of a phase locked loop. (10 Marks)
- 8 a. Define performance parameters of voltage regulators. (04 Marks)
- b. With a neat circuit diagram explain the operation of a precision voltage regulator. (08 Marks)
- c. Design a voltage follower type regulator circuit using 741 op-amp with following specifications;
- (i) Output voltage 12V
- (ii) Maximum load current = 50 mA. (08 Marks)
