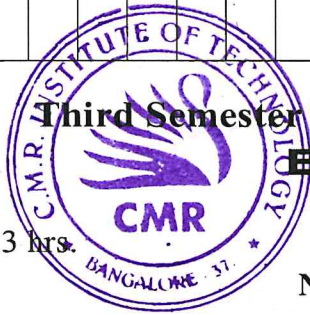


--	--	--	--	--	--	--	--	--	--



Third Semester B.E. Degree Examination, July/August 2021 Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions.

- 1 a. Define Ideal and practical voltage and current sources with the help of neat circuit diagram and characteristic curves. (04 Marks)
- b. Find the equivalent Resistance between terminals A and B using Y- Δ transformation in the network shown in Fig Q1(b).

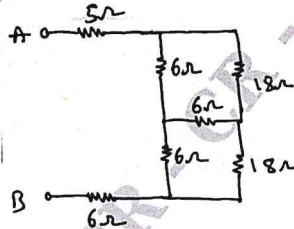


Fig Q1(b)

(06 Marks)

- c. Using mesh current analysis find the value of V_2 such that current through 4Ω resistance is zero.

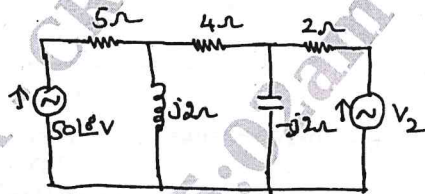


Fig Q1(c)

(06 Marks)

- 2 a. For the Network shown in Fig Q2(a) find node voltage V_d and V_c .

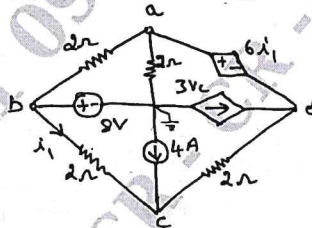


Fig Q2(a)

(08 Marks)

- b. With respect to series Resonant circuit define i) Resonant frequency (f_r) ii) Half power frequencies. (04 Marks)
- c. For the network shown in Fig Q2(c) draw the dual circuit. Also write nodal equations for the dual network.

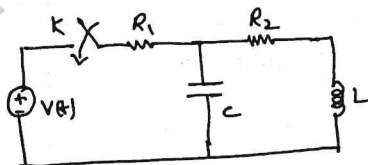


Fig Q2(c)

(04 Marks)

- 3 a. State and explain Thevenin's theorem. (05 Marks)

- b. Using Millman's Theorem find the current through $R_L = 10\Omega$ in the circuit shown in Fig Q3(b)

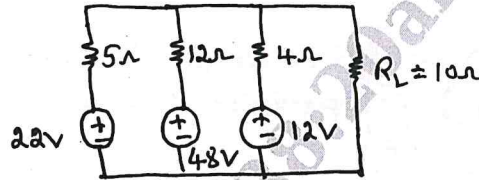


Fig Q3(b)

(05 Marks)

- c. Verify Reciprocity theorem for the circuit shown in Fig Q3(c).

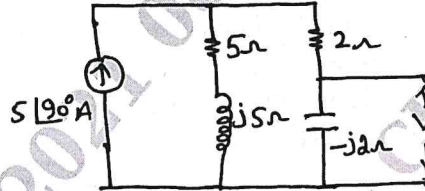


Fig Q3(c)

(06 Marks)

- 4 a. State and Prove maximum power Transfer theorem for D.C circuits. (05 Marks)
 b. In the circuit shown in Fig Q4(b). Find the value the current 667Ω resistor using Norton's theorem.

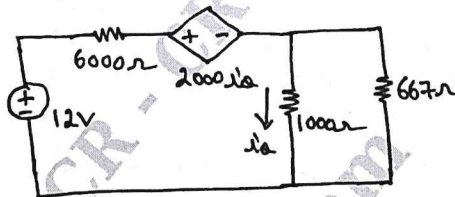


Fig Q4(b)

(06 Marks)

- c. Using super Position Theorem find the current through 2Ω resistor in Fig Q4(c).

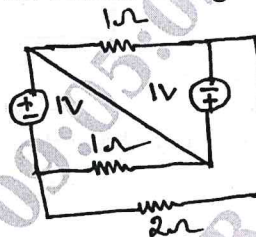


Fig Q4(c)

(05 Marks)

- 5 a. Using classical method find and sketch $i(t)$ for $t > 0$ in the circuit shown in Fig 5(a)

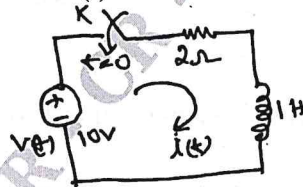


Fig Q5(a)

(08 Marks)

- b. In the network shown in Fig Q5(b) $V = 10V$, $R = 10\Omega$, $L = 1H$, $C = 10\mu F$ and $V_c(0) = 0$. Find $i(0^+)$, $\frac{di(0^+)}{dt}$ and $\frac{d^2i(0^+)}{dt^2}$, if switches is closed at $t = 0$

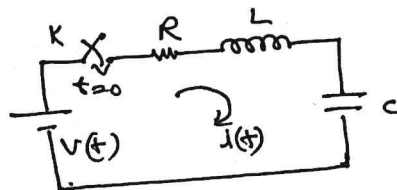


Fig Q5(b)

(08 Marks)

- 6 a. In the circuit shown in Fig Q6(a) the switch 'S' is moved from 'a' to 'b' at $t = 0$. Find i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$. If $R = 1\Omega$, $L = H$, $C = 0.1\mu F$ and $V = 100V$, Assuming steady state has been achieved with switch 'S' at 'a'.

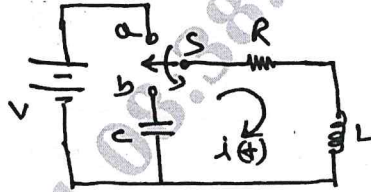


Fig Q6(a)

(08 Marks)

- b. Find and sketch voltage across capacitor $V_c(t)$ for $t \geq 0$ in the circuit shown in Fig Q6(b)

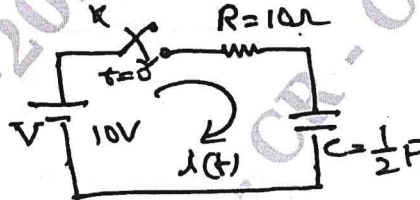


Fig Q6(b)

(08 Marks)

- 7 a. Using convolution Integrals find the inverse Laplace transform of the following functions

i) $F(s) = \frac{1}{s(s+1)}$ ii) $F(s) = \frac{1}{(s-a)^2}$

(08 Marks)

- b. Using Laplace transformation method find the expression for current $i(t)$ when switch 'K' is closed at $t = 0$ in the network in Fig Q7(b).


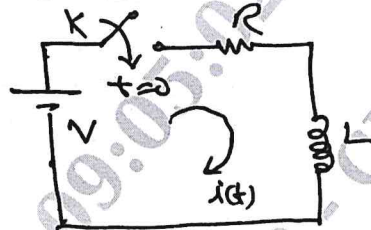


Fig Q7(b)

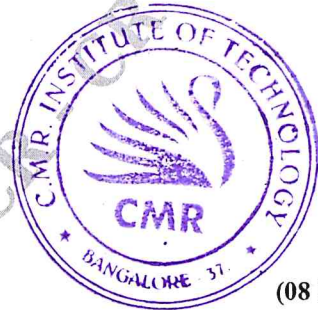

(08 Marks)

- 8 a. State and prove Initial value theorem and final value theorem.

(08 Marks)

- b. Find the Laplace transform of i) $\delta(t)$ ii) e^{-at}

(04 Marks)

- c. Find the Laplace Transform of saw tooth waveform shown in Fig Q8(c)

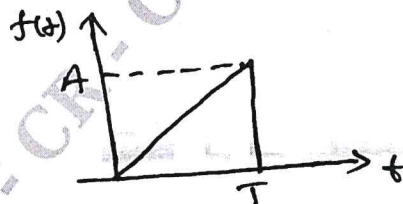


Fig Q8(c)

(04 Marks)

- 9 a. A delta connected three phase load with the impedances of $(28 + j0)\Omega$, $(25 + j45)\Omega$ and $(0 - j65)\Omega$ are connected across a 3 phase 230V, 50Hz symmetrical RYB supply. Find the line and phase currents in magnitude and phase. Draw the necessary circuit diagram.

(08 Marks)

- b. Define Poles and Zeros of network functions.

(04 Marks)

- c. Determine Z-parameters for the circuit shown in Fig Q9(c)

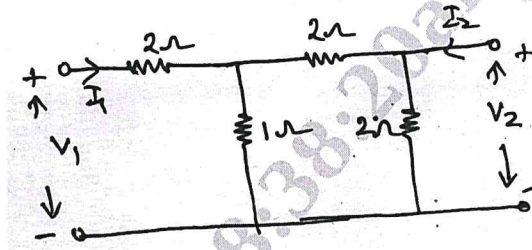


Fig Q9(c)

(04 Marks)

- 10 a. Find out transmission parameters for the network shown in Fig Q10(a).

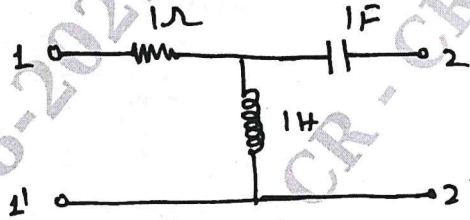


Fig Q10(a)

(08 Marks)

- b. For the network shown in Fig Q10(b) find the driving point function $Z(s)$ and plot the poles and zeros on s-plane.

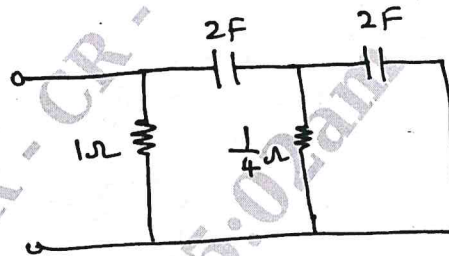


Fig Q10(b)

(08 Marks)

CMRIT LIBRARY
BANGALORE - 560 037