 


# CBCS SCHEME

17EE35



## Third Semester B.E. Degree Examination, July/August 2021 Digital System Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions.

- Define and explain combinational logic with neat figure. (04 Marks)
  - $y = f(A, B, C) = A + BC$ . List all Min terms and Max terms. (06 Marks)
  - Simplify  $Q = f(A, B, C, D, E) = m_0 + m_1 + m_2 + m_{27} + d_{20}$ . Using K-Map and write logic diagram for reduced Boolean equation. (10 Marks)
- Write truth table K-Map and logic diagram for half subtractor. (04 Marks)
  - Simplify  $Q = f(v, w, x, y, z) = M_4 M_{12} M_{15} M_{17}$ . Using Quine – Mc Clusky method. (10 Marks)
  - Two motor  $M_2$  and  $M_1$  are controlled by three sensors  $S_1, S_2$  and  $S_3$ .  $M_2$  is to run any time all three sensors are on (true). The other motor is to run whenever sensors  $S_2$  or  $S_1$  but not both are on and  $S_3$  is off. For all sensor combinations where  $M_1$  is on  $M_2$  is to be off except when all three sensors are off and then both motors must be off. Write Boolean output equations. (06 Marks)
- Define explain decoder. (05 Marks)
  - Implement full subtractor using 74138 and NAND gate only. (08 Marks)
  - Define and explain digital MUX. (07 Marks)
- Realize Boolean equation  $T = f(w, x, y, z) = \Sigma m(1, 2, 5, 7, 12, 14)$ , Using 8 to 1 MUX. (08 Marks)
  - List the steps of general approach to combinational logic design. (06 Marks)
  - Write a note on cascading type 1 bit comparator with truth table and diagram. (06 Marks)
- Write a note on SR latch using NAND gate. (05 Marks)
  - Write characteristics table, excitation table characteristics equation of JK flip-flop. (07 Marks)
  - Compare Moore model and Mealy model to representing sequential machines. (08 Marks)
- Implement Divide by 8 Binary ripple counter using JK flip-flop 7476. Write timing diagram and logic diagram. (07 Marks)
  - Design synchronous self starting Mod-6 upcounter using T flip-flop. (09 Marks)
  - Explain shift right and shift left operations with figure for registers block. (04 Marks)
- Write transition table for given state diagram (Ref. Fig Q7(a)).

 


Fig Q7(a)

1 of 2

(08 Marks)

b. List the steps of synchronous sequential circuit analysis. (12 Marks)

8 a. Write transition excitation table state table, state diagram and timing diagram for the sequential machine given in Fig Q8(a).

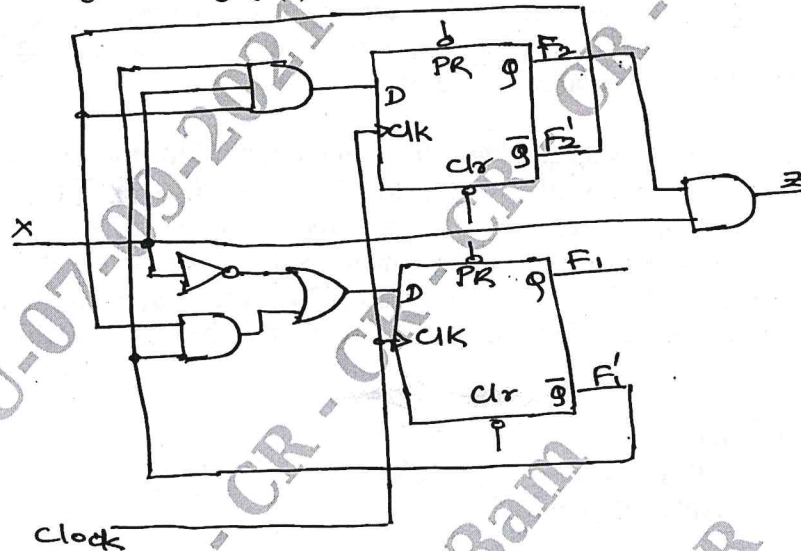


Fig Q8(a)

b. Write a note on decade up counter. (08 Marks)

(12 Marks)  
(08 Marks)

9 a. Write a note on Data types used in VHDL with examples and specifications. (08 Marks)

b. What are the fundamental sections that comprise a VHDL code? Explain with any example code. (12 Marks)

(08 Marks)  
(12 Marks)

10 a. Explain how VHDL evolved in early stages of development. (09 Marks)

b. Write note on Major capabilities of verilog. (11 Marks)

(09 Marks)  
(11 Marks)

CMRIT LIBRARY  
BANGALORE - 560 037

\*\*\*\*\*