 


CBCS SCHEME



15EE35

Third Semester B.E. Degree Examination, July/August 2021 Digital System Design

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions.

- 1 a. Express the following equations into proper canonical forms and in decimal notations
 - i) $F_1(a, b, c) = a\bar{b} + a\bar{c} + bc$
 - ii) $f_2(A, B, C) = \bar{A}\bar{B} + C$. (06 Marks)
- b. Simply the following equations using K Map and implement using logic gates
 - i) $f(a, b, c, d) = \pi M(0, 3, 4, 7, 8, 10, 12, 14) + d(2, 6)$
 - ii) $f(w, x, y, z) = \Sigma m(0, 2, 8, 10, 11, 12, 14, 15)$ (10 Marks)
- 2 a. Simplify using Quine Mc Cluskey method.
 $P = f(a, b, c, d) = \Sigma m(2, 3, 4, 5, 13, 15) + \Sigma(8, 9, 10, 11)$. (10 Marks)
- b. Solve using 3 variable MEV Kmap with d as MEV.
 $f(a, b, c, d) = \Sigma m(0, 1, 3, 5, 6, 11, 13) + d(4, 7)$. (06 Marks)
- 3 a. What is a magnitude comparator? Design a 2 bit binary comparator. (10 Marks)
- b. Realize the following function using 8:1MUX with a, b, c as select lines
 $f(a, b, c, d) = \Sigma m(0, 1, 5, 6, 7, 9, 10, 15)$ (06 Marks)
- 4 a. Write the function table and draw the interfacing diagram of ten key keypad interfaces to a digital system using decimal to BCD encoder. (08 Marks)
- b. Using active high output 3:8 line decoder, implement the following functions.
 $F_1(A, B, C, D) = \Sigma m(0, 1, 2, 5, 7, 11, 15)$ and $f_2 = (A, B, C, D) = \pi(3, 7, 9, 13)$. (08 Marks)
- 5 a. Explain the working of Master Slave JK flip-flop with the help of logic diagram, function table, logic symbol and timing diagram. (10 Marks)
- b. Obtain the characteristics equation of JK flip-flop and T flip-flop. (06 Marks)
- 6 a. Design a synchronous Mod 6 counter using JK flip-flop. (08 Marks)
- b. Design a 4bit register using positive edge triggered DFF to operate as indicated in the table below.

Mode	Select	Register
a_1	a_0	Operation
0	0	Hold
0	1	Clear
1	0	Complement
1	1	Circular right shift

CMRIT LIBRARY
BANGALORE - 560 037

(08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 7 a. Compare Mealy and Moore models of a clocked synchronous sequential circuit. (04 Marks)
 b. Construct the excitation table, transition table and state diagram for the Moore sequential logic circuit given below in Fig Q7(b).

 


Fig Q7(b)

(12 Marks)

- 8 a. Construct a sequential logic circuit single input single output by obtaining the state and excitation table for the given diagram using JK flip – flop. (Ref. Q8(a))

 


Fig Q8(a)

(10 Marks)

- b. Draw the state diagram for a sequence detector to detect the sequence 110. (06 Marks)
- 9 a. Explain the structure of VHDL module and verilog module with an example of half adder. (08 Marks)
 b. Explain shift operators of VHDL and verilog with an example of 4bit vector 1101. (08 Marks)
- 10 a. Draw the block diagram of a 4bit look ahead carry adder and write the data flow description for its boolean functions in verilog. (08 Marks)
 b. Draw the logic diagram, of a D latch and write the VHDL code description. (08 Marks)
