

CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15EC33

Third Semester B.E. Degree Examination, June/July 2017 Digital Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Convert the given Boolean function into
- $Y = f(a, b, c) = (a + b)(a + c)$ minterm canonical form (04 Marks)
 - $P = f(a, b, c) = (a + b)(b + c)(\bar{c} + a)$ maxterm canonical form. (04 Marks)
- b. Using K-map determine the minimal sum of product expression and realize the simplified expression using only NAND gates. (08 Marks)
- $M = f(W, X, Y, Z) = \sum (1, 4, 5, 6, 11, 12, 13, 14, 15).$

OR

- 2 a. Simplify the given Boolean function using Quine – McCluskey method :
 $Y = f(a, b, c, d) = \sum (0, 2, 3, 5, 8, 10, 11).$ Verify the result using k-map. (12 Marks)
- b. Distinguish between prime implicant and Essential prime implicant. (04 Marks)

Module-2

- 3 a. Define Decoder. Implement the following multiple output function using IC 74138 and external gates. Also write the truth table. (06 Marks)
- $P = f_1(X, Y, Z) = \sum (1, 2, 5, 6)$
 $Q = f_2(X, Y, Z) = \pi (3, 5, 6, 7).$
- b. Implement the following Boolean function using 8:1 multiplexer : (10 Marks)
- $Y = f(A, B, C, D) = \overline{ABD} + ACD + \overline{BCD} + \overline{ACD}$

OR

- 4 a. Design and implement 4-bit look ahead carry adder. (08 Marks)
- b. Design and implement BCD to Excess-3 code converter. (08 Marks)

Module-3

- 5 a. Explain the working principle of gated SR latch. (06 Marks)
- b. Explain the working of master slave JK flip-flop with the help of a logic diagram, function table, logic symbol and timing diagram. (10 Marks)

OR

- 6 a. With a neat logic diagram, explain the working of positive edge triggered D flip-flop. Also draw the timing diagram. (08 Marks)
- b. Derive the characteristic equation for JK and T flip-flop. (08 Marks)

Module-4

- 7 a. Describe the working principle of universal shift register with the help of logic diagram and mode control table. (08 Marks)
- b. Illustrate the operation of 4-bit binary ripple counter using logic diagram and timing diagram. (08 Marks)

OR

- 8 a. Design a synchronous Mod-6 counter using clocked T flip-flop. (10 Marks)
 b. Explain Mod-4 ring counter using D flip-flop. (06 Marks)

Module-5

- 9 a. Explain Mealy and Moore sequential circuit models. (04 Marks)
 b. For the logic diagram shown in Fig Q 9(b).
 i) Write input and output equations
 ii) Construct transition table
 iii) Draw state diagram. (12 Marks)

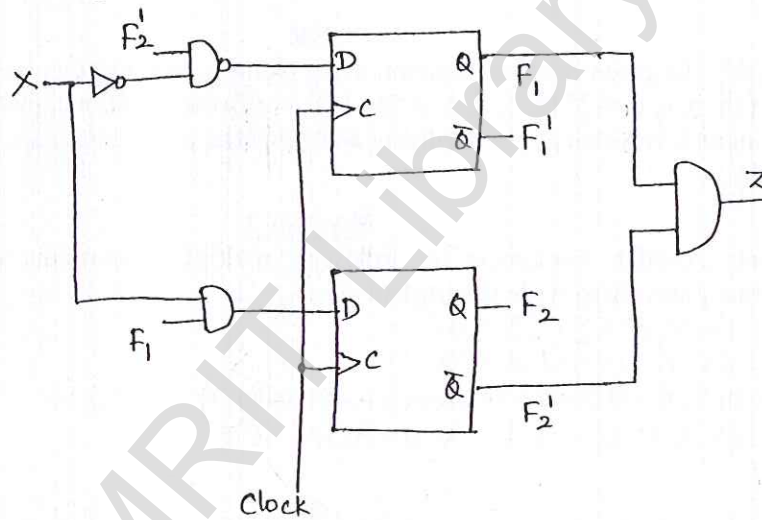


Fig Q9(b)

OR

- 10 a. Define the terms as applied to sequential circuit :
 Input variable, output variable, Excitation variable and state variable. (04 Marks)
 b. Design a sequential circuit for a state diagram shown in Fig Q 10(b). (12 Marks)

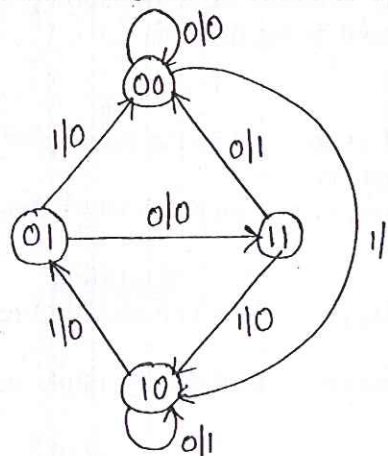


Fig Q10(b)