

--	--	--	--	--	--	--	--	--	--

**Fourth Semester B.E. Degree Examination, June/July 2017**  
**Fundamentals of HDL**

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting  
at least TWO questions from each part.**

**PART – A**

- 1 a. Explain in brief verilog data types and operators with example. (11 Marks)
- b. List different modeling styles. Define significances of each modeling style. (06 Marks)
- c. Find the value of expression  $X_1$ ,  $X_2$ ,  $X_3$  for the following VHDL signal declaration,  
Signal a : bit := '1' ;  
Signal b : bit – vector (3 down to 0) := "1010";  
Signal c : bit – vector (0 to 3) := "0010";  
 $X_1 = C \text{ sll } 2$   
 $X_2 = b \text{ sra } 3$   
 $X_3 = a \overline{b(2)} \overline{c(1)}$  (03 Marks)
- 2 a. Design a 4 : 1 Mux and implement the same using Boolean equation in verilog. (05 Marks)
- b. Design 3 × 3 unsigned combinational array multiplier in VHDL assigning a delay 5 ns. (10 Marks)
- c. Write a verilog description for a SR latch: (i) Use a characteristic equation. (05 Marks)  
(ii) Use two logic gates.
- 3 a. architecture sig of dummy is  
Signal trigger, sum : integer := 0 ;  
Signal Sig 1 : integer := 1 ;  
Signal Sig 2 : integer := 2 ;  
Signal Sig 3 : integer := 3 ;  
begin  
    process (trigger)  
    begin  
        Sig 1 ← Sig2 + Sig3 ; Sig2 ← Sig1 ;  
        Sig 3 ← Sig2 ; Sum ← Sig1 + Sig2 + Sig3 ;  
    end process; eng Sig ;  
architecture Var of dummy is  
Signal trigger, Sum : integer := 0;  
Begin  
    Process (trigger)  
    Variable Var 1 : integer := 1 ;  
    Variable Var 2 : integer := 2 ;  
    Variable Var 3 : integer := 3 ;  
    Begin  
        Var1 := Var2 + Var3 ; Var 2 := Var 1 ;  
        Var3 := Var2 ; Sum ← Var1 + Var2 + Var3 ;  
    end process ; end Var ;  
The trigger value changes at t = 10 ns, the statements are executed only once.  
Evaluate the value of sum at t = 10 nS + Δ for above 2 cases. (06 Marks)
- b. Design 4-bit ripple adder using for loop only and implement the same using VHDL. (07 Marks)
- c. Write a behavioral description in verilog for JK flip flop using if and else if statement only. With active low clock and asynchronous reset. (07 Marks)

- 4 a. Design a 3-bit synchronous even counter using D flip flop with active high hold and implement the same in structural description in verilog. (10 Marks)
- b. Write the HDL programs for N+1 bit magnitude comparator using,  
 (i) Generate and generic in VHDL.  
 (ii) Generate and Parameter in verilog. (10 Marks)

**PART – B**

- 5 a. Write a code to convert integer to signed Binary (4 – bit) using procedure. (08 Marks)
- b. Bring out the difference between procedure and function with an example. (07 Marks)
- c. Write a note on verilog file processing. (05 Marks)
- 6 a. Write the block diagram and function table of a SRAM, using this write VHDL description of  $16 \times 8$  SRAM. (08 Marks)
- b. Package array is  
 Constant P : integer := 2 ;  
 Constant N : integer := 2 ;  
 Constant M : integer := 1 ;  
 Subtype wordg is integer ;  
 type Single 1 is array (P downto 0) of wordg ;  
 type Single 2 is array (N downto 0) of Single 1 ;  
 type arry 3 is array (M downto 0) of single 2 ;  
 end array;  
 library IEEE;  
 Use IEEE.STD-LOGIC-1164.ALL;  
 Use work.arry.all;  
 Entity Ex is  
 Part (N, M, P: integer ; z : out integer);  
 End Ex;  
 Architecture Ex<sub>1</sub> of Ex is  
 Begin  
 Process (N, M, P)  
 Variable t ; integer ;  
 Constant y; arry 3:=(((5, 4,3),(8, 9, 10),(32, 33, 34)),((42, 43,44),(52, 53,54),(-10, -7, -5)));  
 begin  
 t := y(M)(N)(P);  
 z <= t; end process ; end Ex<sub>1</sub> ;  
 (i) What is the value of the following element of y?  
 Y(0, 0, 0), Y(0, 0, 1), Y(0, 0, 2), Y(0, 1, 2), Y(1, 1, 2), Y(1, 2, 2)  
 (ii) If we change all (N downto 0) and (M downto 0) in package array to (0 to N) and (0 to M). What will be the values of the elements in part (i). (08 Marks)
- c. Which line in the above program 6(b) attaches a package to the VHDL program? Explain each word in that line and significance of each word. (04 Marks)
- 7 a. Write mixed-language description of a master slave JK-ff with a clear input invoking a VHDL entity from a verilog module. (12 Marks)
- b. Discuss the facts of the mixed language description. (08 Marks)

- 8 a. Define synthesis. With a neat flow chart, explain the steps involved in a synthesis. (08 Marks)  
b. Write a behavioral code in verilog for a 2 to 4 decoder with a active low output. Show the gate level synthesis for the code. (06 Marks)  
c. Extract the gate level synthesis for the verilog code below:

```
module example (BP, ADH);  
input [2 : 0] BP;  
output [3 : 0] ADH;  
reg [3 : 0] ADH;  
always @(BP)  
begin  
    if (BP<=2) ADH = 15 ;  
    else if (BP>=5) ADH = 0;  
    else ADH = BP*(-5) + 25 ;  
end end module
```

(06 Marks)

\*\*\*\*\*

CMRIT Library

CMRIT Library